



**ELECTRONICS  
TODAY  
INTERNATIONAL**

**PRIZES, PRIZES, PRIZES**  
in great Maruni contest

Nov. 1980  
\$1.60\*NZ\$1.75

# COMPACT STEREO

Easy to build, low cost amp delivers 20 W/ch

**Electronic thermometer**  
**Soil moisture indicator**  
**Pinball electronics**




**POWER MOSFETS – technology & techniques**

**Soundout 200 W stereo amp reviewed**

**Audiosound AM101 tuner**


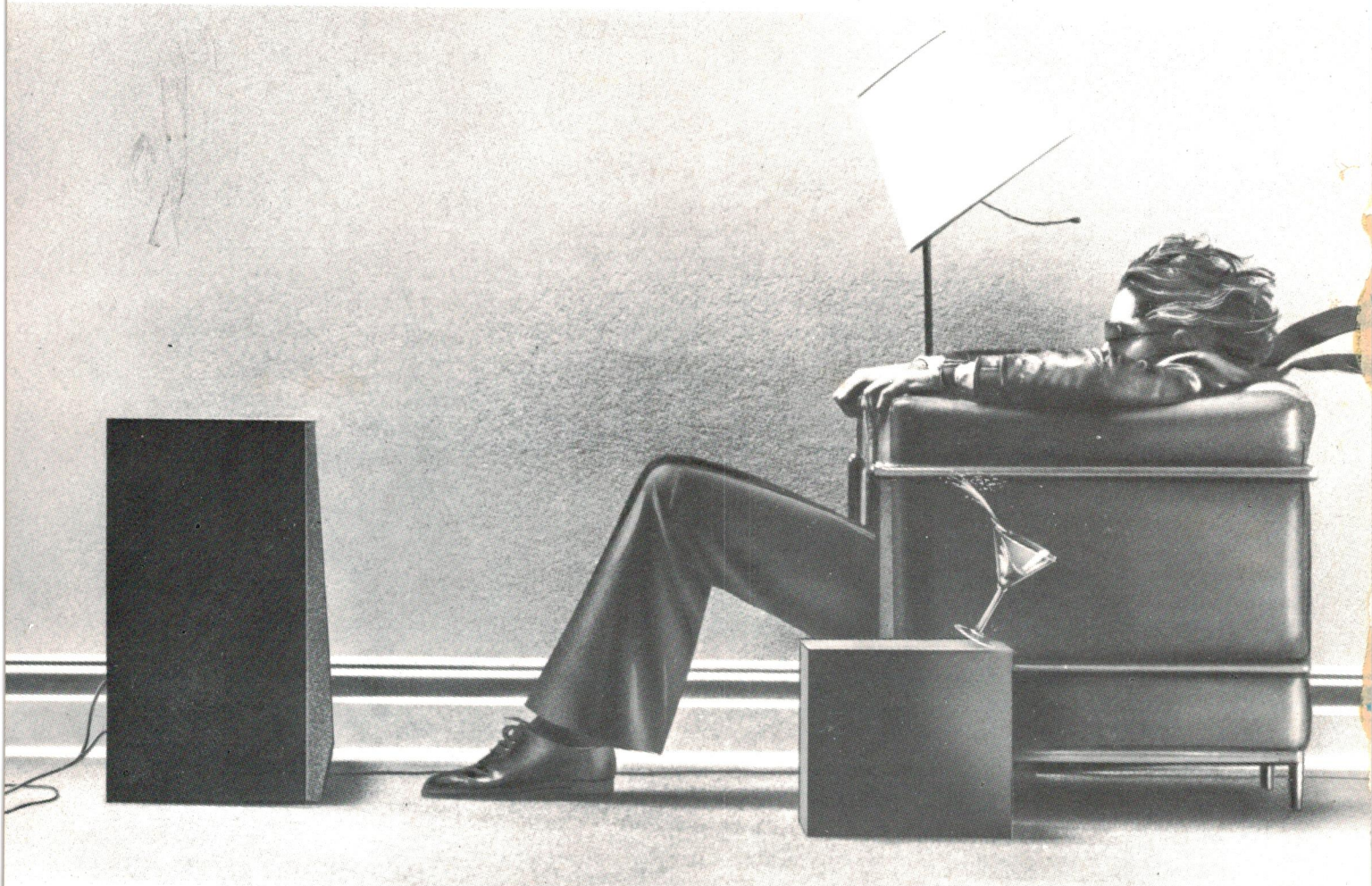
# AFTER 500 PLAYS OUR HIGH FIDELITY TAPE STILL DELIVERS HIGH FIDELITY.



If your old favourites don't sound as good as they used to, the problem could be your recording tape.

Some tapes show their age more than others. And when a tape ages prematurely, the music on it does too.


What can happen is, the oxide particles that are bound onto tape loosen and fall off, taking some of your music with them.

At Maxell, we've developed a binding process that helps to prevent this. When oxide particles are bound onto our tape, they stay put. And so does your music.

So even after a Maxell recording is 500 plays old, you'll swear it's not a play over five.

Distributed by  
**HAGEMEYER**

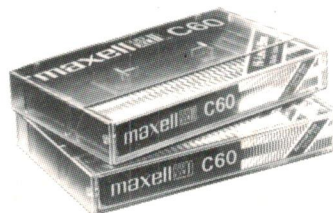For further information on Maxell Tapes  
write to Maxell Advisory Service,  
P.O. Box 307, North Ryde, N.S.W. 2113



**maxell**<sup>®</sup>  
simply excellent

WT191/80





# ELECTRONICS TODAY INTERNATIONAL

Registered for posting as a publication —  
Category B

## QUICK INDEX

### FEATURES:

- 15** Pinball Wizardry
- 23** The Superconducting Transistor
- 106** Bose Contest Winners
- 114** Power MOSFETs — the Technology, the Techniques
- 89** BASIC Programming — Special Offer on New Books

### SOUND SECTION:

- 109** Sound News
- 125** Maruni Contest — \$3000 in Prizes
- 138** Audiosound AM101 AM Tuner Reviewed
- 146** Review of the Soundout S400 Stereo Amp.

### PROJECTS & TECHNICAL

- 26** 476: Series 3000 Compact Stereo Amp
- 38** 255: Electronic Thermometer
- 51** 247: Soil Moisture Indicator
- 46** Short Circuits: Electronic Odometer
- 58** Radio Direction Finding with the DX-160
- 67** Lab Notes: Transistor Arrays — the 3046/3056/3086
- 78** Ideas For Experimenters
- 83** Shoparound
- 129** PC Board Patterns

NO DOUBT many of you have seen the recent 'advertising' campaign on television and in the general press — "have a go, Australia" — aimed at stirring up a bit of national entrepreneurial drive. Whether the campaign will have the desired effect or not would be hard to measure, but we wholeheartedly endorse the general sentiments. We're an Australian-owned, edited, printed and published magazine, and proud of it. One of our many roles is to bring the activities of electronics manufacturers, distributors, importers and retailers to your attention. We'd like to add to that — 'Australian electronics manufacturers in particular'. Every week — no, every day! — we're deluged with press releases from a diverse range of electronics companies (and the word 'electronics' there is used in its loosest sense). Unfortunately, too few of these press releases are from Australian companies involved in electronics manufacturing.

We've been taken to task recently by a number of readers who have written saying that we give little publicity to Australian firms. One letter, prompted by our September editorial, from a local manufacturer of sound equipment is published on page 87 of this issue. It echoes the sentiments of many letters we have received on the subject.

There are several facets to the question, however. Firstly, we are unable to seek out items or stories on companies too often — there is just not enough time or manpower to do it. But we do make the effort and for us, it is well rewarded, judging from reader reaction.

Secondly, so many local electronics companies don't promote themselves. It doesn't necessarily require hiring a PR firm or consultant — a first class idea if you are big enough to afford it — but a little effort can go a long way. There are a number of small technical writing agencies around who can assist. It's no use sitting back complaining that the media won't give you a go — it's up to you to "... have a go".

The ball's in your court.



Roger Harrison  
Editor



# advertisers

A.P. Products	128
Anderson Digital	99
Audio Engineers	122
Aust. Guarantee Corp.	159
Applied Technology	75
Ampec Electronics	134
AED	56
Aust. Business	144
Audio Design	142
A&R Soanar	153
Audio Kits	148
Advanced Electronic Systems	140
Bose Aust.	112
Barratt Lighting	7
Brian Bambach Electronics	142
Bell Instruments	70
Belle Lumiere	150
Box Hill Tech.	86
Convoy	110, 111, 113, 133, 145
Computerland in Melbourne	13
C.I.S.A.	79
Consolidated Marketing	42, 43
Cash-More Sound Systems	133
Chadwick Audio	136
Computer Country	90
Computerware	90
Defence Force Recruiting	158
Dick Smith	6, 21, 36, 37, 45, 50, 84, 85, 96, 154
Dicker Data	49
Diggerman Electronics	70
Delosound	140
DSA Concert Systems	148
David East	68
Ellistronics	62, 63
Elmeasco	124
Electro-Voice Aust P/L	126
Electronic Agencies	57, 150
Electronic Calculator Discounts	86
Emac Industries	141
Electrocraft	141
Emona Enterprises	150
Edible Electronics	
Energy Control	132
Electronic Components & Equipment	22
Ferguson Transformers	88
General Electronic Services	14
Hagemeyer	2, 163
Hitachi	24, 104, 105
John F. Rose	25
Jaycar	74
John P. Young & Assoc	12
Kodak A/Asia	102
Logic Shop	22
Looky Video	86
McWilliams Wines	100
Magrath's P/L	10
Maruni Corp	108
Micro 80	93
Mensa Computers	94
Micro Gear	97
Microcomputer House	90
National Panasonic A/Asia	164
Northpoint Hi Fi	136
Parameters	101
Philips Elcoma	117
Pre Pak Electronics	48
Plessey	22
Rod Irving	55, 66, 72
Radio Parts	76
Radio Despatch	76
Superscope Aust. P/L	121
Sony (Aust) P/L	107, 127
SM Electronics	80, 141
Systems Automation	76, 77
Speedy Communications	151
Sevlen Lighting	132
S.I. Microcomputers P/L	82
S.W.T.P. (Australasia) P/L	88
Sydney Opera House	132
Software Source	86
TDK Aust.	137
Tasman Electronics	47
VSI	44, 131
Vicom International	35
Warburton Franki	156
World Imports	148




# ELECTRONICS TODAY INTERNATIONAL



## COVER

This month's cover features our star project — the Series 3000 compact stereo hi-fi amplifier, and the LED soil moisture indicator. Composition and photo by Ivy Hansen.

## features

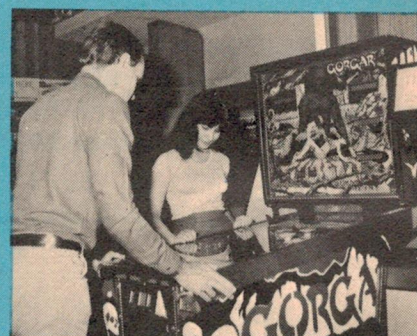

### PINBALL WIZARDRY

15

Modern pinball machines are using increasingly sophisticated electronics to control deflection, lamps, scoring, displays and sound effects. Read how microprocessors keep it all happening.

### THE SUPERCONDUCTING TRANSISTOR

23

Superconducting materials can be used to make junctions analogous to p-n semiconductor junctions.

### RADIO DIRECTION FINDING WITH THE REALISTIC DX-160

58

Make a simple modification to your DX-160 receiver, construct a loop antenna and you've got yourself a radio direction finder. This article shows how to go about it.

### POWER MOSFETS

114

Mightier yet and mightier! MOSFETs used to be only low power devices, but now there are some that can handle 1000 V and 5 A. Read how they are made and how they can be used.

### CONTEST — WIN A MARUNI MICROPHONE AND A SET OF HEADPHONES

125

You've got twenty chances to win a microphone and headphones worth \$150 in this month's great contest.

## news

### NEWS DIGEST

8

Australia's own communications satellite; All solid storage battery; Earth's magnetic field will flip over; Second Ceduna Earth station etc.

### PRINTOUT

91

Compucolor II review; Findex portable microcomputer; New Vector systems; Sorcerer and 2650 hints and programs etc.

### COMMUNICATIONS NEWS

152

Review of Icom IC2A handheld transceiver; State of the Art contest results.

### SHORTWAVE LOGGINGS

155

Singapore changes; Himalayan opportunities; Kampuchea in English.



## projects




### 476: SERIES 3000 COMPACT STEREO HI-FI AMPLIFIER 26

We think this one's a winner — a small stereo amplifier that delivers 20 W per channel with low distortion and costs less than \$90 to build!
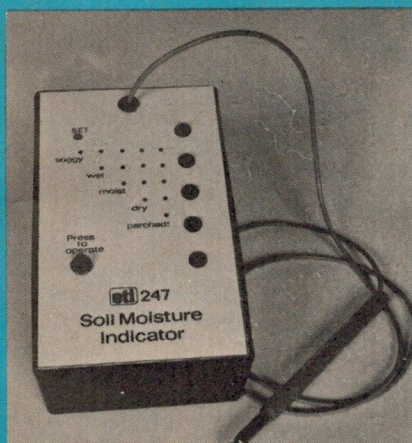
### 255: ELECTRONIC THERMOMETER 38

This local or remote indicating thermometer uses the new LM3911 temperature sensing IC. It's simple to construct and easy to read.



### 247: SOIL MOISTURE INDICATOR 51

If you don't have very green fingers, this rugged and reliable instrument will help you tell if your plants are thirsty or saturated.

### LAB NOTES —

#### TRANSISTOR ARRAYS 67

The excellent matching of transistors on integrated arrays makes them ideal for current mirrors, differential amps and a host of other circuits. This article discusses a typical array — the 3046/3056/3086.

#### SHOPAROUND 83

#### BOSE CONTEST WINNERS 106

Find out who won the five Bose car stereos in our July contest — and where you went wrong in your own entry!

## sound

### SOUND NEWS 109

Sony Biotracer tonearms; L & D budget loudspeakers; All-in-one sound centre.



### AUDIOSOUND AM101 AM TUNER 138

This Australian-made AM tuner easily outperforms most other AM units and even approaches FM reception quality.

### SOUNDOUT S400 STEREO AMPLIFIER 146

Lightweight, well designed and well protected, this 200 W per channel sound reinforcement amplifier should be very appealing to professionals.

## general

### IDEAS FOR EXPERIMENTERS 78

Solid state conversion for TD20D RF Generator; 'Computer music' simulator; Dummy car alarm.

### SHORT CIRCUITS 46

Electronic odometer

### LETTERS 87

### IONOSPHERIC PREDICTIONS 157

### ELECTRONICS BOOKS FROM ETI 64

Beginners' books, data books, circuit books etc.

### COMPUTER BOOKS OFFER 89

### PC BOARDS 129


### MINIMART 130

### KITS FOR PROJECTS 160

### ETI SERVICES 161

### DREGS 162

## next month

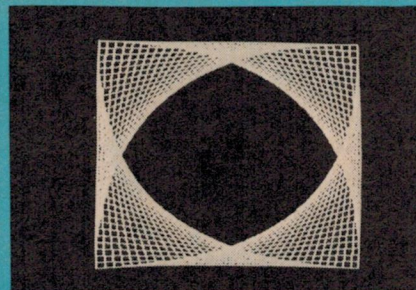

### MATROX VIDEO BOARDS REVIEWED


Craig Barratt looks at two stackable S-100 video graphics boards, the ALT 256 and ALT 512, from Matrox — see what smart things you can do with them.

### HAVE YOU ALWAYS WANTED A REALLY GOOD HI-FI AMP ?

Well this one should fill the bill. Forget about SID, TIM, THD and noise, David Tilbrook has designed a superb integrated amplifier featuring MOSFET power output devices and specs unrivalled in any similar amplifier, be it kit or commercially made.
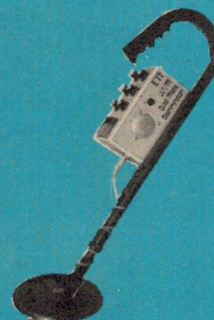
### BUILD A pH METER

This project is straightforward and inexpensive. Using a locally made pH probe and featuring a 3½ digit LCD readout, it should have wide application. Keep your fish tank or swimming pool clean — balance the water's pH — use it in the school lab, etc, etc.



### COMING SOON !

### DISCRIMINATING METAL DETECTOR

Gold fever returned to Australia when the 27kg Hand of Faith nugget was found by a couple using a metal detector back in October. Get amongst it with our 'quad mode' detector. This design features three T/R modes of operation plus VLF, variable ground balance control, variable discriminate control, pre-wound search head plus incredible penetration and sensitivity.

Although these articles are in an advanced state of preparation, circumstances may affect the final content. However, we will make every attempt to include all features mentioned here.




**the most  
compelling  
story in  
Australia's  
aviation  
history**

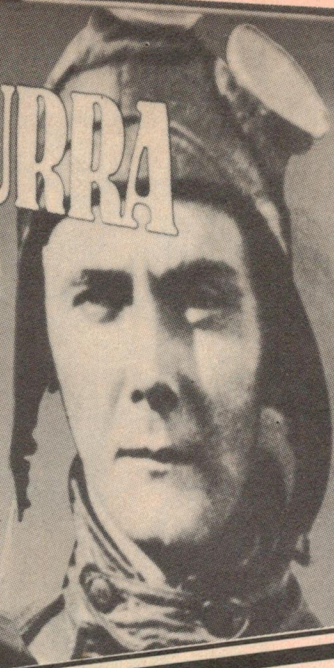**KOOKABURRA**

the most compelling  
story in Australia's  
aviation history

Research by Dick Smith  
Story by Pedr Davis



**DICK SMITH'S  
SEARCH FOR THE**

**KOOKABURRA**

Research by Dick Smith Story by Pedr Davis

EDUCATE YOUR FAMILY AND FRIENDS WITH  
THIS INCREDIBLE BOOK!

This book presents the first account of the 'Kookaburra' and the men who flew the plane. It describes the harsh conditions endured by the first aviators in their daring quests to break records over long distances, or to carry passengers and mail across the continent.

This compelling account of great courage, daring and determination, gives a fascinating glimpse at the spirit of excitement which was evident in those pioneering days of Australia's aviation history.

READ DETAILS OF THE KOOKABURRA

**GOLD REEF**

IT HAS YET TO BE FOUND!

**130 PAGES HARDBACK**

INCLUDES MAPS &  
NEWSPAPER REPRODUCTIONS  
OF THE TIME

ALL THIS  
FOR ONLY  
**\$12.95**

Cat. B-9500

OVER 100 B&W AND  
PHOTOS COLOUR

SOME NEVER PUBLISHED BEFORE!

**MAKES A  
MAGNIFICENT  
CHRISTMAS GIFT!**

**14 DAY TRIAL OFFER!!!**

YES, please send me a copy of 'Kookaburra'. I understand I can return it in 14 days for a full refund.

Name .....

Address .....

P/cod\$ .....

Payment by cheque ☐ bankcard ☐

**DICK SMITH ELECTRONICS  
MAIL ORDER CENTRE**

P.O. Box 321, North Ryde, NSW, 2113. Ph: (02) 888 3200.

Bankcard No. .... Expiry date .....

Signature .....

ALSO AVAILABLE AT NEWSAGENTS AND DICK SMITH STORES



**FREE POST & PACKING!**




# STAGE & EFFECTS LIGHTING

## ALL YOUR REQUIREMENTS AUSTRALIA WIDE

### DIMMERS

BARRATT LIGHTING IS PROUD TO ANNOUNCE ITS NEW RANGE OF DIMMER SYSTEMS — DESIGNED AND MANUFACTURED HERE IN AUSTRALIA.

#### JANDS JL24/8 AND JL36/12

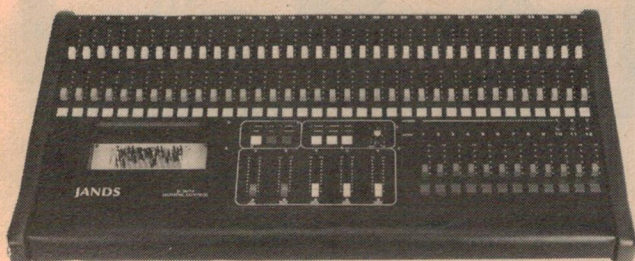


These new generation lighting control desks have been designed by Jands as cost-efficient, state of the art units — with features not previously available in standard dimmer desks.

##### FEATURES (24 and 36 Channel Desks)

- 2 presets and masters.
- Scenemasters with pin-matrix.
- Variable rate chaser over 3 scenemasters.
- Flash-to-full buttons on each channel and on each master.
- Ad-kill function allows instant kill when any one flash button is pressed.
- Masters on chaser, scenemasters and overall.
- Optional desk lamps.
- Talk back link.
- Parts bin and padded armrest.

The Jands JL24/8 and JL36/12 offers a perfect package for most applications — BANDS, CABARET, THEATRE, SCHOOLS — anywhere accurate, fast and simple lighting control is needed.

#### CEITEX DIMMER RACK

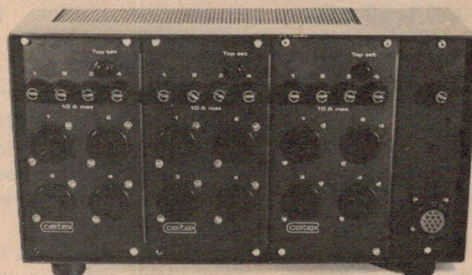

After 4 years of research and development, Ceitex have released a 12 channel dimmer rack, compatible with Jands and Strand dimmer desks.

The Ceitex dimmer rack is a 12 x 2000 watt system, designed to run directly into 3 phase power at 30 amps per phase. Standard size allows rack mounting with the system quite happy to tour — being of very robust construction.

##### FEATURES

- 12 x 2000 watt channels.
- Front trimming access to set top level.
- Drives inductive loads (Hotspots, Rainlights etc).
- Advanced RF filtering — less buzz, pop and plop than any comparable system.
- Modular construction — 3 x 4 way modules with easily removable triacs.
- Dimmer rack will interface with almost any desk currently available — self sensing interface.

#### JANDS DESKS AND CEITEX RACKS — THE PERFECT COMBINATION.

#### 1981 STAGE LIGHTING COURSE

Barratt Lighting is promoting an intensive stage lighting course, to be held on Saturday 17th and Sunday 18th January, 1981. The course will cover a broad spectrum of the Stage and Effects Lighting Industry. The cost is \$25.00, including refreshments, notes, and a night out on the Saturday night.

To enrol, or for further information, contact Barratt Lighting Pty. Ltd.

Call your nearest Barratt Lighting agent for hire or sale of Australia's best range of stage lighting equipment.

Not all agents carry complete stocks at any one time — phone ahead first. In any case, our ex-Sydney despatch to our agents is super-fast.

**SYDNEY:** Ceitex 2/33 College St, Gladesville (02) 896-2900

**WOLLONGONG:** Trilogy Electronics 40 Princes Hwy, Fairy Meadow (042) 83-1219

**NEWCASTLE:** Your Move Lighting 37a Beaumont St, Hamilton (049) 69-3560

**BRISBANE:** Harvey Theatrical Lighting 21 Crosby Rd, Albion (07) 262-4622

**BRISBANE:** Rave Light & Sound 95 Bridge Rd, Fortitude Valley (07) 52-3310

**GOLD COAST:** Rave Audio Visual 2388 Gold Coast Hwy, Mermaid Beach (075) 38-3331

**MELBOURNE:** Clearlight Shows 17 Alex Ave, Moorabbin (03) 553-1446

**MELBOURNE:** Lighting Corporation 131 Brighton St, Richmond (03) 429-5122

**ADELAIDE:** Hiwatt Lighting 37 Angus St, Nth Adelaide 5006 (08) 212-2033

**ADELAIDE:** Optical Acoustics 22 Finnis St, Nth Adelaide 5006 (08) 267-2049

**ACT:** Topstage Productions 8/14 Kembla St, Fyshwick ACT 2609 (062) 80-4694

**PERTH:** Stagecraft 1142 Hay St, West Perth 6005 (09) 321-9363.

**PERTH:** Kosmic Sound 1074 Albany Hwy, Bentley (09) 361-8981

**HOBART:** Good Oil Sound 310 Liverpool St, Hobart (002) 23-5151

Also available Australia-wide at Strand Rank Electronic outlets.

Distributed nationally by

Telex AA25298

**BARRATT LIGHTING** PTY. LTD.

140 Myrtle Street, Chippendale, NSW 2008.

NOW OPEN: New One-Stop Lighting Shop Showroom. All products ex-stock.

New Phone No. (02) 698-8499



## 'Our' satellite gets go ahead

Australia is to have her own communications satellite, which will also be able to broadcast TV and radio programmes direct to homesteads in isolated areas.

**The satellite, which will be launched towards the end of 1984, is currently expected to cost around \$250 million.** pean Space Agency's Ariane rocket, it has not yet been possible to decide where and by whom the satellite will be launched.

Although it is well known that cost estimates for such large scale projects tend to increase exponentially with time, we understand the Government has no plans at present to organise a public lottery to raise the money!

Because of the setbacks encountered by both NASA's Space Shuttle and the Euro-

The satellite and its associated earth stations, for which tenders will be invited at the end of October, will be owned and managed by the Overseas Telecommunications Commission (Australia). OTC are always keen to remind us that they are an entirely separate statutory body and are quite independent of Telecom.



### Automatic distortion analyser

**Level setting, tuning and nulling are performed automatically by the latest THD analyser from Tektronix.**


The AA501 analyser, with its companion SG505 oscillator, is designed to cut measurement costs by reducing the amount of time spent by skilled operators in setting up equipment. An option allows measurement of intermodulation distortion as well, on signals conforming to SMPTE, DIN or CGIF standards. For easy readout there's a 3½ digit LED display that indicates distortion in dB or percentage terms. Signal input to the AA501 is displayed in dB, dBm or volts and detector response is selectable for true rms or average.

A special feature of the analyser section is a 'reference

memory' circuit to simplify measurements of gain/loss, frequency response and signal to noise ratios.

The oscillator is said to be accurate to within 0.0003% over the whole audio range and to have a frequency response that varies no more than 0.1 dB from 10 Hz to 20 kHz. A step attenuator gives calibrated outputs from +10 dBm to -60 dBm in 10 dB steps with variable attenuation in between.

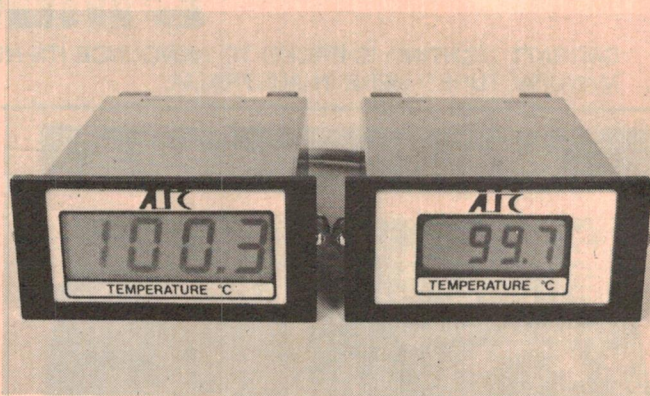More information is available from Tektronix Australia Pty. Ltd., 80 Waterloo Road, North Ryde, NSW 2113. Phone (02)888-7066.



### Versatile digital panel meter

**The Amalgamated Instrument Co. recently released a versatile LCD digital panel meter that can be supplied to suit a variety of measurements — from dc voltage to temperature, pressure etc.**

The panel meter is locally designed and manufactured and can be obtained with a 12.5 mm or 19 mm high liquid crystal display.

The meters shown in the photograph here are configured to read temperature.

As optional extras the instrument can have recorder output, alarm relay contact closure or

proportional control output. The meter can be powered from either 12 Vdc or 240 Vac. Price for the basic unit (12 Vdc supply) is \$160.50, the 240 Vac model costs an extra \$20.

Size is 96 mm wide by 48 mm high by 126 mm deep.

Details from AIC at P.O. Box 305, Narrabeen NSW 2101. (02)452-2648.

### All solid battery

**Storage batteries with a capacity seven times that of lead/acid types are being developed at The University of New South Wales.**

Dr Les Harris of the Department of Physics is working to perfect an all solid cell with a lithium alloy anode and a cathode made of titanium disulphide. The latter is known as an intercalation compound because it has microscopic pores in which ions can be trapped.

The electrolyte will be lithium iodide in powder form. Complex physical and chemical interactions that take place when the compound is mixed with other electrolytic powders have enabled Dr Harris to increase its basic conductivity by five hundred times.

Despite a predicted storage capacity of 200 wathours per kilogram, this kind of battery

could never be used to power an electric vehicle because it would not be capable of the high discharge rates needed to accelerate from a standing start. Its most likely application is as a storage battery for solar generated electrical energy.

### ERRATA

In the **ETI-475 AM Tuner**, details of RFC1 were left off the parts list. This is a Philips type VK200 and consists of a six-hole ferrite bead with 22 swg tinned copper wire passed through it five times. The bead is a type 4312-020-31550 and is commonly available. Also, in the antenna details the copy beneath the antenna matching coil should read: "For use with small loops 6-8 turns" and "For use with large loops 2 turns".




## Did you miss it?

In last month's issue there was a loose insert which gave details of a new publication called the "Australian Microcomputer Handbook".

Produced by Computer Reference Guide, the book contains detailed summaries of the extensive range of microcomputers which are currently being sold in Australia. There are also eleven chapters on microcomputers and microcomputer systems, which cover everything from the Architecture of the CPU to Word Processing, from Basic Programming to User Markets. The book sells for \$22 including post and handling.

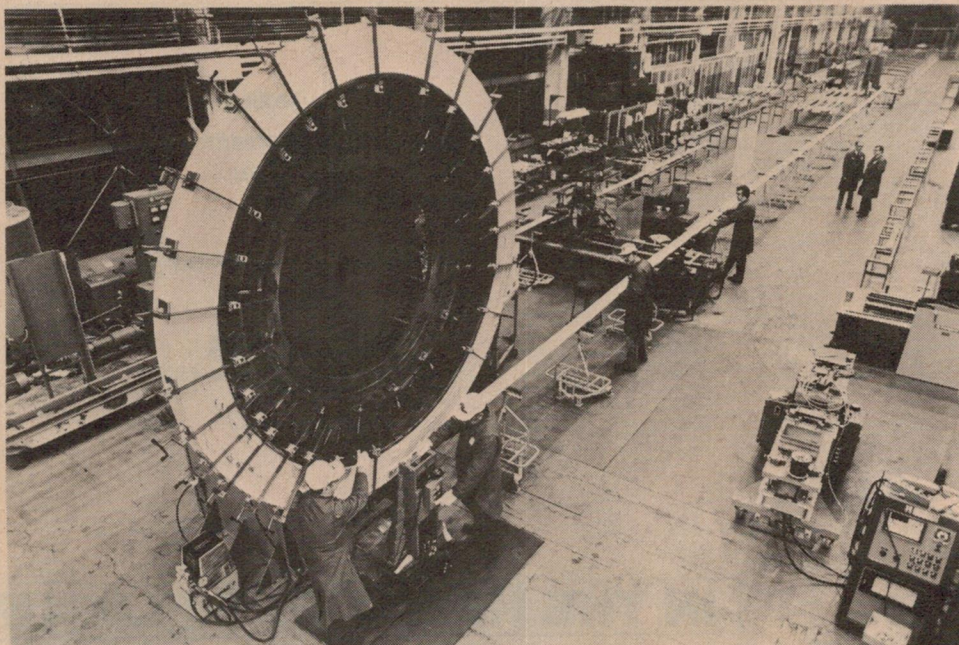If you missed the insert in your issue, you can obtain more details and an order form from Computer Reference Guide, Suite 204, 284 Victoria Avenue, Chatswood, NSW 2067. (02) 411-2567. Mention ETI.



### SOME COIL !

Technicians at the US Westinghouse Electric Corporation wind another layer of copper onto a large magnetic field coil for use in the Tokamak Fusion Test Reactor (TFTR) at Princeton University. Westinghouse is making 22 coils for the fusion device. Each is wound with over 450 m of copper conductor weighing 11 200 kg, to a 3 m inside diameter and 4¼ m outside diameter.

Princeton University's Plasma Physics Laboratory will use the coils as part of a scientific proof-of-principle experiment on the use of Tokamak devices for fusion power under the US Department of Energy's fusion energy programme.


The water-cooled coils provide the magnetic field which serves as the primary containment for the plasma, which will reach temperatures near that of the sun — 100 million °C. The first coil will be shipped during 1980.

## Another new face at ETI

Pictured here is William Fisher, our new sub-editor. Actually he's been working for us since the end of May, but was too shy to have his photograph taken before.

William, who came to Australia in November of last year, was born in the UK. In 1966 he was admitted to the London School of Economics to study philosophy but after a year there he decided that science was much more attractive and moved to the University of Nottingham. He graduated in 1971 with an honours degree in Physics and went to work as electron microscopy technician at the London School of Hygiene and Tropical Medicine.

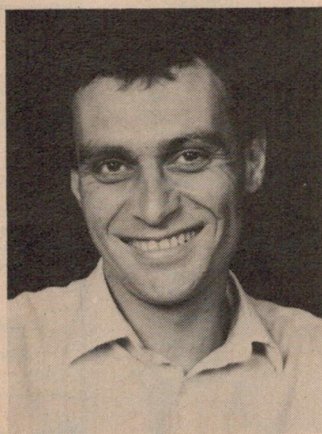Two years later he said goodbye to the world of leprosy and amoebic dysentery and became a technical writer for the Foxboro instrumentation company writing instruction manuals for industrial process control systems. In 1975 he be-



gan working for UK publishers Marshall Cavendish and stayed on their staff for two years, after which he became a freelance editor and scientific writer.

## The Earth's magnetic field will flip

Recent satellite data suggests that the Earth's magnetic field will "flip over" soon (geologically speaking) — perhaps 1200 years hence.

Paleomagnetic evidence shows that the Earth's magnetic field flips over, the north and south magnetic poles exchanging position, at intervals ranging from 50 000 to one million years.

It seems from geophysical studies of the remanent magnetism in crustal rocks that the last reversal was about 700 000 years ago.

The coming flipover (or magnetic flip-flop) is suggested from data gathered by Magsat, a small satellite that burned up in the atmosphere back in June. Analysis of the satellite's data has confirmed previous observations that the strength of the Earth's magnetic field is slowly declining. According to Magsat,

it's on the wane at about 1% per decade.

If it continues to decline at the same rate (a big if) the field should reverse about 1200 years from now. However, geophysicists say that other factors could precipitate an earlier or later change.

How a decline and reversal of our magnetic field would affect us is an open question. Certainly, it would influence the ionosphere and magnetosphere greatly but what effects it would have on climate etc are open to speculation.

Some theorists have linked previous field reversals to mass extinctions of fauna (dinosaurs etc), but there is little hard evidence.



# MAGRATHS



HAVE YOU  
A CHRISTMAS  
GIFT PROBLEM?  
SOLVE IT BY GIVING A  
SCOPE PRODUCT FROM MAGRATHS.

IF YOU  
CAN'T VISIT  
MAGRATHS, THEY  
WILL POST IT TO YOU.

## IN THE HEART OF MELBOURNE

### MORE **SCOPE** FROM MAGRATHS


SELECT THE HEAD & BASE TO SUIT YOUR NEEDS —

**SCOPE PANAMUSE** hold it anywhere you want it —  
tilts turns and rotates to any position.

**SCOPE PANAMUSE** SELF SELECTION CHART :


#### STEP 1

##### SELECTION OF HEADS

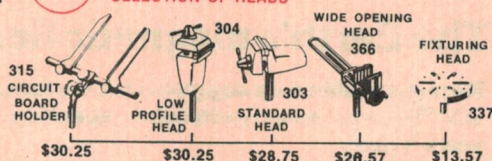


#### STEP 2

##### SELECTION OF BASES

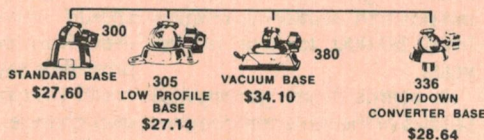



#### STEP 3

##### SELECTION OF BASE MOUNTS

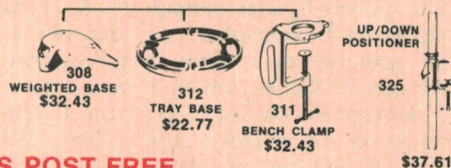


ALL ITEMS POST FREE

### POPULAR COMBINATIONS

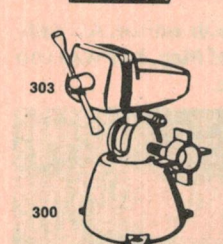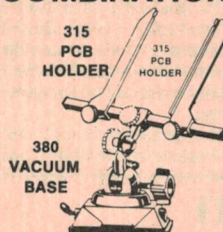

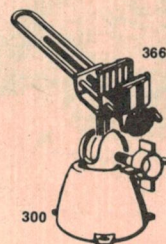STANDARD HEAD (303) AND  
STANDARD BASE (300)



WIDE OPENING HEAD (366)  
AND STANDARD BASE

### MINI SUPERSPEED 20-75 WATTS 5 Second Heating \$21.40

MANUAL TEMPERATURE CONTROL OPERATES FROM SCOPE TRANSFORMER CODE : M.S.

### SUPERSPEED 150 WATTS 5 Second Heating CODE : S.S. \$19.31

MANUAL TEMPERATURE CONTROL OPERATES FROM SCOPE TRANSFORMER

### STEP DOWN TRANSFORMER

240V/3.3V  
CODE : TF \$21.50

### AUTOMATIC TEMP. CONTROL TC60 — 240 VOLT IRON

SELECT ANY TEMPERATURE BETWEEN 200°C — 400°C 13 TIPS. AVAILABLE  
CODE : TC60 0.8mm — 6.4mm \$44.00

### METAL ETCHING PEN

WRITES ON ANY METAL  
OPERATES FROM SCOPE TRANSFORMER  
CODE : MEP \$21.90

### "SELF" CLEANING SOLDER REMOVER

(REPLACEABLE) TEFLON NOZZLE  
CODE : SR 3A \$13.95

### 30X POCKET MICROSCOPE FOR :—

\$29.50. • PRINTERS  
• COIN COLLECTORS  
• ELECTRONICS  
CODE : MK III BUILT IN LIGHT EASY FOCUS SYSTEM

## FOR ALL YOUR ELECTRONIC COMPONENTS



## Dual polarisation for new earth station

**The second satellite earth station at Ceduna in South Australia will be able to handle twice as much information as its sister station.**

This is because it is designed to interact with the next generation of Intelsat communications satellites, which will be able to transmit and receive two different signals simultaneously on the same frequency channel. This will be made possible by giving one signal a left-handed and the other signal a right-handed polarisation.

Another innovation is the use of non-refrigerated low-noise amplification of received signals. Instead of maintaining the whole amplifier in a cryogenic environment, thermal noise is reduced by cooling only the components of the front end by means of the Peltier effect. This

is a thermoelectric phenomenon whereby a current flowing through the junction of two dissimilar metals will lower the junction's temperature. The cooling effect is only effective over a small volume but with miniaturised components this is not a problem.

Unlike the original earth station at Ceduna (which will stay fully operational), the new station does not have the electronics mounted directly behind the dish.

Instead, a beam waveguide fitted with some highly polished steel mirrors is used to convey signals between the equipment room and the antenna.

## Fifty-six channel voice logger

**Stancil-Hoffman's latest voice logging recorder can record up to 56 voice channels for more than 24 hours on a single reel of tape.**


The CRM 5600 uses a tape 1100 metres long and 2.54 cm wide, running at the very low speed of 0.4 cm per second (one quarter the speed of an audio cassette deck). Bandwidth is 300 Hz to 3 kHz, which is adequate for recording speech intelligibly.

Voice logging recorders are used to give accurate documentation of vocal communications in such areas as air traffic control and military operations, where they may be essential for resolving disputes or tracing the cause of accidents.

The tape of the CRM 5600 may be run continuously or allowed to stop when all channels are silent, turning on again immediately and automatically as soon as any channel is opened again. One of the fifty-six tracks may be used to record a digital time signal so that an automatic search mode can search the whole day's tape in three minutes to locate a particular time.



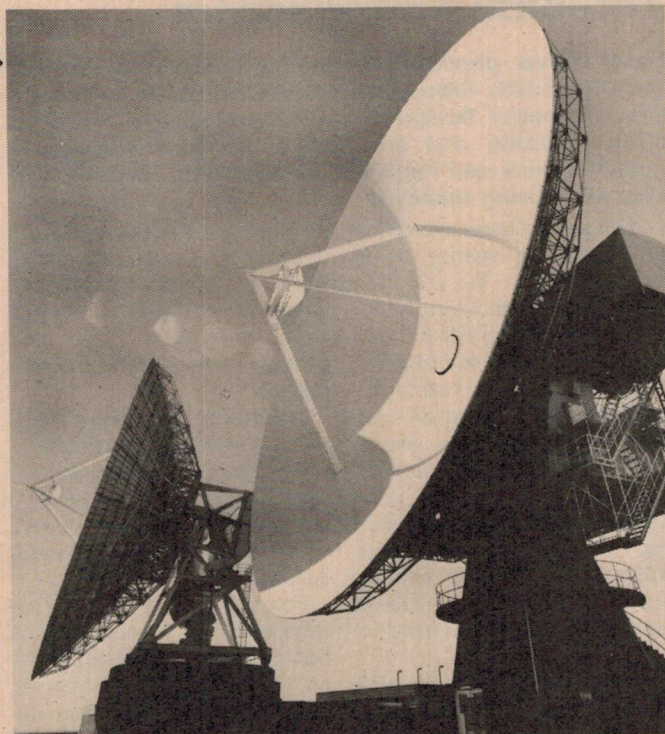More information from the distributors, Rank Electronics Pty. Ltd., P.O. Box 632, Chatswood, NSW 2067. Phone (02)406-5666.



## OTC will track for ESA

**The OTC's earth station complex at Carnarvon in West Australia will be used to track the European Space Agency's launch of two satellites next year.**

The meteorological satellite Meteosat 2 and the Indian communications satellite Apple will be launched into geostationary orbits next February, using the Ariane rocket. The project is still on schedule, despite the spectacular failure of the last Ariane launch on May 23 this year when thermal instability in the combustion chambers caused the rocket to explode and destroy its payload.

By itself, Ariane does not have enough power to take satellites into geostationary orbits, so small 'apogee boost motors' are used to lift the payloads from

elliptical transfer orbits. ESA is experiencing some technical problems in getting these motors ready in time for the launch and may have to swallow its pride and buy American equivalents instead.

Except for the launch station itself at Kourou in French Guyana, the Carnarvon earth station will be the only one in the world to provide tracking and monitoring facilities for both the satellites involved in the February launch. OTC are now contracted to monitor the European Space Agency's launches for the next five years.

## Twelve into one does go !

**Special combiners designed for the Australian Air Force enable common antenna working of twelve transmitters or receivers.**

Each channel is continuously tunable over the range of 225 to 400 MHz and the standard equipment allows frequency separations as little as 1%. With the use of an additional filter for each channel, this separation

can be reduced to as little as 0.5%.

Power rating is 250 watts average per channel and each module can be removed for maintenance without disabling the others.



## Technical writing service

**David Glover, previously Marketing Services Manager for the Dick Smith Group, has established Glover & Associates: Technical Design Group — providing a complete design, writing and art service aimed specifically at manufacturers and importers of electronic products and their advertising agencies.**

"Our service takes over where an advertising agency leaves off" says Glover. "We've got the right balance of technical knowledge and creative skill to make sure that brochures and point-of-sale material are both effective in communicating technical information and are visually arresting and easily absorbed."

"Too often otherwise good ads and brochures are spoilt by copy that's obviously been written by someone with no technical knowledge and is either hard to understand or simply misleading."


With the increasingly wide range of technical products on the market it's become crucial

for a product to be presented so that buyers can quickly understand and assess the product. Good promotional material is often enough to give one product an edge over its competition.

Another of the Group's specialties is instruction manuals.

"A good instruction or assembly manual can save a company a fortune in service calls and helps ensure repeat custom."

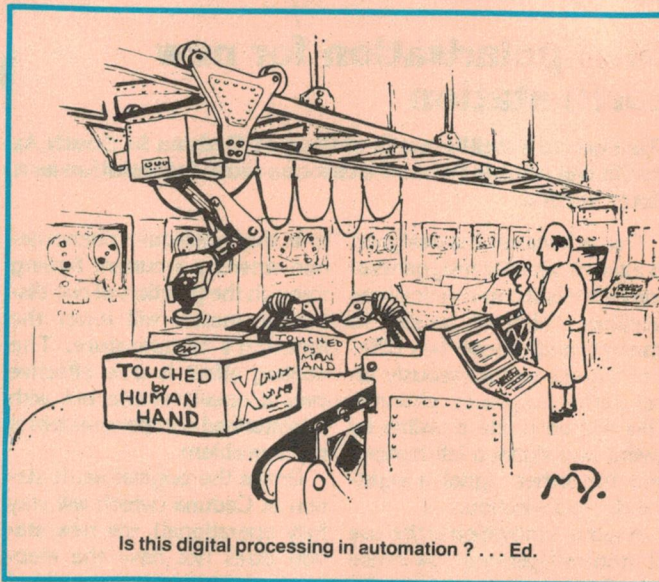For more information on the services of the Group, contact David Glover on (02) 449-7454 or write to 17 Alma Street, Pymble 2073. (This is an unedited press release — Ed.).



Is this digital processing in automation? ... Ed.

## Locally made instrument wins big contract

**A quarter million dollar contract to supply Telecom Australia with direct reading cable fault locators has been won by Melbourne-based manufacturer Aegis Pty. Ltd.**

The contract covers the supply of the CZ.8000 Direct Reading Cable Fault Locating instrument which is designed to locate shorts, crosses, earth faults etc in telephone cables.

It can indicate faults at distances up to 40 km with an accuracy of 0.5%, according to Aegis.

Distance to the fault is indicated directly in metres on a digital display. Compensation is provided in the instrument to

account for variations in wire gauge and cable temperature. Reading accuracy is unaffected by fault resistances up to 1M $\Omega$ , say Aegis.

Aegis won the contract against strong competition, including Hewlett Packard and 3M. Aegis has been manufacturing cable locating and fault finding equipment for over ten years and currently has three instruments under contract to Telecom.

## Electronic lightbulb to save power?

**The General Electric Company of the U.S.A. has developed an electronic light bulb which the company says will generate as much light as a normal 150 W conventional bulb, but consumes only one-third of the power.**

Known as the Halarc bulb, the new lightbulb employs a radio frequency generator to ionise the gas within the bulb, generating an electric arc which provides the light.

As the RF starting circuit can give rise to interference the American FCC must give their approval to the bulb before General Electric can embark on

a 10 000-unit test marketing of the Halarc bulb.

Otherwise, the FCC regulations would have required every bulb to be tested by the consumer or by General Electric once every three years to ensure it was not creating RF interference and this was felt to be impractical.

**Brian Dance**

## SERVICE ENGINEER

Sydney

Our client is an Australian subsidiary of a major international company which specialises in the manufacture and distribution of high technology products. The Australian Company is seeking to appoint a Service Engineer to liaise with customers throughout NSW and service microprocessor-based instrumentation used in analytical chemistry. He will operate from a central Sydney location.

**QUALIFICATIONS AND EXPERIENCE:** This is a senior position calling for a person who can direct and supervise the activities of other service engineers and who can communicate readily with customers.

The person sought will possess tertiary qualifications in electronics and will have a working knowledge of modern microprocessor technology, spectroscopy and chromatography.

The successful candidate will have an outgoing personality and be capable of working on his own. He will probably be between 25-35 years of age.

**CONDITIONS:** An attractive salary will be negotiated. A company vehicle, superannuation and other benefits are also available.

**APPLICATIONS:** May be made in complete confidence by telephoning (02) 27 2687 mentioning position NA 2257 or by writing to the address below:

EXECUTIVE SELECTION DIVISION.

**JOHN P. YOUNG  
AND ASSOCIATES  
(N.S.W.) PTY. LTD.**

MANAGEMENT & PERSONNEL CONSULTANTS  
Caltex House, 167 Kent Street, Sydney, N.S.W. 2000.  
Branches throughout Australasia & London, New York.





# archives

*the price breakthrough in  
performance business computers.*

Success in today's business world demands efficiency and financial accuracy. But the ever-increasing cost and complexities of doing business are forcing you to find new ways to cut labour cost as well as gain tighter control over your business.

The ARCHIVES BUSINESS COMPUTER can give you the control you need to be successful, all in one economical desk-top cabinet.

The ARCHIVES BUSINESS COMPUTER can do your daily business functions such as accounts receivables and payables, general ledger and inventory control. It can keep track of stock on hand, stock on order, and supplies to be ordered. As a Word Processor the ARCHIVES BUSINESS COMPUTER can do your correspondence, text editing of manuals, contracts and proposals. The ARCHIVES BUSINESS COMPUTER can do virtually any information handling or record keeping operation you are presently doing plus many desirable operations that cannot economically be performed by manual methods.

The Archives disk storage can reduce entire filing cabinets to convenient 5¼ inch disks and instantly retrieve any information that you may need when you need it.

Sound incredible? The ARCHIVES BUSINESS COMPUTER is that and more!

It's a business assistant. One that never forgets, never loses reports, makes efficient use of its time and is completely trustworthy.

The ARCHIVES BUSINESS COMPUTER is also easy to work with. So easy in fact, it's no more difficult to operate than any other office machine. While the ARCHIVES BUSINESS COMPUTER is handling the extra work load, you can have more time to develop new business in the field.

There is no question that the major area restricting your business growth is in the office. This is one place where employee efficiency is still in the dark ages - requiring the handling of paper, forms and files. What you really need is not the physical presence of obsolete forms and letters, but the information and data they contain. You need the Archives Business Computer.

The Archives Business Computer offers you an economical way to individualised computing power. You can take it anywhere there's work to be done. Plug it in, turn it on, and it's working for you giving you instant access to the information you need.

Designed especially for a small business or single department in a large company, the Archives Business Computer is a system you can understand and use with a high degree of efficiency without being a computer specialist.

Incorporating quality and reliability the Archives Business Computer provides you with today's and tomorrow's best value in a computer system. The Archives Business Computer is a system to help your business grow.

The Archives Business Computer is backed by competent and qualified technical support for both equipment maintenance and software aid as well as continuing personalised service.


One of the best investments you can make in this inflationary economy is the Archives Business Computer. In fact, virtually every business enterprise can benefit in some practical way from business computing.

A full scale demonstration of the Archives Business Computer will help you draw positive conclusions about how your business can improve its cash flow, reduce costs and risks, improve customer service, increase sales, and improve your employee productivity.

It's time to make a move for the future.  
It's time to contact Computerland  
Melbourne your Archives dealer.
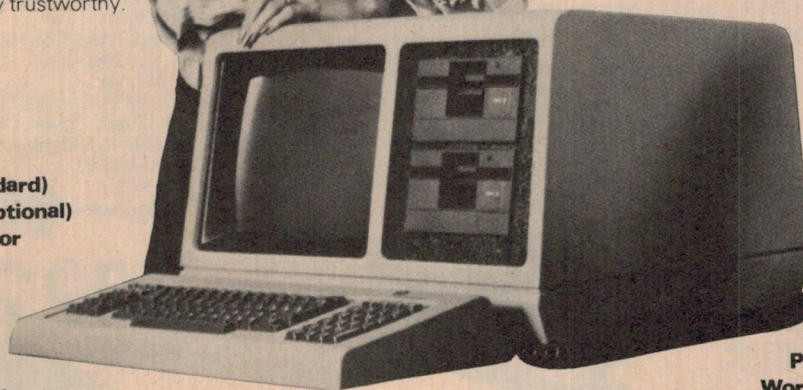
## FEATURES

**Z80 4MHz Processor**  
**64 K RAM Standard**  
**744K Bytes Storage (Standard)**  
**1½ Megabytes Storage (Optional)**  
**12" Green Phosphor Monitor**  
**25 Lines x 80 Display**  
**CP/M Operating System**  
**Selectric Style Keyboard**  
**S100 Expansion Inbuilt**  
**Microprocessor Keyboard**  
**240 x 100 Graphics Format**  
**Numeric Keypad and Function Keys.**



## SOFTWARE

**Microsoft Fortran**  
**Microsoft Basic**  
**Microsoft Cobol**  
**General Ledger**  
**Stock Control**  
**Mail List**  
**CBasic 2**  
**Accounts Payable**  
**Accounts Receivable**  
**Property Management**  
**Word Processing System**  
**Microsoft Basic Compiler**

# ComputerLand<sup>®</sup> in Melbourne

555 Collins St. • Melbourne, Vic. • Australia 3000 Phone 62 5581 • 62 6737 • Telex AA37007





# TOMORROW'S TECHNOLOGY IS IN OUR HANDS.



## ONE PHONE CALL PUTS IT IN YOURS.

Whatever you want in the field of electronics, no doubt you want it to happen fast.




That, quite simply, is what GES is all about. We have the range. And we have the names. No problem is too large or too small. (And the same applies to orders).

We have world wide technical back-up, on-line stock control, an in-house engineer who is only too happy to offer technical advice and

fast service on indent orders.

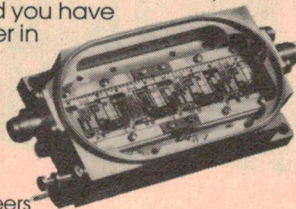Team this with large stocks on major lines and twenty years of business experience and you have the quickest, most efficient dealer in tomorrow's technology. GES.




### Prime Agencies

- Robinson Nugent • Union Carbide
- Kemet Capacitors • Rockwell
- Microprocessors • E.F. Johnson
- AvanteK • Redpoint
- Masterite Industries • Harwin Engineers
- E-Z Hook • Berk-Tek • Continental Specialties • Electrolube
- Erg • Lee Green Precision Instruments • Mini-Circuits
- Piezo Technology • Technit • Transco Products • Elu Elektro - Union GMBH • Compas Microsystems • OPCOA

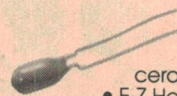
### Components Listing

- Microprocessors, Integrated Circuits
- I.C. Sockets - Production - MIL-SPEC Gold & Tin
- Ribbon Cable and Cable Connectors, Edge Connectors
- Kyna/Tefzel Wire 30 AWG, 26 AWG, 24 AWG, - 10 colours
- D.I.L. Switches colour coded. Keyswitches and Keyboards



- Spacers, Terminals - feedthrough - stand-offs
- Heatsinks PCB type and extrusion
- Capacitors - solid tantalum - tag tants - ceramic and film
- E-Z Hooks and Test Leads, Circuit Hardware

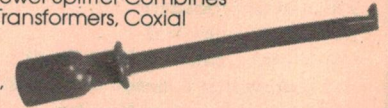- Fuses and Fuse Holders
- Crystal Oscillators, Crystal Ovens, Crystals, Monolithic Crystal Filters • L.E.D. Displays
- Antennas - Microwave
- Amplifiers, Attenuators, Oscillators, Transistors
- Double Balance Mixers, Power Splitter Combines
- Frequency Doublers, R/F Transformers, Coaxial Microwave Switches and Waveguide Switches
- EMI-RFI Shielding material, L.C.D. Connectors



# 439 2488



General Electronic Services Pty. Ltd.  
99 Alexander Street, Crows Nest, NSW. 2065.

GES/MM/CWA





# Pinball wizardry

Ever wondered how a pinball machine works? This article takes you for a guided tour of these complex machines.

**Neil Dunn**

Until quite recently, that seductive demon the pinball machine rattled and clattered its way through a five year life span totally unaided by modern electronic technology. Many of these vintage models are still in service today. With their innards exposed they resemble an old fashioned telephone exchange — there are banks of relays, solenoid operated rotary switches and motor driven counters. All of this electro-mechanical gadgetry is usually powered by a single 28 V source.

Alternating current is used for the

solenoid array, which gives the high current relay contacts at least some chance of survival.

General illumination for the scenery and back glass is provided by 6.3 V 'dial lamps'. Bayonet cap mounted types are used for greater reliability. With anything up to 30 of these lamps used for general illumination and a similar number switched intermittently by relays, currents can easily reach 18 amps. It doesn't require much imagination to visualise the effect of a short on the tightly packed wiring loom if the light-


ing circuit is unprotected!
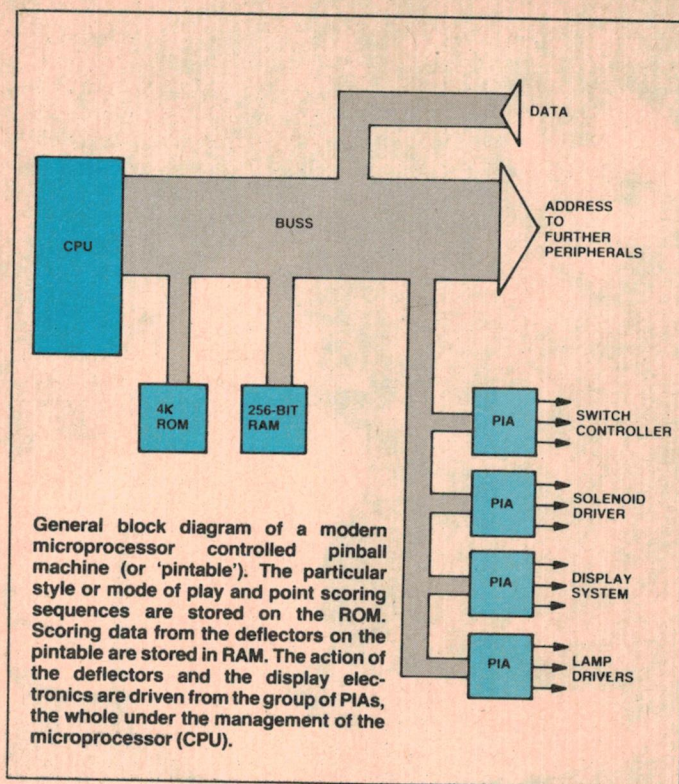
## Playing the game

A brief review of the game will be helpful at this point. The player starts by projecting a 24 mm steel ball to the top of a sloping playfield area. The fun really begins as the ball commences its short but eventful journey to the dreaded outhole at the bottom of the playfield.

During its travel the ball will come into contact with various strategically placed obstacles. These fall into two ►





categories: passive defectors, which are simply high quality rubber O-rings stretched around posts, and active defectors which, generally speaking, sense the presence of the ball by means of leaf switches and use solenoid power to increase its speed on some new, and usually quite random, trajectory.



Every time the ball hits a deflector the player scores points — perhaps ten, perhaps ten thousand — which are accumulated in a mechanical counter. Simple logic circuits are usually incorporated so that particular sequences of deflector impacts accumulate bonus points. If the score reaches a predetermined total, the player wins a free game.

The player can try to hold the ball in play, and thereby gain points towards that elusive free game score, by controlling two or more 'flipper' arms which are capable of diverting the ball from its downward path.

To prevent anyone tilting the whole table to keep the ball in play, most pinball machines include one or more mercury or pendulum switches which make contact when the table is tilted more than a few degrees, actuating a relay which stops the game.
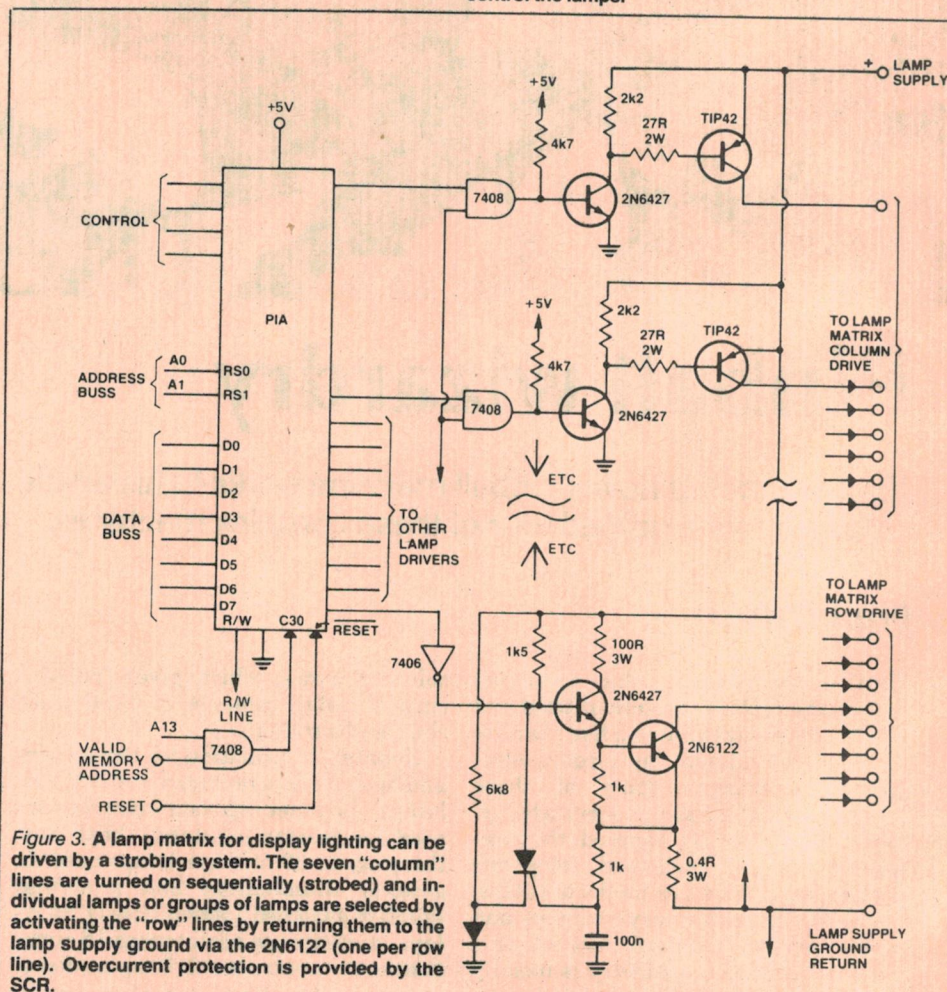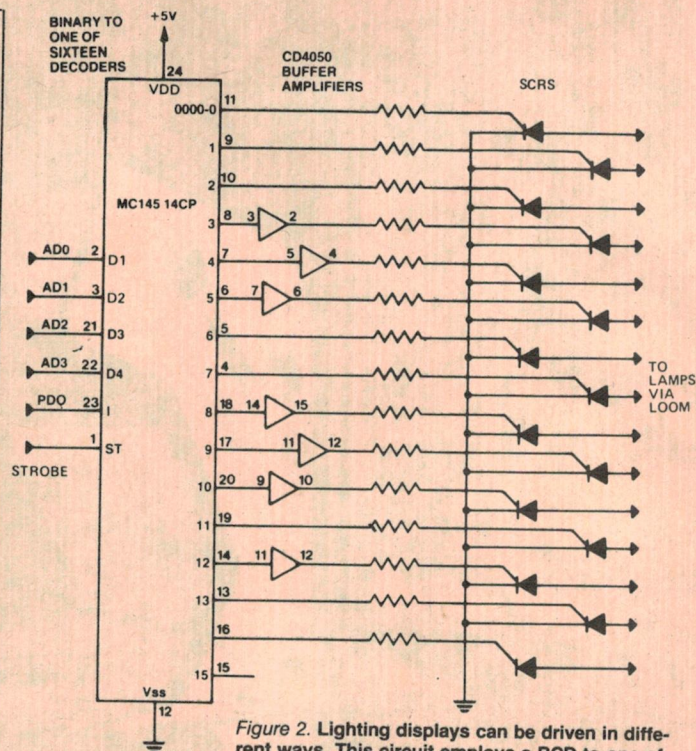
## Flippers

These electro-mechanical devices have not been changed or adapted to electronic control in even the newest generation of microprocessor driven pintables. The power required for this function is quite considerable. Most





flipper solenoids, which are linked to the flipper bar by connecting rod and crank pin, operate from about 24 V and draw starting currents around 10 amps.

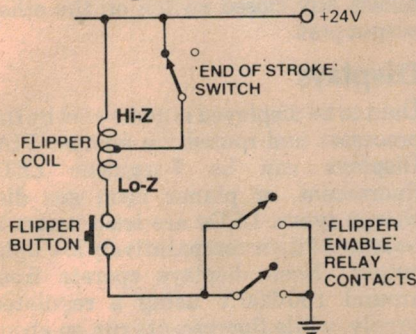


Figure 1. The flippers are driven by a solenoid having two coils — one high impedance (Hi-Z), one low impedance (Lo-Z).

Figure 1 shows a typical flipper circuit. The 'flipper enable' relays are closed when a coin is inserted in the slot. Note that in the rest state the 'end of stroke' switch is closed. This means that the higher impedance coil of the solenoid is effectively shorted out. Pressing the flipper button causes a high current to flow in the Lo-Z coil which generates

an intense magnetic field, operating the flipper.

At the end of the flipper stroke a mechanical linkage opens the 'end of stroke' switch. This cuts off the low impedance coil and allows current to flow through the high impedance coil instead, which maintains a strong enough magnetic field to hold the flipper in position without drawing excessive power.

## Lighting

The more modern machines, with their strobing light shows and spectacular artwork are much more inviting than their predecessors. There may easily be as many as 60 lamps, which are controlled or driven in one of two ways.

The first alternative is to use individually driven transistors or SCRs. A typical circuit is shown in Figure 2. The SCRs or transistors (usually low power Darlington's) are driven directly from TTL outputs or in some cases, CMOS running at 5 V.

The second method is to form a matrix of seven strobe lines and eight return lines. Figure 3 illustrates this. The

eight strobe line drivers are turned on sequentially and only one is on at a time. A lamp anywhere in the matrix can be controlled simply by controlling the return line driver at the time the lamp's strobe line is active. All the return lines may sometimes be switched in at the same time so that each strobe driver must be able to conduct eight times the current of each of the return line drivers, but only for 1/8th of the time. This strobing technique reduces power supply current. Because each lamp's duty cycle is only 1 in 8, a high voltage supply is needed to put a strong enough pulse through the filament to provide a satisfactory RMS power output. Overcurrent protection is usually provided in the return line drivers as short circuits in lamp holders would otherwise be disastrous! This arrangement will allow the system to withstand a permanent short circuit on any lamp circuit without any other lamp being affected.

Data and strobe signals are usually provided directly by a microprocessor. As with all matrices of this type, isolating diodes are used on each lamp so that only one strobe line at a time will be active. Scanning speed is invariably high enough to eliminate flicker, so that all lamps may appear to be illuminated simultaneously.


In the system using individual SCRs the data source is usually a CMOS 4-to-16 line decoder/latch driving 15 lamps. Four of these are used, each one being accessed by the processor as a separate 4-bit output port. The disadvantage of this is that only four lamps can be on simultaneously.

## Microprocessors

The most popular choice of CPU is the 6800 series. Around 3-4 Kbytes is typical for ROM space and about 256 bytes of RAM. At least part of this RAM is low power CMOS (usually 5101-L3) with battery backup from lithium or auto-recharging nickel cadmium cells. This special requirement is due to the accounting functions normally found in a pinball machine. Records are kept of the number of coins through each of the coin slots, the number of free games won and special scoring functions etc. All of this data must be maintained during the power off period.

One point of interest with battery supported RAM is that the processor must be held in a reset state during power down. It is otherwise possible that RAM data could be corrupted as supply voltages fall.

The chip enable input on the CMOS RAM is usually driven from the system reset line to ensure RAM validity. ▶

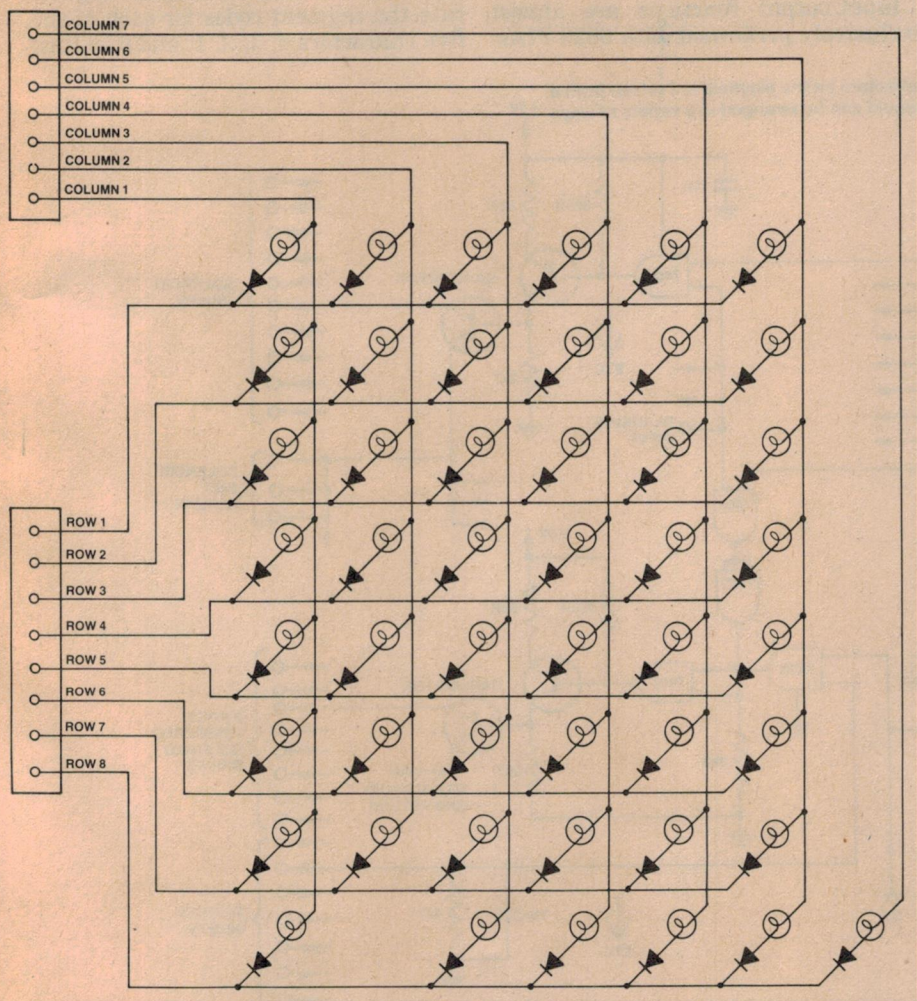



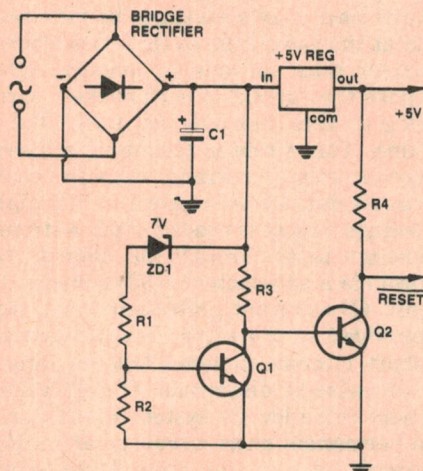
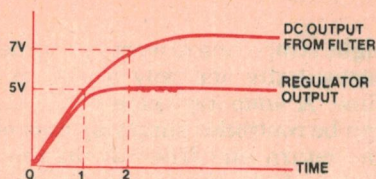


Figure 4. Power-up/power-down reset circuitry ensures RAM validity at all times.

The power-up/power-down reset circuit shown in Figure 4 is typical. It relies for its operation on the voltage differential between input and output terminals of the +5 V regulator. When power is turned on, the voltage across

the filter capacitor C1 starts to rise, providing base current to Q2 via R3. Q2 will therefore conduct and its Vce will be low, thereby providing reset to the system as the regulated 5 V supply rises.

Note that Q1 is not conducting at this early stage because the zener voltage of ZD1 must first be overcome to provide base current to Q1. As the filter capacitor voltage rises still further and ZD1's voltage is eventually surpassed, Q1 conducts and diverts the base current away from Q2. Hence Q2 stops conducting and the reset is removed (time 2 on the graph). Since the processor and clocks etc. have been capable of running since time 1 (when the voltage across C1 reaches 5 V), an effective power up reset has been produced. If power is removed the reverse process takes place as the filter capacitor discharges below seven volts and Q1 is turned off.

The processor is not kept particularly busy, its major tasks being to scan and update the digit display and to scan the 50 or so switches that may exist. During a game the processor is of course performing calculations on scores and making logical decisions as each playfield switch is engaged.

Input/output functions are almost exclusively performed with 6820 PIAs.


Again a matrix technique is used to oversee as many as 60 independent switches. The PIA provides 1-in-8 strobe pulses on one output port and senses any closed switch on the other output port.

## Displays

Data to be displayed is generated by the processor and routed via another PIA. Displays can be 7-segment LED, fluorescent, or planar neon gas discharge types. LEDs are least common because of their comparatively low light output. Neon displays operate from around 180-200 V using a regulated supply, while fluorescents run on about 60 V.

The cathodes of corresponding elements of each digit in the display are connected in common to make seven separate cathode data lines. A CMOS 4-bit-to-7-segment latched decoder feeds a constant current transistor driver in each of these lines with a 1 or a 0, depending on which segments have to be lit to display a particular character. To see how the system works, let's suppose that the processor wants to display the number 43210. First it sends signals to the decoder to make it generate the segment codes for each of the five characters 4, 3, 2, 1, and 0 in turn

Figure 6. The various solenoids used for the active defectors on the playfield are driven from a PIA. Switch inputs for scoring and to activate the solenoid can be arranged in a variety of ways (see text and Figure 7 on page 20).

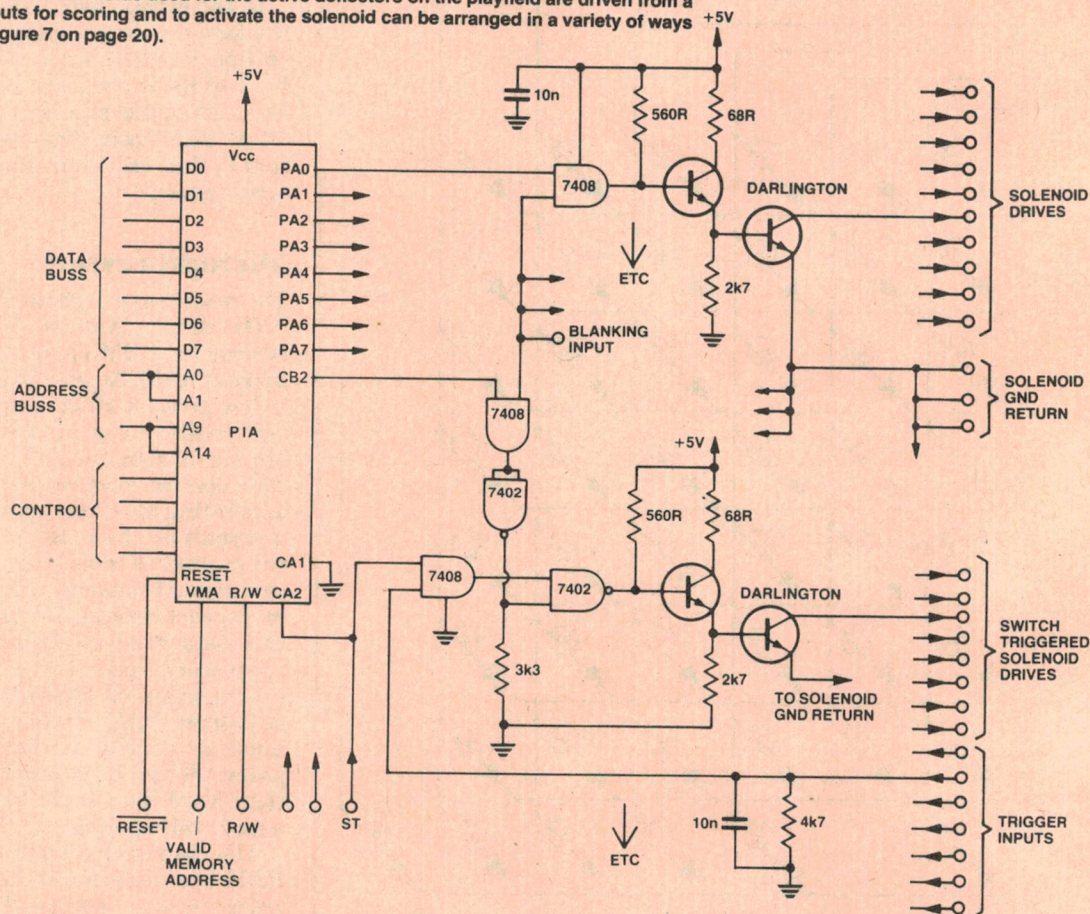



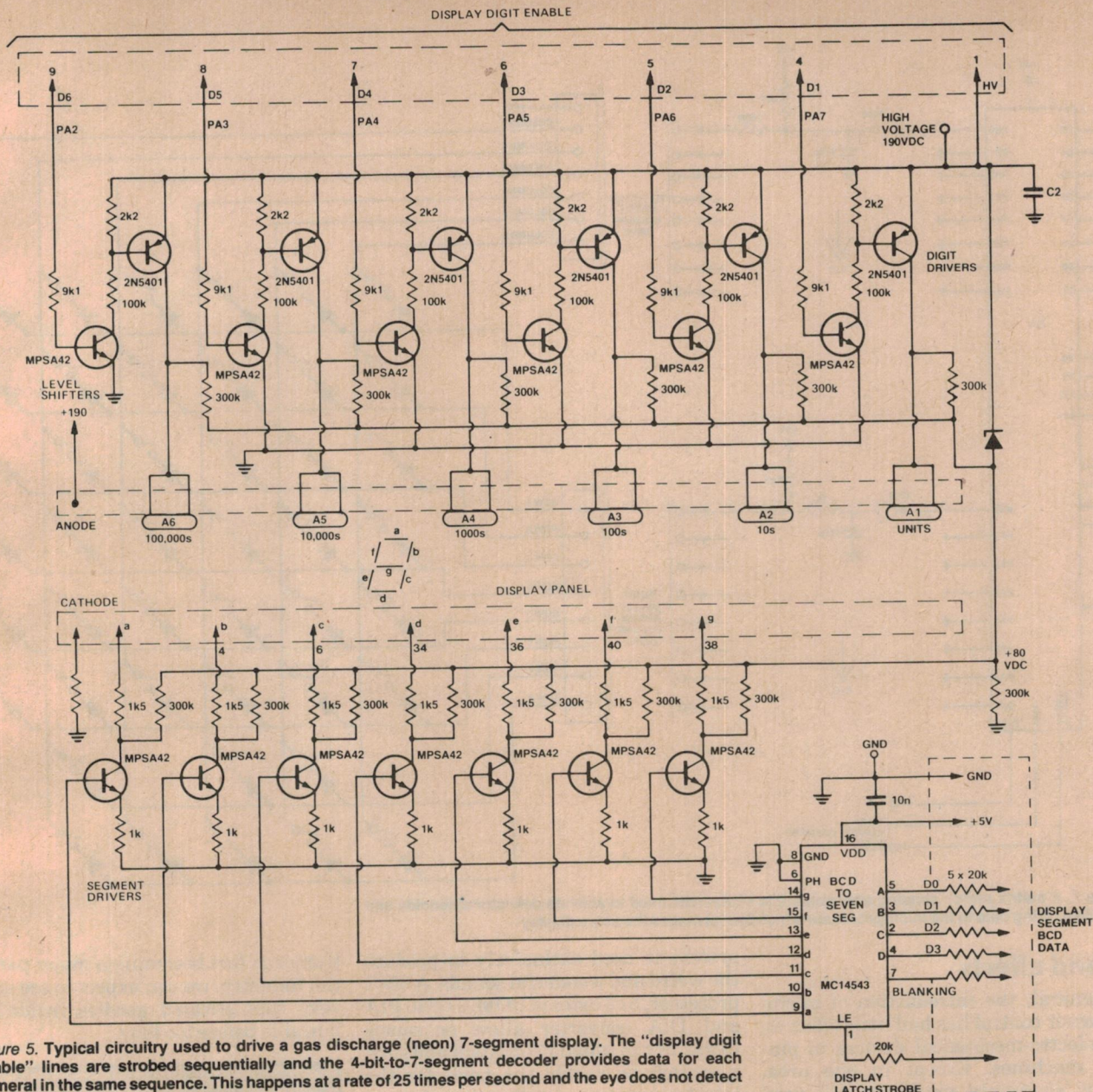


Figure 5. Typical circuitry used to drive a gas discharge (neon) 7-segment display. The "display digit enable" lines are strobed sequentially and the 4-bit-to-7-segment decoder provides data for each numeral in the same sequence. This happens at a rate of 25 times per second and the eye does not detect any flicker.

and repeat the sequence for as long as 43210 is meant to be displayed. If all six anode lines (one for each digit in the display) were activated, the result would be that the numbers 44444, 33333, 22222, 11111, and 00000 appeared on the display successively. But the anode for each digit is program controlled by another signal from the processor to make sure that it is only raised to operating voltage when the correct segment code is being presented to the cathodes. A multiplexer scans all six anodes in turn with the result that the correct character is displayed in each location. If the scan rate is faster than 25 times a second the human eye does not detect any flicker and the number 43210 appears to be steadily displayed.

Because of their high operating voltages, neon displays need high voltage driver transistors such as

MPSA42s. Anode voltage is equal to the supply voltage in the 'on' state and about half this value in the 'off' state. Cathodes are driven towards ground when they are 'on' and held at half supply voltage when 'off'. This is done to stop possible arcing between cathodes and adjacent anodes.

Fluorescent displays work at a lower voltage and are most commonly driven by integrated devices, their filaments being supplied with ac from a separate transformer secondary winding.

## Deflectors

Obviously, the active deflectors are the only ones that present any control problems. 'Bumpers' and 'kicking rubbers' run at around 24 volts and draw three to five amps. Back emf from their solenoids at turn off is quenched by 1 A diodes mounted at the coil terminations. The driver transistors are

typically BD647 or TIP120 Darlington. The 2 V Vce sat. of a Darlington would not permit continuous operation of these devices without considerable heatsinking, but since all these active deflectors are only intended for momentary operation, heatsinks are not used.

There are two common methods of sensing/driving these devices. In the first, sense switches mounted on the device are detected directly by the processor, which calculates the new score and selects the appropriate solenoid driver, usually via a PIA and a 4-to-16 line decoder (74154).

The alternative method is to use two sets of switches on the device. One set actuates a transistor switch (BD647 and gating), which provides solenoid power. The other switch, which is usually mechanically coupled to the solenoid plunger, provides the score input to the processor.







**AT  
LAST!**


# A LABORATORY QUALITY 6.5MHz CRO AT A HOBBYIST PRICE!

Here's what 'Electronics Australia' had to say:

'... this neatly styled little oscilloscope should be just the shot for the hobbyist who cannot afford an expensive CRO ... now a CRO has been placed within the financial reach of most hobbyists ... our overall impression of the Q-1280 oscilloscope is that it represents good value for money.'

This is it! The new Dick Smith Q-1280 laboratory oscilloscope. With a useable bandwidth to beyond 6.5MHz, it's the ideal budget cro for everyone!

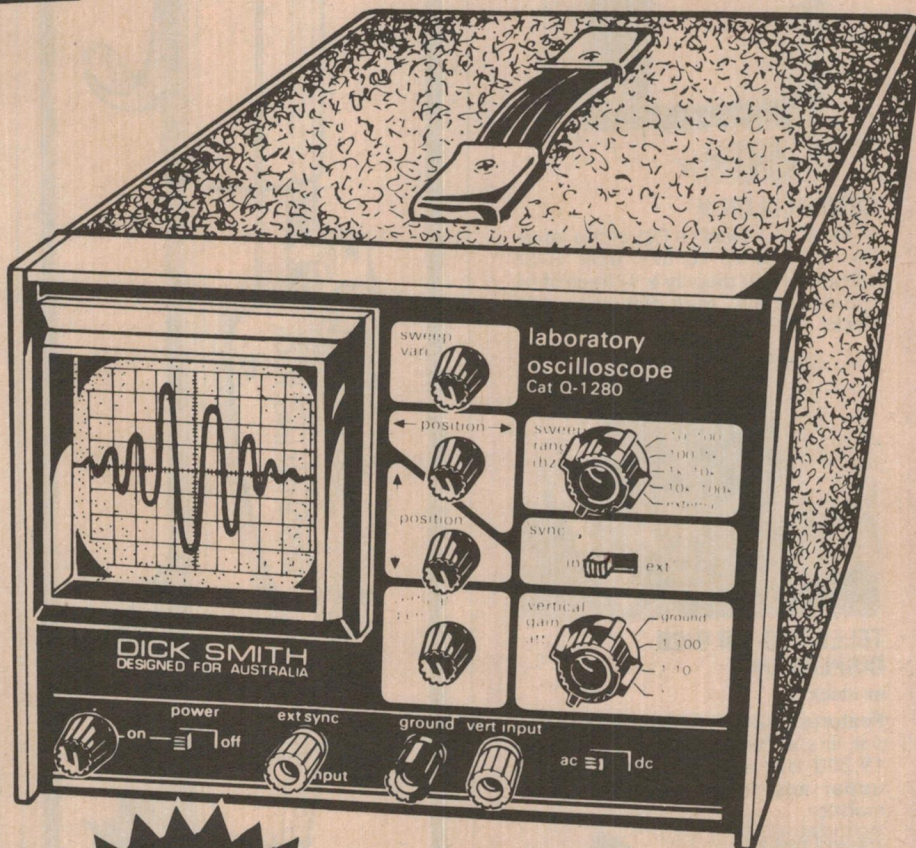- HOBBYISTS
- AMATEURS
- SCHOOLS
- UNIVERSITIES
- SERVICEMEN



**COMES  
COMPLETE  
WITH  
COMPREHENSIVE  
USER'S  
MANUAL**

**ALL THIS FOR  
ONLY**

**\$199<sup>00</sup>**

Cat. Q-1280

## SPECIFICATIONS:

Vertical Deflection Sensitivity: 10mV/DIV  
Horizontal Deflection Sensitivity: 500mV/DIV  
Time base - Sweep Frequency: 10Hz to 100KHz in 4 ranges  
Synchronising: Internal and external.  
Power Requirements: 100/234V, 50/60Hz, approximately 10W  
Dimensions: 202(w) x 160(h) x 306(d)mm. Weight: Approximately 3.8kg.

**\$6.00 Freight anywhere in Australia  
THAT'S BELOW COST!**

## DICK SMITH ELECTRONICS

**NSW** 125 York Street, SYDNEY 290 3377  
818 George Street, BROADWAY 211 3777  
162 Pacific Hwy, GORE HILL 439 5311  
30 Grosse Street, PARRAMATTA 683 1133  
613 Princes Hwy, BLAKEHURST 546 7744  
147 Hume Hwy, CHULLORA 642 8922  
531 Pittwater Road, BROOKVALE 93 0441  
145 Parramatta Road, AUBURN (Opening soon!)

**VIC** 263 Keira Street, 166 Logan Road, 842 Gympie Road, 96 Gladstone Street, 60 Wright Street, 414 William Street.  
**QLD** 399 Lonsdale Street, 656 Bridge Road.  
**ACT** 166 Logan Road, 842 Gympie Road, 96 Gladstone Street, 60 Wright Street, 414 William Street.  
**SA** 166 Logan Road, 842 Gympie Road, 96 Gladstone Street, 60 Wright Street, 414 William Street.  
**WA** 166 Logan Road, 842 Gympie Road, 96 Gladstone Street, 60 Wright Street, 414 William Street.

**WOLLONGONG** 28 3800  
**MELBOURNE** 67 9834  
**RICHMOND** 428 1614  
**BURANDA** 391 6233  
**CHERMSIDE** 59 6255  
**FYSHWICK** 80 4944  
**ADELAIDE** 212 1962  
**PERTH** 328 6944

**bankcard**  
welcome here

**SHOPS OPEN 9AM to 5.30PM**  
(Saturday: 9am till 12 noon)  
**BRISBANE:** Half hour earlier.  
**ANY TERMS OFFERED ARE TO  
APPROVED APPLICANTS ONLY**  
**RE-SELLERS OF DICK SMITH  
PRODUCTS IN MOST AREAS OF AUSTRALIA.**



**MAIL ORDER CENTRE: PO Box 321, NORTH RYDE NSW 2113. Ph 888 3200. PACK & POST EXTRA.**



# \$ THE LOGIC SHOP PTY. LTD.

DISCOUNT SHOPPING for your professional Microcomputer and terminal requirements.



## COMPUCOLOR II


**ex stock** (Reviewed on P91 of this issue)  
Features: • up to 32K user RAM  
• Eight colour display • 32 lines of 64 characters • 5" Mini disk drive • 40 tracks, 48 TPI



## TELEVIDEO TVI 912B DISPLAY UNIT

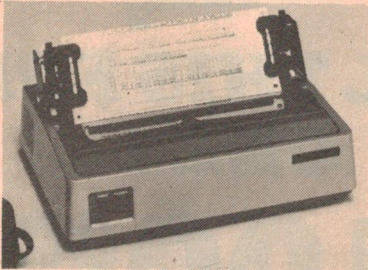**ex stock**

Features: • 24 lines at 80 characters per line • Transmission rates 75 — 19,200 Bd. • 96 character ASCII upper and lower case • 12 inch monitor.



## MICROLINE 80 PRINTER

**ex stock**

Features: • 80 char/sec • 80 and 132 char/line • 9 x 7 dot matrix • Character or graphics printing • **Plug compatible to TRS-80.** ® Rgd. Tm. Tandy Corp.

### SPECIAL

5¼ Diskettes — \$3.95 ea. inc. tax.


\$ THE LOGIC SHOP PTY. LTD.

212 High St., PRAHRAN, VIC. 3181. Tel: 51-1950.  
91 Regent St, CHIPPENDALE NSW. 2008  
Tel: 699-4910

TRS-80 ® is a registered trade mark of Tandy Electronics.

• FAST • CLEAN • EFFICIENT

## SOLDAVAC DESOLDERING TOOL

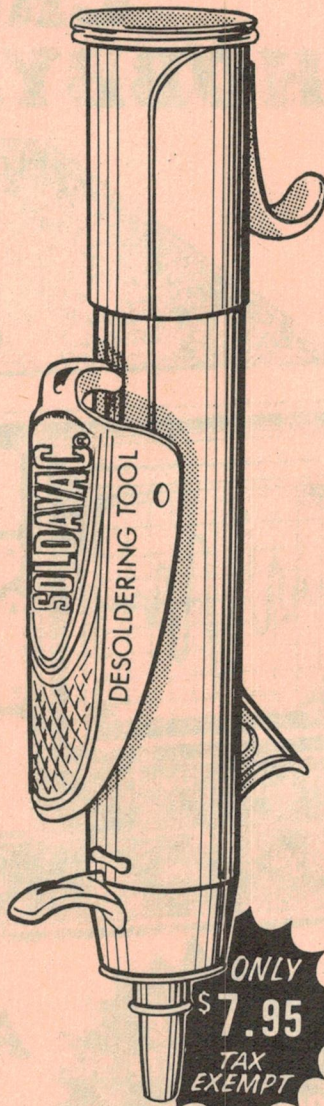

ONLY  
\$7.95  
TAX EXEMPT

Constructed of tough, shatter-proof plastic with a heatproof tip, SOLDAVAC desoldering tool is lightweight and its spring operated suction is designed for one hand operation.

Look for

**SOLDAVAC**

at your regular suppliers.

Or write for further details to:  
**ELECTRONIC COMPONENTS AND EQUIPMENT**

64 Sturt St, Adelaide,  
South Australia, 5000.

Phone: (08) 21-25-999

Telex: AA 89417

Mail Order, add 55c P&P



**PLESSEY**  
COMPONENTS

## NEW PRODUCT

**NOVOL**


**NON VOLATILE  
LOGIC  
256 BIT MEMORY  
(64 x 4)**

## MN9210

- Electrically alterable
- Non-volatile memory
- MNOS technology (not NMOS)
- plus 5 V minus 12 supply
- Low current programming supply minus 39 V
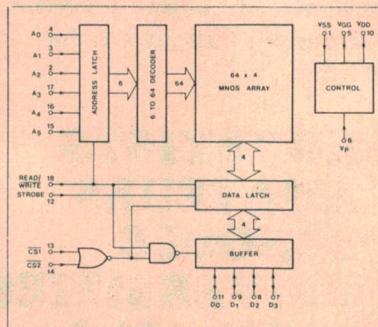
## FEATURES

- Guaranteed data retention of one year in the absence of applied power.
- Latching data and address inputs.
- Three-state outputs on data lines.
- TTL/CMOS compatibility
- Single word preprogramming facilities.
- Temperature range minus 40 degrees C plus 70 degrees C.
- 18-pin dual-in-line package.



This is a new addition to our existing range of Novol.

MN9102 — 4 bit data latch

MN9105 — 4 decade BCD counter

MN9106 — 6 decade UP counter

MN9107 — Counter to 100 hours

MN9108 — Counter to 10,000 hours.



**PLESSEY**  
COMPONENTS

PO BOX 2, VILLAWOOD,  
NSW 2163.

PHONE: (02) 72-0133.



# Semiconductor research brings us the "superconducting transistor"

Researchers at the Argonne National Laboratory, in Illinois USA, have developed a special transistor that relies on the superconducting properties of semiconductors operated at very low temperatures.

**Brian Dance**

A VERY GREAT deal of research effort has been involved in the investigation of the behaviour of semiconductor junctions at very low temperatures. Now workers at the Argonne National Laboratory, Illinois, have developed an experimental superconducting transistor.

When it was discovered that an energy band gap exists in superconductors, it was natural to ask how this energy band gap compares with the well-known energy gap in semiconductor materials. In superconductors the

energy band gap is considerably smaller than in ordinary semiconductor devices, but this is probably not the most important difference. In the ground state no charge carriers have an energy large enough to lift them above the band gap; in semiconductors the material is a perfect insulator in the ground state, whereas in superconductors it is a perfect electrical conductor and it is this difference which is so vital. The normal properties of semiconductors due to the band gap are masked in superconductors by the phenomenon of zero resistance in these materials.

## A transistor

The problems arising from the extremely highly conductive ground state in superconductors can be overcome by using very thin insulating barriers between the elements of a superconducting device. These techniques have resulted in the construction of a device which is a close analogue of the conventional semiconducting transistor.

The new device is of great scientific interest from the theoretical point of view. Although the first device has a current gain of only four, workers at Argonne see no reason why similar devices with a current gain of about one hundred cannot be made using similar techniques. Although it is a little early to discuss applications for the superconducting transistor, it seems probable that it will be used as an ultra-low noise amplifier in cryogenically cooled electronic equipment. As the device will operate only at very low temperatures where superconductivity can exist, applications will be limited to research laboratories and to special industrial work where the problems associated with very low temperatures can be solved.

In the superconducting transistor, the barriers must be thick enough to prevent the Cooper electron pairs (which are the current carriers in the ground state) from penetrating the insulating layer, but single electrons in the excited state must be able to penetrate easily through the barrier. It has been found that a barrier about 3nm in thickness is suitable and that such a barrier reduces

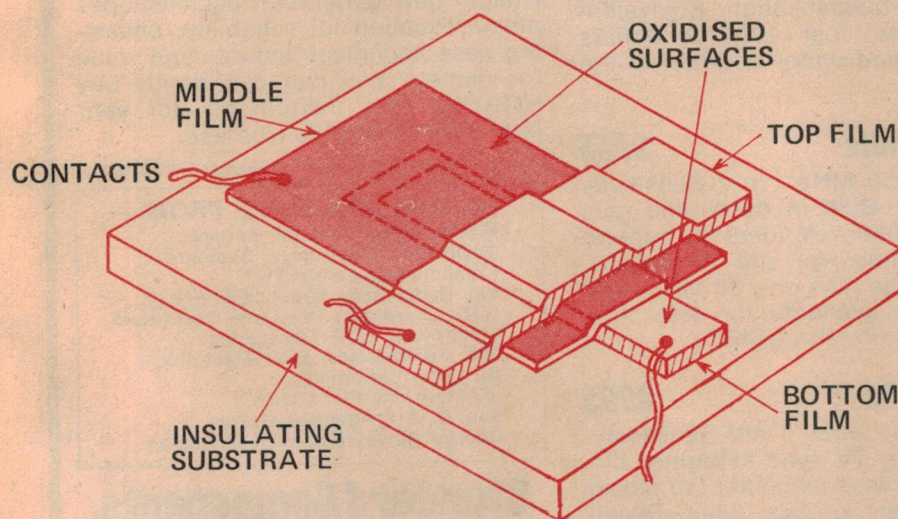



Figure 1. Basic construction of the 'superconducting transistor'. The top and bottom films are totally insulated where they overlap.



the tunnelling of Cooper pairs (the Josephson effect) to a negligible amount. A junction between two superconductors made in this way has certain similarities to a conventional semiconductor junction.

The superconducting transistor is a three terminal device constructed by stacking three thin films of aluminium on top of one another and oxidising the surfaces to form two insulating layers between the films. The structure is shown in Figure 1, the top and bottom films being totally insulated where they overlap.

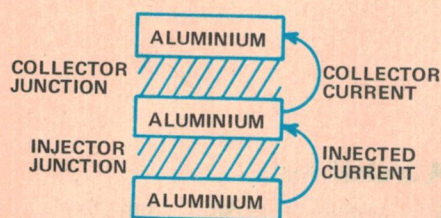The upper oxide junction between the two top superconducting layers serves to break up the Cooper pairs and injects single higher energy electrons into the middle film. The second junction amplifies this current of injected electrons by a cyclic tunnelling process. The bottom



Cutaway view of the junction showing the layered arrangement.

layer is similar to the collector of a conventional transistor, the middle layer is like the base and the upper layer is like the emitter.

The multiplication of charge carriers depends on two crucial effects. One of these is the tunnelling of the injected electron into the lower (collector) layer and the other is the subsequent combination of this electron with a similar electron which has tunneled through the barrier to form a Cooper pair; this creates a new excited electron in the middle (base) film. The process is then repeated until it is eventually terminated by energy dissipation after appreciable multiplication has taken place.

The collector power supply provides the energy required to regenerate excited charge carriers in the middle film and to keep the multiplication process occurring. The original signal creates the injected electrons.

The transfer function of a superconducting transistor is shown in Figure 2. This shows the injected current into the base region on the horizontal axis and the change in the collector current on the vertical axis. The four lines, in order of decreasing slope, are for temperatures of 0.625K, 0.650K, 0.695K and 0.703K, so although the lines are very

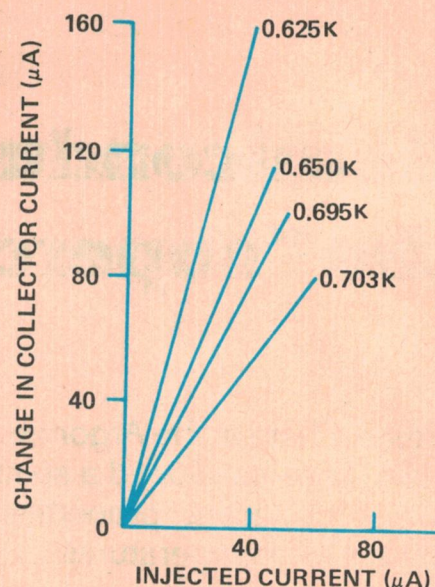



Figure 2. The transfer function of a superconducting transistor. Note the linearity of the function.

linear, the collector current is very temperature dependent.

Readers requiring further information on this new device should refer to the paper by K.E. Gray 'The Superconducting Transistor', *Applied Physics Letters*, Volume 32, part 6, pages 392 to 395, 15th March 1978.




## HITACHI OSCILLOSCOPES

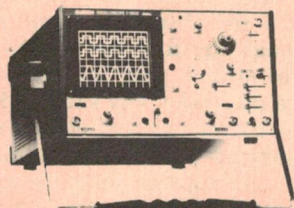

### V550 50 MHz

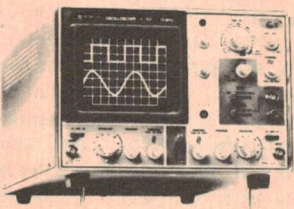**\$1,795**


Professional quality oscilloscope with many unique usable features: 50 MHz Dual Trace, Third Trace Trigger View, 1 mV/Div. Sensitivity, Delayed Sweep, X10 Sweep Magnification. Equivalent Oscilloscopes cost 100s of dollars more. Supplied under contract to the A.B.C.



### V302 30 MHz

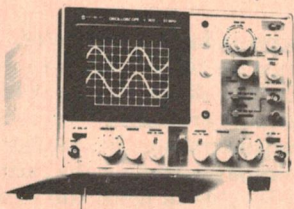**\$955**

Dual Trace 30 MHz 1 mV Sensitivity per division. Built in delay line plus many other features. Ideal for general purpose, transceiver and TV service, and digital use. The only 30 MHz 1 mV oscilloscope available for less than \$1,000. In use by the CSIRO.



### V152 15 MHz

**\$595**

Dual Trace 15 MHz, 1 mV Sensitivity, XY operation, TV sync separator circuit. Sweep times magnifier (10 times) Trace rotation Z Axis Input. Excellent value for money. Supplied to many Government Departments and National TV Service Companies.

HITACHI—  
YOUR MIGHTY  
RIGHT HAND!



Hitachi new generation oscilloscopes are unequalled for reliability, operating ease, technical features and value for money. You can confidently buy HITACHI Test Instruments for year after year of trouble-free use.

Prices + S/Tax 15%. Subject to change. FOT Sydney.

#### HITACHI AVAILABLE FROM:—

N.S.W. Radio Dispatch Service,  
David Reid Electronics, Standard Components, Emtronics.  
Vic. Radio Parts Group, Ellistronics,  
G.B. Telespares, Teleparts, David Reid Electronics, EQC Electronics.  
Qld. Audiotronics, ECQ Electronics,  
St. Lucia Electronics.  
S.A. Bee Jay Electronics.  
Tas. D. & I. Agencies Hobart,  
George Harvey Electric Launceston.

**Standard Components  
Pty. Ltd.** "STOCKISTS IN  
ALL STATES"

10 Hill St., Leichhardt N.S.W. 660-6066



## SOLVE YOUR APPLICATION PROGRAMMING PROBLEMS WITH

### SELECTOR III — C2 \$300 and SELECTOR IV \$500

running on our 64K, twin 8" floppy disk drive OPAL 1000 system with the CP/M 2.2 operating system. The OPAL 1000 can be expanded to grow with your database needs. Send \$1.00 to join our mailing list and to receive your 72 page HARDWARE and 102 page SOFTWARE catalogue.

#### SELECTOR III — C2

Data-base processor to create and maintain multi key data bases. Its features include:

- On-line record definition ● Menu selected, interactive functions ● Stored record definitions ● Stored command selection, report and sort definitions ● On-line data entry, deletion and updating ● Entry verification and editing ● Error detection and comments ● Up to 24 assigned keys per record ● Partial key recall ● Duplicate keys allowed (any number) ● Recall by key in ascending or descending order ● Recall by file sequence ● Recall by relative record number ● Fast machine language key merge facility ● Build new key from existing file ● Rebuild key file if a system crash occurs ● Query by multiple Boolean selections ● Sort on up to 24 fields ● Unlimited report combinations ● Formatted report generation ● Grand-summary and control break sub-summaries ● Label printing ● User sub-program entry and exit points supplied ● Source is supplied (CBASIC 2).

Program library included:

- Sales Activity ● Inventory ● Accounts payable ● Accounts receivable ● Name & Address — Appointments — Events ● Client/Patient file ● Check/Expense register ● Library.

#### SELECTOR IV

SELECTOR IV is a totally self-contained system providing complete data, procedural, query and report definition functions. It allows records to be managed on a one-for-one basis as well as in batch mode where several files can communicate with each other in a variety of ways. It uses the capabilities of an addressable terminal making the entry and editing of data smoothly efficient.

The facets of SELECTOR IV which make it more functional than any other system in its price range include:

**Multiple Key fields.** Of the up to 80 data fields each record can contain, any or all may be assigned to be "keys" so that records can be recalled, individually or consecutively, by the contents of those fields. Most systems either have no key capability, or a data file that must be re-sorted each time a new key is assigned. With SELECTOR IV, data records never have to be sorted.

**Batch, Multiple File Processing.** Because of its multiple key capability, SELECTOR IV can process records from several different files at the same time. It can freely move information from one file to another. It can do it on a conditional basis depending on the content of data within any record. It can arithmetically process one field against another or a constant value, It can convert MANAGER to MANGR, delete redundant records, multiply the QUANTITY in a transaction file against the STOCK PRICE of inventory records, add the results to a Receivables file and update a Journal file, all as the result of a simple procedure definition that can be executed whenever needed.

**Data Definitions.** Records can be structured just as you require. Files can be re-defined and converted as necessity dictates. SELECTOR IV is internationally flavored. It allows dates to be formatted according to any country's convention and can be very useful for genealogical applications.

**Selection Utilities.** SELECTOR IV allows records to be selected, in any order, according to the most definitive, compoundable criteria, either for reporting purposes, or to create uniquely defined new data bases. It can conditionally transform records to new formats and perform arithmetic procedures in the process.

**Reports.** With two report generators at your disposal, your data can be made absolutely productive. Both allow inputs from several different files, with conditional and arithmetic processing. The first is oriented to reporting to you about your data, such as "for each salesperson, list Total sales, Commissions earned, Gross profits produced and products sold, for each department, for each month, in each city, for the third and fourth quarters". SELECTOR IV takes care of the formatting. You just specify what information you want. You can designate up to 80 actual and derived fields to be reported upon.

The second report generator produces output in any form that you want. Anything from gummed labels, to dated, automatically sequentially numbered invoices, complete with text paragraphs can be produced on printed continuous forms of plain paper.

**Hard and Floppy Disk Oriented.** SELECTOR IV is as at home on a 5 1/4" floppy disk as well as the OPAL 5-5. It will manage as many records as your operating system can handle. Files can communicate to each other from different "logical" devices. It runs under any 52k (or larger) CP/M (1.4x or 2.xx) compatible operating system and CBASIC version 2.05 or later. It requires a 24 line by 80 column (or larger) cursor addressable terminal.

# JOHN F. ROSE

## COMPUTER SERVICES PTY. LTD.

33-35 ATCHISON STREET, ST. LEONARDS, N.S.W. 2065 AUSTRALIA





## Series 3000 compact stereo amplifier

**Phil Wait**

"Small is beautiful" when you have a premium on space, but there's no need to sacrifice performance. This amp delivers 20 W/channel, has low distortion and costs less than \$90!

THE TREND to living in 'compact' accommodation such as units, town houses and inner city terraces, has led to a demand for appropriately sized household goods and furniture — including hi-fi equipment. The major hi-fi manufacturers all leapt into this market last year, releasing various combinations of separate components and integrated arrangements generally tailored to a size to stack conveniently

on a shelf or bench top and not take up precious space.

This project is aimed at those readers who want something to fill that requirement but want to 'roll their own' to save money or just to gain the satisfaction of having done it themselves.

Apart from that, this project is ideal for the beginner with a little construction experience who wants a 'meaty' project to tackle. This unit is quite

simple to build as the majority of components are mounted on a single printed circuit board and the interwiring has been simplified with the use of 'ribbon' cable.

Despite the low price, compared to other such projects around, this unit is not a 'cheap' amplifier. The performance is demonstrably better than similar amplifiers that cost a great deal more and it can be teamed with some of

### SPECIFICATIONS

#### Power output

25 W RMS, one channel driven  
20 W RMS, both channels driven

#### Distortion (refer to graph)

1 kHz: 0.03% @ full power  
0.013% @ 12W RMS  
10 kHz: 0.08% @ full power

#### Frequency response

Phono: within 1 dB, RIAA  
Other inputs: within  $\pm 0.5$  dB  
from 10 Hz to 20 kHz;  $-3$  dB @ 40 kHz

#### Hum

Phono:  $-60$  dB w.r.t. 10 mV input  
Other inputs:  $-70$  dB w.r.t. 200 mV input

#### Noise

Phono:  $-80$  dB w.r.t. 10 mV input  
Other inputs:  $-86$  dB w.r.t. 200 mV input

#### Tone controls (see text)

Bass:  $\pm 10$  dB @ 50 Hz  
Treble:  $\pm 10$  dB @ 12 kHz

#### Slew rate

15 V/ $\mu$ s

#### Separation

Phono: 46 dB  
Other inputs: 40 dB

#### Sensitivity

Phono: 2.5 mV for full output  
Other inputs: 200 mV for full output

#### Tape output level

200 mV



# compact stereo amplifier

our previously published hi-fi projects to obtain quite a respectable hi-fi set up.


## The design

Overall design is fairly conventional, except for the output stage, but we have paid attention to such details as transient intermodulation and slew limiting distortion as well as keeping total harmonic distortion within acceptably low limits.

The preamp stages employ common integrated circuits op-amps. The power amplifiers employ a differential input stage driving a complementary-symmetry class-B power stage. The output devices are TIP31C/TIP32C 'flatpack' transistors arranged such that a simple heatsink can be mounted on the pc board — which can be seen in the internal photograph. A conventional transformer/bridge rectifier power supply is used and speaker anti-thump circuitry is provided too.

The output stage of each channel is capable of delivering 25 watts (single channel) into an 8 ohm load. If you're building the amplifier as a Christmas present for your kids, in the interest of tranquillity, family relations and the sanity of the family cat/(dog/budgie/goanna) the power output might seem 15 - 20 watts too much. By the simple expedient of using a lower voltage transformer and changing a few resistors, the amp will deliver only five watts(\*). This also reduces the heatsink requirement and the overall price (as the transformer's less expensive). The two different types of transformer are given in the parts list.

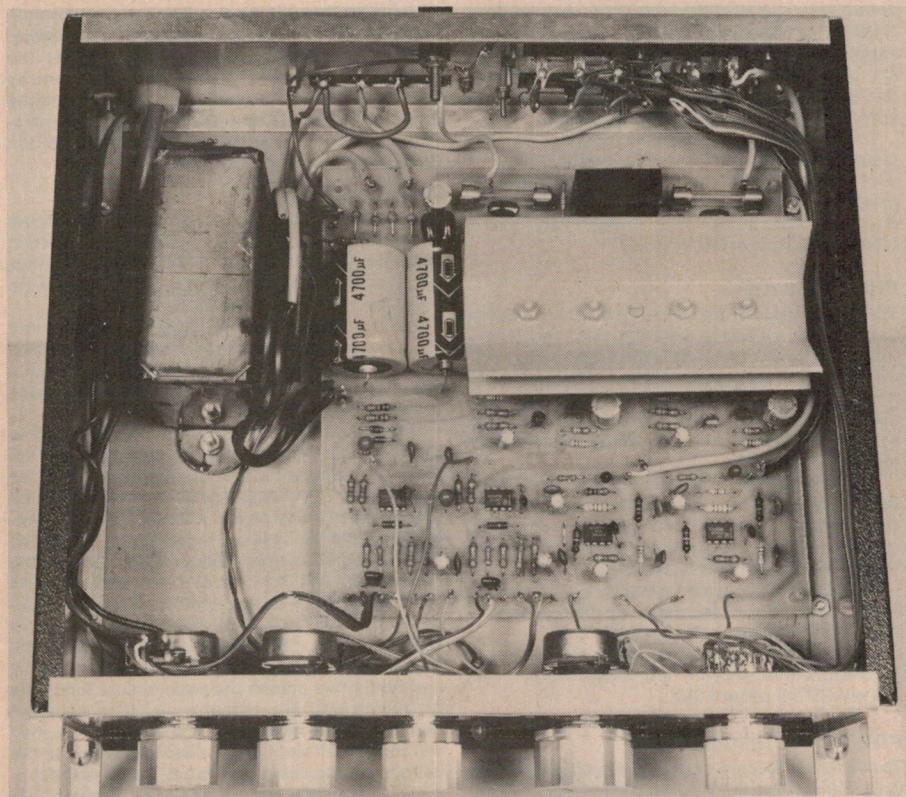\*Psst — kids. If the old fella has built you a five watt amp you can make it up to a 20 W/ch amp without much fuss. Read on.





Internal view of the completed project shows the general layout and obvious simplicity — almost everything's on the pc board. We haven't anything much to say about the external appearance as it speaks for itself! Scotchcal transfers for the front and rear panels will be available from suppliers — see Shoparound on p.83.

When you turn an amplifier on or off, a loud thump may come from the speaker. This transient may have sufficient energy to destroy the speaker! It is caused by the supply line voltage rising (at switch-on) or falling (at switch-off) at different rates. This may cause the output to the speaker to swing wildly between the positive and negative supply rails under the worst-case conditions — spectacular, but costly if your speakers can't handle it. Consequently, we have provided an anti-thump circuit which only connects the speakers after a short delay whenever

the amplifier is turned on. When the unit is turned off, the speakers are immediately disconnected, before the supply rails have a chance to fall appreciably.
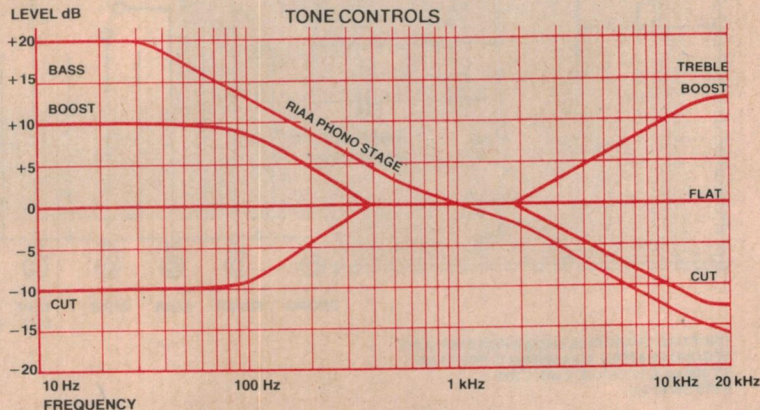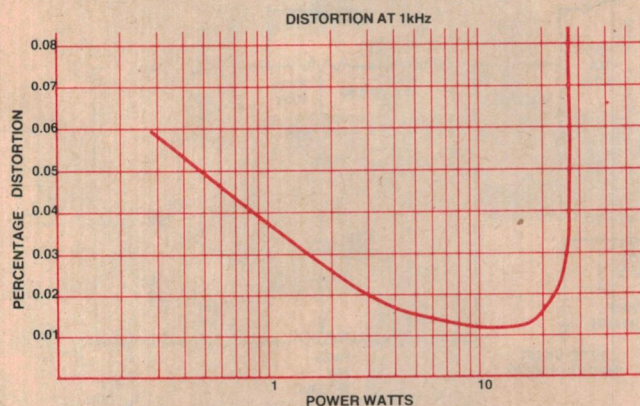
## Construction

We chose to assemble the amplifier in a Horwood instrument case measuring 255 mm by 255 mm by 78 mm overall. These are supplied with black, vinyl covered steel top and side panels and plain aluminium front and rear panels. Handles are attached either side of the ►





# Project 476

## HOW IT WORKS — ETI 476

This amplifier employs common IC op-amps in the phono and preamp stages driving a class-B power amplifier employing discrete circuitry. The power supply is conventional, employing a transformer and bridge rectifier with capacitor-input filters to derive positive and negative supply rails and incorporating a speaker anti-thump circuit.

The following description applies to one channel only as both channels are identical, except for component numbering. Components are numbers IC1, R1, C1 etc in one channel, IC101, R101, C101 etc in the other. Ganged controls are labelled SW1a, b or RV1a, b etc.

### PHONO STAGE

The phono input, from a moving magnet turntable cartridge, is applied to the input of IC1, an LM301, via an R-C network (C1, R1) which provides a roll-off at subsonic frequencies. The feedback network for IC1 (R3, R4, R5, R6 and C4, C5) provides the correct RIAA compensation. Output from this stage goes to the Source switch, SW1, via C7/R7.

Resistor R7 maintains the negative side of C7 at 0 V to prevent speaker thump when operating the Source switch. The purpose of C6 is to reduce the gain of IC1 to unity at dc so that the dc offset at its output is maintained at a low value.

Capacitor C3 provides stability compensation for IC1. Resistor R2 and capacitor C2 provides RF interference immunity for the input of IC1.

Overall gain of the phono amp is about 300 and is designed to provide full power output with 2.5 mV RMS input at 1 kHz.

### PREAMP-TONE CONTROL

The Source Switch selects the various inputs, applying them to the Volume Control, RV1, via the Tape Monitor Switch, SW2.

Output from the Volume Control passes to the input of the preamp-tone control stage via C8. Conventional tone control circuitry around the feedback of IC2 provides boost and cut at 12 kHz for Treble and 50 Hz for Bass. However, unlike conventional controls we have only provided a range of  $\pm 10$  dB for reasons explained in the text.

General gain for this stage is around 10, and input sensitivity is 200 mV RMS for full power out-

put. The slew rate for this stage has been set at 15 V/us so that it is slower than the power amplifier. This has been done by selecting the value of the compensation capacitor, C11 to limit the speed to that required. The R-C network formed by R15 and C12 provides additional slew rate limiting at the output of the tone control stage. This technique avoids transient intermodulation distortion developing in the power amplifier.

### POWER AMPLIFIER

Keen-eyed readers will recognise similarities between this circuit and the ETI-452 Guitar Practice Amplifier (Jan 1980) and the ETI-453 General Purpose Amplifier Module (April 1980). There's no need to re-invent the wheel!

Ten transistors are employed (Q1 to Q10) in a discrete component design. Transistors Q1 and Q2 form a differential input stage. Q4 provides a constant current source for the input stage emitters, biased by R24 and LED1.

Output from the preamp-tone control stage is applied to the Balance control, and thence to the input of the power amplifier stage via C13 to the base of Q1. The collector of Q1 is directly coupled to the base of Q3, an emitter follower which is directly coupled to the base of the pre-driver, Q5. Diodes D1, D2 and D3 maintain about 1.8 V between the bases of Q7 and Q8. Each of these transistors will drop about 0.6 V across their base-emitter junctions. This leaves a total of 0.6 V to be dropped across the two 27 ohm resistors R27 and R28. Since these are of equal value, each drops 0.3 V and holds this across the base-emitter junctions of Q9 and Q10, the output transistors. As these two transistors require 0.6 V to be biased on, they will remain off until the applied signal raises the voltage on the bases above 0.6 V (with respect to 0 V). Only a little more than 10 mA through R27 and R28 will supply the extra 0.3 V to turn on the output transistors.

Transistor Q6 provides a constant current sink (or source, depending on your point of view) for the collector current of Q5, increasing the gain of the drive stage, Q5, and decreasing distortion. There is approximately a one volt drop across R26 (and incidentally, R19).

Emitter ballast resistors are included in the output stage, these being resistors R29, 30 and R31, 32. Their main purpose is to help prevent thermal

runaway in this application and stabilise the gain of each output transistor. They play a secondary role as fuses in the event of a fault condition causing heavy conduction in the output devices. Hence, the text advises these resistors be mounted up off the pc board on their leads.

Negative feedback is supplied by the potential divider formed by resistors R23 and R20. The capacitor C3 represents a short circuit to the common rail (0 V) for ac signals in the audio range. Gain of the stage across the audio range is thus the ratio of R23 to R20, about 12 in this case. At very low frequencies the impedance of C3 increases, decreasing the gain of the power amplifier by increasing the amount of negative feedback. Capacitor C16 increases the speed of the ac feedback at high frequencies.

The base of Q1 is tied to 0 V and as the whole amplifier is dc-coupled, the quiescent output voltage will be held to a value less than about 50 mV.


Output from the power stage is taken via a set of contacts on the anti-thump relay and a 2 A fuse, for speaker protection. The R-C network R33 and C17 provides output phase lag compensation.

The output stage devices — a TIP31C and complementary TIP32C — operate in pure class-B, the effects of crossover distortion being reduced by the feedback arrangements. These devices will deliver 25 W into an 8 ohm load. Only a modest heatsink is required as quiescent dissipation is low. The output devices are operated close to their SOAR limit under certain conditions, but no problems should arise. Lower power output can be arranged by reducing the supply rail voltage (see text).
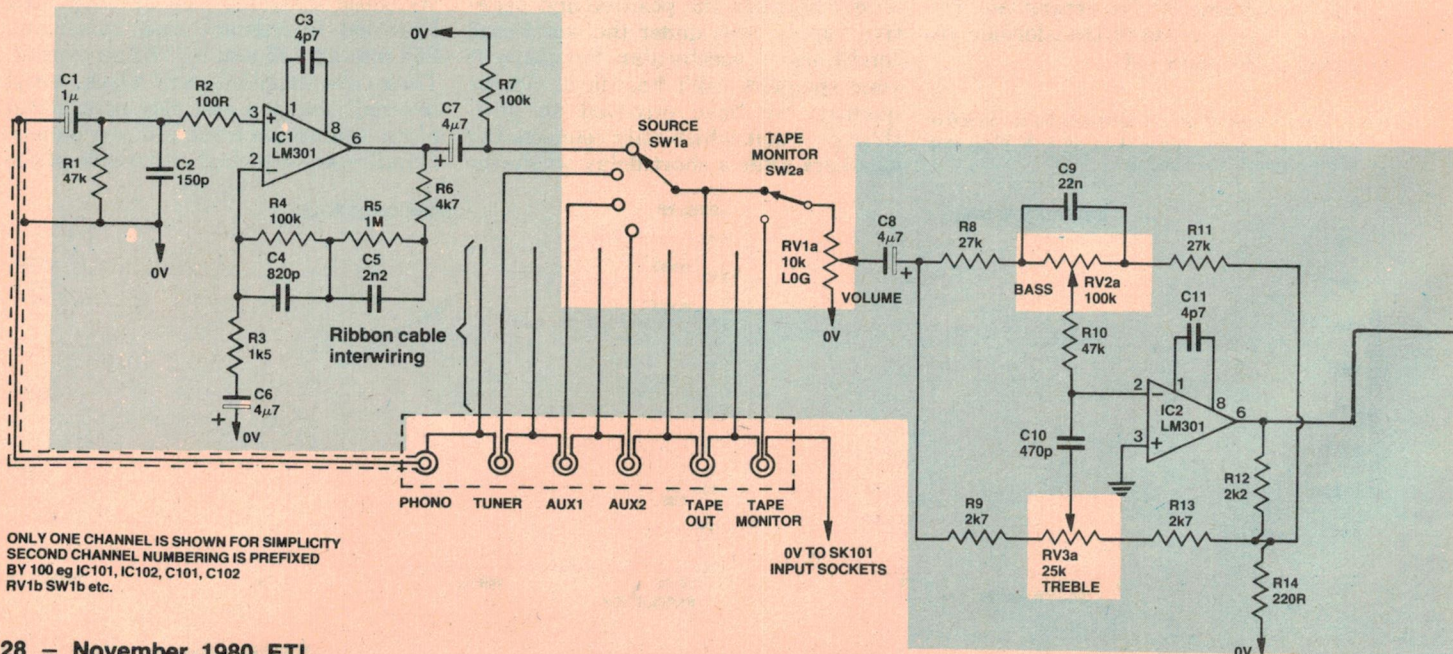
### POWER SUPPLY

The 240 Vac mains input is applied to the primary of the power transformer via the power switch, SW3, which isolates both active and neutral leads. A 'spike' suppression capacitor (C26) is connected on the mains input side of the power switch.

The secondary of the mains transformer consists of two windings connected in series, the 'centre tap' providing the 0 V return line. A bridge rectifier comprising diodes D4 to D7 provides positive and negative supply rails. The main supply rail voltages will depend on the transformer chosen for the desired power output as per the text.





# compact stereo amplifier

Smoothing for each supply rail is provided by C20 and C21. Capacitors C22 and C23 reduce the supply rail impedances at high frequencies. The phono and preamp-tone control stages require  $\pm 12$  Vdc supply rails and these are derived by conventional shunt zener regulators involving R36, R37, ZD1 and ZD2. Capacitors C24 and C25 provide bypassing for these supply rails. LED2 is a 'power on' indicator.

## ANTI-THUMP


The anti-thump circuit involves D8, Q11, C18 and C19, R34 and R35 plus RL1. The object is to isolate the speakers from the power amplifier until the supply rails have stabilised following switch on and to isolate the speakers once again when the amplifier is turned off, before the supply rails have decayed.

The relay RL1 has two sets of contacts which are connected normally open. These contacts are in series with each channel's speaker output line, between the power output stage and the speaker protection fuse.

At switch on, D8 rectifies one side of the transformer secondary, rapidly charging C18, establishing collector supply for Q11 before the bridge rectifier smoothing capacitors have time to charge to a significant voltage. Until such time as C20 charges to 12 volts, Q11 has no base bias and is turned off. Thus, relay RL1 remains unoperated. As the voltage on C20 rises, capacitor C19 will charge via R35. When the voltage on C19 rises to about 12 V, Q11 will turn on and RL1 will operate, connecting the speakers. The R-C network formed by R35/C19 provides a time delay such that the voltage on C19 will only reach about 12 V after the voltage across C20 has risen to the full supply voltage. The delay is several seconds.

When the unit is switched off, C18 will rapidly discharge and the current through RL1 will drop below that required to hold it operated well before the supply smoothing capacitors (C20 and C21) discharge.

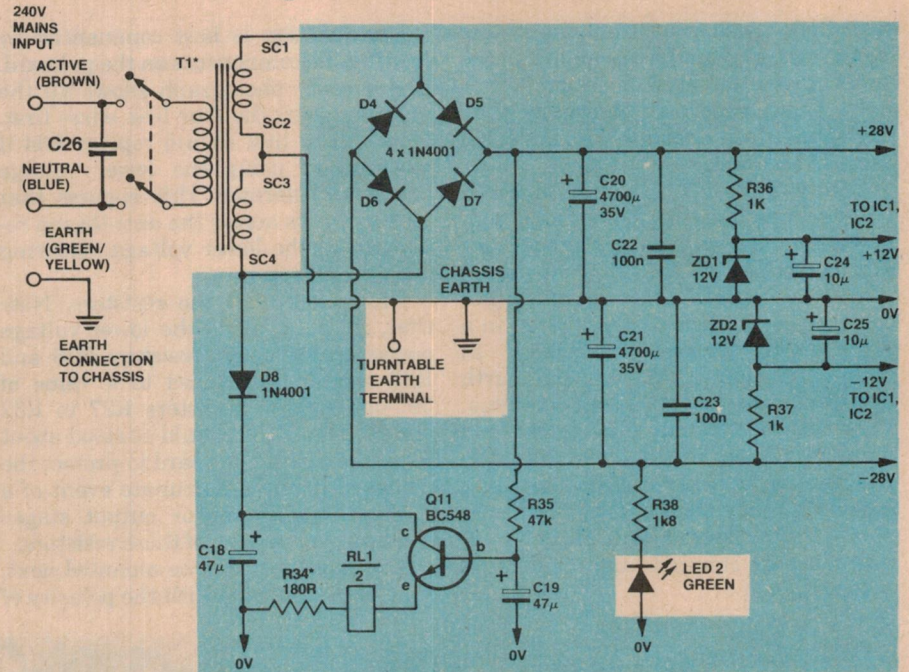Resistor R34 limits the current through the relay to a safe maximum value when Q11 is on. Note that it is not required if the lower voltage transformer is used.




Power supply and speaker anti-thump circuit. A transformer with a secondary rated at 20 - 0 - 20 V at 1.5 A will provide 20 W per channel. For 5 W per channel operation, a 12 - 0 - 12 V at 0.8 A transformer is required. In the latter case, reduce the values of R36 and R37 to 390 ohms each and short out R34.

front panel and these can be obtained in plain aluminium or black anodised. We made up a black Scotchcal label with white lettering (i.e: 'reverse') for the front panel and used brushed satin aluminium knobs. The whole effect is quite attractive.

The layout of the controls on the front panel is kept quite simple. There are only two toggle switches — power and tape monitor. A stereo/mono switch was thought unnecessary as it would add to

the cost and clutter up the simple front panel layout. They are rarely used these days in any case. The rear panel holds the input and output connectors, power cord and an earth terminal for other equipment such as a turntable, headamp or whatever.

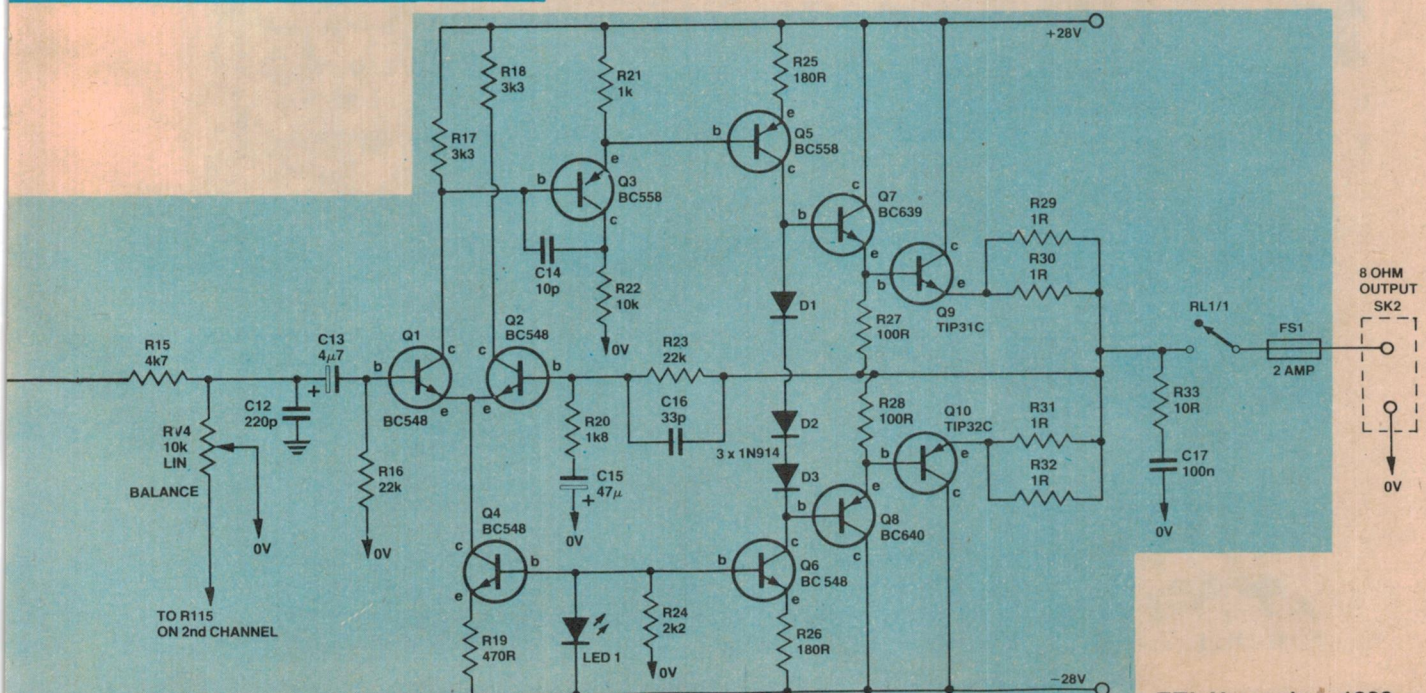We used an internally-mounted heat-sink for the four output stage devices, made from a sheet of 16 gauge aluminium. This heatsink is the minimum recommended for 20W/channel opera-





# Project 476

tion. If you wish, the output transistors can be mounted on the rear panel, in the space above the speaker output terminals. Their leads may be connected to the pc board with hookup wire or ribbon cable in this case.

You will notice from the internal photographs that the phono input connection to the pc board is made with shielded cable, but the other inputs are made via a length of 20-wire ribbon or rainbow cable. This cable is wired in a signal-earth-signal-earth fashion so that each signal wire has an earth either side to provide some shielding. This we tried as an experiment and found it very successful. It simplifies the wiring enormously compared to using individual shielded cables. There was only a slight degradation in the cross-talk between channels and no increase in hum levels.


Construction is best commenced by loading the components on the pc board. The overlay photograph shows all the details. Insert the four link wires first. Note that a link should replace R34 if you intend using the lower voltage power transformer. This ensures that 12 V appears across the anti-thump relay coil at the lower voltage, ensuring correct operation.

Next mount all the resistors. Note that, if you're using the lower voltage power transformer, resistors R36 and R37 should be reduced to a value of 390 ohms each. Resistors R27 to R32 and R127 to R132 should be stood about 4 - 5 mm above the board to protect the pc board in the unfortunate event of a fault in the driver or output stages causing overheating of these resistors.

The capacitors can be mounted next. As usual, take care with the polarity of

the electrolytic and tantalum capacitors. The lead length on the low value ceramic capacitors C3, C11, C14 and C103, C111, C114 should be kept as short as possible. Mount them so that the body of the component is right down on the pc board. The mains transient suppression capacitor is mounted off the pc board, but this is discussed later.

Now you can mount all the semiconductors, except the output transistors. Here too, take care with the orientation of the devices. The pinouts of the BD639s and BD640s do not have the base lead between the emitter and collector leads like most small signal transistors, so take care with these devices. Pay particular attention to the orientation of the diodes D1 to D3 and D101 to D103 as these set the voltages on the bases of the output transistors. If they are inserted the wrong way round

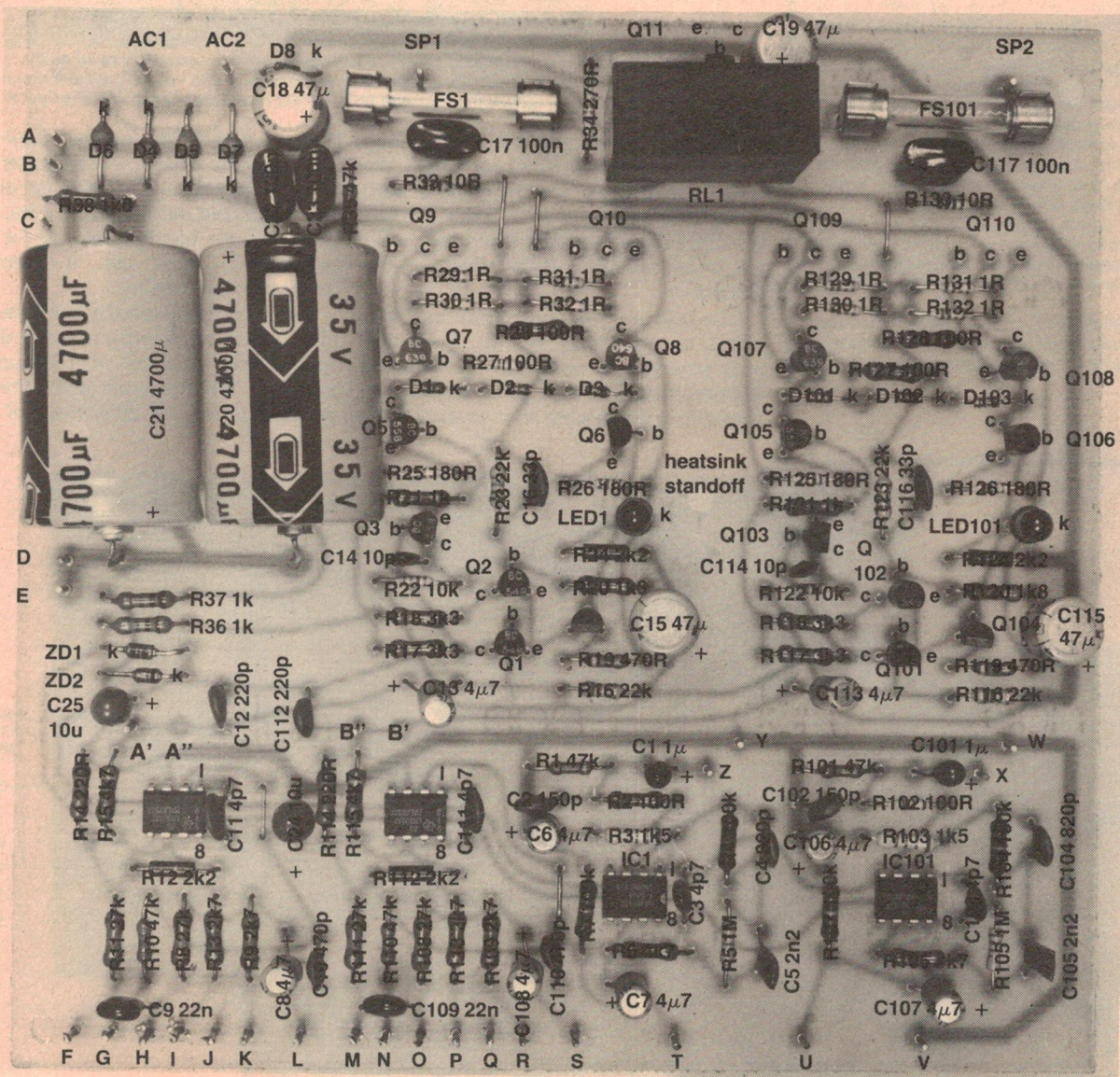



# compact stereo amplifier

(or are open circuit for some reason) the output transistors won't last long, as we found out to our detriment! Apart from the disappointment, the smell is dreadful! If in doubt, use a multimeter to check the diode. Remember that the positive lead of an ohmmeter has the internal battery negative connected to it. Thus, this lead will be connected to the cathode of the diode when the ohmmeter indicates a low resistance (i.e. diode conducting).

Mount the relay, fuse clips and fuses next. Some fuse clips are hard to solder so to prevent overheating the pc board, first file the plating off the edge of the pins on each clip before you attempt to solder them in.


For all the external connections to the board we used pc board pins. They aren't essential, but they do make it considerably easier to wire the board to the other components. These pins are mounted at this stage.

If you haven't already noticed, there are two pads on the board, just above IC2 and IC102, that appear to have no purpose. Circuit-wise, these pads are located at the input to the power stage of each channel and are marked A' and B' on the overlay photograph. By breaking the track between the points marked A'

and A'', and B' and B'', the preamp output and power amp input can be separated to provide connections for "preamp out — main in" sockets so that equipment such as a graphic equaliser may be used in conjunction with this unit. For those readers including this provision, the output impedance of any equipment used to drive the power stages of this unit should be between 4k and 10k.


The output stage transistors are mounted on the board last of all. If you mount them as we have done, drill and bend up the aluminium heatsink first. The accompanying drawing gives all the details. The 'fin' mounts on top of the L piece and the two are held tightly together with four nuts and bolts. Smear thermal compound between the two mating surfaces and insert the bolts with their heads on the side that will face the pc board. Make sure that the surface on which the transistors mount is both smooth and flat. Smooth the sur-

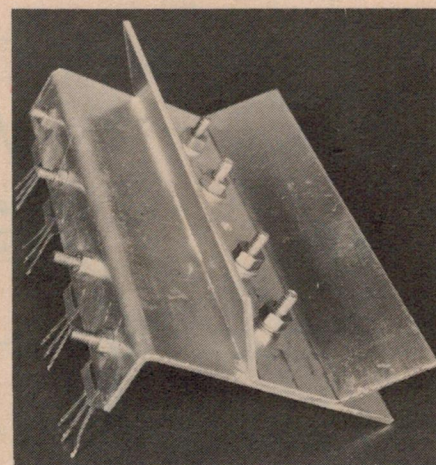face with emery paper if necessary. By the way, don't paint the heatsink. We painted ours to experiment with colour photographs inside the completed unit and found it adversely affected the thermal capacity of the heatsink. ▶



The transistors mounted on the heatsink assembly, ready to mount on the pc board.

## COMPONENT PINOUTS

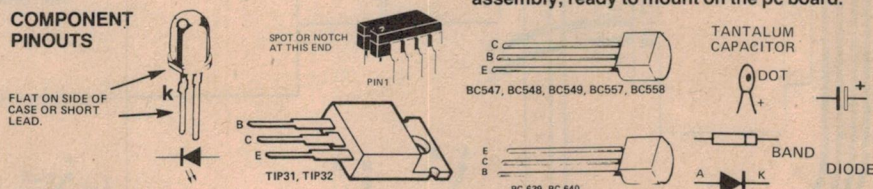

## PARTS LIST — ETI 476

### Resistors

all 1/2W, 5%

R1, 10, 35, 101	47k
R110	47k
R2, 27, 28, 102	100R
R127, 128	100R
R3, 103	1k5
R4, 7, 104, 107	100k
R5, 105	1M
R6, 15, 106, 115	4k7
R8, 11, 108, 111	27k
R9, 13, 109, 113	2k7
R12, 24	2k2
R112, 124	2k2
R14, 114	220R
R16, 23	22k
R116, 123	22k
R17, 18	3k3
R117, 118	3k3
R19, 119	470R
R20, 120, 38	1k8
R21, 36, 37, 121	1k
R22, 122	10k
R25, 26, 125	180R
R126, 34	180R see text
R29 - 32	1R
R129 - 132	1R
R33, 133	10R

### Capacitors

C1, 101	1u electro or tantalum
C2, 102	150p ceramic
C3, 103, 11, 111	4p7 ceramic
C4, 104	820p ceramic
C5, 105	2n2 greencap
C6, 7, 8, 13, 106	4u7, 16V electrolytic
C107, 108, 113	4u7, 16V electrolytic

C9, 109	22n greencap
C10, 110	470p ceramic
C12, 112	220p ceramic
C14, 114	10p ceramic
C15, 115	47u, 16V electrolytic
C16, 116	33p ceramic
C17, 22, 23, 117	100n greencap
C122, 123	100n greencap
C18, 19	47u, 35V electrolytic
C20	4700u, 35V electrolytic
C24, 25	10u, 16V tantalum
C26	10n to 100n, 240VAC
	Rated capacitor (value not critical)

### Semiconductors

IC1, 101	LM301
IC2, 102	LM301
Q1, 2, 4, 6, 11	BC548, BC108
Q101, 102, 104, 106	BC548, BC108
Q3, 5, 103, 105	BC558, BC178
Q7, Q107	BC639
Q8, 108	BC640
Q9, 109	TIP31C
Q10, 110	TIP32C
D1 - D3, D8	1N914, 1N4148
D101 - 103	1N914, 1N4148
D4, 5, 6, 7	1N4001, A14A or sim.
ZD1, 2	12V, 400mW zener diode
LED1, 101	red LED, TIL220R or sim.
LED2	green LED
	TIL220G or sim.

### Potentiometers

RV1	10k dual gang log.
RV2	100k dual gang lin.
RV3	25k dual gang lin.
RV4	10k single gang lin.

### Miscellaneous


SW1	two pole, four position wafer switch
SW2	DPDT miniature toggle switch
SW3	DPST 240V rated miniature toggle switch
SK1, 101	six RCA sockets on insulated panel
SK2	set of spring contact speaker terminals on insulated panel
T1	For 25 Watts output 20 - 0 - 20V secondary at 1.5 amps
	Ferguson type PF3993 or similar
	For 5 Watts output 12 - 0 - 12V secondary at 800mA
	Ferguson type PL24/20VA or sim.
FS1, 101	2 Amp, 3AG fuses with pc board mounting clips
RL1	DPDT pc board mounting relay with 12 Volt coil, Takamisawa type VB 12 STAN or Pye 265/12/G2V

ETI 476 pc board, heatsink (see text), black screw terminal for turntable earth connection, Horwood case type 93/10/V (255 mm wide x 255 mm deep x 76 mm high), power cord and 3 pin plug, four 12 mm pc board standoffs, clamping grommet for power cord, nuts, bolts, length 20 wire ribbon cable, length shielded cable.


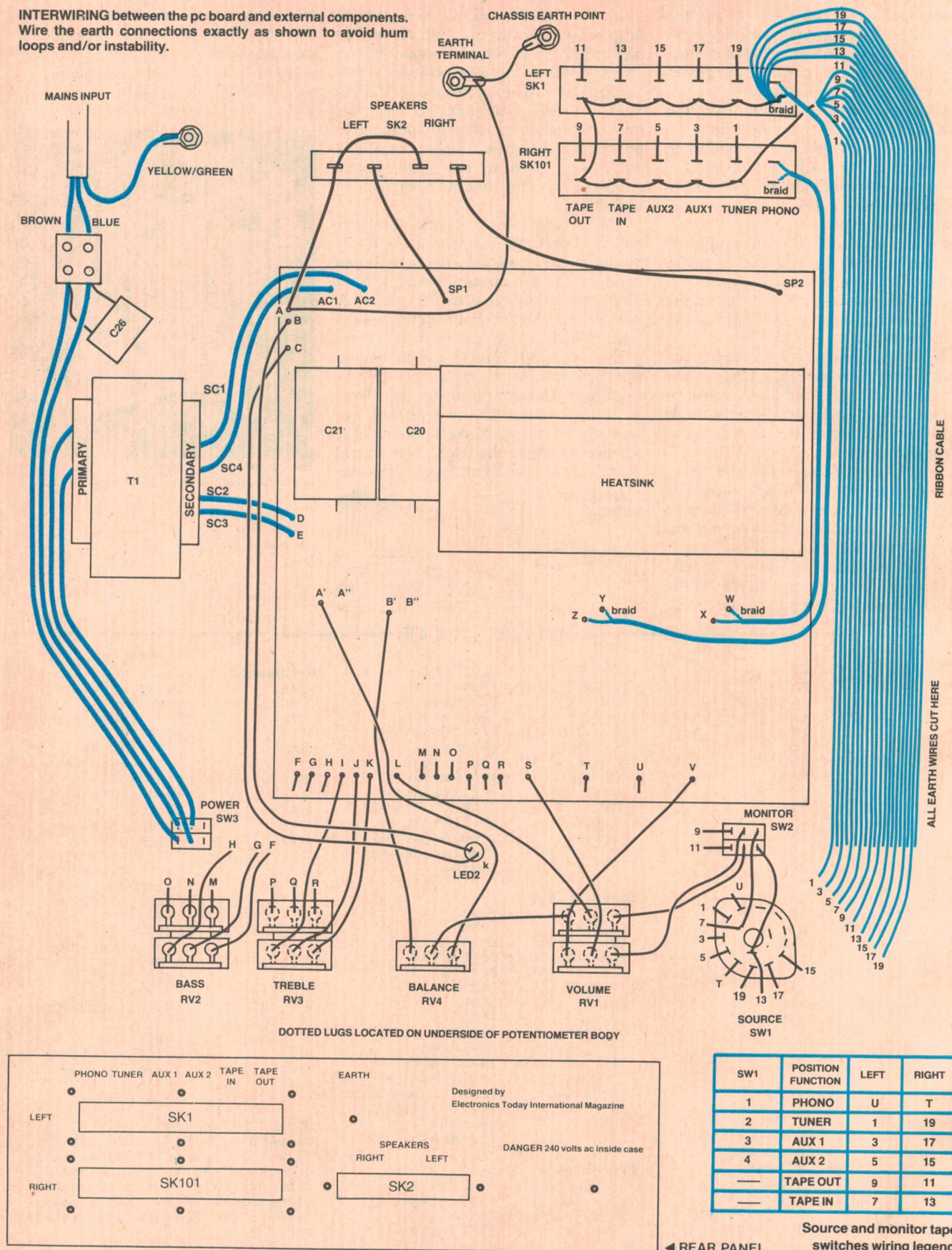
# Project 476

INTERWIRING between the pc board and external components. Wire the earth connections exactly as shown to avoid hum loops and/or instability.





# compact stereo amplifier

Mount the output transistors as shown in the accompanying diagram. Note that a mica or plastic washer and insulating bush must be used with each one. Smear a small amount of thermal compound on both sides of the mica or plastic washer before you mount and screw the bolts down firmly to get good thermal contact between the transistor body and the heatsink.

Check that you have the transistors in the correct order and check also that there are no shorts between the collector pins and the heatsink.

Before the heatsink/transistors assembly can be mounted, bolt a 25 mm standoff pillar on the pc board as indicated on the overlay photograph. This is to secure the heatsink and relieve stress on the transistor leads.




Once you have the heatsink and output transistors all together, bring the assembly to the pc board and insert the leads of the transistors in the appropriate holes. A small pair of needle-nose pliers helps here. Push the transistor leads through the board such that they protrude about 2mm on the copper side of the board. Bolt the heatsink to the standoff and then solder the transistor leads.

That completes the pc board assembly.

Next step is the metalwork. If you have purchased a pre-drilled case, just check that all fits and there are no burrs. If you've purchased an undrilled case, first thing to do is to disassemble it and scribe the hole positions on the front and rear panels as per the metalwork drawings. If you're going to use a Scotchcal front panel, this may be used as a template for drilling with the added assurance that all will fit when the holes are drilled. Don't take the backing off the Scotchcal at this stage as once it is stuck down to anything, you can't remove it without damaging the panel.

Carefully drill and de-burr all the holes. Slots are cut in the rear panel to accommodate the strips of RCA input/output connectors and the speaker connector strip. These can be cut using a 'nibbling' tool, which requires a single hole to be drilled, or by drilling a succession of holes and filing the edges of the slot straight.

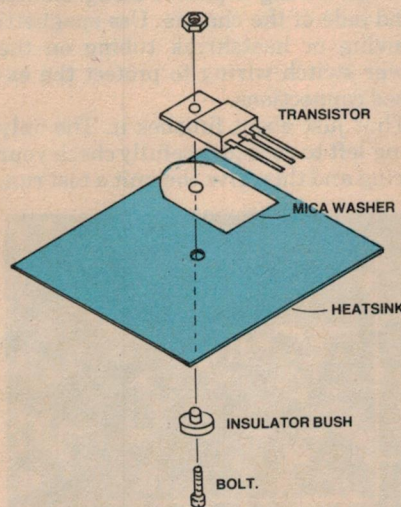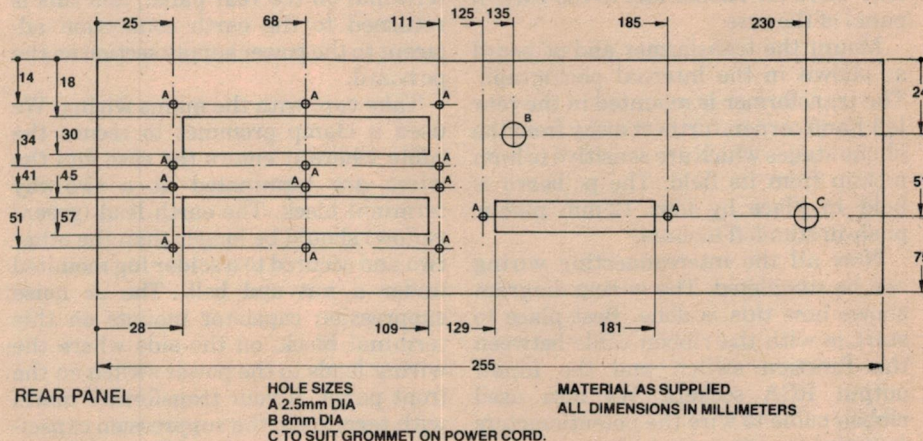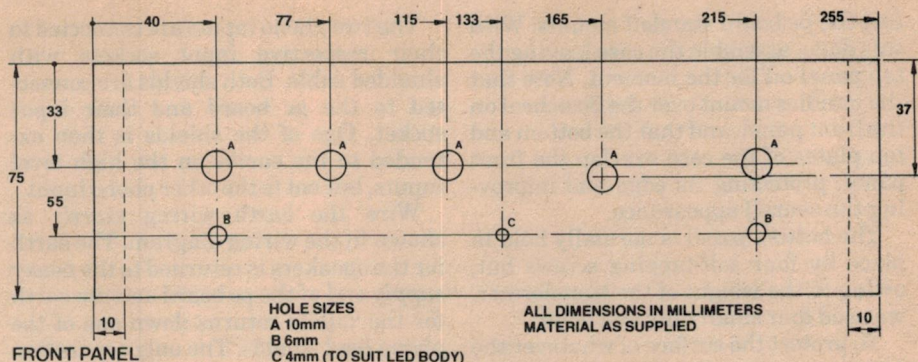With the front panel drilling completed, the Scotchcal can be positioned and stuck down. Take care, making sure that it is properly aligned. With the Scotchcal in position, mount the front panel components, noting the potentiometers are slightly angled to ensure the centre of their range corresponds to





Assembling a flatpack transistor to a heatsink.

the centre of the knob pointer. The bass control faces upside down to the other controls so that its terminals face away from the power switch. Note that the power and tape monitor toggle switches are sideways operating.

Mount the rear panel components next, making sure there are no shorts between the terminals and the chassis.

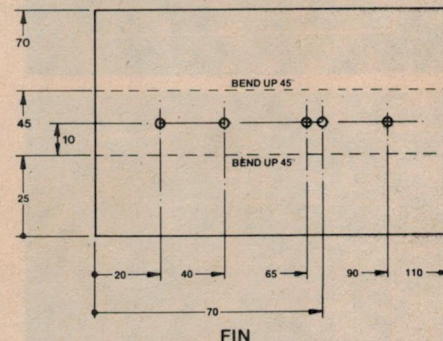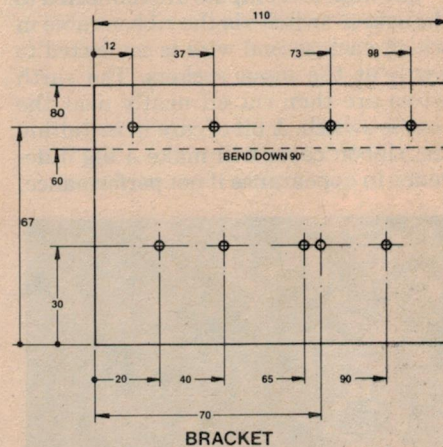The bottom panel of the case needs to be drilled to suit the transformer mounting holes, mains terminal block ▶



HEATSINK DIMENSIONS FOR 25 WATT UNIT.  
FOR 5 WATTS USE SINGLE BRACKET WITHOUT FIN.  
ALL DIMENSIONS IN MILLIMETERS  
MATERIAL 16g ALUM. SHEET  
DRILL ALL HOLES 3mm DIA



# Project 476

and the pc board standoff mounts. With this done, assemble the case leaving the top panel off for the moment. Note that the handles mount over the Scotchcal on the front panel, and that the bottom and top plates of the case overlap the front panel, protecting its edge and improving the overall appearance.

The bottom panel is normally held in place by four self-tapping screws but, owing to the weight of the transformer, we used four small nuts and bolts.

To protect the surface of whatever the equipment may stand on, we attached four 'stick-on' rubber feet to the bottom panel of the case.

Mount the transformer and pc board as shown in the internal photograph. The transformer is mounted in the rear left hand corner, furthest away from the phono stages which are sensitive to hum pickup from its field. The pc board is held in place by four 12 mm plastic push-in standoff mounts.

Now all the interconnecting wiring can be completed. The wiring diagram shows how this is done. Best place to start is with the ribbon cable between the function switch and the input/output RCA sockets. We also used ribbon cable to wire the potentiometers as it makes quite a neat job.

The high level inputs are connected to the source switch via the ribbon cable in which each second wire is connected to earth at the input sockets. The earth wires are then cut off neatly near the source switch. A bit of care in installing the ribbon cable will make a big difference in appearance if not performance.

The two phono inputs are connected to their respective input sockets with shielded cable. Both shields are connected to the pc board and their input socket. One of the shields is then extended to the earths on the high level inputs, but not to the other phono input.

Wire the earth wiring *exactly* as shown in the wiring diagram. The earth for the speakers is returned to the *power supply* end of the pc board and the earth for the inputs returns down one of the phono lead shields. The only connection to the chassis is made near the earth terminal on the rear panel, and this is returned to the earth connection adjacent to the power supply section on the pc board.

Take care with the mains wiring. We used a clamp grommet to secure the cable where it enters the case and the wires are terminated at a two-way terminal block. The earth lead (green/yellow) should be longer than the other two and secured to a solder lug mounted under a nut and bolt. The ac noise suppression capacitor mounts on this terminal block, on the side where the wiring leads to the power switch on the front panel. If your transformer comes with terminals, the suppression capacitor can be mounted there. All the 240 Vac wiring is passed along the left hand side of the chassis. Use spaghetti sleeving or heatshrink tubing on the power switch wiring to protect the exposed connections.

That just about finishes it. The only thing left to do is to carefully check your wiring and then give the unit a test run.

With no inputs and no speakers connected, turn the unit on. The LED on the front panel should light as should the two LEDs on the pc board. With a sensitive multimeter, check the voltage on the output terminals of each channel. You should read no more than 100 mV. Because the output stage operates in class-B there is no bias adjustment.

If all is well, turn the unit off, connect loudspeakers and a turntable or tape deck and you're ready to rock!






## Trials

We gave the unit a thorough trial, running it into 'odd' loads etc, running it heavily into clipping and conducting extensive listening tests. The accompanying photographs taken from the oscilloscope in our lab show how the amplifier performs with square wave drive at different frequencies throughout the audio range plus one shot showing the amplifier's output when driven into clipping with a sine wave input. Performance of the unit is clearly very good.

Just to convince ourselves, and you skeptics amongst the readers, we have also included a photograph taken from the screen of a Hewlett Packard model 3580A spectrum analyser we have on loan from Tech-Rentals for some development work (you'll be seeing more about it in the months to come — keep reading!). As you can see, this amplifier has quite a creditable performance.

For listening tests we used a pair of our Series 4000/2 three-way loudspeakers in an average sort of domestic environment with a Sansui turntable and Shure M91 cartridge. Overall sound is very clean, with well defined bass and crisp top end and it was obvious that any sonic 'faults' were not contributed by the amplifier. The unit drove the Series 4000/2 speakers effortlessly to levels liable to raise neighbour complaints!

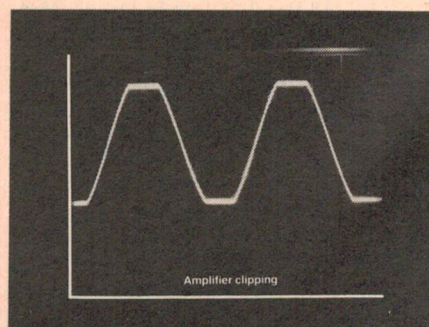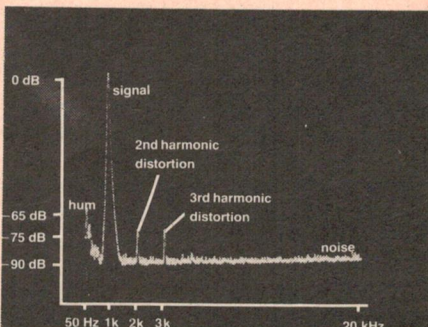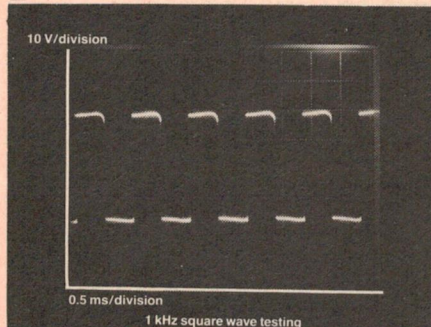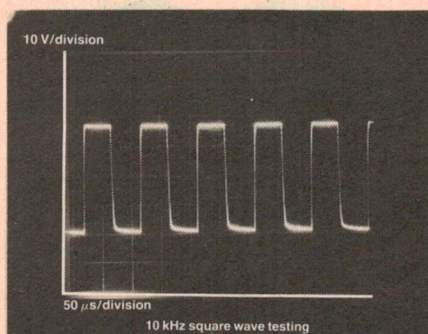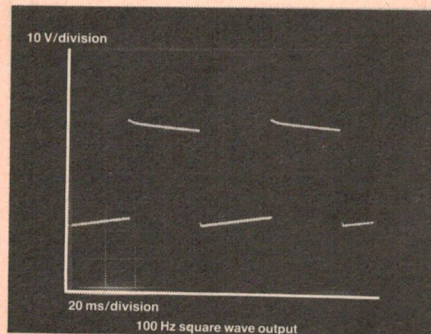We think you'll be as pleased with the Series 3000 Compact Stereo Amplifier as we are.





From ICOM, of course. Each of these brilliantly designed transceivers utilizes a special *micro-computer* equipped with ICOM designed programming to offer you features and operational flexibility you won't find elsewhere. *Memory Scan* allows you to

monitor three different memory channels. *Program Scan* scans continuously between two programmed frequencies. Scanning speed is adjustable.

VICOM carries ICOM's compact all mode transceivers in configurations to cover 143.8-148.2MHz and 50-54MHz.

(The IC551D model will even provide 100 watts on 6 metres!)

All are backed with VICOM's 90 day warranty and technical/spares back-up. But of course, all this is the kind of quality and service you naturally expect when ICOM and VICOM get together.

## 3 Highly intelligent ways to cover your transceiver needs at Vicom

### IC260A 2M. FM/SSB

**MOBILE:** For mobile, DX, local calls and satellite work. Features dual VFO's, continuous tuning (LED readout), MOS FET's in RF and 1st mixer stages—plus Noise Blanker, CW Break-in, CW monitor, APC and much more. 10w output.



### IC251A 2M. ALL MODE FIXED OR PORTABLE:

FM, USB, LSB and CW coverage makes this unit ideal for use in mobile, DX, local or satellite work. Features include continuous tuning, of course, with 7 LED readout, dual VFO's, built-in 240 AC and DC power. 1.5w audio output makes for easy listening even in noisy surroundings.

### IC551 10w 50-54MHz FIXED OR PORTABLE:

All of ICOM's best features including all mode capability, SSB, CW, AM and FM. Two VFO's, built-in 240 AC or DC power. Noise blanker. Excellent spurious and intermodulation characteristics. 2 watts audio output.



### Vicom International Pty Ltd

68 Eastern Road,  
South Melbourne, Vic. 3205.  
Phone (03) 6996700

339 Pacific Highway,  
Crow's Nest, NSW. 2065.  
Phone (02) 4362766



N.S.W. 436 2766 or 635 6399  
Vic. 699 6700 or 836 8635

Qld. 35 2522 or 341 5377  
Tas. 44 3882 or 349 932

W. Aust. 446 3232  
S. Aust. 43 7981

Townsville 772 2633  
N.T. 81 5411

A.C.T. 31 6685  
N.Z. 28 7946



## PARTS FOR NEW KITS

If a kit you want to build is not listed, the parts may be available anyway. Check the Dick Smith Catalogue, or call in to your nearest Dick Smith store.

**ELECTRONIC MUSIC GENERATOR** (See EA November)  
Complete kit, including instructions ..... Cat K-3512 \$12.50  
PCB only ..... Cat H-8382 \$1.90

**TRAIN CONTROLLER** (See EA November)  
PCB ..... Cat H-8381 \$1.90  
All other components for this kit (including case) are normal stock lines

**'3000' STEREO AMPLIFIER** (See ETI November)  
PCB ..... Cat H-3631 \$7.50  
All other components for this project are normal stock lines.

**MOISTURE INDICATOR** (See ETI November)  
PCB ..... Cat H-8321 \$1.90  
All other components for this project are normal stock lines.

**ACOUSTIC COUPLER** (See EA September)  
Complete kit, including metalwork, etc. .... Cat K-3605 \$75.00  
Printed Circuit Board only ..... Cat H-8380 \$4.00

**EXPANDED SCALE AUTOMOTIVE VOLTMETER** (See ETI Sept.)  
Printed Circuit Board ..... Cat H-8630 \$1.50  
LM3914 IC ..... Cat Z-6295 \$4.25  
Choose round or rectangular, large or small LEDs to suit your particular application.

**CHASER** (See EA August)  
Complete kit, including front panel ..... Cat K-3145 \$69.50  
PCB only ..... Cat H-8379 \$5.95

**NASA POWER CHOPPER** (See EA August)  
Short form kit (All components & PCB) ..... Cat K-3325 \$16.50  
PCB only ..... Cat H-8378 \$3.00

**LEDS AND LADDERS GAME** (See EA August)  
Complete kit inc. printed panel ..... Cat K-3390 \$15.75  
PCB only ..... Cat H-8378 \$3.00

**LED TACHO** (see ETI August)  
Short Form Kit (includes PCB components etc, but no case - build it into your dash board) ..... Cat K-3240 \$24.50

**FAST NICAD CHARGER** (See ETI August)  
PCB only ..... Cat H-8627 \$3.00  
(All other components in this kit are normal stock lines)

**GUITAR/PA PREAMP** (See ETI August)  
Short form kit PCB & components, no transformer or case) ..... Cat K-3035 \$29.50

**300 WATT AMPLIFIER** (See EA June)  
Printed Circuit Board only ..... Cat H-8376 \$9.95  
(Most other components are normal stock lines)

**TV CRO ADAPTOR** (See EA May)  
Complete Kit ..... Cat K-3060 \$29.95  
Printed Circuit board ..... Cat H-8375 \$3.75

## EA's NEW MUSIC GENERATOR


This is a great little kit for the beginner or the experimenter - it uses a very special IC which is pre-programmed with two popular tunes. A few more components and a printed circuit board make the kit complete. It plays a complete melody - including chords (not just a few bars as other ICs). It is intended for novelty or alarm applications: with a suitable amplifier it could be used as a singing doorbell.

**ONLY \$12.50**

Cat K-3512
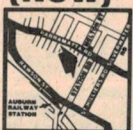
## OPENING SOON AT AUBURN (NSW)

Yes, another new store will soon be opening in Sydney's Western Suburbs. Right on Parramatta Rd, near the Auburn Motor Inn. Watch your local papers for the opening date!



**145 PARRAMATTA RD AUBURN.**

## MAJOR DICK SMITH RE-SELLERS:

**ATHERTON, QLD:** Tableland Radio Service  
2 Jack Street, Phone 912 017

**BAIRNSDALE, VIC:** Odyssey Electronics  
101 Main Street, Phone 525 282

**BENDIGO, VIC:** Summer Electronics  
95 Mitchell Street, Phone 431 877

**BLACKHEATH, NSW:** Goodwin Electronics  
123 Station Street, Phone 878 379

**BROKEN HILL, NSW:** Crystal TV Rentals  
86 Crystal Street, Phone 8897

**COFFS HARBOUR, NSW:** Coffs Harbour Electronics  
3 Coffs Harbour Plaza, Park Ave, Phone 525 684

**DARWIN, NT:** Kent Electronics  
42 Stuart Highway, Phone 814 749

**FAIRY MEADOW, NSW:** Trilogy Wholesale Elect.  
40 Princes Hwy, Phone 831 215

**GEELONG, VIC:** Electrox  
133 Malop Street, Phone 97 827

**GERALDTON, WA:** KB Electronics & Marine  
381 Main Street, Phone 212 176

**GOSFORD, NSW:** Tomorrow's Electronics & Hi Fi  
98 William Street, Phone 247 246

**HOBART, TAS:** Aero Electronics  
123a Bathurst Street, Phone 348 232

**KINGSTON, TAS:** Kingston Electronics & Records  
Channel Court, Phone 296 802

**LAUNCESTON, TAS:** Advanced Electronics  
5a The Quadrant, Phone 317 075

**LISMORE, NSW:** Decro Electric  
Cor Magellan St & Brunner Hwy, Phone 214 137

**MACKAY, QLD:** Stevens Electronics  
42 Victoria Street, Phone 511 723

**MARYBOROUGH, QLD:** Keller Electronics  
218 Adelaide Street, Phone 214 559

**MORUYA, NSW:** Coastal Electronics  
43 Vulcan Street, Phone 742 545

**MT GAMBIER, SA:** Hutchesson's Communications  
5 Elizabeth Street, Phone 256 404

**MUSWELLBROOK, NSW:** Silicon Chip Electronics  
Suite 3, 98 Bridge Street, Phone 43 1096

**NAMBOUR, QLD:** Nambour Electronic Shop  
Shop 4, Lowan House, Ann St, Phone 411 604

**NEWCASTLE, NSW:** Elektron 2000  
181 Wharf Road, Phone 262 644

**NOWRA, NSW:** Lyrebird Electronics  
50 Berry Street, Phone 525 525

**ORANGE, NSW:** M&W Electronics  
48 McNamara Street, Phone 626 491

**ROCKHAMPTON, QLD:** Purely Electronics  
15 East Street, Phone 21 058

**SOUTHPORT, QLD:** Amateur's Paradise  
121 Nerang Street, Phone 322 644

**SURFERS PARADISE, QLD:** Viking Electronics  
3108 Gold Coast Hwy, Phone 322 644

**TAMWORTH, NSW:** Sound Components  
78 Brisbane Street, Phone 681 363

**TOOWOOMBA, QLD:** Hunts Electronics  
18 Nail Street, Phone 328 984

**TRARALGON, VIC:** Power'n'Sound  
15 Franklin Street, Phone 743 638

**VINCENT, QLD:** Tropical TV  
249 Fulham Road, Phone 791 421

**WAGGA, NSW:** Wagga Wholesale Electronics  
82 Forsyth Street

**WALGETT, NSW:** P.J. O'Brien Electronics  
82 Waa Street, Phone 243

**WINDSOR, NSW:** Hawkesbury Electronic Centre  
111 George Street, Phone 773 411

**WODDONGA, VIC:** A & M Electronics  
78a High Street, Phone 244 588

**WHYALLA NORRIE, SA:** Mollor Enterprises  
Shop 2, Forsyth Street, Phone 454 764

## DON'T FORGET: ONLY 9 WEEKS TO CHRISTMAS!!!

Need a few ideas for someone into electronics? Go no further than your nearest Dick Smith store!

## IT'S CUTE!

It's called a 'Cutie Phone'!

You've probably seen phones like this one in the movies. Here it is - in Australia! It gives push-button dialling, last number re-dial and folds down when not in use. Great for a bed-side phone, etc.

NOTE: Although this phone connects directly to standard Australian telephone lines, current regulations do not permit them to be used for this purpose.

**\$69.50**



## THE DICK SMITH SOLDERER'S SPECIAL!



ALL ITEMS AVAILABLE SEPARATELY

### 1: 30W, 240 VOLT IRON

A budget iron for the hobbyist: beginner or expert. Ideal for all electronic assembly work. Cat T-1300. Normally \$9.75

### 2: 250g ROLL SOLDER

Economy pack of popular 1.25mm solder: enough to last you for many, many projects. Cat N-1619. Normally \$4.95 roll

### 3: SOLDERING STATION

Our incredibly popular 3-in-1 stand which holds PCB at any angle, iron and solder. Incredibly versatile: you'll wonder how you got along without it! Cat T-5700. Normally \$19.50

**ALL THREE FOR ONLY \$29.90**

## SPACE INVADERS™!!

WHY SPEND HUNDREDS OF DOLLARS PLAYING ARCADE MACHINES: BUY YOUR OWN!



Hand-held version of the popular game. Works just like the big ones, but doesn't cost a fortune to use! Amazing micro-computer technology makes hand-held space invaders a reality!

**\$24.50**

Cat X-1150

### SPACE INVADERS AND BLOCKBUSTER!

**\$29.95**

A more elaborate version - and this one also has a second game: Blockbuster! Easy to play, great sound effects, with various options to make the game even more exciting. Battery operated, so they can take it anywhere. Cat X-1152

## MORE THAN AN ORGAN



IT'S MICROCOMPUTER CONTROLLED! With this remarkable organ you can not only play tunes, you can record them in the computer memory for later playback! And it also plays its own repertoire - just in case you're feeling lazy! Battery operated, a superb gift idea! Cat X-1158

**\$29.50**

## TIME IT! STOP IT!

**\$39.50**



This superb new liquid crystal stop watch/clock is just the go for today's sportsman: whether you're taking part, or sitting on the sidelines! Huge, easy to read digits giving time to 1/100 second, also does lap times, etc. And when you're not using it as a stopwatch, it's a highly accurate clock! Incredible value: similar models sell for \$100 and more! Cat X-1041

## Dear Customers,

Quite often, the products we advertise are so popular they run out within a few days. Or unforeseen circumstances might hold up goods so that advertised lines are not in the stores by the time the advert appears. Please don't blame the store manager or staff: they cannot solve a dock strike on the other side of the world, or even locate a shipment that has gone astray.

What we are trying to say is that, if you're about to drive across town to pick up a particular line at a Dick Smith Store, why not give the store a ring first (addresses and phone numbers below) - just in case! Thanks.

Dick Smith and Staff

## TOP VALUE MAINS IRON

Dick's own 240V fully approved mains soldering iron. Supplied with free solder sample, great value for hobbyist & technician alike. 25W rating.

**COMPARE OTHERS AT \$14 AND MORE!!**

**\$9.75**

T-1300

## NEW RANGE OF SOUND CARE EQUIPMENT JUST ARRIVED!

You asked for it: so here it is! Economy sound care equipment that will do a really professional job on your records and cassettes. Something for everyone, at a bargain price!

Cassette winders, labels and reel locks. Cat C-7086 \$2.95  
Cassette head care kit. Cat C-7088 \$2.95  
Cassette head demagnetiser and cleaning fluid. Cat C-7090 \$4.50  
Deluxe record cleaner. Cat C-7092 \$3.95  
Deluxe record cleaning arm and brush. Cat C-7094 \$4.95

## WOTTA BARGAIN!

We've just bought a HUGE shipment of these incredibly popular push button telephone dials - so our cost has dropped. You reap the benefit of Dick's huge bulk buying power! Simply substitute for any rotary phones (no soldering required) current regulations do not allow you to use them for this purpose. Cat X-1175

**NOW: \$39.50**



Cat Q-1242

## BUYING BY MAIL?

**ORDER VALUE:** P&P  
\$5 (min) to \$9.99 \$1.00  
\$10.00 to \$24.99 \$2.00  
\$25.00 to \$49.99 \$3.00  
\$50.00 to \$99.99 \$4.00  
\$100 or more \$5.50

NOTE: These charges apply to goods sent by post in Australia only. Large and bulky items cannot be sent by post.

If you prefer, we will despatch your order by Comet Road Freight to anywhere in Australia for only \$6.00 - that's below what it costs us! Large and bulky items are normally sent by Comet unless you specify differently (eg by rail or air - you pay freight on delivery)

# DICK SMITH ELECTRONICS



399 Lonsdale Street  
Ph (03) 67 9834



656 Bridge Road  
Ph (03) 428 1614




166 Logan Road  
Ph (07) 391 6233



842 Gympie Road  
Ph (07) 59 6255



414 William Street  
Ph (09) 328 6944

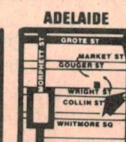

60 Wright Street  
Ph (08) 212 1962



96 Gladstone Street  
Ph (062) 80 4944



263 Keira Street  
Ph (042) 28 3800



**AS SEEN  
IN OCTOBER  
ELECTRONICS AUSTR.**

**GREAT  
GIFT IDEA  
FOR BUDDING  
NUCLEAR  
PHYSICISTS!**



Cat K-3471

## Do-it-yourself ATOMIC BOMB (Short form kit)

Yes! You asked for this one: the fantastic do-it-yourself Atomic Bomb described in the October Electronics Australia. A great hit at parties: imagine the reaction you would get next cracker night! This kit comes complete with the two storey building as specified in the kit (unfortunately, it won't fit in the box, so we include a 'rain check' redeemable at any real estate agent. You specify the area you want to devastate).

The kit is complete to the last nut and bolt with the exception of the uranium. However, this should not be a problem, as the construction article gives full instructions on how to go about stealing your own.

No self respecting terrorist should be without this kit. Come to think of it, if all self-respecting terrorists built themselves a bomb, there would be no self-respecting terrorists left!

NOTE: Life expectancy of bomb constructors is invariably reduced dramatically: like to a few hours or less!

NOTE: NO U<sup>235</sup> SUPPLIED WITH THIS KIT  
— YOU MUST OBTAIN YOUR OWN!

**ONLY \$19280472<sup>00</sup>**

## NEW YAESU FRG-7700 COMING SOON!

In a word — WOW!

This incredible new receiver has absolutely everything the serious SWL could possibly want: all mode reception (yes, even FM — so you can use converters for 'upstairs'); tunes down to 150kHz & up to 30MHz; has a cont. variable RF attenuator; 3 positions of selectivity on AM... it must be far and away the best receiver available anywhere! And yes, it has a digital readout! And it has an optional memory unit for programming up to 12 frequencies for instant recall!



D-2840

**DUE IN STOCK  
EARLY DECEMBER  
WORTH WAITING FOR!**

**DON'T BUY AN R-1000  
BEFORE YOU SEE THIS BEAUTY!**

## RADIO COMMUNICATIONS Two New References from the Radio Society of Great Britain

Stocks of both of the much sought-after and very hard to get 'Radio Communication Handbooks' are now arriving. Published by the RSGB, many people believe them to be BETTER than the ARRL handbook! Starts with the fundamentals, goes through to the details! A perfect study reference for the ACP examinations.

Vol 1 (480pp) hard cover (Cat. B-2030) \$24.50  
Vol 2 (334pp) hard cover (Cat. B-2032) \$19.50



### Reference books

LOGIC — TTL DATA MANUAL

Huge 765 pages crammed with data on popular TTL-type IC's. Worthy of a place in every experimenter's & hobbyist's reference library. Cat B-4021 \$6.50

Analog Applications Manual

Ever wondered where designers get their ideas from? Wonder no more: 416 pages of interesting and useful applications for Signetics linear integrated circuits. Cat B-4031 \$6.00

## INCREDIBLE BARGAIN!

### Superseded Amateur Radio Handbooks

WOW! We've made an incredible scoop purchase of Amateur Radio Handbooks direct from the publisher. These are the 1978 issues: the last of the ones that contain useful value data! Great for novices, beginners, etc.: here's your chance to own the amateur's 'bible' at a tiny fraction of the current price!

**\$15 VALUE!** Cat B-2217  
**HURRY! LIMITED STOCK!**



## WHY BUY BATTERIES? THEN THROW THEM AWAY!

### NiCads are cheaper!

It's a fact: Nicad batteries work out far cheaper in the long run. They may be dearer at first, but if you work out the price vs. number of charges, you'll agree. Nicad batteries are ideal for replacing conventional 'AA' cells (1.2V is normally close enough).

Only \$2<sup>05</sup> each

Or \$1<sup>80</sup> ten or more.

### Can't charge Nicads? Problem solved!

This great new Nicad charger cartridge from ADR plus our multi-voltage adaptor — you're in business. Simply place 2 to 4 Nicads in the cartridge, plug in the adaptor and you're away. Come back in 15 hours and they're fully charged!

Cat M-9518

Cat M-9525 \$9.50 \$1.95

### SNIP IT!

Incredible! These remarkable snips are ideal for the hobbyist, the housewife, the student, the lab... they cut just about anything! Even Tinsplate and leather! Quality NZ made snips will last for years, too.

**\$2<sup>95</sup>**

Cat T-4930

## DON'T PAY 35¢ EACH FOR 1% RESISTORS...

Manufacturers... Laboratories... Government departments... Are you sick of paying 'through the nose' for high tolerance resistors? We've seen many people advertising them for as much as 35¢ each! If you need premium quality, 1% tolerance and unbeatable prices, you cannot go past our range of metal film resistors.

**They're only 6¢ each ONE OFF:  
even cheaper in bulk quantities!**

## More of Dick's BONZA BULK BUY BARGAINS: BEWDY!



How's this for a bargain: a superbly made 4POT relay with 12 volt (185 ohm) coil at near half price! Yes, hundreds of uses for the professional, the hobbyist and the experimenter. And for 10 or more, the price drops to just \$2.50 — incredible! Cat S-7000

\$2<sup>90</sup>

Unbelievable price: Famous quality Memorex reel-to-reel tape at pre-1974 prices! Yes, 2400 ft Memorex tape on 7" reel, in box, for around 1/3 off current price while stocks last.

Cat C-3406



## STILL AVAILABLE!

### Dick Smith's Fun

### Fun Way into

### Electronics, Vol 1.

### VALUE PACK:

The book and both kits (worth over \$19)

for only \$17<sup>50</sup>!

Just in case atomic bombs aren't your scene, Dick has the incredibly popular 'Fun Way into Electronics' (Vol 1), together with both kits of parts, in a special value pack. All the projects in Fun Way 1 are battery operated, with no soldering — so they're completely safe for even the youngest beginner. If you're looking for a different Christmas gift idea: this is it!

**FUN WAY TWO BOOK AND KITS  
NOW AVAILABLE ALSO: SEE OUR  
ADVERT ELSEWHERE IN THIS ISSUE.**

## HARD OF HEARING?

This could be the answer: a telephone amplifier! Just connect the suction cup to your phone case (no electrical connection) and listen: it will amplify whatever you say into the handset as well as whatever is heard. So it's ideal for 'conference' listening, etc. Another quality Dick Smith exclusive import and just look at our low, low price!

Cat X-1174

**\$12<sup>50</sup>**

## NEW EDUCATIONAL SOFTWARE TO SUIT THE DICK SMITH SYSTEM 80 (ALSO RUNS ON TRS-80)

### Learning Fun 1:

### Scurvy Invaders.

A unique program that combines basic maths drill with the ever-popular 'Space Invaders' game: practising maths has never been so much fun! Before being able to take each shot with the laser gun at one of the dreaded Scurvies, the player has to feed the 'correct data' into the spaceship's computer. Sound effects, with three levels of difficulty. Requires a 16K machine. This program was written by a NSW primary school teacher. Cat X-3694

### Learning Fun 2:

### Hangman/Concentration.

Two programs which are not only great fun to play, but also help to increase familiarity with words. Hangman is the computer version of the well-known word guessing game — complete with graphics of the 'man' getting hanged. The words can be chosen by the computer or by a second player. Concentration is the computer version of the TV quiz game, trying to guess mystery food words. Requires 16K machine. Cat X-3696

### Learning Fun 3: Alphabet

### Countdown/Rhyme Time

Two computer games which are a lot of fun, and give players of any age practice in selecting and manipulating words. Rhyme Time also helps to increase their skill in spelling and vocabulary. In Alphabet Countdown, random words from a list must be arranged alphabetically in the shortest possible time. Rhyme Time displays a list of unfinished rhymes, and the player must type in the missing word from the clues given in the rhyme. The player's percentage correct is displayed. 16K. Cat X-3698

**(ON CASSETTE) EACH ONLY \$9<sup>95</sup>**

## PRICES SLASHED ON DISKETTES

Look at these incredible new low prices for quality 5 1/4 inch diskettes! Both styles (hard and soft sector) to suit most disk drives. And the savings are even greater if you buy in quantity! Hurry: stocks cannot last long at this ridiculous price!

1-10 \$4.95  
10-100 \$3.95  
100 up \$3.50!!

Hard Sector: Cat X-3505  
(Suit Micropolis drives)  
Soft Sector: Cat X-3510  
(Suit Pertec drives)

## HUGE SAVINGS ON FAST 4116 RAMS, TOO...

Don't be conned into paying top dollar for RAMs by misleading ads: Ours are guaranteed prime spec, 250NS 4116 RAMs ideal for almost all applications. And they're available either singly, or in 16K packs with upgrade data for popular computers.



Single 4116 RAMs, Cat Z-9310 \$7.90  
16K kit, (8 x 4116) Cat X-1186 \$59.95

## THE ATARI VCS\* IS HERE!

\*Video Computer System Cat X-1400



**\$269<sup>00</sup>**

This is it: the video computer everyone is talking about. The incredible Atari Video Computer System. It's much, much more than a TV game computer: for this incredible device accepts a huge number of plug-in cartridges to give years of family fun with thousands of game variations! And even more, with an optional program (which you can buy at many large department stores) this computer can ACTUALLY BE PROGRAMMED IN 'BASIC' COMPUTER LANGUAGE!

As we said, it's much more than a video entertainment computer!

**AND YES — IT HAS 'SPACE INVADERS'!!!**

### WHY WASTE MONEY ON 'PENNY ARCADES'?

CARTRIDGES CURRENTLY AVAILABLE:

Video Chess (X-1404) \$59.95  
Night Driver (X-1413) \$39.95  
Bowling (X-1409) \$39.95  
Street racer (X-1414) \$39.95  
Sky Diver (X-1407) \$39.95  
Breakout (X-1411) \$39.95  
Air/sea battle (X-1408) \$39.95  
Outlaw (X-1410) \$39.95  
P&P free if bought with console.

## WOULD YOU LIKE TO WORK WITH US?

Dick Smith Electronics is expanding — if you've been watching your local press you'll probably have noticed this already!

Opening new stores requires new staff. Good staff. Electronics enthusiasts who can be trained to become professional sales people and managers. If you're talented and enthusiastic, we offer good wages and conditions. If you're above average, promotion can be very rapid. (One of our salesmen became general manager three years later!)

No matter what area you live in, if you'd like to work with us, drop us a line. When we open a store in your area, we'll be in touch...

Send your application to:  
The Personnel Manager,  
Dick Smith Electronics Pty Ltd  
PO Box 321,  
North Ryde, NSW 2113

## COMPUTER HOTLINE... (02) 888 2002


Having computer problems? Or perhaps you'd like to buy a computer but don't quite know which one you want? Phone our computer hotline. 9AM to 5PM Monday to Friday for friendly, helpful advice about computers. Note the special number:

# DICK SMITH ELECTRONICS

SYDNEY	BROADWAY	BLAKEHURST	BROOKVALE	CHULLORA	GORE HILL	PARRAMATTA	MAIL ORDER AND SERVICE CENTRES:
125 York Street Ph (02) 290 3377	818 George Street Ph (02) 211 3777	613 Princes Hwy Ph (02) 546 7744	531 Pittwater Road Ph (02) 93 0441	147 Hume Hwy Ph (02) 642 8922	162 Pacific Hwy Ph (02) 439 5311	30 Grose Street Ph (02) 683 1133	Cnr Lane Cove & Waterloo Rds, North Ryde NSW 2113 (Monday to Friday, 9AM to 5PM only)
							SHOPS OPEN: 9AM to 5.30PM MON. TO FRI. 12 NOON SATURDAY (Brisbane 1/2 hour earlier)





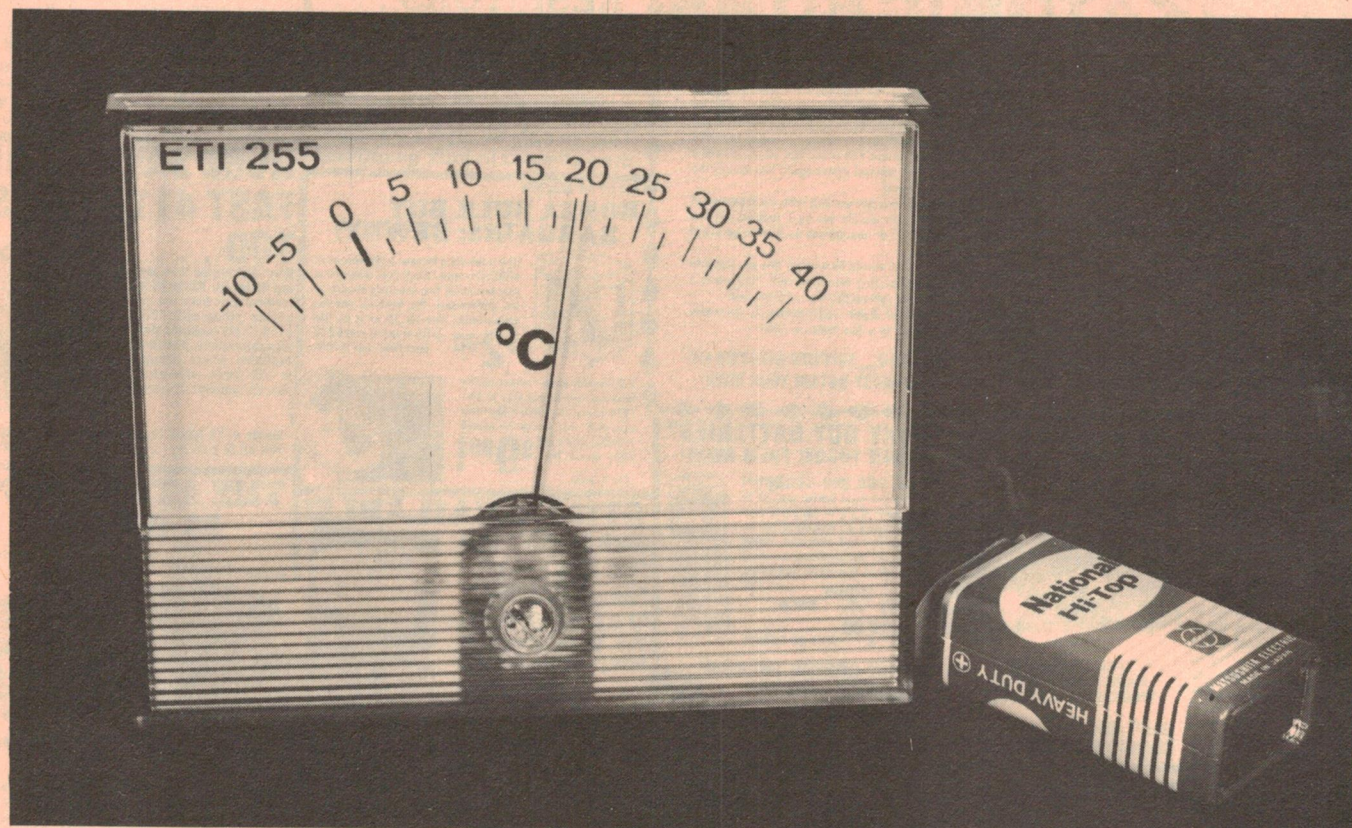

## Electronic temperature meter is easy to read and easy to build

**Jonathan Scott**

This handy little thermometer can be used for local or remote indication of temperatures.

THIS TEMPERATURE meter project can stand alone or you can mount it in a desk top or even in the dash of your car if you don't mind cutting a hole for it. (If you've built all the ETI projects for motorists your dash must look like a piece of swiss cheese by now, so one more hole won't matter!)

Why an electronic thermometer, you may ask? What's wrong with the ordinary mercury-in-glass type that's been with us for hundreds of years? It's hard to read, that's what. You have to go right up close to see the scale. And mercury thermometers are fragile, too.

If you want to be able to read off temperature on a nice clear dial you need some kind of electric or electronic

sensing element. There are several kinds of sensors you might use, including thermocouples, thermistors and diodes, all of which have their own advantages and drawbacks.

We chose to use a temperature sensing IC, the LM3911, recently introduced by National Semiconductor. There's a more detailed description of it on page 40, but basically it relies on the well-known fact that a transistor's base-emitter voltage varies with temperature — the warmer the transistor gets the greater the b-e voltage.

Because the LM3911 chip includes its own amplifier, it's very easy to use it to drive a meter. Apart from the IC and the meter, the only components in this pro-


ject are five resistors and a trimpot. By choosing different values of resistors, you can build this temperature meter so that it indicates any temperature range you choose as long as it's between  $-25^{\circ}\text{C}$  and  $+85^{\circ}\text{C}$ .

We've specified resistor values to make the meter read from  $-10^{\circ}\text{C}$  to  $+40^{\circ}\text{C}$ , which should be fine for most locations, but in case you live somewhere like Birdsville we've also given values for a temperature range of  $-10^{\circ}\text{C}$  to  $+90^{\circ}\text{C}$ . But you don't have to stick to the ranges we suggest. Opposite you'll find formulae for calculating the necessary resistance values for any temperature range.

One more useful feature of this project ►



# temperature meter

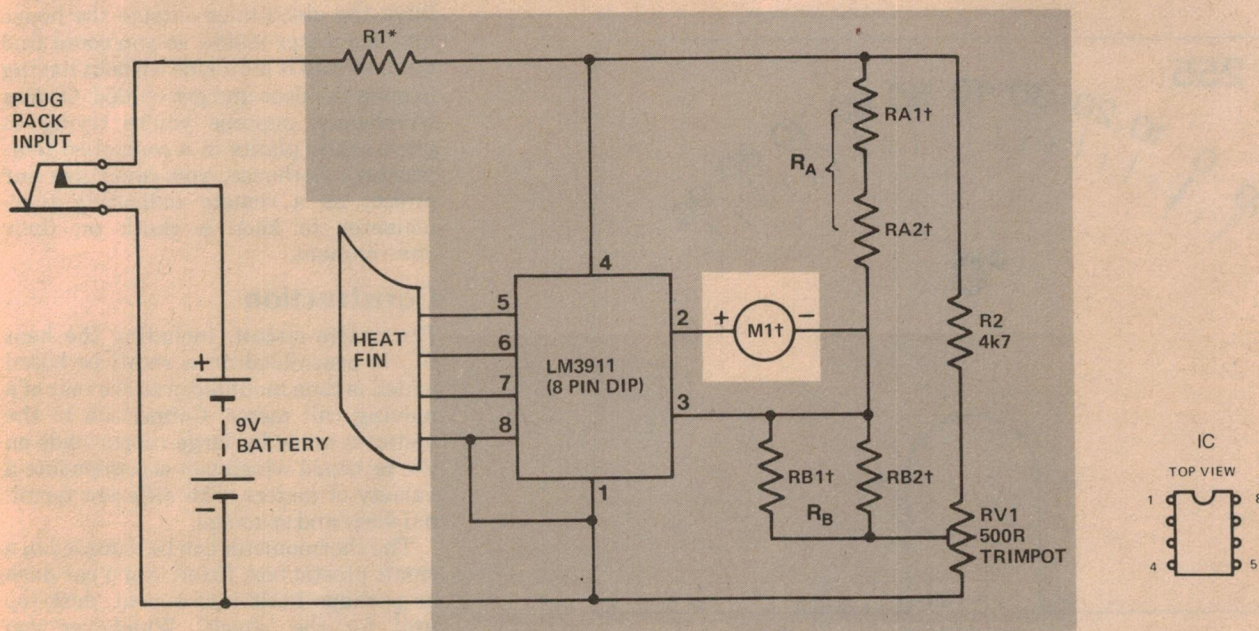

\*R1 = 470R (¼W or ½W) for 9 V operation; 1k8 for 12 V battery (11 - 15 V) operation.  
 †See table below for resistor values to suit different meter ratings.

## HOW IT WORKS — ETI 255

Almost all the functions take place inside the LM3911 chip. Pins 5 - 8 are thermally connected to an internal temperature sensor circuit and transmit the external temperature from a small sheet of copper. The copper fin will generally be at air temperature.

An internal voltage reference, connected between pins 1 and 4, regulates the supply rail to 6.8 volts for the chip and external circuitry. The dropping resistor R1 sets the current to about 3.5 mA, maintaining about 1.2 mA to the IC and about 2.5 mA to the external circuit. It is desirable to keep the current into the IC as low as possible to prevent excessive temperature rise in the chip giving rise to inaccurate readings.

An internal op-amp sinks current from pin 2 in order to hold the voltage on pin 3 at a level which is linearly proportional to the temperature on the sensing pins. The meter, M1, monitors the current into pin 2 giving a reading which is directly proportional to temperature. The resistors RA and RB are calculated to give the required zero reading and full-scale temperatures. We have included a table with suitable values as well as formulae so you can roll your own.

The meter reading is linear with temperature and is calibrated to cover the desired range.

The trimpot RV1, compensates for variations between different ICs as well as compensating for temperature rise within the chip.

## SUGGESTED VALUES

Range (°C)	Meter F.S.D.	RA1	RA2	RB1	RB2
0 to +100 (note: 85 max.)	100 µA	10k	6k8	27k	270k
0 to +50	50 µA	10k	6k8	27k	270k
-10 to +90	100 µA	8k2	8k2	27k	480k
-10 to +40	50 µA	8k2	8k2	27k	480k
-10 to +40	100 µA	8k2	zero	82k	15k

NOTE: maximum rated temperature is 85°C; minimum is -25°C.

Other temperature ranges can be covered, within the specified limitations of the LM3911, the required range resistor values being calculated from these formulae:

$$R1 = \frac{V_s - 6.9}{0.0035} \dots \dots (1)$$

VS = supply voltage

$$R_A = R_{A1} + R_{A2} \dots \dots (2)$$

$$R_B = \frac{1}{1/R_{B1} + 1/R_{B2}} \dots \dots (3)$$

$$\text{Let } T_1 = T_0 + 5 \dots \dots (4)$$

using equation (4), calculate 'M'

$$M = \frac{T_1}{685} \dots \dots (5)$$

where T0 = zero scale reading in °K  
 and T (°C) = T (°K) - 273 \dots \dots (6)


$$\text{then } R_B = \frac{10^4}{M \cdot s} \dots \dots (7)$$

$$\text{and } R_A = \frac{10^4}{s(1 - M)} \dots \dots (8)$$

where s = meter sensitivity in µA/°C  
 (For example; if you choose a 100 µA meter and wish to cover a range of 50°C, then s = 2 µA/°C)



# Project 255

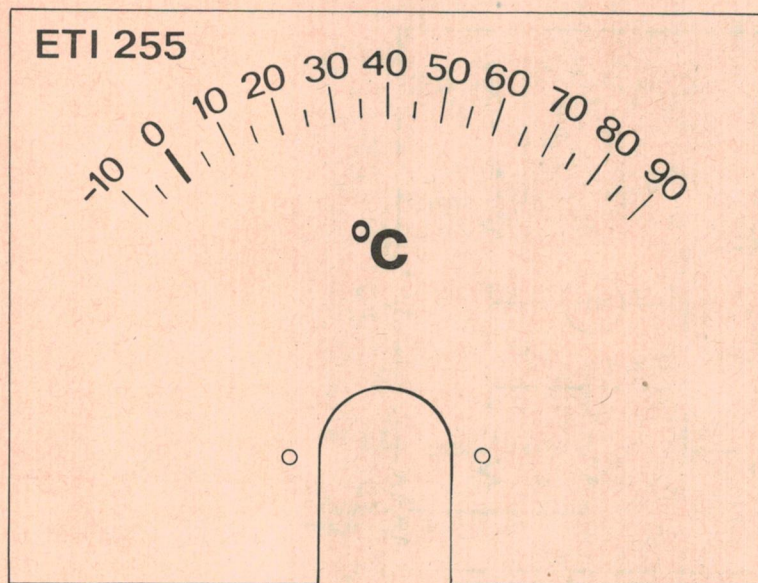

Full size artwork for meter scale covering  $-10^{\circ}\text{C}$  to  $+90^{\circ}\text{C}$ . Note that the limit for the LM3911 is  $+85^{\circ}\text{C}$ .

## THE LM3911 — HOW IT WORKS

The LM3911 is a highly accurate temperature measurement IC for use over a  $-25^{\circ}\text{C}$  to  $+85^{\circ}\text{C}$  temperature range. Fabricated on a single chip it includes a temperature sensor (pins 5 — 8), stable voltage reference (pins 1 and 4) and an operational amplifier.

The output voltage on pin 2 is directly proportional to temperature in degrees Kelvin having a sensitivity of  $10\text{mV}/^{\circ}\text{K}$ . By using the appropriate external resistors with the internal op-amp, any temperature range can be selected.


An active shunt regulator across the supply pins provides a stable 6.8 volt reference for the sensing circuitry, and allows the use of any supply voltage with the correct dropping resistor.

The input bias current is low and relatively constant with temperature to ensure high accuracy when a high source impedance is used. The output pin can be returned to a supply up to 35 volts to allow the circuit to drive lamps or relays.


The temperature sensing element uses the difference in base-emitter voltages of two transistors operating at different current densities. Since this output depends only on transistor matching, very good stability and reliability can be obtained.

The op-amp can either be connected as an amplifier to give a linear temperature/voltage output or as a comparator to switch the output at a preset temperature. Therefore, the device can be used either as a measuring instrument or as a temperature controller.

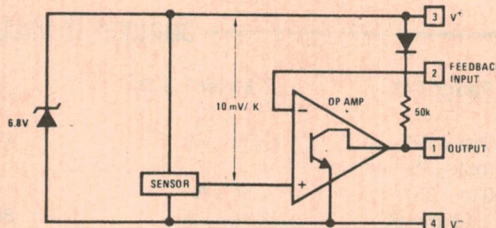The output can be calibrated for degrees Celsius, Fahrenheit or Kelvin.



Internal block diagram of the LM3911.

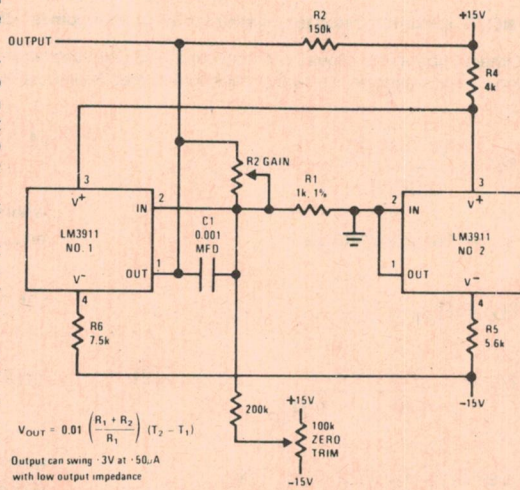

Output can swing  $-3\text{V}$  at  $50\mu\text{A}$  with low output impedance

\*The 0.01 in the above equation is in units of  $\text{V}/^{\circ}\text{K}$  or  $\text{V}/^{\circ}\text{C}$  and is a result of the basic  $0.01 \text{ V}/^{\circ}\text{K}$  sensitivity of the transducer

Two LM3911s can be configured as a differential thermometer.

is that the meter doesn't need to be closely connected to the IC and the rest of the circuitry. You could, for example, have the electronics outside the house and the meter inside, so you could find out how cold it is outside without having to open the door and get chilled. Or less frivolously, suppose you're trying to grow exotic plants in a controlled temperature hothouse, you could use our project as a remote indicating thermometer to keep a check on their environment.

## Construction

The entire circuit, including the heat fin, is assembled on a small pc board which is then mounted onto the rear of a moving coil meter. Connection to the meter is made by large copper pads on the pc board which can accommodate a variety of meters with different terminal sizes and spacings.

The thermometer can be mounted in a small plastic box, fitted into a car dash or perhaps built into a neat, desk-top unit for the 'shack'. Whichever you choose, be sure to leave a large enough hole in the box to allow free air flow across the heat fin so the meter reads the room air temperature and not that inside the box. If a remote reading unit is required the pc board can be mounted away from the meter.

The first job is to drill the holes into the pc board to suit the type of meter you have. Next fit all the components as shown in the overlay, taking care with the orientation of the IC and the polarity of the battery or power supply connections. The value of  $R_1$  is different depending on whether the unit is operated from a 9 V supply (battery or plugpack) or a 12 V supply (vehicle battery or plugpack). Values are beneath the circuit. The values of  $R_A$  and  $R_B$  are selected from the table for the required temperature range and meter used. Note that  $R_A$  consists of two resistors in series ( $R_{A1}$  and  $R_{A2}$ ), while  $R_B$  consists of two resistors in parallel ( $R_{B1}$  and  $R_{B2}$ ). Either 2% tolerance or selected 5% tolerance metal film resistors should be used for the sake of accuracy.


Power from a plugpack is applied through a shorting type socket so the unit can be battery operated when the plugpack lead is removed.

The 50 mm by 20 mm heat fin is cut from a small piece of 0.25 mm thick copper shim. Solder it to the pc board track connected to pins 5 - 8 of the IC (see overlay photo). A larger size fin may be used, but we found this one works nicely. In fact, the circuit will work well without any heat fin, but has a longer response time. Make sure the


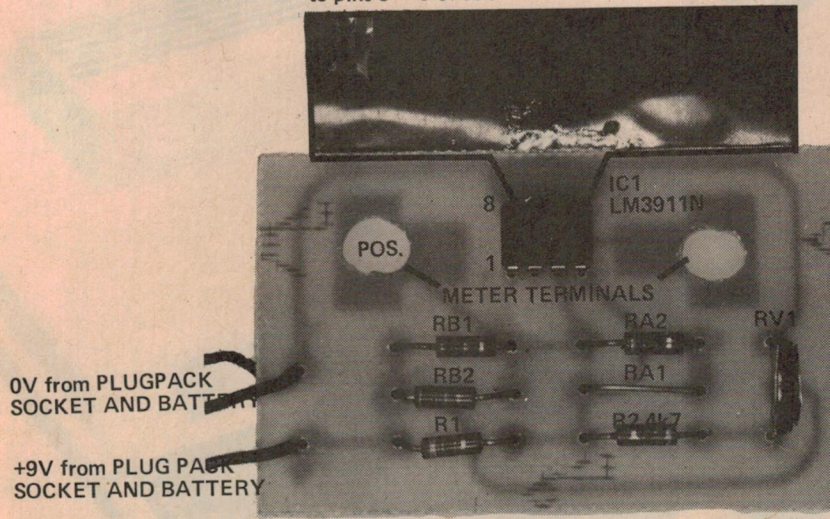
# temperature meter

Copper sheet connected  
to pins 5 - 8 of IC1



## PARTS LIST — ETI 255

IC1	LM3911N
R1	470R or 1k8
RA1	See table
RB1	"
RA2	"
RB2	"
R2	4k7
All resistors should be 2% or selected 5%, 1/4W or 1/2W metal film types.	
RV1	500R miniature vertical mounting trimpot
M1	50 or 100 microamp meter (to suit range). University TD 106 or similar.
ETI-255 pc board; case (if required); plug pack adaptor socket and 9V Plug Pack (Ferguson PPA-9/500 or similar); 9V battery (No. 216) and battery clip if required; small piece of 0.25 mm shim copper.	

Apply power and adjust the zero set trimpot which should be capable of adjusting the reading about  $\pm 10^{\circ}\text{C}$ .

## Calibration

Place the unit and a reference thermometer (choose a good one) in a cool place close together and after a few minutes note the difference in readings. Adjust the trim pot for the correct reading.

Two different meter face scales have been included for two temperature ranges,  $-10^{\circ}\text{C}$  to  $40^{\circ}\text{C}$  and  $-10^{\circ}\text{C}$  to  $90^{\circ}\text{C}$ . Values have also been calculated for  $0^{\circ}\text{C}$  to  $50^{\circ}\text{C}$  and  $0^{\circ}\text{C}$  to  $100^{\circ}\text{C}$  scales to allow standard scales on  $50\mu\text{A}$  and  $100\mu\text{A}$  meters to be used.


Full size artwork for meter scale covering  $-10^{\circ}\text{C}$  to  $+40^{\circ}\text{C}$ . Scotchcal meter scales will be available from suppliers — see Shoparound on page 83.



Rear view of the instrument showing general assembly. You may prefer to use a rechargeable NiCad type, rather than the dry battery shown, for battery operation of the unit.

fin is not touching any other part of the circuit.

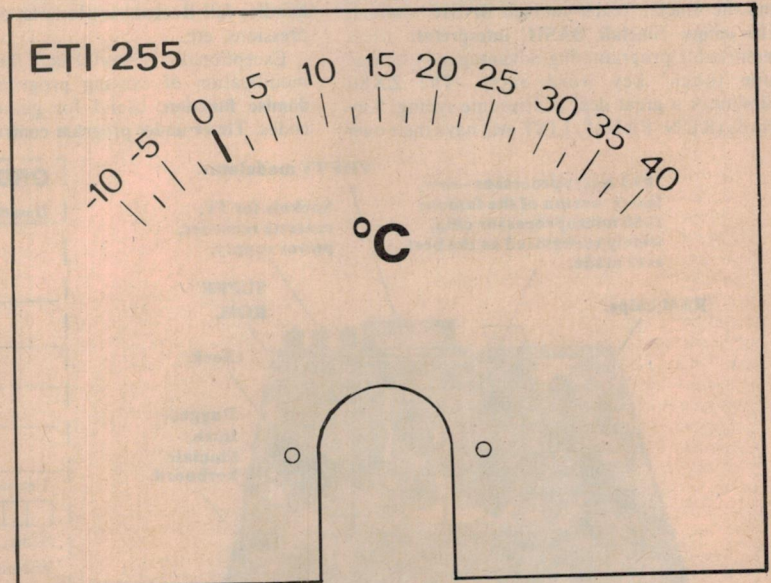Finally, fit the meter after cleaning the meter pads on the pc board. The spring washer supplied with the meter should be assembled on the copper side of the board so it digs into the surface of the copper for good contact. If this is not done the meter connections may become a high resistance when the copper tarnishes after use.





# Australia's first under \$3000 COMPUTER...

**\$295**  
INCL. ZX80 BASIC  
MANUAL

Remember — all prices shown include sales tax, postage and packing.

N.B. Your Sinclair ZX80 may qualify as a business expense.

## Sinclair ZX80 - British made.

Until now, building your own computer could cost you around \$600 — and still leave you with only a bare board for your trouble. The Sinclair ZX80 changes all that. For just \$295 you get **everything** you need including leads for direct connection to your own cassette recorder and television. The ZX80 really is a complete, powerful full-facility computer matching or surpassing other personal computers costing much more. The ZX80 is programmed in BASIC and you could use it for anything from chess to running a power station.

Two unique and valuable components of the Sinclair ZX80: the Sinclair BASIC interpreter and the Sinclair teach-yourself BASIC manual. The unique Sinclair BASIC interpreter: offers remarkable programming advantages — unique 'one touch' key word entry. The ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST etc) have their own


single key entry. Unique syntax check. Only lines with correct syntax are accepted into programs. A cursor identifies errors immediately, preventing entry of long and complicated programs with faults only to discover them when you run.

Excellent string handling capability — takes up to 26 string variables of any length. All strings can undergo all rational tests (e.g. comparison). The ZX80 also has string input to request a line of text; strings do **not** need to be dimensioned. Up to 26 single dimension arrays. FOR/NEXT loops nested up to 26. **Variable names** of any length. BASIC language also handles full Boolean arithmetic, conditional expressions, etc.

Exceptionally powerful edit facilities, allows modification of existing program lines. **Randomise function**, useful for games and secret codes. **Timer under program control**. PEEK and

POKE enable entry of machine code instructions,USR causes jump to a user's machine language sub-routine. **High resolution graphics** with 22 standard graphic symbols. The Sinclair teach-yourself-BASIC manual 96 page book free with every kit.

Fewer chips, compact design, volume production means **MORE POWER FOR YOUR DOLLAR!** The ZX80 owes its low price to its remarkable design; the whole system is packed onto fewer, newer more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system and monitor. And the ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer because the ZX80's brilliant design packs the RAM so much more tightly. (Key words occupy just a single byte). You can add to the memory via the expansion port, giving a maximum potential of 16K.

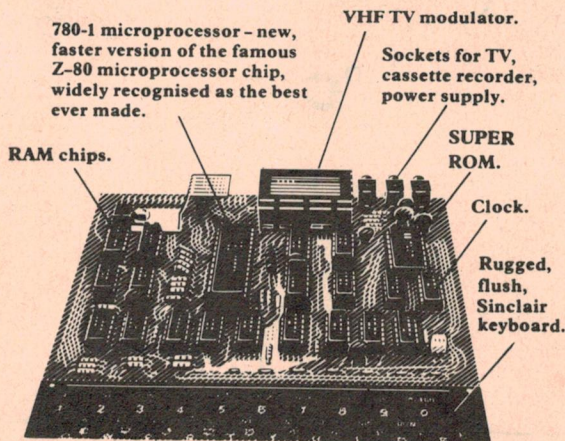

### ORDER FORM:

SINCLAIR EQUIPMENT (AUSTRALASIA) PTY. LTD.  
308 High St., Kew 3101, Vic. Tel. 861 6224.

Quantity	Item	Item Price	Total
	Ready-assembled Sinclair ZX80 Personal Computer(s). Price incl. ZX80 BASIC manual, excl. mains adaptor.	\$295.00	
	Mains Adaptor(s) (600Ma at 9V DC nominal unregulated).	\$ 9.50	
	Memory Expansion Board(s) takes up to 3K bytes.	\$ 28.50	
	RAM Memory chips — standard 1K bytes capacity.	\$ 10.00	
	Sinclair ZX80 Manual(s) free with every ZX80 computer.	\$ 15.00	
I enclose cheque/Bankcard/Diners Club/Amex		TOTAL	

Name \_\_\_\_\_ ETI  
Address \_\_\_\_\_ Postcode \_\_\_\_\_



# they're here!



# LINSAC

## SINCLAIR ZX80

### SOFTWARE

(and more to come)

# C-12 CASSETTES, \$12

per pack  
including  
postage &  
packing

**PROGRAMS ON CASSETTE WITH FULL DOCUMENTATION.**  
**ALL PROGRAMS RUN ON BASIC ZX80 SYSTEM UNLESS OTHERWISE STATED.**

**ZX80 COMPANION  
87 PAGE BOOK**

**\$16**

Book is arranged so that the intending user of the ZX80 entering computing may start using the system and gradually gain a better appreciation of the machine and facilities. The informed computer user will find the later sections useful in applying his knowledge to the ZX80 which has brought a breath of fresh air to the personal computer scene.

Linsac Software comes on C12 Cassettes with **Full Documentation** including

- Program Listing • User Instructions • List of Variables with Meanings
- Program Description • Sample Program Run

#### GAMES PACK ONE CONTAINS

- G001 Three Towers**  
Rearrange the rings to build a new tower.
- G002 Number Guessing**  
Find the hidden number with hints from the ZX80.
- G003 Mastermind**  
Break the four digit code.
- G004 Sketcher**  
Draw patterns of your choice with memory mapping.
- G005 Hurdle**  
Hunt the horrible hurdle in the 15x15 grid.
- G006 Nim**  
The familiar game of skill.
- G007 Symbol Simon**  
Try and match the complex increasing pattern.

#### GAMES PACK TWO CONTAINS

- G008 Nine Lives**  
A word game for two players — possibly fatal.
- G009 The Maze Game**  
Find the treasure as the maze grows around you.
- G010 Plain Sailing**  
Steer a yacht against dangerous currents.
- G012 Noughts & Crosses**  
The ZX80 plays an excellent strategic game.
- G013 Chinese Puzzle**  
Can you rearrange the blocks in the right way?
- G014 Tower of Hanoi**  
The game of antiquity.
- G015 Battleship**  
Realistic naval artillery action.

#### GAMES PACK THREE CONTAINS

- G011 Fruit Machine (2-4K)**  
The ZX80 as a one-armed bandit.
- G016 Four in a Line (4K)**  
A 2 player game arranging patterns of counters.
- G017 Zombies**  
You are surrounded by zombies on a desert island.

#### EDUCATION PACK ONE CONTAINS

- E001 Maths Drill**  
Two levels of difficulty included.
- E002 Dot recognition**  
Recognise the number of a random dot pattern.
- E011 Musical Notes**  
Teaches children notes on the scale.
- E004 Spelling Quiz**  
The teacher sets five words to be tested.
- E007 Day Finder**  
Gives the day of the week for a date.

#### EDUCATION PACK TWO CONTAINS

- E005 Graph Plotter**  
Plots quadratic equations.
- E006 Prime Factors**  
Calculates prime factors of given numbers.
- E008 Number Bases**  
Conversions and calculations in different bases.
- E009 Bar Charts**  
Plots bar charts from supplied data.
- E010 Statistics**  
A collection of statistical routines.

#### UTILITY PACK ONE CONTAINS

- U001 Memory Display**  
Displays 80-byte blocks of memory (char/hex).
- U002 Hex Code Monitor**  
Handles machine code routines.
- U003 Renumber**  
A full renumber routine.
- U004 Memory Search**  
Finds and displays byte patterns.

#### C-12 CASSETTE ORDER FORM

SINCLAIR EQUIPMENT (AUSTRALASIA) PTY. LTD.  
308 High St., Kew 3101, Vic. Tel. 861 6224

Item	Quantity	Total
Games Pack One		
Games Pack Two		
Games Pack Three		
Education Pack One		
Education Pack Two		
Utility Pack One		
ZX80 Book		
Total		


I enclose cheque/Bankcard/Diners Club/Amex

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Name .....

Address ..... Postcode .....



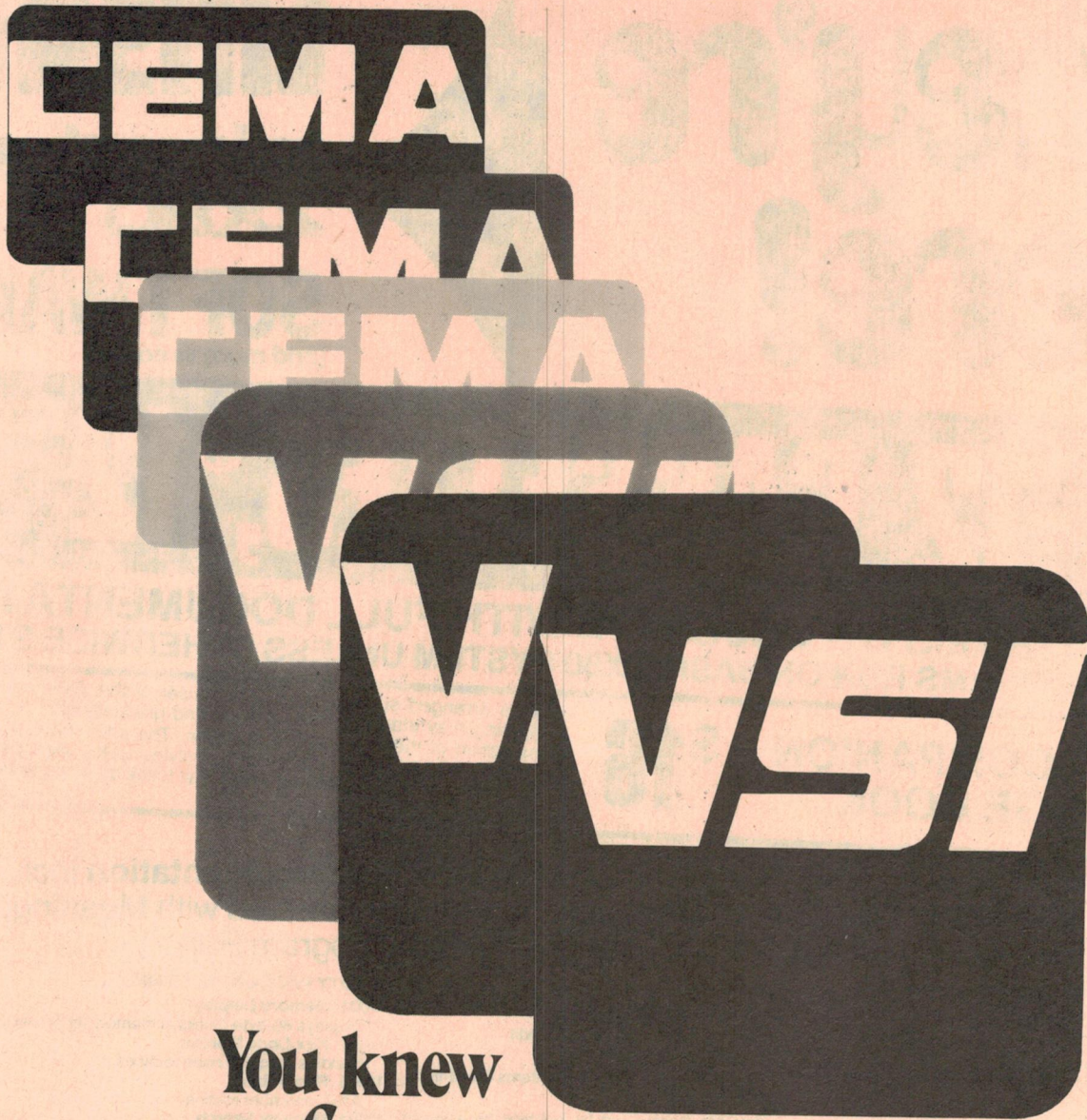

You knew  
us as Cema  
We're now called  
**VSI Electronics Australia**



**VSI  
ELECTRONICS  
(AUSTRALIA)  
PTY LTD**

**SYDNEY 439 8622 MELBOURNE 877 5311 ADELAIDE 516 483 BRISBANE 52 4261 PERTH 328 8091**



# If you're really serious about finding GOLD...

**These books  
tell all!**




## METAL DETECTING IN AUSTRALIA

You too can join the ranks of the rich – just go out and dig up some gold! This book tells you how, when, where and why. It is invaluable for the serious treasure seeker. Cat B-4520

**\$4.50**
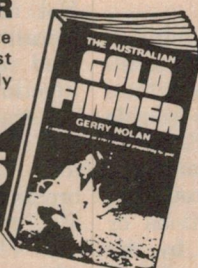
## THE AUSTRALIAN GOLDFINDER

Just released – this up-to-the-minute reference book shows you the latest way to make a fortune – electronically with a metal detector. How to use them, what to look for, even checking for 'fools gold'. Take it with you on your next trip! Cat B-4525



**\$1.95**

## STOP PRESS

**\$1,000,000 GOLD NUGGET  
FOUND BY AMATEUR  
PROSPECTOR EARLY OCTOBER  
IN VICTORIA!  
WILL YOURS BE NEXT???**

## IS THIS THE ULTIMATE?

THE DICK SMITH/D TEX SCANNER 1

## GOLD FINDER

There are a lot of detectors around, but none can match the Scanner 1 Goldfinder. Check the features out – and then the price. It is far and away the best value metal detector in Australia today!

- ★ TWIN SEARCH COILS
- ★ GROUND REJECTION
- ★ DUAL MODE FULL RANGE DISCRIMINATION
- ★ ADJUSTABLE SENSITIVITY
- ★ MADE IN USA EXCLUSIVELY FOR DICK!



Cat X-1075



Terms available to approved applicants – or use your Bankcard!

## HUGE PRICE/TECHNOLOGY BREAKTHROUGH!

## TRACKER T-R

Most metal detectors can't tell treasure from rubbish. This one can, as the discriminator microprocessor can compare ferrous and non-ferrous metals. Other discriminator type detectors sell on the Australian market for \$300 to \$480.00 – look at this one!



Cat X-1065

This system uses a microprocessor circuit which replaces all the conventional complicated knobs – so it is very simple to use. It is NOT a 'toy' type detector with a BFO circuit: it is a true T-R (transmit-receive) type with highly sophisticated circuitry.

**YES! A FULL TRANSMIT/  
RECEIVE FOR LESS THAN \$300.00!!!!**

## DICK SMITH ELECTRONICS

**NSW** 125 York Street,  
818 George Street,  
162 Pacific Hwy,  
30 Grose Street,  
613 Princes Hwy,  
147 Hume Hwy,  
531 Pittwater Road,  
145 Parramatta Road,  
**SYDNEY** 211 3777  
BROADWAY  
GORE HILL  
PARRAMATTA  
BLAKEHURST  
CHULLORA  
BROOKVALE  
AUBURN  
290 3377  
211 3777  
439 5311  
683 1133  
546 7744  
642 8922  
93 0441  
(Opening soon!)

**VIC** 263 Keira Street,  
399 Lonsdale Street,  
656 Bridge Road,  
**QLD** 166 Logan Road,  
842 Gympie Road,  
96 Gladstone Street,  
60 Wright Street,  
414 William Street,  
**ACT**  
**SA**  
**WA**

**WOLLONGONG** 28 3800  
**MELBOURNE** 67 9834  
**RICHMOND** 428 1614  
**BURANDA** 391 6233  
**CHERMSIDE** 59 6255  
**FYSHWICK** 80 4944  
**ADELAIDE** 212 1962  
**PERTH** 328 6944

**MAIL ORDER CENTRE: PO Box 321, NORTH RYDE NSW 2113. Ph 888 3200. PACK & POST EXTRA.**

**bankcard**  
welcome here

**SHOPS OPEN 9AM to 5.30PM**  
(Saturday: 9am till 12 noon)  
**BRISBANE: Half hour earlier.**  
**ANY TERMS OFFERED ARE TO**  
**APPROVED APPLICANTS ONLY**  
**RE-SELLERS OF DICK SMITH**  
**PRODUCTS IN MOST AREAS OF AUSTRALIA.**





## Electronic Odometer

F.O. Eliason


THIS DEVICE, which is inexpensive and easy to build, will measure accurately how far a vehicle has travelled over the ground. It is of particular interest to persons who want to know accurately how far they have travelled down any of the thousands of unmarked bush tracks in Australia.

The device works by counting the revolutions of the back wheel of the vehicle using a phototransistor which looks at a white strip painted on the tyre. Signals from the phototransistor are processed in an integrated circuit to provide pulses at high enough level to operate a relay. Counting is achieved by making the relay operate in parallel with a function key on a cheap electronic pocket calculator.
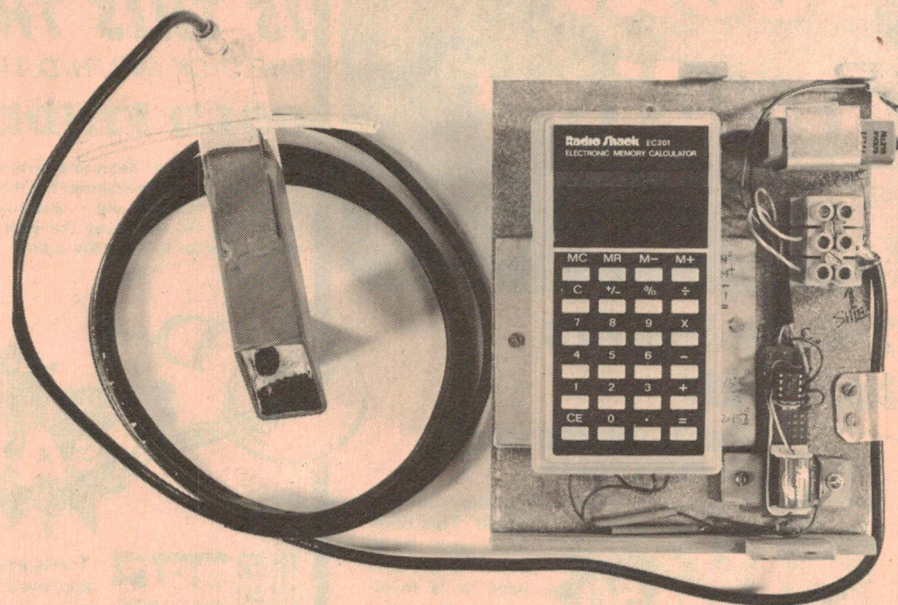
### The Circuit

A 555 is connected to operate in the monostable mode as shown in the circuit. Its operation is controlled by a phototransistor type 4PT100 which has excellent sensitivity. The base connection of the phototransistor is not used.

Under "dark" conditions the collector-emitter resistance of the phototransistor is high and this holds the 555 in the 'off' state (pin 3 low). When the phototransistor is illuminated its resistance falls and the voltage at pin 2 falls. When this reaches about two thirds of the supply voltage, pin 3 is switched to the high state. Potentiometer RV1 provides control of the triggering point of the 555, permitting adjustment of the level of lighting which



Overall view of my odometer. The calculator and electronics are attached to a chipboard base. The phototransistor sensor is mounted on the wheel guard and connects via shielded cable.

is to trigger the device.




The output from pin 3 operates a small reed relay. This can be any small relay with a coil resistance greater than 60 ohms. The type used was a Marble MEL 400, available from Dick Smith.

A Tandy pocket calculator type EC-201 was chosen to do the counting because successive unit additions or subtractions can be achieved by the operation (after setting up) of one function key, in this case the (=) key.

Not all cheap calculators have this "totalling" facility. The contacts of the reed relay are paralleled across this function key.

Care has to be exercised when opening the calculator to ensure that the four moulded locking tags are not broken off. When opened, peel the sheet of switch retaining plastic back from the area of the = switch and solder two 100 mm long tails to the printed circuit runs leading to each side of this

### COMPONENT PINOUTS

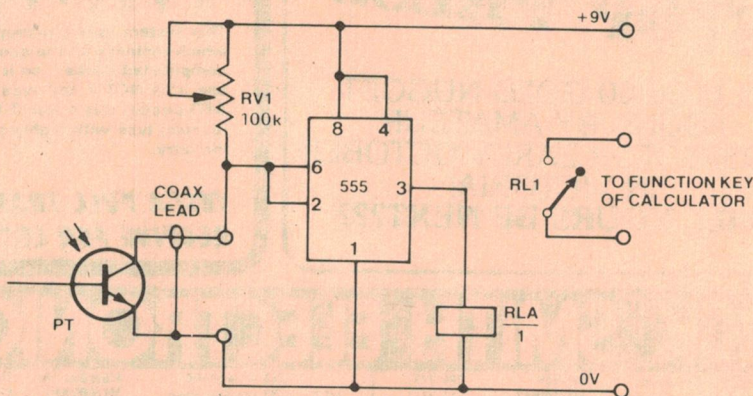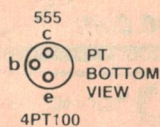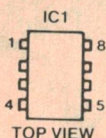

The circuitry is simplicity itself. The potentiometer (RV1) provides control of the triggering point of the 555. The function key you use on the calculator will depend on the make — the Tandy EC-201 (like most) will totalise using the = key, others employ the + key.



switch. Spend some time preparing the surface and ensure that a good soldered joint is made.

The switch board inside the calculator sits on four plastic spigots and a way has to be found to get the board back onto these spigots while closing the case, otherwise there might be problems with the relative positioning of the keys on the case and the switches on the printed circuit board. When you have closed the calculator I suggest that you secure the wires to the case with epoxy glue to take the strain off the soldered connections.

The sensor assembly is shown in the photograph. It is made of 23 mm square-section lightweight steel tube with a flange welded to it to match the turned-in flange of the mudguard. It is secured to the mudguard by two self-tapping screws.

One end of the tube is sawn off at an angle to give an end parallel to the tyre. The other end is drilled and a small steel tube welded over the hole to form a gland. The purpose of the gland is to take the strain of the cable off the elec-

trical connections of the device inserted into the tube and to make it watertight. When mounted, the sensor is no more than 20 mm from the tyre.

The phototransistor, which incidentally can be obtained from Tandy, and terminals were fixed to a strip of paxolin and slipped into the sensor tube and sealed in place with silicone rubber. To eliminate the effect of glare, a small plastic tube, painted with matt black, was slipped over the phototransistor and held in place with silicone rubber. The coax lead was fed through the gland and soldered to the terminals. The gland was then sealed with epoxy glue and the sensor tube was sealed with silicone rubber.

A point which must be taken into consideration is movement of the wheel vertically with respect to the mudguard (when the vehicle is laden or when it lunges). The ideal mounting point for the sensor is at 3 o'clock. Thought should also be given to covering the end of the sensor tube with clear plastic to keep it free from dust and water.

The few components used in associ-

ation with the calculator were mounted together with the calculator on a wooden board as shown in the photograph. In the arrangement shown, the calculator and relay circuit each have their own nine volt batteries.

## Setting up

Test the circuit in stages during construction. Set RV1 to mid position to start with and adjust it subsequently to take account of the light level. The unit is so simple that there is really nothing else to do. This unit has been used at speeds up to 50 kph but it might do a lot more and be of some interest to rally drivers. Cyclists might even be interested. I built my system to help me find my way to remote gold mining sites located in the depths of State forests.

The advantage of using a calculator to do the counting is that, apart from being ready-made, it will allow a constant to be keyed in so that it will display the exact distance travelled in yards, metres, miles etc., instead of just wheel revolutions.

# TASMAN ELECTRONICS

12 Victoria Street,  
Coburg 3058.  
Phone (03) 354-5062.

## 74LS-

74LS00	33	74LS107	65
74LS01	30	74LS109	50
74LS02	30	74LS113	50
74LS04	40	74LS114	75
74LS05	50	74LS123	1.50
74LS08	30	74LS125	70
74LS09	30	74LS133	30
74LS10	30	74LS138	1.10
74LS11	55	74LS151	1.00
74LS12	30	74LS155	60
74LS14	80	74LS157	75
74LS15	75	74LS160	70
74LS16	60	74LS163	80
74LS20	30	74LS164	1.40
74LS21	35	74LS165	1.40
74LS27	30	74LS169	1.90
74LS28	35	74LS174	65
74LS30	30	74LS175	90
74LS32	30	74LS190	1.60
74LS37	40	74LS191	1.30
74LS38	40	74LS192	1.15
74LS40	30	74LS193	1.00
74LS42	45	74LS194	1.20
74LS47	1.20	74LS195	1.00
74LS73	60	74LS196	1.60
74LS74	40	74LS197	1.60
74LS75	50	74LS221	1.50
74LS78	65	74LS247	1.95
74LS85	1.40	74LS251	85
74LS86	60	74LS253	85
74LS90	60	74LS257	75
74LS92	1.00	74LS259	3.30
74LS93	85	74LS279	95
74LS95	1.00	74LS290	1.30

74LS365	80	7440	30
74LS366	80	7441	2.50
74LS367	90	7442	80
74LS368	65	7447	1.10
74LS373	2.40	7448	1.10
		7450	30
		7451	30
		7453	30
		7454	30
		7460	30
		7470	50
		7472	55
		7473	55
		7474	35
		7475	45
		7476	40
		7480	1.00
		7483	1.40
		7485	1.40
		7486	55
		7489	2.90
		7490	40
		7491	1.00
		7492	80
		7493	50
		7494	1.15
		7495	1.00
		7496	1.10
		74100	2.00
		74107	70
		74121	70
		74123	85
		74132	1.30
		74145	1.50

## 7400-

7400	25
7401	25
7402	25
7403	25
7404	25
7405	30
7406	60
7407	45
7408	25
7409	25
7410	25
7412	90
7413	55
7414	60
7416	60
7417	65
7420	25
7421	30
7422	35
7425	60
7426	40
7427	40
7430	30
7432	30
7437	40
7438	40
7439	50

74150	1.50	1N3493R	1.70
74151	1.40	1N4001	0.08
74153	1.40	1N4002	10
74154	1.40	1N4004	10
74157	1.40	1N4007	20
74160	1.70	1N4148	0.06
74165	1.70	1N5060	45
74172	1.40	1N5404	40
74173	2.60	1N5408	80
74175	1.20	P600G	90
74180	1.50	ST2	55
74192	1.80	ST4	80
74193	1.80		
74176	1.80		
74176	1.50		
74367	80		

## DIODES

A14P	75
AAV30	40
BA102	70
BA244	22
BAW62	12
BP104	2.80
BR100	30
BYX10	70
BYX71-350	1.20
HP5082/2800	2.50
OA47	40
OA90	20
OA91	20
OA202	80
OA636-1000	70
1N3493	1.70

## BRIDGE RECT.

MDA201	95
MDA2504	4.20
MDA3501	4.20
VJ448	4.60
VM48	1.50
W02	75

Mail Orders, \$1.00  
Min. P&P Please.





# Checkout our Specials

**25W 8Ω 3WAY SPEAKER KIT SALE!**

WALNUT finish, ready-made boxes, black speaker cloth.

8 WOOFER + 5 MID-RANGE + 3 TWEETER + X OVERS + wire and innerband + screws!

Can be finished in 2 hours!  
Great sound!  
55Hz-18KHz resp.

**PER PAIR \$69**

ASSEMBLED & TESTED **\$109**

**CORAL SUPA-WALU DO-IT-YOURSELF**

CORAL AUDIO

High quality, famous name kits, complete with speakers, crossover, mtg. screws, terminals, name badge, instructions for building cabinets to suit and installation.

65A 1 6" 2 way 30W, 50Hz-20KHz pair \$52  
65A 1 8" 3 way 35W, 50Hz-20KHz pair \$58  
85A 6A 8" 2 way 35W, 50Hz-20KHz pair \$65  
105A 1 10" 3 way 50W, 40Hz-20KHz pair \$97  
105A 1A 10" 3 way 50W, 40Hz-20KHz pair \$109  
125A 1 12" 3 way 60W, 30Hz-20KHz pair \$133

**50W 8Ω 3WAY HI-FI SPEAKERS - for car or home**

50Hz-20KHz PAIR ONLY

**\$95**

4 SPEAKERS ON A DRAFFLE

**12V CAR CASSETTE TAPE HEAD DEMAG. PROBE**

RESTORES OUTPUT AND H.F. RESPONSE.

**\$1.99**

SCOOP! Save \$5 were \$6.99

**CANNON PLUGS & SOCKETS**

LOOK! SPECIAL PRICES!

XLP-3-11 PLUG \$3.20  
XLP-3-32 SOCKET \$1.80  
XLP-3-31 PLUG \$3.95  
XLP-LNE-11 \$4.65  
240V AC PANEL SOCKET XLP-LNE-32 \$2.90  
240V AC LINE SOCKET XLP-LNE-12 \$4.35

**PHILIPS TRIPLERS**

FOR COLOUR TV

As used in Pys, Philips, Krustler etc and most German colour TVs.

**\$12**

**NEW CLIP-IN PHONE DIALERS**

Install in mins! Only 3 wires to connect!

**\$29.99** Now **\$10**

Save \$19.99

Specially designed to replace Aust. rotary dials. Not approved by Telecom under current reg.

**ETI-084 CAR BURGLAR ALARMS**

DETECTS VOLTAGE DROP! FLASHING LED WARNING!

Assembled, easy to install PCB, add only keyswitch (66-70) or hidden switch - use car horn or siren speaker (\$17-90) ONLY WHILE THEY LAST!

**\$10**

**75mm LABORATORY OSCILLOSCOPE**

VERTICAL DEFLECTION - 10 DIV  
HORIZONTAL DEFLECTION - 10 DIV  
TIME BASE - 100μs/div to 100ms/div  
In 4 ranges  
SYNCHRONIZING - Internal and external  
POWER REQUIREMENTS - 100/230V, 50/60 Hz approx.  
10 WATT

Dimensions: 200mm (H) x 150mm (W) x 100mm (D)  
Weight: approx. 3.5 kg  
PLUS - a comprehensive instruction manual

Same specs as Dick Smiths Q-1280 but \$20 cheaper! Worth it!

Also 150mm model same specs, extra features

**\$299** Model **\$269** Model **\$150**

**PL-259 PLUGS**

with in-built reducer etc

**NEW TOP QUALITY**

PUSH **40** OR **10** ON TYPE EA FOR \$3.50

Importer sacrifices stock!

**ELECTRICAL TERMINAL BLOCKS**

EA **50c**

(12 FOR 50c) MULTIPLES OF 12

**50W 8Ω 3WAY HI-FI SPEAKERS - for car or home**

50Hz-20KHz PAIR ONLY

**\$95**

4 SPEAKERS ON A DRAFFLE

**12V CAR CASSETTE TAPE HEAD DEMAG. PROBE**

RESTORES OUTPUT AND H.F. RESPONSE.

**\$1.99**

SCOOP! Save \$5 were \$6.99

**CANNON PLUGS & SOCKETS**

LOOK! SPECIAL PRICES!

XLP-3-11 PLUG \$3.20  
XLP-3-32 SOCKET \$1.80  
XLP-3-31 PLUG \$3.95  
XLP-LNE-11 \$4.65  
240V AC PANEL SOCKET XLP-LNE-32 \$2.90  
240V AC LINE SOCKET XLP-LNE-12 \$4.35

**PHILIPS TRIPLERS**

FOR COLOUR TV

As used in Pys, Philips, Krustler etc and most German colour TVs.

**\$12**

**THIS MONTH ONLY! 1ST-30TH NOVEMBER**

**POST FREE**

WE PAY. YOU SAVE 10%

**LOOK**

Phone orders 24 hours a day

Between Leichardt & Ashfield  
6 Kms CITY  
PARRAMATTA RD  
ST  
Lewisham Station

**NEW CLIP-IN PHONE DIALERS**

Install in mins! Only 3 wires to connect!

**\$29.99** Now **\$10**

Save \$19.99

Specially designed to replace Aust. rotary dials. Not approved by Telecom under current reg.

**ETI-084 CAR BURGLAR ALARMS**

DETECTS VOLTAGE DROP! FLASHING LED WARNING!

Assembled, easy to install PCB, add only keyswitch (66-70) or hidden switch - use car horn or siren speaker (\$17-90) ONLY WHILE THEY LAST!

**\$10**

**75mm LABORATORY OSCILLOSCOPE**

VERTICAL DEFLECTION - 10 DIV  
HORIZONTAL DEFLECTION - 10 DIV  
TIME BASE - 100μs/div to 100ms/div  
In 4 ranges  
SYNCHRONIZING - Internal and external  
POWER REQUIREMENTS - 100/230V, 50/60 Hz approx.  
10 WATT

Dimensions: 200mm (H) x 150mm (W) x 100mm (D)  
Weight: approx. 3.5 kg  
PLUS - a comprehensive instruction manual

Same specs as Dick Smiths Q-1280 but \$20 cheaper! Worth it!

Also 150mm model same specs, extra features

**\$299** Model **\$269** Model **\$150**

**ETI-084 CAR BURGLAR ALARMS**

DETECTS VOLTAGE DROP! FLASHING LED WARNING!

Assembled, easy to install PCB, add only keyswitch (66-70) or hidden switch - use car horn or siren speaker (\$17-90) ONLY WHILE THEY LAST!

**\$10**

**75mm LABORATORY OSCILLOSCOPE**

VERTICAL DEFLECTION - 10 DIV  
HORIZONTAL DEFLECTION - 10 DIV  
TIME BASE - 100μs/div to 100ms/div  
In 4 ranges  
SYNCHRONIZING - Internal and external  
POWER REQUIREMENTS - 100/230V, 50/60 Hz approx.  
10 WATT

Dimensions: 200mm (H) x 150mm (W) x 100mm (D)  
Weight: approx. 3.5 kg  
PLUS - a comprehensive instruction manual

Same specs as Dick Smiths Q-1280 but \$20 cheaper! Worth it!

Also 150mm model same specs, extra features

**\$299** Model **\$269** Model **\$150**

**PL-259 PLUGS**

with in-built reducer etc

**NEW TOP QUALITY**

PUSH **40** OR **10** ON TYPE EA FOR \$3.50

Importer sacrifices stock!

**ELECTRICAL TERMINAL BLOCKS**

EA **50c**

(12 FOR 50c) MULTIPLES OF 12

**50W 8Ω 3WAY HI-FI SPEAKERS - for car or home**

50Hz-20KHz PAIR ONLY

**\$95**

4 SPEAKERS ON A DRAFFLE

**12V CAR CASSETTE TAPE HEAD DEMAG. PROBE**

RESTORES OUTPUT AND H.F. RESPONSE.

**\$1.99**

SCOOP! Save \$5 were \$6.99

**CANNON PLUGS & SOCKETS**

LOOK! SPECIAL PRICES!

XLP-3-11 PLUG \$3.20  
XLP-3-32 SOCKET \$1.80  
XLP-3-31 PLUG \$3.95  
XLP-LNE-11 \$4.65  
240V AC PANEL SOCKET XLP-LNE-32 \$2.90  
240V AC LINE SOCKET XLP-LNE-12 \$4.35

**PHILIPS TRIPLERS**

FOR COLOUR TV

As used in Pys, Philips, Krustler etc and most German colour TVs.

**\$12**

**THIS MONTH ONLY! 1ST-30TH NOVEMBER**

**POST FREE**

WE PAY. YOU SAVE 10%

**LOOK**

Phone orders 24 hours a day

Between Leichardt & Ashfield  
6 Kms CITY  
PARRAMATTA RD  
ST  
Lewisham Station

**PRE-PAK electronics**

P.O. Box 43, CROYDON 2132

la West St. Lewisham, N. S.W.

Ph: 569-9797 **ADPOST 10%**

Phone or MAIL ORDER

**bankcard**

☐ Cheque ☐ Postal Order ☐ Charge to my Bankcard Account (Please don't send cash)

Account No. **496**

Expiry Date \_\_\_\_\_

Cardholder's Signature \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_

**PRE-PAK electronics**

P.O. Box 43, CROYDON 2132

la West St. Lewisham, N. S.W.

Ph: 569-9797 **ADPOST 10%**

Phone or MAIL ORDER

**bankcard**

☐ Cheque ☐ Postal Order ☐ Charge to my Bankcard Account (Please don't send cash)

Account No. **496**

Expiry Date \_\_\_\_\_

Cardholder's Signature \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_

**VORTEX cassette mechanisms**

Missing only record/playback head, knobs and counter.

Suit experimenters, spares etc.

**\$10**

**JAP SEMICONDUCTOR MANUALS**

1. TRANSISTOR SUBSTITUTION MANUAL  
2. TRANSISTOR MANUAL  
3. LINEAR IC MANUAL  
4. DIODE MANUAL  
5. FET MANUAL

SOLD OUT! **\$5** each

**DE-SOLDERING WICK**

WAS \$2.25 Now **\$1.75**

**HEAVY DUTY MINI RELAYS**

24v 700mA 10A% contacts

**\$1.49**

**TRANSFORMERS**

All new, 240v input, guaranteed by Mal

830	0-6V-18V 1A	4.50
811	26V 1A, 6.3V 1A	4.90
761	31V 1A, 6.3V 1A	4.90
101	50V 1A x 2 windings, 6.3V 5.50	
110	110V 3A, 26V 1A	5.90
112	200V C.T. 15A, 6.3V 5A	6.00
185	12V 5A, 26V 1A	3.95

**LOWEST PRICED SWITCHES SALE**

8 ON-(ON) SPDT 10 FOR \$7  
D. ON-OFF-(ON) (3P)  
E. (ON)-OFF-(ON)  
J. ON-(ON) DPDT 10 FOR \$9  
L. ON-OFF-(ON) DPDT (6P)  
J. ON-OFF-(ON)

SPDT 3P A. ON-ON 90c Mini Toggle Switch  
Mini Toggle Switch F. ON-ON \$1.35  
DPDT 6P

Mini SPST ON-OFF 20c  
ROCKER 10 for \$1.50

**the super specials.**

4-6.5mm stereo line sockets	10 for \$1
10-10-18 circular heatinks	10 for \$1
10-NE2 neons 90v working 10 for \$1	
50-1/2" rubber grommets	50 for \$1
3-EHT 9 pin Valve sockets 3 for \$1	
50-10-3 insulating bushes	50 for \$1
20-asst. RF, IF, OSC coils	20 for \$1
10-asst. trimmer capacitors	10 for \$1
200-1/2W resistors, ass't. short lead	\$1
40-TV, radio knobs for service, ass't.	\$1
6-3AG in-line plastic fuseholders	8 for \$1
8-6.3V 0.15A dial lamps	8 for \$1
3-ferrite baluns for VHF	3 for \$1
4-0.47uF 400v poly capacitors	\$1
Ignition Interference Kit for Car Stereo	\$1
3-8x2 1/2" diam ferrite rods	\$1
1-2 1/2" (57mm) 8a. speaker	\$1
110V DC 13KA 3PDT 10A relay	\$1
47-90v DC 3PDT Cradle relay	\$1
3-3 pin mini plug/socket	\$1
6-mini DPDT slide switches	\$1
10-metres speaker cable	\$1
5-2uF non-pol. capacitors	\$1
12-metres ass't. cals. hook-up wire	\$1
2-1000uF 25v PCB electros.	2 for \$1
2-500uF 25v digtal electro	ea \$1
2-Jabel coil aligning tools	pr \$1
5-PVC trans. radio tuning gags	\$1
3-HT Ignition Suppressor res. 15K	\$1
Valve output transformers C.P. ea \$1	
10-flg. heatinks, 70-91, 10 for \$1	
10-plastic knobs, brown or white	\$1
5-4-20Pf ceramic trimmer caps	\$1
5-0-50Pf cer. air-spaced trimmers	\$1
12-Pot nuts and washers	12 for \$1
80 way P.C.B. edge connector 0.156	\$1
Cut to length ne244 - over 12' long!	

**the super specials.**

IN4004	400v 1A rect.	10c
IN4007	1Kv 1A rect.	15c
IN5404	400v 3A rect.	30c
IN5408	1Kv 3A rect.	40c
IN914	IN4148 diode	10c
RED LED	std. 5mm	20c
RED LED	std. 5mm	18c
GREEN LED	std. 5mm	25c
ORANGE LED	std. 5mm	35c
LM380	2 Watt IC	\$1.50
2N3055	TO-3 trans	\$1.00
10-0.47uF 35Vw Tag Tantalum Caps		\$1
10-0.47uF 100Vw Green caps		\$1
10-0.1uF 100Vw Greencaps		\$1
8-0.22uF 100Vw Greencaps		\$1
3-1-5uF 100Vw Greencaps		\$1
10-47uF 6.3Vw Tag Tant Caps		\$1
10-2-2uF 20Vw Tag Tant Caps		\$1
12-0.68uF 35Vw Tag Tant Caps		\$1
20-10uF 65Vw axial Electro		\$1
18-22uF 65Vw axial Electro		\$1
25-100uF 10Vw axial Electro		\$1
20-100uF 16Vw PCB Electro		\$1
10-100uF 16Vw axial Electro		\$1
10-220uF 25Vw axial or PCB		\$1
8-250uF 6.4Vw axial Electro		\$1
15-330uF 16Vw axial Electro		\$1
15-330uF 35Vw axial Electro		\$1
5-47uF 50Vw axial or PCB Electro		\$1
8-1000uF 10Vw axial Electro		\$1
2-2500uF 6.3Vw axial Electro		\$1
6-1uF 50Vw Philips Poly. caps		\$1
30-0.1uF 160Vw Philips Poly. caps		\$1
10-0.1uF 400Vw Polyester caps		\$1
8-0.22uF 400Vw Polyester caps		\$1
20-assorted 400Vw Poly caps		\$1

**the super specials.**

IN4004	400v 1A rect.	10c
IN4007	1Kv 1A rect.	15c
IN5404	400v 3A rect.	30c
IN5408	1Kv 3A rect.	40c
IN914	IN4148 diode	10c
RED LED	std. 5mm	20c
RED LED	std. 5mm	18c
GREEN LED	std. 5mm	25c
ORANGE LED	std. 5mm	35c
LM380	2 Watt IC	\$1.50
2N3055	TO-3 trans	\$1.00
10-0.47uF 35Vw Tag Tantalum Caps		\$1
10-0.47uF 100Vw Green caps		\$1
10-0.1uF 100Vw Greencaps		\$1
8-0.22uF 100Vw Greencaps		\$1
3-1-5uF 100Vw Greencaps		\$1
10-47uF 6.3Vw Tag Tant Caps		\$1
10-2-2uF 20Vw Tag Tant Caps		\$1
12-0.68uF 35Vw Tag Tant Caps		\$1
20-10uF 65Vw axial Electro		\$1
18-22uF 65Vw axial Electro		\$1
25-100uF 10Vw axial Electro		\$1
20-100uF 16Vw PCB Electro		\$1
10-100uF 16Vw axial Electro		\$1
10-220uF 25Vw axial or PCB		\$1
8-250uF 6.4Vw axial Electro		\$1
15-330uF 16Vw axial Electro		\$1
15-330uF 35Vw axial Electro		\$1
5-47uF 50Vw axial or PCB Electro		\$1
8-1000uF 10Vw axial Electro		\$1
2-2500uF 6.3Vw axial Electro		\$1
6-1uF 50Vw Philips Poly. caps		\$1
30-0.1uF 160Vw Philips Poly. caps		\$1
10-0.1uF 400Vw Polyester caps		\$1
8-0.22uF 400Vw Polyester caps		\$1
20-assorted 400Vw Poly caps		\$1

**the super specials.**

IN4004	400v 1A rect.	10c
IN4007	1Kv 1A rect.	15c
IN5404	400v 3A rect.	30c
IN5408	1Kv 3A rect.	40c
IN914	IN4148 diode	10c
RED LED	std. 5mm	20c
RED LED	std. 5mm	18c
GREEN LED	std. 5mm	25c
ORANGE LED	std. 5mm	35c
LM380	2 Watt IC	\$1.50
2N3055	TO-3 trans	\$1.00
10-0.47uF 35Vw Tag Tantalum Caps		\$1
10-0.47uF 100Vw Green caps		\$1
10-0.1uF 100Vw Greencaps		\$1
8-0.22uF 100Vw Greencaps		\$1
3-1-5uF 100Vw Greencaps		\$1
10-47uF 6.3Vw Tag Tant Caps		\$1
10-2-2uF 20Vw Tag Tant Caps		\$1
12-0.68uF 35Vw Tag Tant Caps		\$1
20-10uF 65Vw axial Electro		\$1
18-22uF 65Vw axial Electro		\$1
25-100uF 10Vw axial Electro		\$1
20-100uF 16Vw PCB Electro		\$1
10-100uF 16Vw axial Electro		\$1
10-220uF 25Vw axial or PCB		\$1
8-250uF 6.4Vw axial Electro		\$1
15-330uF 16Vw axial Electro		\$1
15-330uF 35Vw axial Electro		\$1
5-47uF 50Vw axial or PCB Electro		\$1
8-1000uF 10Vw axial Electro		\$1
2-2500uF 6.3Vw axial Electro		\$1
6-1uF 50Vw Philips Poly. caps		\$1
30-0.1uF 160Vw Philips Poly. caps		\$1
10-0.1uF 400Vw Polyester caps		\$1
8-0.22uF 400Vw Polyester caps		\$1
20-assorted 400Vw Poly caps		\$1

**the super specials.**

IN4004	400v 1A rect.	10c
IN4007	1Kv 1A rect.	15c
IN5404	400v 3A rect.	30c
IN5408	1Kv 3A rect.	40c
IN914	IN4148 diode	10c
RED LED	std. 5mm	20c
RED LED	std. 5mm	18c
GREEN LED	std. 5mm	25c
ORANGE LED	std. 5mm	35c
LM380	2 Watt IC	\$1.50
2N3055	TO-3 trans	\$1.00
10-0.47uF 35Vw Tag Tantalum Caps		\$1
10-0.47uF 100Vw Green caps		\$1
10-0.1uF 100Vw Greencaps		\$1
8-0.22uF 100Vw Greencaps		\$1
3-1-5uF 100Vw Greencaps		\$1
10-47uF 6.3Vw Tag Tant Caps		\$1
10-2-2uF 20Vw Tag Tant Caps		\$1
12-0.68uF 35Vw Tag Tant Caps		\$1
20-10uF 65Vw axial Electro		\$1
18-22uF 65Vw axial Electro		\$1
25-100uF 10Vw axial Electro		\$1
20-100uF 16Vw PCB Electro		\$1
10-100uF 16Vw axial Electro		\$1
10-220uF 25Vw axial or PCB		\$1
8-250uF 6.4Vw axial Electro		\$1
15-330uF 16Vw axial Electro		\$1
15-330uF 35Vw axial Electro		\$1
5-47uF 50Vw axial or PCB Electro		\$1
8-1000uF 10Vw axial Electro		\$1
2-2500uF 6.3Vw axial Electro		\$1
6-1uF 50Vw Philips Poly. caps		\$1
30-0.1uF 160Vw Philips Poly. caps		\$1
10-0.1uF 400Vw Polyester caps		\$1
8-0.22uF 400Vw Polyester caps		\$1
20-assorted 400Vw Poly caps		\$1

**the super specials.**

IN4004	400v 1A rect.	10c
IN4007	1Kv 1A rect.	15c
IN5404	400v 3A rect.	30c
IN5408	1Kv 3A rect.	40c
IN914	IN4148 diode	10c
RED LED	std. 5mm	20c
RED LED	std. 5mm	18c
GREEN LED	std. 5mm	25c
ORANGE LED	std. 5mm	35c
LM380	2 Watt IC	\$1.50
2N3055	TO-3 trans	\$1.00
10-0.47uF 35Vw Tag Tantalum Caps		\$1
10-0.47uF 100Vw Green caps		\$1
10-0.1uF 100Vw Greencaps		\$1
8-0.22uF 100Vw Greencaps		\$1
3-1-5uF 100Vw Greencaps		\$1
10-47uF 6.3Vw Tag Tant Caps		\$1
10-2-2uF 20Vw Tag Tant Caps		\$1
12-0.68uF 35Vw Tag Tant Caps		\$1
20-10uF 65Vw axial Electro		\$1
18-22uF 65Vw axial Electro		\$1
25-100uF 10Vw axial Electro		\$1
20-100uF 16Vw PCB Electro		\$1
10-100uF 16Vw axial Electro		\$1
10-220uF 25Vw axial or PCB		\$1
8-250uF 6.4Vw axial Electro		\$1
15-330uF 16Vw axial Electro		\$1
15-330uF 35Vw axial Electro		\$1
5-47uF 50Vw axial or PCB Electro</		



## Don't play games with your company's money.

Our entry level computer system is the first step in a full range of computer products. Not the last step in a full range of computer games.


We call it VIP. The Vector Intelligent Partner. And with a price of just \$4200, you can't get more computer for your money.

VIP has all the assets and none of the liabilities of other entry level systems. It starts off with a lot more disk capacity. It has the same computational power, uses the same software as our larger systems, and can be upgraded at any time. So you avoid the expense of new hardware and software when you outgrow your current system.

You'll be able to do low cost word processing, mail list sorting, database management and accounting. You can even do software development.

VIP is perfect for salesmen, real estate brokers, insurance agents, small business owners and corporate department heads.

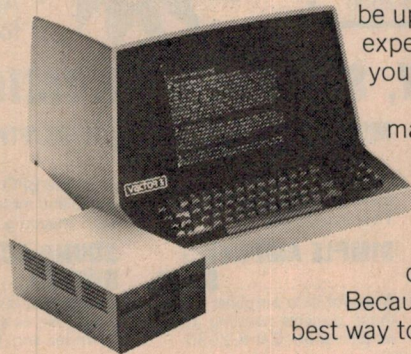Because at Vector, improving your business is the best way to improve our business.



# VECTOR

## Economy Sized Computers™

Australian Distributor



DICKER DATA PROJECTS Pty Ltd

31 Cawarra Road, Caringbah NSW 525 4707 524 5639 Telex 70182



# AT LAST!

STOP PRESS! FIRST PRINTING  
SOLD OUT! NEW PRINTING  
NOW UNDERWAY!

## DICK SMITH'S FUN WAY INTO ELECTRONICS VOL 2

- Twenty exciting and useful projects to build
- Learn how to make your own printed circuit boards
- How to use a multimeter. ● How to solder
- AND MUCH, MUCH MORE!

Cat  
B-2605

Yes! The first printing of Dick Smith's Fun Way into Electronics Volume 2 **sold out** in just a few weeks! A new print run is currently underway, so if you've been unable to obtain a copy of 'Fun Way II', try again soon: it should be back in stock.

'Fun Way II' makes an ideal Christmas gift for anyone interested in electronics: all the projects are easy to build, and none of them costs more than \$8.50! (most are under \$5.00).


And with our 7-day money back guarantee, you cannot lose: if you're not completely happy with the book, you may return it in original condition within 7 days for a full refund of purchase price. What could be fairer?

### 'FUN WAY ONE' STILL AVAILABLE!

Don't forget that 'Dick Smith's Fun Way into Electronics Volume One' is still available from your nearest Dick Smith store, or most good booksellers and newsagents. 'Fun Way One' is intended for the complete beginner - no soldering is required! And it's only \$4.95.

B-2600

**ONLY  
\$6.95**

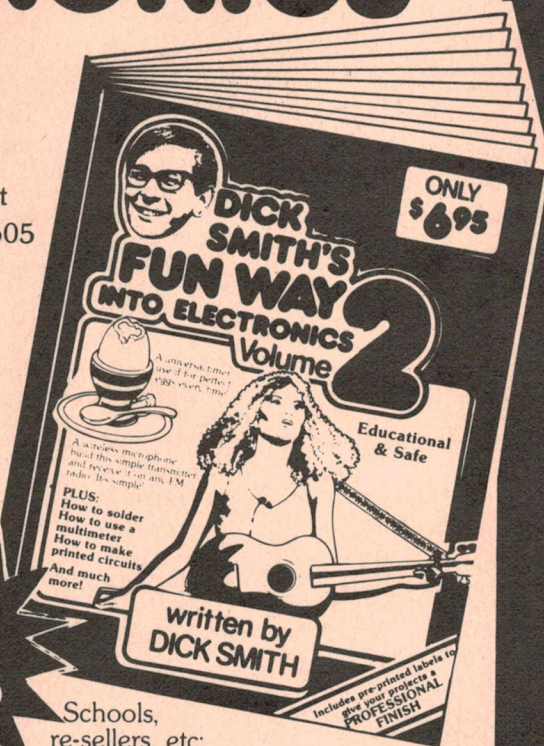

Schools,  
re-sellers, etc:  
Ask about our incredible discounts  
for bulk quantities: books or kits!

## FUN WAY TWO KITS: EASY, SAFE & ECONOMICAL!

### MULTI-PURPOSE LED FLASHER .... \$2.75

A really simple kit that can be used as a warning device, electronic jewellery, etc. Cat K-2621

### DING DONG DOORBELL ..... \$4.00

Welcome visitors to your home with this integrated circuit doorbell! Cat K-2622

### MORSE CODE TRAINER ..... \$4.00

This simple oscillator circuit lets you learn Morse code the easy way! Cat K-2623

### UNIVERSAL TIMER ..... \$5.00

Use it as an egg timer, a dark-room timer, etc: in fact, it's got a lot of applications! Cat K-2624

### ELECTRONIC DICE ... \$4.75

Throwing a dice is old hat: do it electronically! Simple circuit has other uses too. Cat K-2625

### MONOPHONIC ORGAN ..... \$7.50

Easy to build, and easy to play! And it even has 'vibrato' - just like the big ones! Cat K-2626

### POCKET TRANSISTOR RADIO ..... \$7.50

Simple to build, and it's nice and small. Listening is so much more fun! Cat K-2627

### TOUCH SWITCH ..... \$4.90

One touch on, next touch off - or 'on while touched'. Dozens of uses in the home. Cat K-2628

### MOSQUITO REPELLER ..... \$4.50

Don't get eaten by mozzies: scare them away electronically. Take it anywhere. Cat K-2629

### SIMPLE AMPLIFIER ..... \$6.00

A useful little amplifier for all those projects needing audio amplification. Cat K-2630

### WIRELESS MIC. .... \$6.50

A tiny transmitter that can be received on any FM receiver. A great little kit! Cat K-2631

### LIGHT ACTIVATED SWITCH ..... \$4.90

Highly useful for alarms, night light switches, etc etc. Sensitive and reliable. Cat K-2632

### METAL/PIPE LOCATOR ..... \$6.00

A simple BFO circuit you can use to find metals, pipes, wiring, etc - maybe gold! Cat K-2633

### SOUND ACTIVATED SWITCH ..... \$6.50

Picks up sound waves and trips a relay. Use as a telephone bell extender, too. Cat K-2634

### HOME/CAR BURGLAR ALARM ..... \$6.00

Learn how burglar alarms work when you install your own! For home or car. Cat K-2635

### ELECTRONIC SIREN ..... \$4.50

Great for alarm use - or where any warning is required. Good for kids toys, too! Cat K-2636

### LED LEVEL DISPLAY ..... \$8.50

This fascinating project shows you the audio level of any amplifier. Cat K-2637

### INTERCOM UNIT ..... \$8.50

Communicate! Build this intercom and talk between rooms, etc. Cat K-2638

### LED COUNTER MODULE ..... \$7.50

Learn how digital circuits work by building a counter. Count slot car laps, etc. Cat K-2639

### SHORTWAVE RECEIVER ..... \$6.50

Listen in to the exciting world of shortwave radio: amateurs, foreign countries! Cat K-2640

# DICK SMITH ELECTRONICS

SEE OUR OTHER ADVERTS IN THIS MAGAZINE FOR OUR STORE ADDRESSES AND RESELLERS





## Soil moisture indicator

**Phil Wait**  
**Simon Campbell**

Don't drown your plants or dry them out! Take some of the guesswork out of watering with this handy little instrument.

EXPERT GARDENERS can tell by touch when their plants have too little or too much water, but the rest of us could use a little help sometimes. This instrument makes use of the fact that the resistance of soil decreases as the soil gets wetter. A constant current is fed through the soil between the two electrodes of a probe and the voltage drop between them is measured. A line of five light emitting diodes is used to give a simple and robust indicator of the moisture content which can easily be recalibrated to suit different soil types.

For this kind of measurement to work, it is important that both of the electrodes are made of the same metal. Dissimilar metals will set up a small electrochemical cell, generating a voltage which can upset the reading.

### Soil and circuitry

If you take an ohmmeter and insert the probes into the soil quite close together the resistance reading you will obtain can vary from as little as 3 k to several megohms. The reading will depend on a number of factors: the distance between the probes, soil density, acidity/alkalinity of the soil, surface area of the probes and the moisture content of the soil. Dissimilar metals in the probe affect the reading as previously explained. If the physical dimensions of the probes are fixed in some way then the greatest variation in soil resistance will be due to the moisture content of the soil. Quite large variations in soil density will have less effect, surprisingly enough.

At first thought, it seems a common moving coil meter could be used in a simple ohmmeter-type circuit. However, with pointer-type displays, non-technical people using the device tend to worry about quite minor variations in the position of the pointer



With the probe in 'soggy' soil, only the top LED will light. In 'wet' soil, the top two LEDs will light — and so on until, with the probe in 'parched' soil, all LEDs will light!

— even if the scale is only calibrated in gross sections. (This gives rise to comments such as: "The needle is two millimetres further up the scale than when I took a reading this morning"). Secondly, the device should be inexpensive and rugged. Whilst we're not accusing gardeners of being clumsy, one must recognise that accidents do happen and few low cost moving coil

meters would survive a one metre drop onto a hard floor!

We opted for the 'all solid state' approach and chose to use an LED display arranged as a sort of bargraph. The resulting project is quite a rugged instrument that gives repeatable results, is easy to build and inexpensive. The unit is powered by four AA cells.

The probe problem was neatly solved ►




# Project 247

using a standard 6.5 mm jack plug. The circuit passes a constant current through the soil via the probe and the resulting voltage drop across the probe connections drives the LED display circuitry. This consists of a series of transistors that turn on in turn as the voltage across the probe connections rises with increasing soil resistance. If the soil is quite dry, all LEDs will light, if the soil is 'soggy' only one (LED5) will light. At this juncture, we should point out that the front panel lettering showing "soggy-wet-moist-dry-parched!" is a little tongue-in-cheek but it does give a general guide as to what the display indicates.
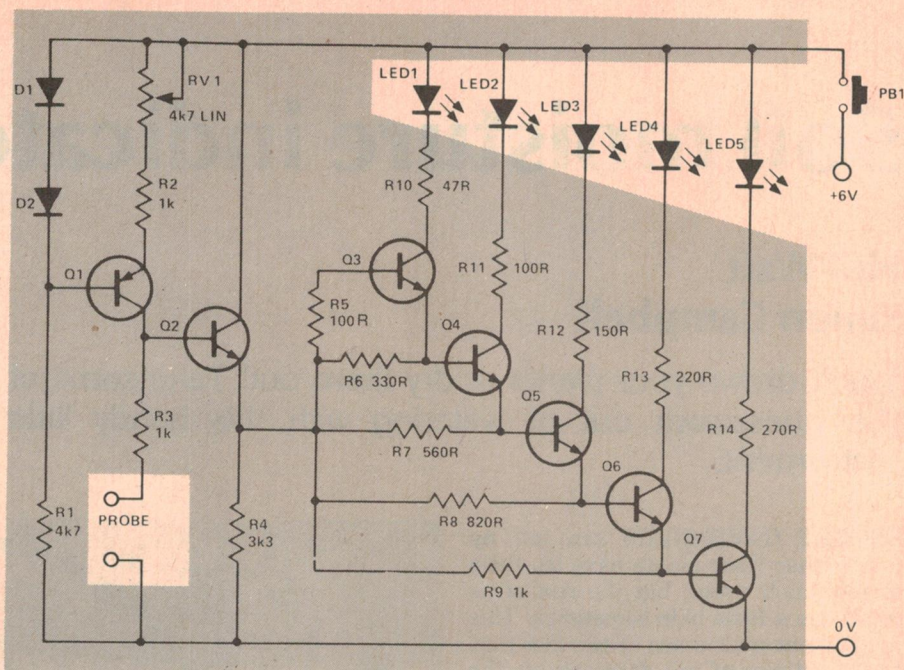
## Construction

Our unit was housed in a plastic zippy box measuring 150 mm long by 90 mm wide by 50 mm high. This is a convenient size and the completed unit is easily held in one hand while the probe is inserted into the soil with the other hand.



## HOW IT WORKS — ETI 247

The electrical resistance of soil varies primarily with the moisture content. The greater the moisture content, the lower the resistance. If a constant current is passed through two electrodes inserted in the soil, the voltage drop occurring across the electrodes will vary with the soil resistance, increasing with increasing resistance. This fact can be used to indicate moisture content of the soil in conjunction with a suitable display.

The circuit employs a constant current generator to pass current through the probe contacts via the soil. The voltage across the probe contacts is then buffered by an emitter follower which drives the display circuitry. This consists of five transistors, the collectors of each driving a LED, each transistor being connected to turn on successively as the voltage across the probe contacts increases with increasing soil resistance. A block diagram is shown in Figure 1 here.

Transistor Q1 and associated components provide the constant current source for the probe contacts. Figure 2 shows the collector characteristics of a typical silicon transistor. They show that, if you hold the base current constant, the collector current will remain substantially constant for a widely varying range of collector voltage. Figure 3 shows the general circuit of a constant current generator. The voltage between the base and the emitter return (common, the +ve supply line here) is fixed by the zener diode. Thus, the voltage across the emitter resistor ( $V_e$ ) is fixed at a value equal to the zener voltage ( $V_z$ ) minus the base-emitter voltage drop of the transistor.

(0.6 V for silicon transistors). With a fixed voltage across  $R_E$ , the current through it will be constant. Thus, the emitter current, and therefore the collector current, of the transistor will be constant. The resistor supplying current to the zener is generally chosen so that zener current is five to ten times greater than the base current of the transistor.

With this circuit, so long as there is about one volt between the emitter and collector, the collector current will remain constant at the chosen value until a load of too large a value robs the collector of its working voltage.

In the project circuit diagram, two forward-biased silicon diodes are used to 'clamp' the base voltage of Q1 to about 1.2 volts below the positive supply rail. Thus, the voltage across RV1/R2 will be about 0.6 V. The collector current can be adjusted by RV1 between a maximum of 600  $\mu$ A and about 100  $\mu$ A minimum.

The collector of Q1 drives the probe contacts via R3. The collector voltage of Q1, which varies with the variation in soil resistance across the probe contacts, drives the base of Q2, which is connected as an emitter follower. The emitter load of Q2 (R4) will thus have a voltage across it directly proportional to the collector voltage of Q1, less the 0.6 V base-emitter voltage drop of Q2.




The voltage across R4 then provides drive to the bases of the display transistors Q3 to Q7.

When the voltage across R4 reaches about 0.6 V, Q7 will turn on and LED5 will light. Now, the emitter of Q6 is connected to the base of Q7 and 'rides' up on the base-emitter voltage

of Q7. The voltage across R4 will have to reach 0.6 V above the base-emitter voltage of Q7, or 1.2 V, before Q6 will turn on, lighting LED4. Similarly, the emitters of Q5, Q4 and Q3 each ride up on the base voltage of the previous transistor and the LEDs will light in turn as the voltage across R4 exceeds successive 0.6 V increments. Thus, LED3 will light when the voltage across R4 reaches 1.8 V, LED2 will light when it reaches 2.4 V and LED1 will light when it reaches 3.0 V. The voltage across R4 will be maximum when there is a high resistance across the probe contacts and thus all LEDs will light when the soil in contact with the probe is dry. When the soil is quite wet, the voltage across the probe contacts will be low and the current set by RV1 should be just sufficient to permit LED1 to light.

Resistors R5 to R9 inclusive limit the base current of the display transistors while resistors R10 to R14 limit the current passed through the LEDs. Resistor R9 is a higher value than R5 so that excessive base current does not occur in Q7 as the voltage across R4 increases. Resistors R6 to R8 are successively higher in value than R5 for the same reason.

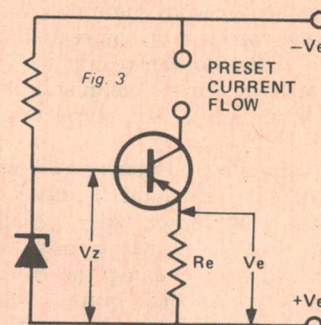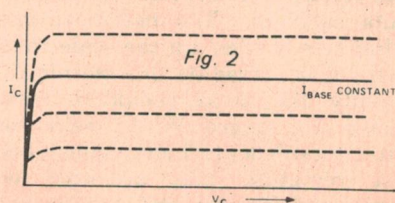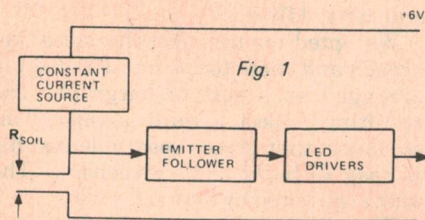The collector currents of transistors Q3 to Q7 will vary with the variation in base current as the voltage across R4 rises and falls. Thus, resistors R10 to R14 have values chosen to limit the maximum current through the LEDs to about 10 - 15 mA.





# soil moisture indicator

## PARTS LIST — ETI 247

### Resistors

	all 1/2W, 5%
R1	4k7
R2,R3,R9	1k
R4	3k3
R5,R11	100R
R6	330R
R7	560R
R8	820R
R10	47R
R12	150R
R13	220R
R14	270R

### Potentiometer


RV1	4k7 min. vert. mounting trimpot.
-----	-------------------------------------

### Semiconductors

D1,D2	1N4148 or sim.
Q1	BC557, BC 177 or sim.
Q2-Q7	BC547, BC107 or sim.
LED1-LED5	any LED, TIL220R or sim.

### Miscellaneous

PB1	momentary push button switch
ETI-247 pc board; four AA batteries with holder; mono phono plug for probe; Pentel pen type R56 for probe handle (or similar); plastic zippy box to suit.	

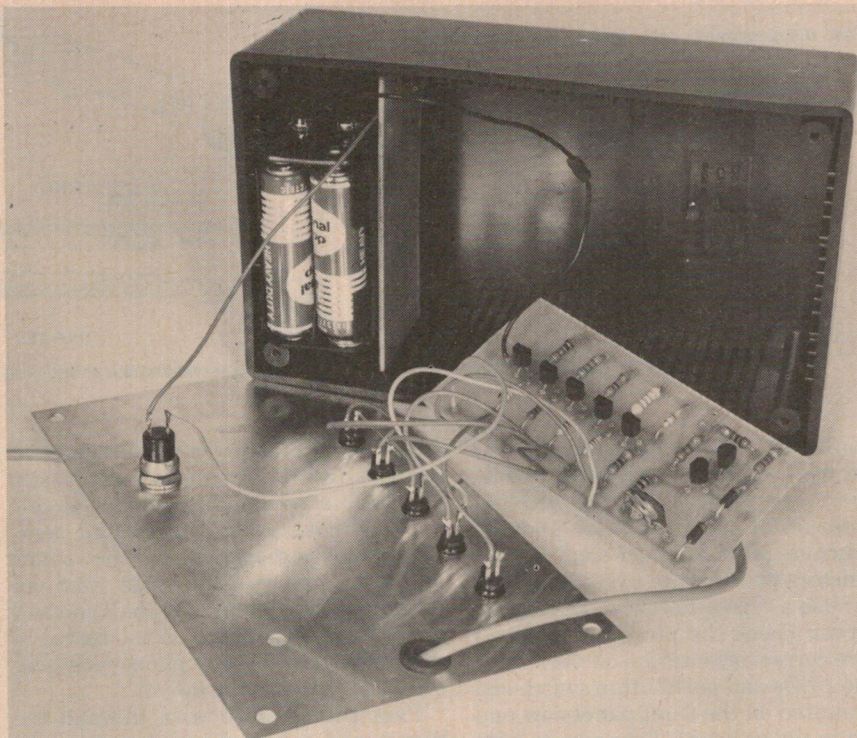

Internal view. Note how the battery holder is held in place.

The five LEDs and the pushbutton switch are mounted on the aluminium front panel and the probe lead is passed through the panel via a grommated hole. Another hole in the panel provides access to the SET trimpot so that the unit can be readily calibrated.


All the other components are mounted on a pc board which fits neatly across the box, held in place by the grooves on the walls which are readily seen in the internal photograph. Although this project could be constructed on matrix board or tag strips, we recommend you use the pc board as it helps prevent wiring errors.

The probe is constructed using a standard 6.5 mm phono jack plug which ensures a constant distance between the electrodes, a uniform contact area to the soil and electrodes of similar material. A ballpoint pen barrel serves as a handle. A piece of pc board with two strips of copper to act as electrodes could equally well be used, but it would be necessary to have the electrodes plated to prevent corrosion which would adversely affect the operation of the project.

It is best to commence construction by drilling the holes in the aluminium panel. We have reproduced the front panel artwork here and you can use that as a guide. There are eight holes altogether. The hole which provides access to the SET trimpot is 4 mm in diameter while all the rest are 6 mm in diameter.

We dressed up our project using a Scotchcal front panel. This gives the unit a permanent finish and a 'professional' appearance. If you are using a Scotchcal front panel then this should be attached to the aluminium panel before any components are mounted on it. Scotchcal panels for this project should be available from a number of suppliers — see Shoparound on page 83.

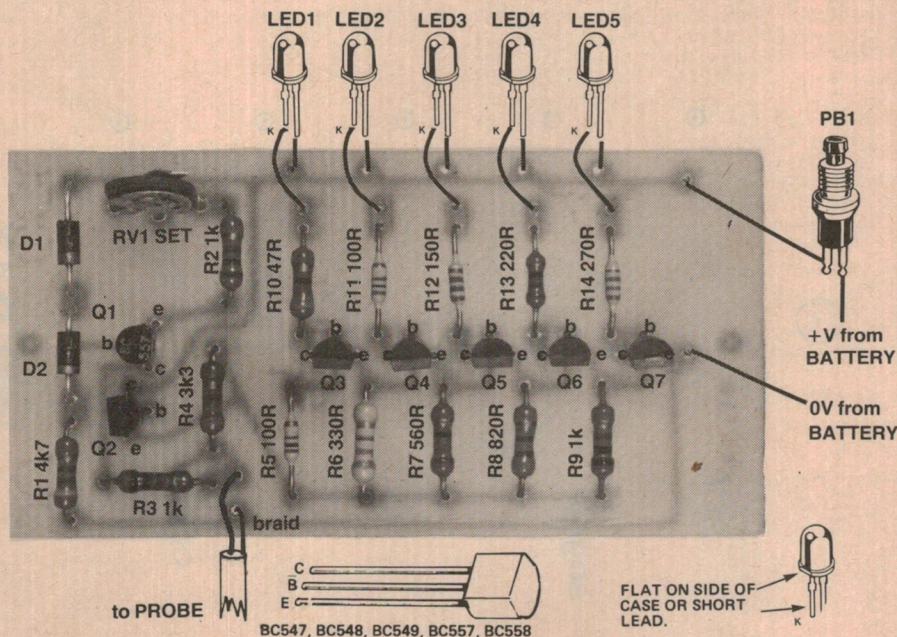
Component overlay for the pc board and external wiring.





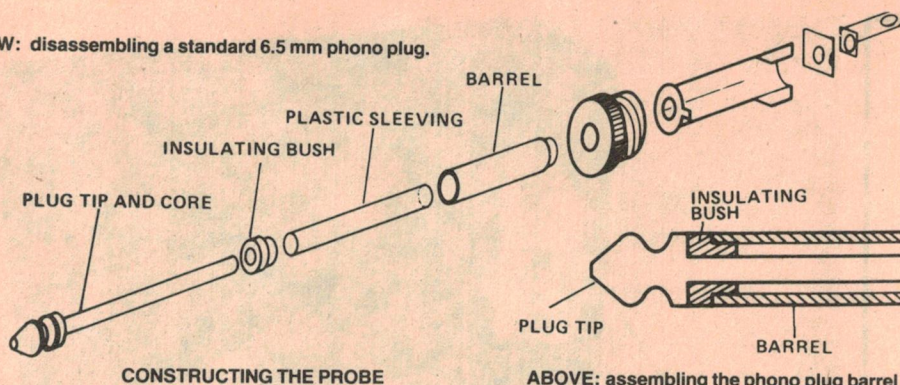
# Project 247

BELOW: disassembling a standard 6.5 mm phono plug.



CONSTRUCTING THE PROBE

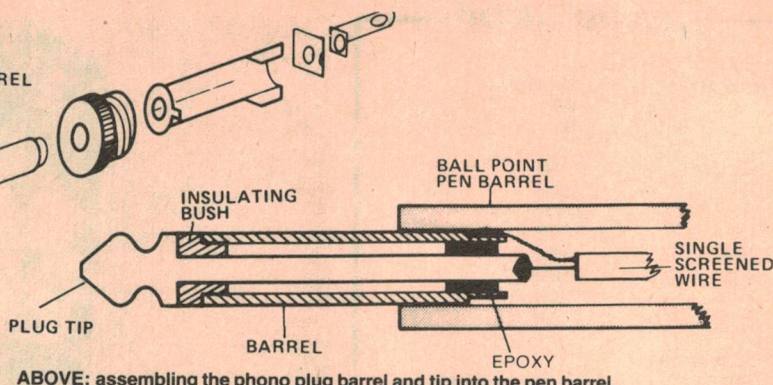

ABOVE: assembling the phono plug barrel and tip into the pen barrel.

Mount the components on the pc board next, using the component overlay here as a guide. Take care with the orientation of the transistors and the two diodes. Most common small signal transistors will work in this circuit, but if you use a type different to that specified then check the pin connections to ensure correct orientation on the board.

The LEDs and pushbutton switch can be mounted on the front panel now and wired to the pc board. Take care to wire the LEDs correctly. A grommet should be mounted in the hole through which the lead to the probe passes. The probe lead is passed through this hole and wired directly to the pc board. Next wire the leads to the battery holder, making sure you have the polarity correct, insert four AA cells and mount the battery holder in place. Note that the retaining piece securing the battery holder in the

zippy box should not be the full depth of the box to allow the battery leads to pass between its top edge and the front panel.

The probe can be constructed next. The exploded diagram here shows how it's done. We cut the ends from an exhausted type R56 Pentel ball pen and used the empty barrel as the barrel of our probe. The 6.5 mm phono jack plug is a neat fit inside the barrel.


Pass the shielded wire through the barrel and solder the end to the jack plug connections as shown in the diagram. Be careful to avoid short circuits between the braid and inner conductor of the cable. Don't use too much heat or the insulation on the inner conductor of the cable will melt back up inside the barrel and you may get intermittent short circuits.

At this stage you can do a dry run (pardon the pun... Ed.). Press the

pushbutton and most or all of the LEDs should light. If not, try adjusting the SET trimpot. If you still have no joy, check your wiring and the orientation of components on the pc board.
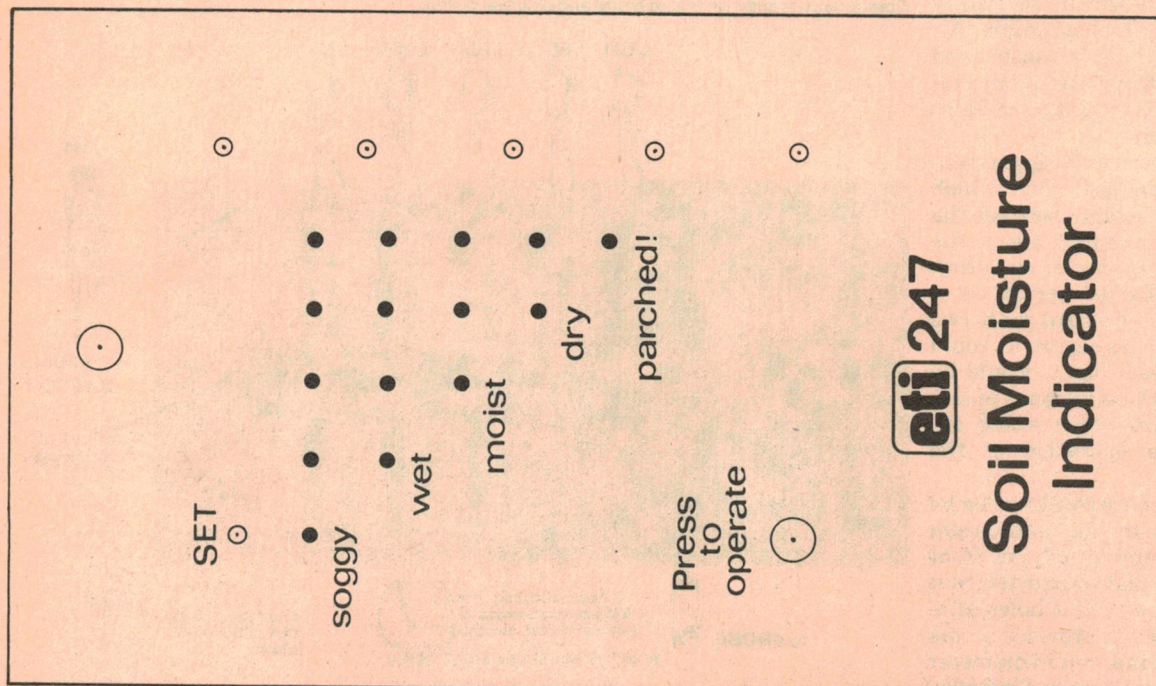
## Setting up

The unit needs to be set to give the correct indication. Set up a few pots with earth 'as you like it', ensuring one is thoroughly dry and one is thoroughly wet. Insert the probe in the wet soil and adjust the SET trimpot so that only the top LED (LED 5) lights. Then insert the probe in the dry soil and see that all the LEDs light. Try the probe in soil of varying wetness and you'll get a good idea of how to interpret the display. After all, correct interpretation of the indication is just as important as the operation of the unit. Once set, the unit should not require any further adjustment. ●



Full size reproduction of the front panel artwork. Scotchcal panels will be available from suppliers — see Shoparound on page 83.



# ROD IRVING ELECTRONICS

425 HIGH STREET, NORTHCOTE 3070, MELBOURNE VICTORIA.

## SCOTCHCAL

### FRONT PANELS FOR ETI AND EA PROJECTS


ETI 452 Guitar Practice Amp	\$4.80
Series 4000 Any colour	\$12.50
Moving Coil Pre Amp	\$2.00
577 Power Supply	\$2.00
455 Loudspeaker Protector	\$2.70
Variable Power Supply	\$2.70
Linear Ohmmeter	\$2.50
Muscle Activity Meter Scale	\$1.40
ETI 576 Electromyogram	\$2.80
561 Metal Detector	\$2.50
EA Capacitance Meter	\$3.50
EA Flash Exposure Meter	\$4.25
EA Sound Triggered Flash	\$3.50
EA Slave Flash	\$1.20
EA Playmaster Graphic Analyser	\$8.50
EA Metal Detector 79md9	\$3.90
EA Pulse Generator	\$4.80
EA Square Wave Oscillator	\$2.50
EA RF Z Bridge	\$3.25
EA Thyristor Tester	\$2.40
EA Quartz Frequency Reference	\$2.70
EA Multi Monitor	\$1.90
EA Experimentors Supply	\$2.80
EA Quiz Master	\$3.70
EA Variable Wiper Delay	\$1.10
EA Playmate Stereo Amplifier	\$4.50

All front panels available from day of release of magazines. When ordering front panels, specify colour of lettering first, then colour of background.

### 10 TURN POTS

1/4" SHAFT. VALUES: 100, 500, 1K, 2K, 5K, 10K, 20K, 50K, 1M.

Inc. tax \$8.50 ea.

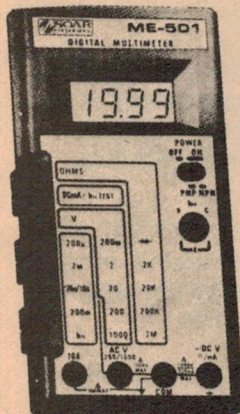

**Soar Model 501A**

**4 digit  
LARGE  
LCD  
DISPLAY**

Send for specs.

**\$77.00**

Add \$3 P&P and certified mail.

### INTERSIL LCD 3 1/2 DIGIT PANEL METER KITS

**INTERSIL ICL7106 \$32.50**

Build a working DPM in 1/2 hour with these complete evaluation kits.

Test these new parts for yourself with Intersil's low-cost prototyping kits, complete with A/D converter and LCD display (for the 7106) or LED display (for the 7107). Kits provide all materials including PC board, for a functioning panel meter. ICL7106EV (LCD)

## KITS & CIRCUIT BOARDS



(Kits of parts including quality fiberglass boards)

### ETI SERIES 4000 AMP

- Complete Kit, woodgrain sides \$179.00
- Rack Mounting ..... \$185.00
- Quality front panel to suit above...\$9.99
- ETI 470 kit of parts .....19.90
- ETI 480 kit of parts 100w (incl. bracket) .....19.75
- ETI 470 PS kit of parts .....19.50 (includes relay, not transformer)
- Transformer to suit .....22.90
- ETI 471 pre-amp .....45.50
- ETI 585R ultra sonic RX .....15.95
- ETI 585T ultra sonic TX .....8.95
- EA 79 SF9 sound flash trigger .....15.00
- All parts available for DREAM computer project.
- P.C.B.'S (all quality fiberglass boards)
- ETI 574 disco strobe .....2.80
- ETI 549A metal detector .....2.75
- DREAM circuit board .....10.90

### Project Boards (Fibreglass)

ETI 043	1.40	ETI 450B	1.90	EA 78N6	3.20
ETI 044	1.30	ETI 480	2.40	EA 78NG4	2.50
ETI 047	1.50	ETI 480PS	2.40	EA 78UT4	3.90
ETI 061	1.40	ETI 481M	2.00	EA 78T3	4.20
ETI 062	1.80	ETI 481PS	3.50	EA 78C5	3.90
ETI 063	1.70	ETI 483	2.20	ETI 470	\$2.90
ETI 064	1.70	ETI 484	3.90	ETI 741	\$9.90
ETI 065	1.70	ETI 485	2.90	ETI 472	\$2.90
ETI 067	1.80	ETI 486	2.90	ETI 576	\$4.90
ETI 068	1.40	ETI 489A	2.50	ETI 574	\$2.80
ETI 071	1.40	ETI 499	1.90	ETI 473	\$4.50
ETI 072	1.80	ETI 528	2.20	ETI 573	\$2.90
ETI 081	1.50	ETI 541	2.20	ETI 577	\$2.90
ETI 083	1.80	ETI 547	2.20	ETI 111B	\$2.30
ETI 084	1.70	ETI 581	2.20	ETI 150S2 60 ETI	
ETI 085	1.30	ETI 583	2.20	260	\$1.90
ETI 130	1.90	ETI 585R	1.60	ETI 261	\$1.90
ETI 134	1.90	ETI 585T	1.40	ETI 262	\$1.80
ETI 135	1.90	ETI 586	2.30	ETI 263	\$2.20
ETI 136	1.80	ETI 603	2.50	ETI 606	\$2.90
ETI 137A	2.90	ETI 604	1.60	79se3	\$3.90
ETI 137B	2.90	ETI 635	2.90	Dream 6800	10.90
ETI 139	1.90	ETI 638A	3.90	79sf10	\$1.90
ETI 245	1.60	ETI 708	1.90	79md9	\$2.60
ETI 417	1.80	ETI 713	3.90	79pg9	\$2.90
ETI 445	1.50	ETI 714	1.90	79ps11	\$2.90
ETI 446	1.90	ETI 717	2.90	79T11	\$2.75
ETI 449	1.50	EA 78A06	2.90	79PC12	\$2.20
ETI 450A	1.90	EA 78TM8	2.00	79EB12	\$2.90

### NEW PROJECT BOARDS

EA 801pg9	\$3.20
EA 80ch7	\$4.90
80 pp7A	\$4.80
80 pp7B	\$2.20
80 pc7	\$2.90
80 M07	\$3.90
80 B7	\$2.50
ETI 564	\$5.90
ETI 262	\$2.90
ETI 324	\$2.90
ETI 250	\$2.50
EA 80tr9	\$4.90
EA 80LL7	\$2.90
EA 80dm9	\$5.90
ETI 326	\$2.20
ETI 475	\$4.50

## NEW PRODUCTS



**HEX KEY PAD \$24.90**

**63-key Keyboard \$55.00**

### RIE are now distributors for 3M Products, including SCOTCHCAL RANGE

8016	Blue on White Plastic	\$4.10
8018	Green on White Plastic	\$4.10
8011	Red on White Plastic	\$4.60
8012	Black on transparent Plastic	\$4.10
8013	Black on Yellow Plastic	\$4.10
8015	Black on White Plastic	\$4.10
8009	Light blue on aluminium	\$4.10
8001	Red on aluminium	\$4.10
8005	Black on aluminium	\$4.60
8007	Reversing film	\$3.75
NOTE: ALL ABOVE SHEETS 10" x 12"		
8500	Photosensitive Developer	\$6.40
3900	Clear Coating (Glossy Finish)	\$9.30
3930	Clear Coating (Matte Finish)	\$9.30
ML-3	Applicator block	\$3.90
ML-4	Developer pads	\$8.90
8002KA	Evaluation Kit	\$55.00

### Attention Sorcerer and TRS 80 owners - MEMORY EXPANSION KITS AVAILABLE

We also offer full service on the popular computer projects and systems.

#### SPECIAL 4116 RAM OFFER

8 of prime spec 4116 IC's	\$64.00
16 of prime spec 4116 IC's	\$120.00
32 of prime spec 4116 IC's	\$220.00

#### STATIC RAM KIT 16K S-100

Kit form	\$249.00
Ass & tested	\$279.00



**Bankcard  
Mail Orders  
Welcome**

Please debit my Bankcard.

Bankcard No. ....

Expiry Date .....

Name .....

Signature .....

All prices current only until 7th November, 1980.

GENERAL ENQUIRIES (03) 489-8131, MAIL ORDER ENQUIRIES (03) 481-1436, RITRONICS WHOLESALE (03) 489-7099.

HEAVIER ITEMS ADD ADDITIONAL POSTAGE, EXTRA HEAVY ITEMS SENT COMET FREIGHT ON.

PRICES SUBJECT TO CHANGE WITHOUT NOTICE. SEND 60c & SAE FOR FREE CATALOGUES.

MAIL ORDERS: PO BOX 235, NORTHCOTE, VICTORIA 3070. MINIMUM PACK and POST \$1.00



# Thank You!

## CLIENTS, CUSTOMERS, AND FRIENDS FOR YOUR OVERWHELMING SUPPORT

IN ORDER TO MEET YOUR GROWING MICROCOMPUTER NEEDS WE HAVE DECIDED TO MOVE TO LARGER PREMISES. "PREVIOUSLY WE WERE OPPOSITE GUILDFORD RAILWAY STATION EXIT, NOW WE ARE EVEN MORE OPPOSITE!"

OUR NEW HOME HAS MORE DISPLAY SPACE COMBINED WITH LARGE OFFICES, WORKSHOPS, DRAWING OFFICES AND LABORATORY SPACE. COMBINING THIS WITH OUR FACTORY NEARBY, WE BELIEVE THAT WE CAN PROVIDE A LEVEL OF SERVICE, ENGINEERING AND MAINTENANCE UNSURPASSED IN SYDNEY.

WE INVITE YOU TO VISIT US FOR A DEMONSTRATION OF SSM MUSIC CARDS, DISCUS 2D FLOPPY DISK SYSTEMS, THE INCREDIBLE DISCUS M26 HARD DISK, HIGH RESOLUTION GRAPHICS DISPLAYS, THE AED "UN-SERIAL" TERMINAL AS WELL AS MANY OTHER SUPERB S100 PRODUCTS.

### STANDARD PRODUCT RANGE

#### S100 Cards by:

● MORROW ● SSM ● GODBOUT ● AED ● AND MANY OTHERS.

#### Software by:

● MICROSOFT ● MICROPRO ● DIGITAL RESEARCH — SEE LIFEBOAT ADS IN US MAGAZINES FOR RANGE!

#### Cabinets for:

● S100 SYSTEMS ● DISK DRIVES ● VIDEO MONITORS ● KEYBOARDS — Our keyboard cases in particular are the sturdiest and classiest in the industry.

#### Disk Systems:

● Floppy Disk systems with CP/M for S100 machines and Sorcerer.  
● 26MByte hard disk systems also with CP/M for \$5250 plus tax. More than twice the data for less money than the opposition!

#### Printers:

● A full range of Printers from Rolls Royce Word Processing types to economy hobby dot matrix units.

#### Prototyping and Developing Gear:

● A good range of Wire Wrap and Solder proto boards and IC sockets.  
● Ribbon cable and connectors.  
● The vector slit'n'wrap wire wrapping tool.  
● Extender cards with and without logic probes and bus termination.  
● EPROM programmers and erasers.

### SPECIALS THIS MONTH

● Due to the possible International crash in serial terminal sales due to the AED invoked 'UN-SERIAL' syndrome, we are forced to sell our last Intertube II serial terminal at cost: \$1190 plus sales tax.

● 2 only KSR33 teletypes: \$300 for older, \$350 for the newer. \$150 below the normal going rate!

● 1 only Motorola wide bandwidth white phosphor video monitor. 'Exceptionally Sharp'. 1 V p-p composite video input, good condition, mains supply built in, "ready to run", \$200.00.

● 3 only power supplies: 5V 6A; 12V 1.5A; -5V 0.5A; 12V 0.5A; -9V 0.5A all precision regulated. Input 110 or 240V AC. Ideal as bench Lab supplies or Motorola Buss supplies.

● Processor Technology HELIOS disk system with PTDOS. Ideal for "SOL" computer owner. This system is valued at above \$2700. Special price \$2000.

● 1 only T1 SILENT 700 TERMINAL — a steal at \$1150!



# MICROCOMPUTER PRODUCTS

130 Military Road, Guildford,  
NSW 2161. Phone (02) 632-6301,  
(02) 632-4966. Telex AA25958.



# Bill Edge's ELECTRONIC SPECIALTIES

New Telephone Number 745-3077, 2 lines. Y \$199.00

115-117 PARRAMATTA ROAD, CONCORD 2137.  
(Corner Parramatta Rd & Lloyd George Ave)

## MAIL CHARGES

\$5 - \$9.99	\$1.00
\$10 - \$24.99	\$2.00
\$25 - \$49.99	\$3.00
\$50 - \$99.99	\$4.00
\$100 or more	\$5.50

All heavy or bulky items (over 20 kg) sent "freight on" through carrier.  
Bankcard welcome - by mail, telephone, or over the counter.



## Electronics Australia Light Chaser Kit



(See EA August '80)  
ONLY \$65.00

Exactly the same case as used in the famous "Electronics Australia" Musicolor Full details in this issue.

Our kits feature a fully pre-drilled case and front panel with high quality knurled aluminium knobs and full instructions to make this very simple to construct kit.  
ONLY \$65.00  
Absolutely everything supplied in kit - all you need is some simple basic tools like screwdriver, soldering iron, etc.

## LED Tachometer



LED TACHOMETER KIT (ETI324)

See details in August '80 ETI. A fantastic little device that will suit all cars with 2 to 8 cylinders, and will inform driver if he is revving too high - hence a good check on petrol consumption. Complete kit available from us - including zippy box and all hardware . . . only \$29.95

## Digital Capacitance Meter Kit

Here is an inexpensive digital capacitance meter which measures from 1pF to 99.99 uF in just three ranges. It's simple to use and features a big bright four-digit display with automatic updating and decimal points. Display digits 13mm high. Case dimensions: 184(d) x 70(h) x 180(w) mm.


ONLY \$59.90

(Kit is complete right down to last nut and bolt).
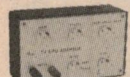
## T.V. CRO Adaptor Kit

(EA May '80) - fantastically popular - turn your old TV into a CRO.  
ONLY \$29.40 (without power adaptor)

Two power adaptors available:  
(i) 240V to 5V/5V d.c. . . . \$9.50  
(ii) 240V to 9V d.c. . . . \$5.95



## Four Input Guitar/Mic pre amp Kit

(to suit ET1466 Modules).  
A really versatile unit with bass, presence, treble and master volume controls. It also has its own power supply on board and can be powered directly from 15-0-15 Volts on power transformer.  
all components and PC board \$29.50

## 10 Watt rms/channel Amplifier only \$24.50



(less metalwork, knobs, power transformer) . . . A FANTASTIC BUY  
Limited stocks.

(See EA August '79 for review). This amp is suitable for crystal ceramic cartridge input. Can be driven from magnetic cartridge with simple addition of special preamp kit . . . \$9.50 . . . preamp can be powered direct from rail voltage of amp (diagram provided).  
Transformer (specially wound for this amp) . . . only \$9.50

## Fantastic ETI Series 4000 Amplifier Kit




Now available in SIX DIFFERENT VERSIONS:

- 1 With wooden sided case and standard power transformer . . . ONLY \$199.00
- 2 With rack mounting case and standard power transformer . . . \$209.00
- 3 With wooden sided case & 'C' core transformer . . . \$209.00
- 4 With rack mounting case and 'C' core transformer . . . \$219.00
- 5 With wooden sided case and toroidal transformer . . . \$231.00
- 6 With rack mounting case and toroidal transformer . . . \$241.00

No change is needed to amplifier circuitry to add the 'C' core or Toroidal Transformers. They are both rated at 28-0-28 volt/2 Amps on secondary and could be used in many applications where A.C. hum, or in the case of the toroidal, where size is also a problem. (Save up to \$70 on locally produced toroidal transformers.)

## Rack mounting ETI 4000 case

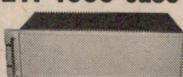

Beautifully designed (supplied in flat pack), satin anodised 1.6mm aluminium front and back panels, with surfaces suitable for screen printing etc. Top and bottom panels of hard wearing black "marvaplate" with 1.0mm steel base. Side panels 3.0mm satin anodised aluminium with chrome handles.

Four aluminium extrusions are used to hold the top, bottom, front and back panels in position.  
Size: 134mm(h) x 419mm(w) x 280mm(d) . . . \$55.00


## Slimline Amplifier Case



Same as used in description on ETI4000 Rack mounting case with overall dimensions: 89mm(h) x 413mm(w) x 280mm(d). - They come with wooden sides or for Rack mounting.

Wooden sided version . . . \$42.00  
Rack mounting version . . . \$49.90  
- beautifully constructed.

## Wooden-sided case

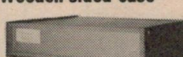

Exactly the same size and same materials as used in ETI4000 rack mounting case, except side panels are made of teak wood (13mm) for a really superb looking case.  
ONLY \$45.00

## 60W Low Distortion Amplifier Module Kit (ETI470)

Complete 60 watt amplifier module kit (as used in ETI4000 amplifier). Absolutely everything including heat sinks and all hardware. Features very low distortion and very simple mechanical construction. Can be used to replace existing amplifier modules and bring your present system up to scratch.  
es. \$29.90

## ETI 471 High Performance Stereo Pre Amp Control Kit

Designed to complement 60 watt ETI470 modules, but is such an exceptional design it can be used to update existing systems or incorporate in new designs, as it has features unheard of in other pre-amp designs, e.g., all connections through RCA sockets and controls going direct to PCB. Everything designed for high performance. Power requirements: +15, -15 Volts DC at less 5 Amp  
\$47.90

## ETI 472 Power Supply Kit

As used in 4000 Amplifier. From 240 V A.C. input gives out + and - 40 volt rails to supply power to amplifier modules. Also gives out + and - 15 volt rails for pre-amp supply. Kit comes complete with transformer.  
• with Standard Transformer . . . \$47.90  
• with "C" Core Transformer . . . \$57.80  
• with Toroidal Transformer . . . \$78.00

## Separate Components for 4000 Amplifier

All components are available separately for the ETI4000 Amplifier.  
• ETI470 PCB . . . \$3.50  
• ETI471 PCB . . . \$9.50  
• ETI472 PCB . . . \$4.50  
• BDV548 . . . \$3.56  
• BDV558 . . . \$3.56  
• Washers and bushes for BDV548/558 (Set of 4) . . . \$1.45  
• Front Panel (drilled) . . . \$15.00

## Transformers

Beautifully engineered toroidal transformer 240V primary to two 28 volt secondary windings at 2 amps.  
This will give a DC rail voltage of 40 volts plus and minus after your power supply - the exact voltage used on innumerable pieces of audio equipment.  
Excellent when used in slimline amplifier cases as is the trend now.  
Not to mention the excellent low hum figures encountered with these types of windings - that's why all \$1000-\$5000 amps are using them.

Grab one before they all go at only \$59.50 - as comparable ones are over \$130 ea.  
(size: 40(h) x 100(d)mm approx.)  
"C" TRANSFORMER . . . \$26.50

## 300 WATTS!

## Playmaster 300W Amplifier Module Kit

(EA June '80)  
The full technical know-how of the "Electronics Australia" staff has been put into designing this superb project.  
The 300 Watt Amplifier Module Kit includes heatsink, thermal cut-out, nuts, bolts, silicon grease, mica, solder - all you need is a soldering iron, screwdriver, a pair of cutters, drill - and Stanley knife - and it's a good idea to have a trusty multitester. (see them from \$9.50)  
MODULE KIT . . . \$75.00

## Power Supply to suit 300W Playmaster

INCLUDES TRANSFORMER & all necessary components to make up power supply kit complete. . . \$52.95

## Power Transformers to suit Playmaster 300 Watt Amplifier

Sprite Fan (4") 240V a.c.  
Recommended by EA for this project. . . ONLY \$29.50

## Chassis & Hardware Pack 300WATT P/M (EA July 80) (Less Case & Fan)

If you have made the amp module, the speaker protector and wish to put them all into a case with the power supply, then you'll need this pack to finish everything off. It includes LED, binding posts, switch, extra resistors and capacitors, wire, front label, nuts, bolts and spacers.  
ONLY \$9.95

Case The ideal case for this amp is the rack-mounting ETI4000 Case for \$55.00 or wooden sided ETI4000 Case for \$45.00 (shown elsewhere in this ad.)


MATT BLACK SPRAY . . . 125gm can . . . \$2.50

## P/M 300W Loudspeaker Protector Kit

(EA July 80)  
For an amplifier of such enormous power output this "loudspeaker protector" is mandatory if you don't want your loudspeakers destroyed and it only costs . . . \$12.95 (includes PC board and all components)
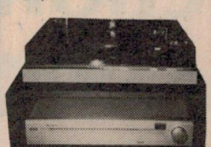
## Sick of making audio kits?

Well - here's your answer - buy a complete 2 speed, S/N Ratio 75db, adjustable speed change turntable already constructed or superb direct drive turntable - both manufactured by one of the most respected hi fi makers in the industry - HITACHI.



## HT-40S Direct Drive Turntable

Engineering at its best.  
Speeds: 2 speed, S/N Ratio 75db, adjustable speed change with inbuilt strobe, - speed deviation .003%.  
Frequency response (with Dual MT-35 Cartridge - INCLUDED) . . . 10-25,000Hz.  
ONLY \$189.00

## FT-3400 AM/FM Stereo Tuner

FM SECTION 88-108MHz, sensitivity - 1.0uV (75d). Frequency response 30 to 15,000Hz, stereo separation 45dB, 3000Hz to 7500Hz.  
AM SECTION 530-1605 kHz, 15uV sensitivity, signal to noise ratio 53dB.  
ONLY \$179.00

## ETI 455 Speaker Protector

Because of the modern trend to use dc coupling in the output stages of modern amps the speaker becomes very prone to accepting a high dc voltage.  
The answer of course is to build a "speaker protector" and one of the best is our ETI455 kit (March '80 ETI) for only \$26.00.  
Included in short form (less case) to enable you to put it into your existing amp.

## Brighten up your stereo speakers

Add a pair of Philips ADO162/TB Tweeters (with crossover capacitors included).  
ONLY \$30.30 PAIR  
- You'll be amazed at the high frequencies you never knew were there.

## Audio Crossover Chokes

Top quality, air-cored, high powered, low DC resistance crossover chokes. Following many requests from our customers we now have these chokes so that you can design your own cross-overs.  
0.5 millihenries . . . \$7.00  
1.0 millihenries . . . \$7.00  
2.5 millihenries . . . \$7.50

## ETI 438 LED Level Meter

Features eight LEDs which tell you exactly what power you are emitting and whether you are clipping (exceeding power ratings of amp). A very simple kit to construct and requires 20-32 V d.c. or 15-20V a.c. to drive.  
Please state Amplifier Power Output when ordering, for matching Resistor.  
ONLY \$11.95

## What else do we carry?

All electronic hardware (boxes, veroboard, PC board, etc.), tools, wire, cable, semiconductors, valves, Hi Fi, Kits, PA Equipment, Microphones, Speakers, Car Radios, Car Tape Players, Car Audio Accessories, intercoms, books, transformers, Resistors, Capacitors, heatinks, coils, TV aerials and accessories, CB accessories and meters.

## Power Amplifier FETS USED IN HIGH POWERED STEREO AMPS

- 25K134 and 25J49 (new on the market).  
. . . \$17.90 per complementary pair . . . or \$8.95 ea.

## Famous TE-15 Grid Dip Meter

It's been around for a long time but still very popular.  
Operates as a grid dip, oscillator, absorption wave-meter and oscillating detector.  
SPECs: - Frequency range: 440kHz - 280MHz in 6 coils.  
STILL ONLY \$89.00

## 125 mm (5") Horn Speakers

ON SPECIAL - ONLY \$7.95 ea.  
SAVE \$1.55



## 3 foot Helical CB aerials

- TOP QUALITY (less base & lead)  
ONLY \$14.50 ea.

A LARGE VARIETY OF DICK SMITH PRODUCTS AT DICK SMITH PRICES AND ON A SUNDAY TOO!

## Transistor Assisted Ignition

(from design in EA Dec. '79)  
Complete kit, right down to last nut and bolt - exactly as made by EA, even using genuine diecast box.  
"Electronic ignition is in but CDI systems are out" - quote from EA. Has dwell extension and results in a hotter spark at high engine speeds and is directly compatible with electronic tachometers. STILL ONLY \$32.50 - (compare our price with others).

## Complete Coral 300mm (12") 4 speaker, 3 way kit

(including woodwork)  
ONLY \$218.00 !!!  
Philips 12" (300mm) 3 way 80W kit . . . \$320r  
Playmaster 12" (300mm) 3 way Kit . . . \$298r  
Mail Order: \$1.00 packing "freight on"



## Coral 250 mm (10") 3 way 3 speaker kit

(50 watts, 8 ohm). Consists of two 10" (250mm) woofers, two 5" (125mm) mid-range and two 2 1/2" (62.5mm) tweeters, with two 3-way crossover networks and all screws, terminals and internal wiring.  
ONLY \$95.00 pair  
Box size requirements: 56cm(h) x 33cm(w) x 27cm(d)

## Coral 200mm (8") 3 way 3 speaker kit

(35 watts, 8ohm). Consists of two 8" (200mm) woofers, two 4" (100mm) mid-range and two 2 1/2" (62.5mm) tweeters with two 3-way crossover networks and all screws, terminals and internal wiring.

## ETI 4000/2 Speaker Kit

Includes all speakers as used in ETI4000/1 system with the exception of the 178mm (7") lower midrange speakers. The crossover network is also different as it is a three way system (in kit form).  
Mail Order: \$1.00 packing.  
"freight on" carrier . . . \$360 pair

## Famous System 80 Computer



ONLY \$750  
With every System 80 sold we are offering FREE SOFTWARE UP TO \$20, and our variety of System 80/TRS80 software is one of the best in Sydney - come in or write for free software listing.  
N.B. VIDEO MONITOR Extra . . . \$149.50

## TRS 80/System 80 Software



MATCH CARDS & BANKSHOT - Two programs on one cassette.  
MATCH CARDS is a concentration type game where you match numbers, letters or graphic shapes. For one or two players. Automatic scoring rates your recall ability.  
BANKSHOT is a billiard-like game for those who think they know all angles. Hit the ball into the pocket, but you must hit a wall first.  
(Cassette) . . . \$11.95

POKER PETE - Play 5 card draw poker. Watch Peter shuffle and deal cards. He will challenge you with bluffs, raises, calls and folds. And Pete has a gun. 3 levels.  
(Cassette) . . . \$12.95

FASTGAMMON(TM) As described in Sorcerer Software, but made for TRS80 or System 80.  
Cassette . . . \$21.95

Disks . . . \$26.95

RUMMY MASTER - Play Rummy against the computer. Exceptional graphics display your hand, the discards and cards that have been melded by you.  
(Cassette) . . . \$12.95

LOWBALL POKER - How low can you go. It's you against Micro Molly and the lowest hand wins. Don't take her for granted - Molly plays an excellent game.  
(Cassette) . . . \$12.95

## ETI 4000/1 Speaker Kit


Includes 2 only AD1225V/8 300mm (12") woofers 2 only AD70501/8 178mm (7") lower midrange, 2 only AD02160/SQB 50mm (2") midrange, 2 only AD161078 25mm (1") dome tweeters, 2 only 4-way crossover networks (designed by ETI and in kit form) plus full instructions on assembly. (box kit separate).  
Mail Order: \$1.00 packing.  
"freight on" carrier . . . \$459 pair

## Complete 4000/1 Speaker System

(including speakers, crossovers and boxes - everything you need to complete this fantastic pair of speakers).  
Mail Order: \$1.00 packing.  
"freight on" carrier . . . ONLY \$699 pair
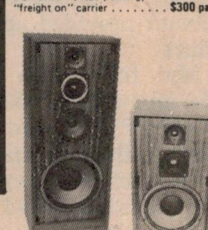
## ETI 4000/1 Speaker Boxes

Includes two professionally assembled speaker boxes exactly as described by ETI for this project - all that is required for you to do is screw speakers and crossovers in (kit form) and in mount in-board end. Walnut finish. Dimensions: 100cm(h) x 39cm(w) x 35cm(d).  
Mail Order: \$1.00 packing.  
"freight on" carrier . . . \$300 pair



## Complete 4000/2 Speaker System

(including speakers, crossovers and boxes - everything you need to complete this fantastic pair of speakers).  
ONLY \$560 pair



# Radio direction finding with the Realistic DX-160

David Jeanes VK2BSJ

WHEN THE Realistic DX-160 came on the market some years ago, the receiver included the Low Frequency band of 150 to 400 kHz. In this band are found marine and aeronautical radio beacons, which transmit omnidirectional signals suitable for direction finding (D/F).

To enable the DX-160 to provide D/F information, a simple modification to the Band A aerial coil is necessary, plus the construction of a loop antenna.

## The loop antenna

By experiment, it was found that four turns of wire wound around the edge of a piece of light plywood, 300 mm square, appeared to match well into the antenna coil of the receiver's Band A. The directional qualities of this loop were excellent. Distinct nulls in signal strength were obtained from several aero beacons in the Sydney-Newcastle area. Signal pickup was more than adequate. Williamtown aero beacon, some 120 km away, was received at good strength. Having resolved the question of the number of turns for the loop, it remained to construct a practical, rugged loop antenna.

Rigid PVC electrical conduit was chosen for the loop housing, as it is inexpensive, easy to work and glue, and several types of elbows and sockets are available.


A one metre length of 6 mm bore PVC conduit, plus four 90° elbows and one T-piece with inspection panel were purchased. A small tin of PVC conduit solvent provided adequate glue for all joints.

My final loop dimensions were 350 mm wide by 220 mm height overall. Cut the PVC conduit with a hacksaw, to provide the side and top sections. Two lower sections are needed to allow the T-piece to be centred at the bottom of the frame.




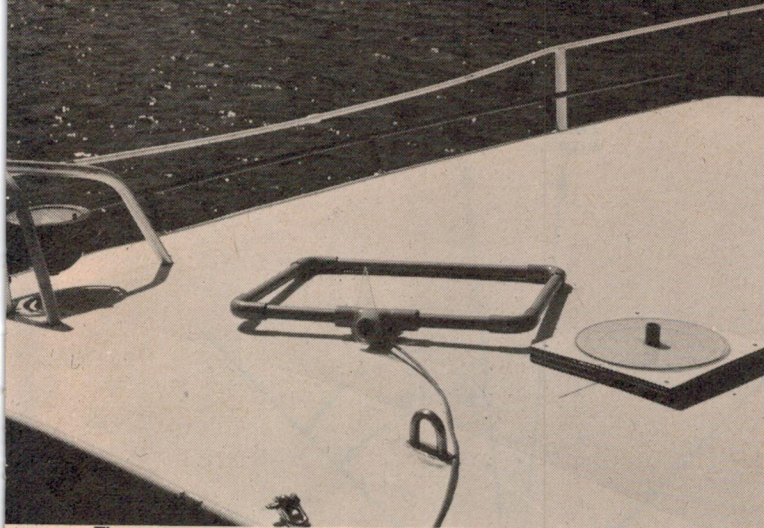David Jeanes' boat, the "Nikki". The DX-160 and D/F loop are installed on board.






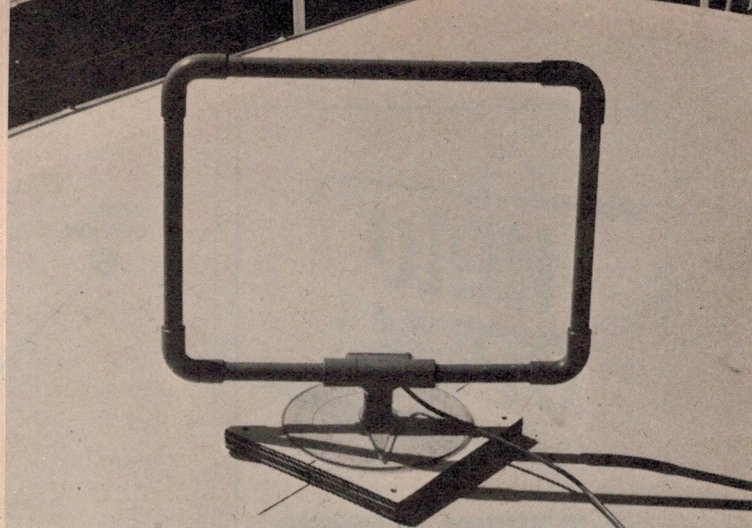
The completed loop assembly has a perspex pointer attached so that the direction may be read off a compass rose on the loop mount.



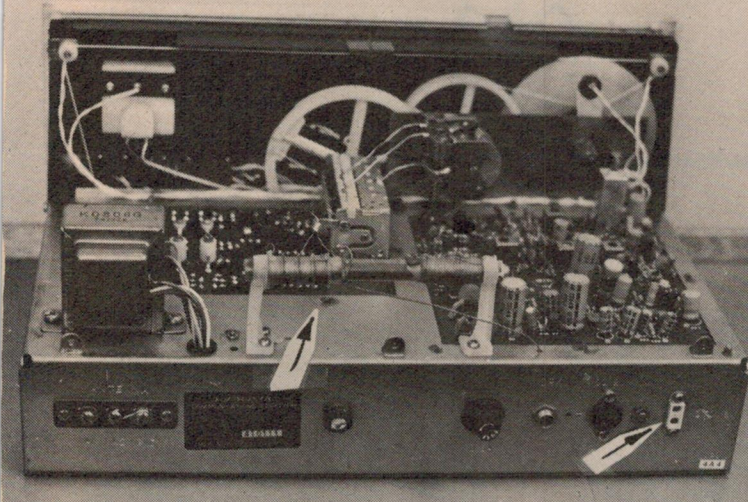The completed loop assembly mounted as described. The compass rose on the base is carefully aligned fore and aft.



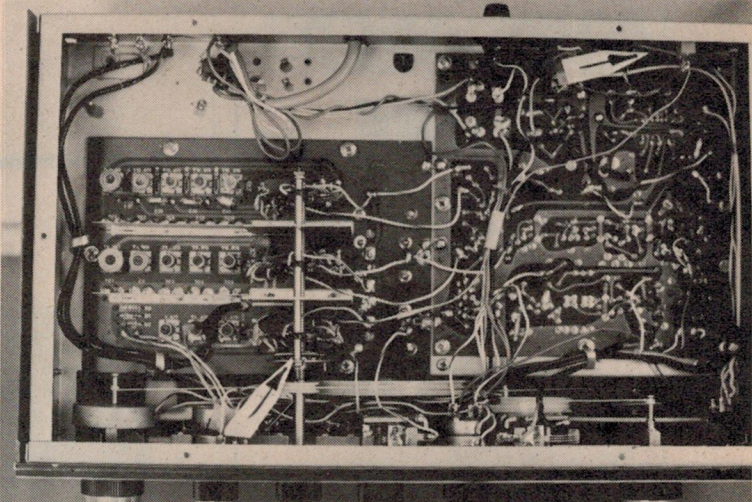The upper arrow shows the four-section Band A loopstick coil. The arrow at lower right shows the STANDBY socket — now used for the loop input.



Underside view of the receiver. Arrow at lower left indicates which wafer section on the bandswitch is re-wired; at right, the STANDBY socket.

Assemble the conduit sections and elbows to check for symmetry. For the loop conductor, I used a length of four-conductor telephone cable. String the cable through the various elements of the loop frame, leaving a few centimetres spare to emerge through the inspection panel of the T-piece.

Using the PVC solvent as directed on the can, cement the sections to the elbows and T-piece, laying the frame on a flat surface to maintain a true shape. When the solvent has cured, trim off the ends of the phone cable, exposing 20-30 mm of the multi-core conductors. The wire colours are black, green, white and red. Solder the green of one cable to the black of the other cable end. Continue with white to green, and red to white. When these three joints are soldered and tape insulated, the black and red ends remaining become the connections of a four turn loop.

Twin conductor shielded audio cable is satisfactory for the feeder between loop and receiver. This cable is soldered to the loop black and red wires. No earth for the shield is required at the loop end.

To provide bearing information, a

perspex pointer is glued to the bottom section of the loop frame T-piece, orientated  $90^\circ$  to the plane of the loop. A base plate for the loop to rotate on was made from a  $360^\circ$  compass rose — cut from an old marine chart. The rose was covered with perspex then glued to a square piece of waterproof plywood. The base plate can be mounted along the fore and aft axis of the vehicle (boat, car etc.) with the  $000$  degree of the rose pointing exactly forward.

If a small section of the 6 mm conduit is glued into the exact centre of the base plate, the loop frame can sit on this axle and be rotated by hand to find a null in the signal strength. When not in use the loop can be slipped off the base and stowed away safely.

## Receiver modification

When the receiver covers are removed, it will be evident that a loopstick antenna system is used for Band A to provide some directional quality. That loopstick coil wound in four segments is T1 and is connected between earth and tag 'A' of the bandswitch wafer.

With the receiver upside down, dial

facing you, the correct wafer section is that nearest the front and the lug in question is at one o'clock.

The STANDBY socket on the rear panel provides an ideal entry for the loop feed line, and a plug is provided. Follow the Standby wiring to the pc board and permanently solder a link across the terminations.

Remove the wire on lug A of the band-switch and wire it to one of the Standby socket terminals. Locate the earth end of T1 primary and wire it to the other terminal of the Standby socket. T1 primary is now isolated from earth and will provide a balanced load for the loop.

All other bands are unaffected by the modification and operate from the regular antenna terminals. The loop feedline braid may be earthed adjacent to the Standby socket.

It is assumed that for D/F operation, the receiver is being operated on 12 Vdc. Mains operation may reduce the effectiveness of loop signals. The Standby switch on the front panel is now redundant and may be wired to switch on the dial lights during 12 V operation.



# NOW OPEN

## DAVID EAST COMPONENT CENTRE

33A Regent Street, Kogarah NSW  
(Opposite Kogarah High School)  
Phone 588-5172

### RESISTORS

1/4W — 5c. 1 W — 8c. PW5's — 45c.

### TRANSISTORS

BC 107, 108, 557, 558 — 33c. BC 559 — 30c. BC 547, 548 — 25c. BC 549 — 27c. BC 109 — 36c. BD 139, 140 — 95c. BC 639, 640 — 75c. 2N3055 (Motorola type) — \$1.30.

### SEMICONDUCTORS

4001, 4011 — 40c. 4016 — \$1. 4017 — \$1.75. 7400, 7402 — 45c. 7490 — \$1. 74C00, C02 — 50c.

### DIODES

IN914 — 5c. IN4004 — 8c. IN4007 — 18c.

### REGULATORS

7805, 12, 15 — \$1.25. 7905, 12, 15 — \$1.75.

### SCR's

C103B (200V, 800 mA) — \$1.16. C106DI (400V, 4A) — \$1.08. C106YI (30V, 4A) — 70c. C122E (500V, 8A) — \$2.56.

### TRIACS

SC141D — \$1.28

### DIACS

ST2 — 38c.

### BRIDGE RECTIFIERS

All 400V, 1.5 amp to 30 amp.

### POTS


Single gang log and linear: 500R-1M — 75c. Trim-pots — 39c. Cermet, Vert & Horiz — 42c.

### LED's


5 mm Clear and Diffused Sankin Type. Red — 22c. Green and Amber — 31c.

Also a large range of capacitors,  
Electros, Greencaps, Tag Tantalums.

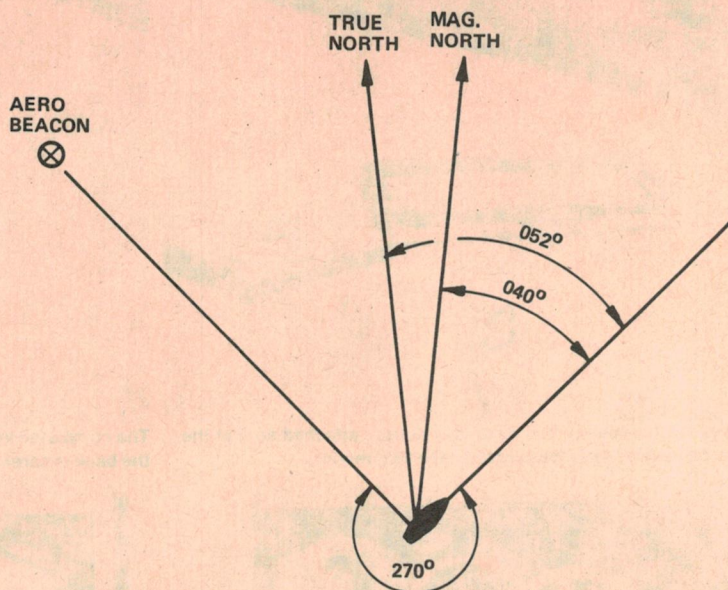**All first quality components  
at prices you CAN afford.**




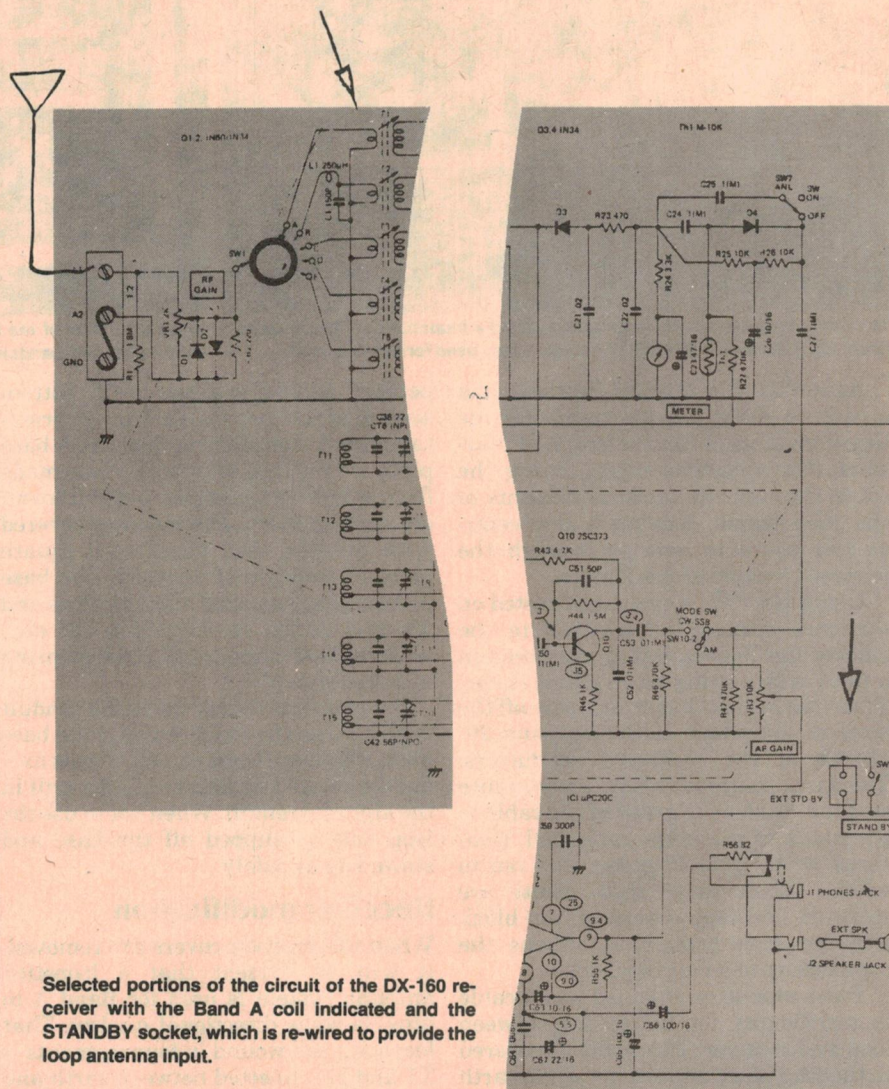How to find the true bearing of the vessel using the radio direction finder.



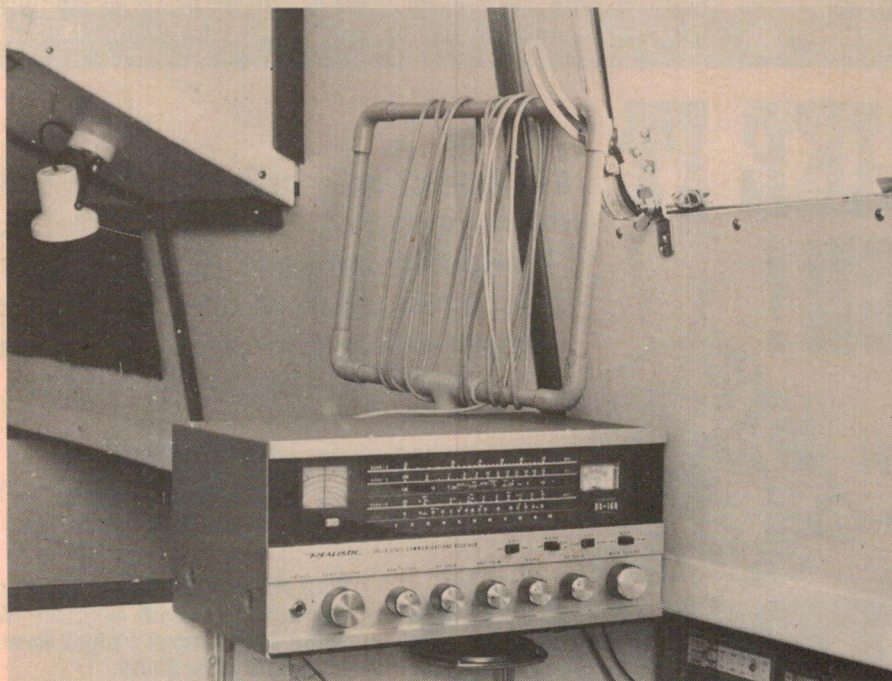Selected portions of the circuit of the DX-160 receiver with the Band A coil indicated and the STANDBY socket, which is re-wired to provide the loop antenna input.





The DX-160 general coverage and D/F receiver is mounted in a convenient place in the cabin of the Nikki. When not in use, the D/F loop antenna is stowed above the receiver.

## D/F operation

As the receiver rear cover is masonite, on-air testing will indicate whether it is necessary to shield the interior from outside signals. If so, aluminium foil may be wrapped around the rear cover, ensuring the foil is earthed.

Aeronautical radio beacons are virtually the only transmissions evident on Band A. A very few marine beacons are spotted around the Australian coast. A list of aero beacons, their frequency, callsign and position in latitude and longitude may be obtained from the Airways Operations Branch, Department of Transport.

With the regular antenna disconnected and the loop mounted on its baseplate, switch to these functions:- band switch to band A

- ANL off
- Mode to CW-SSB
- AVC to FAST
- RF gain advanced about  $\frac{3}{4}$  way
- BFO to 12 o'clock
- Audio gain as desired


Tune in an aero beacon and note the morse identification. Adjust the tuning for a beat note of comfortable pitch. Adjust antenna trim for minimum S-meter reading. Rotate the loop for a signal null and note the bearing indicated by the pointer against the compass rose. Swing the loop  $180^\circ$  and note the bearing of the second null. In almost all situations the general direction of the transmitting station is known, so that the correct null and bearing is easily ascertained.

To plot the bearing on a chart or map, the heading of the vehicle must be known. On my vessel, the magnetic compass is adjacent to the loop. The loop is swung for a null and simultaneously the compass heading is noted. In the example shown, assume the compass course, corrected for deviation, is  $040^\circ$  magnetic and the relative loop bearing of the aero beacon is  $270^\circ$ . A magnetic

course of  $040^\circ$  off the NSW coast where magnetic variation is  $12^\circ$  east, would mean that the vessel was in fact heading  $052^\circ$  True. Add the true heading,  $052^\circ$  to the relative radio bearing of  $270^\circ$  and we obtain the true direction of the aero beacon of  $322^\circ$ . To plot the bearing from the aero beacon to the ship, subtract  $180^\circ$  from  $322^\circ$ , giving  $142^\circ$ . Draw a line from the aero beacon in the direction of  $142^\circ$  and the ship will be somewhere along this bearing line.

A second bearing, taken shortly after the time of the first bearing, from a second aero beacon, would provide a bearing line which would cut across the first. The intersection of these two lines gives the ship's position. The accuracy of the position depends primarily on the correctness of the vehicle's heading at the time of the bearings. Other errors peculiar to direction finding by radio are outside the scope of this article. Briefly listed, they are:- quadrantal error caused by metallic objects in the vicinity of the loop; coastal refraction applicable to ships at sea and 'night effect' where distant signals on the same frequency or skywave signals from the selected beacon cause the loop null to fluctuate away from the true direction.

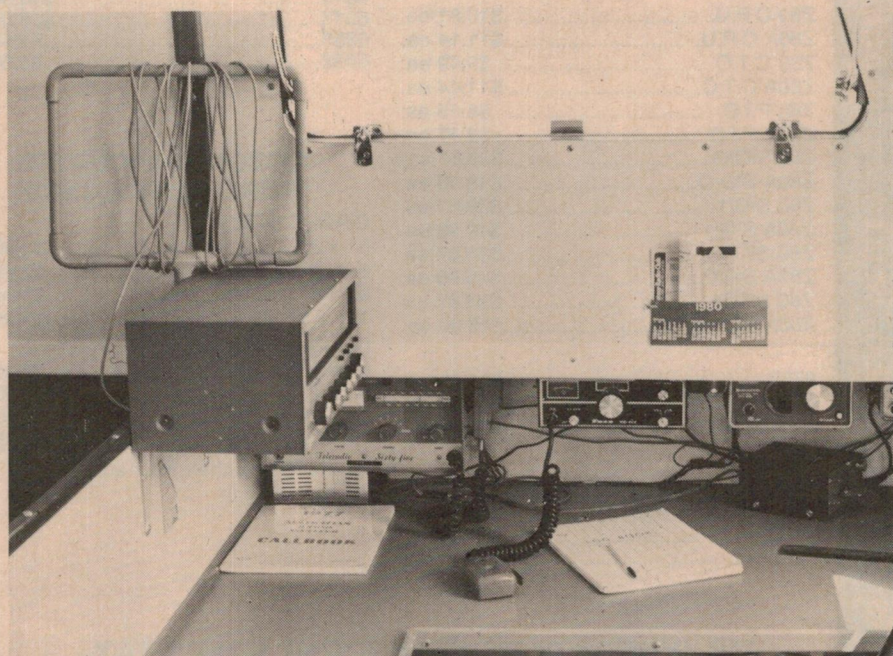Broadcast stations are not satisfactory for direction finding purposes because the band is crowded with signals, identification of the station is difficult and its exact position is often unknown. Ground wave propagation is reduced at the higher broadcast frequencies and skywave propagation enhanced at night. ●



The 'electronics' aboard the Nikki includes a Teleradio 65 marine transceiver, a Swan 40m monoband rig, 146 MHz FM rig, a depth sounder and assorted other items.





Ellistronics now stock in excess of 2000 different types of semiconductors plus computer components and systems. Altogether we have over 8000 various electronic components. The largest range available in Melbourne



**YES! WE ACCEPT BANKCARD.** All prices valid month of issue. Heavy items sent Comet freight forward. Minimum post \$3.00.

**289 LATROBE ST. MELBOURNE. 3000**  
**PHONE (03) 602-3282, 602-3836. TELEX AA37758 LSTRON.**

**OUR LOWEST PRICES EVER**  
**RUSH FOR THESE FULL SPEC. PRIME I.C.'S**  
**WHILE STOCKS LAST**

2716. 450ns Single 5v Supply ..	\$11.95 ea.
2716. 200ns Single 5v Supply ..	\$19.50 ea.
2114. 450ns .....	\$2.95 ea.
2114. 300ns .....	\$3.90 ea.
2708. 450ns .....	\$6.40 ea.

Z80 C.P.U. ....	\$10.81 ea.
Z80A C.P.U. ....	\$11.14 ea.
Z80 C.T.C. ....	\$9.49 ea.
Z80A C.T.C. ....	\$11.44 ea.
Z80 P.I.O. ....	\$6.65 ea.
Z80A P.I.O. ....	\$8.57 ea.
Z80 SIO/O .....	\$38.67 ea.
Z80A SIO/O .....	\$49.90 ea.
Z80 SIO/1 .....	\$38.67 ea.
Z80A SIO/1 .....	\$49.90 ea.
Z80 SIO/2 .....	\$38.67 ea.
Z80A SIO/2 .....	\$49.90 ea.
Z80 SIO/9 .....	\$38.67 ea.
Z80A SIO/9 .....	\$49.90 ea.

2732 .....	\$66.00 ea.
MB 8414 (2114 CMOS 250ns) ..	\$21.00 ea.
65 x 08 1k x 1 CMOS .....	\$9.00 ea.

**FLOPPY DISC CONTROLLERS**

FD 1771 .....	\$37.00 ea.
FD 1791 .....	\$62.00 ea.
FD 1793 .....	\$62.00 ea.

**ALL PRICES PLUS 15 PERCENT SALES TAX**  
**APPLICABLE**

**8 BIT MPU'S**

6802 .....	\$11.80 ea.
6808 .....	\$10.50 ea.
6809 .....	\$46.77 ea.
6821 .....	\$5.10 ea.
6840 .....	\$7.84 ea.
6845 .....	\$38.94 ea.
6847 .....	\$28.00 ea.
6850 .....	\$4.40 ea.
6852 .....	\$5.50 ea.

**RISTON 3000 COATED**  
**FIBREGLASS BOARD**

**SINGLE SIDED**


6" x 3" .....	\$1.60 ea.
6" x 6" .....	\$2.30 ea.
9" x 6" .....	\$3.35 ea.
12" x 12" .....	\$7.95 ea.

**DOUBLE SIDED**

6" x 3" .....	\$2.30 ea.
6" x 6" .....	\$3.30 ea.
9" x 6" .....	\$4.10 ea.
12" x 12" .....	\$9.45 ea.

Full range of chemicals available.

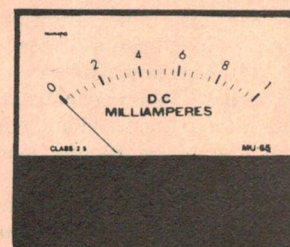
**DIRECT IMPORT PANEL**  
**METERS**  
**AT LOW, LOW PRICES**



**MU-65** 1MA — 120 ohms  
100uA — 1400 ohms


Dimensions: Overall — 100mm(W) x 82mm(H)  
Scale — 100mm(W) x 50mm(H)  
Mounting: Hole required — 63mm  
Bolts centres — 80mm(W) x 64mm(H)  
Nuts and washers provided

**\$10.18 ea. plus \$1.52 tax**

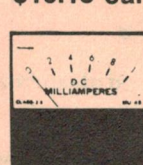

**MU-45**  
O-1MA-120 ohms  
O-50UA-1400 ohms  
O-5ADC-3 Shunt  
O-30VDC-100 ohms

**\$6.91 ea. plus \$1.04 tax**

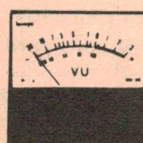

**MU-45 VU METER**  
VU (0dB equals 1mW into 600ohms)  
— 1,000ohm

**\$7.93 ea. plus \$1.11 tax**

**MU-45 DIMENSIONS**

Overall — 58mm(W) x 52mm(H)  
Scale — 58mm(W) x 31mm(H)  
Hole required — 44mm  
Bolt centres — 38mm(W) x 38mm(H)  
Nuts and washers provided  
10 or more less 10 percent





### AUSTRALIAN MADE WELLER SP25D MARKSMAN

Mains voltage constant heat 25 watt with 5/32 tip (lightweight 185 grams). Made in Australia Weller gives you better value in soldering irons than most imported irons. Fully guaranteed.

**\$9.75 ea.**  
TAX EXEMPT

**SPECIAL FOR THIS MONTH AT ONLY \$54.95 ea.**

### WELLER WTCPN SERIES TAX EXEMPT LOW VOLTAGE, TEMPERATURE CONTROLLED SOLDERING STATION

A transformer powered soldering station, complete with a low voltage, temperature controlled soldering pencil. The special Weller "closed loop" method of controlling maximum tip temperature is employed, thereby protecting temperature sensitive components while the grounded tip protects voltage and current sensitive components. The soldering pencil features a stainless steel heater construction, a non-burning silicon rubber cord and a large selection of iron plated tips in sizes from .8 mm diameter to 6 mm diameter with a choice of tip temperature of 600°F/315°C, 700°F/370°C and 800°F/430°C.

A redesigned transformer case features an impact-resistant noryl for durability and protection against accidental damage, a quick connect/disconnect plug for the soldering iron, extra large wiping sponge, tip tray to store extra tips, plus an improved off-on switch with a long-life neon indicator light, a non-heat sinking soldering pencil holder and a 2 m flexible 3-wire power cord. The soldering iron is normally provided with a PTA7-1.6 mm screwdriver 700°F/370°C tip.

#### SPECIFICATIONS


**Power Unit** • Power input 240 Volts 50 Hz 60 Watts Int. • Transformer Output Voltage — 24 Volts (Full Load)  
• Power Unit Size — 113mm x 187.3mm x 92mm • 2 Metres, 3 Wire Power Cord.  
**Soldering Pencil** • Soldering Pencil Wattage — 48 Watts • Tip Voltage \*To Ground .01 Volts P-P • Pencil Weight — 50 gram (W/O Cord) • Recovery Time (From 100°F Drop) W/PTA7 Tip = 11 Sec.



**S2010** PVC weatherproof re-entrant horn/speaker. Very attractive "off white" colour. 8 ohm 5 Watt RMS. Ideal P.A. use. Individually boxed.

**SPECIAL PRICE \$5.95 ea.**  
exempt  
**\$6.84 inc. tax**

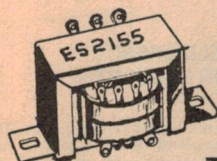Ellistronics are direct distributors for Weller, Hitachi and Trio. For quantity discounts etc. ask for Trade Division.



### TOP QUALITY LOW COST TRANSFORMERS

#### R-2150

Primary: 240V AC.  
Secondary Voltage: 12.6 volts CT.  
Secondary Current: 150mA.  
Termination: Flying leads.

**\$3.80 ea. 10 up \$3.34 ea.**

#### R-2155

Primary: 240V AC.  
Tapped Secondary Voltages: 6.3, 7.5, 8.5, 9.5, 12.6, 15.

Secondary Current: 1 amp.  
Termination: Solder lugs on transformer.

**\$5.75 ea. 10 up \$5.06 ea.**

#### R-6672

Primary: 240V AC.  
Tapped Secondary Voltages: 15, 17.5, 20, 24, 27.5, 30.

Secondary Current: 1 amp.  
Termination: Solder lugs.

**\$7.48 ea. 10 up \$6.44 ea.**

**S2000 8"** (200mm) wide range general purpose. Includes transformer, mounting holes for P.A. and background use. Very smooth over-all response 45 Hz-12 KHz. Fitted to a 1.9 cubic ft vented enclosure they sound unbelievable.  
**8 Ohm 8 Watt RMS 5.6 oz magnet.**  
**\$6.00 TRADE, \$6.95 Inc. tax**



### EXTRA SPECIAL

2N 3055 TRANSISTORS  
FULL SPEC. MOTOROLA  
55c ea. plus 15c tax  
MJ 2955 TRANSISTORS  
65c ea. plus 18c tax

### TEXAS INSTRUMENTS CALCULATORS



Ti 25 .....	\$19.04
Ti 30 SP .....	\$22.85
Ti 50 .....	\$38.09
Ti 55 .....	\$54.09
Ti 58C .....	\$141.50
Ti 59 .....	\$295.00
PC-100C .....	\$215.00
(Printer/Plotter for Ti 58C and Ti 59)	

Speak and Spell .....	\$77.78
Dataman .....	\$24.26
Little Professor .....	\$17.62
AC9131 AC Adaptor/Charger for Ti 58C/59 .....	\$7.06

All calculators plus 15 percent sales tax if applicable.  
Full range of Texas calculators and accessories in stock.

**If we are not No.1 now, we soon will be.**



# Radio & Electronics Books

## BERNARD BABANI (publishing) LTD

### 160: COIL DESIGN & CONSTRUCTION MANUAL B.B. Babani

- Complete book on how to design and make RF, IF, audio and power coils, chokes and transformers. Every type is discussed and calculations given. Covers AM and FM radio and TV.

96 pages

Price \$2.75

### 202: HANDBOOK OF ICs EQUIVALENTS AND SUBSTITUTES. B.B. Babani

- One of the most complete IC equivalent and substitute guides yet published. Full data on over 9500 ICs. Covers digital and linears of all types from UK, USA, Japan, Germany, France, Czechoslovakia etc.

128 pages

Price \$3.70

### 221: 28 TESTED TRANSISTOR PROJECTS R. Torrens

- Some circuits are completely new — others are more familiar designs. The projects can be split into simple building blocks to enable readers to combine circuits for specialised needs.

96 pages

Price \$4.60

### 224: 50 CMOS IC PROJECTS R.A. Penfold

- CMOS ICs are suitable for an extraordinarily wide range of applications, are cheap and easy to obtain. Here are a number of interesting and useful projects in four general categories: (1) Multivibrators, (2) Amplifiers and oscillators, (3) Trigger devices, (4) Special devices.

112 pages

Price \$3.50

### 225: PRACTICAL INTRO TO DIGITAL ICs D.W. Easterling

- This book introduces the reader to digital ICs (mainly TTL 7400 series). Besides a number of simple projects, contents include details of a Logic Test Set which enables constructors to identify and test digital ICs. Also includes digital counter-timer.

80 pages

Price \$4.60

### 227: BEGINNERS GUIDE TO BUILDING ELECTRONIC PROJECTS R.A. Penfold

- Enables total beginners to tackle practical electronic so he or she can confidently build electronics projects such as published in ETI and other magazines and books. Subjects include component identification, tools, soldering, various building methods, cases, legends etc. Practical basic projects are also included.

112 pages

Price \$4.60

### BP1: 1ST BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES B.B. Babani

- Complete transistor equivalents guide. More than 25 000 transistors with alternatives and equivalents. Covers devices made in UK, USA, Japan, Germany, France, Europe, Hong Kong etc. See also BP 14 (below).

80 pages

Price \$2.25

### BP 14: 2ND BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES B.B. Babani

- The second book contains data on devices not included in the first. This book supplements BP1, no data is duplicated.

208 pages

Price \$4.05

### BP 24: 52 PROJECTS USING IC 741 Rudi & Uwe Redmer

- Originally published in German, this book achieved huge European sales. Now translated into English with copious notes, data and circuits, this book is a must for those interested in any way in this inexpensive and most versatile IC.

80 pages

Price \$3.50

### BP 33: ELECTRONIC CALCULATOR USERS HANDBOOK M.H. Babani

- An invaluable book for all calculator users. Presents formulae, data, methods of calculation, conversion factors etc, often with examples. Includes way to use simple four-function calculator for Trig functions (sin, cos, tan); Hyperbolic functions (sinh, cosh, tanh); Logs, Square Roots & Powers.

Comprehensive conversion factors incorporated, including length, area, volume & weight through specialised conversions such as viscosity, illumination, cargo shipping measures etc. Also formulae for discounts and mark-up, currency conversions, interest, solutions of equations, binary and octal numbers, areas and volumes, stats and maths etc.

208 pages

Price \$3.50

### BP 36: 50 CIRCUITS USING GERMANIUM, SILICON, ZENER DIODES R.N. Soar

- Contains 50 interesting and useful circuits and applications in many different branches of electronics.

64 pages

Price \$2.75

### BP 37: 50 PROJECTS USING RELAYS, SCRs & TRIACS F.G. Rayer

- Relays, SCRs and Triacs have a wide range of applications — from motor speed control, dimming, heating, timers, light-sensitive circuits, warning devices, light modulators, priority indicators, circuit breakers etc. Book gives tried and proven circuits which will tolerate wide latitude of components and values allowing easy modification to suit special needs.

112 Pages

Price \$4.60

### BP 39: 50 (FET) FIELD EFFECT TRANSISTOR PROJECTS F.G. Rayer

- Field effect transistors are used in many circuits. The projects here include amplifiers and converters, test equipment and receiver aids, tuners, receivers, mixers and tone controls, plus miscellaneous devices. The FET used is not critical and many other types will work as well. This book will be of interest to all enthusiasts, shortwave listener, radio amateur, hi-fi buff or general electronics experimenter.

112 pages







Price \$4.60

### BP 40: DIGITAL ICs AND PIN CONNECTIONS Adrian Michaels

- Equivalents and pin connections of a popular user-orientated selection of digital ICs. Shows details of packaging, families, functions, manufacturer and country of origin. Includes devices by Fairchild, Ferranti, Harris, ITT, Motorola, National, Philips, RCA, Signetics, Sescocem, SGS-Ates, Siemens, SSSI, Stewart Warner, AEG-Telefunken, Texas, Teledyne. Companion volume to BP 41 — Linear ICs.

320 pages

Price \$9.00

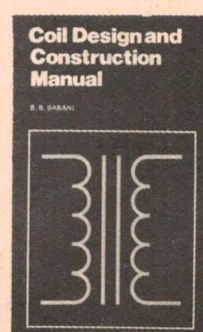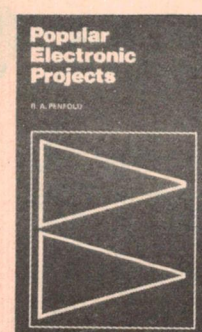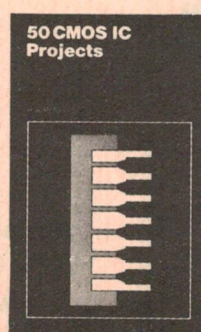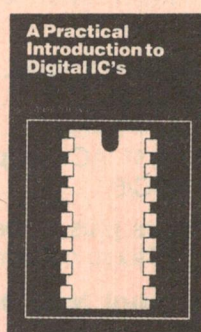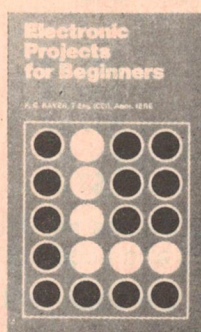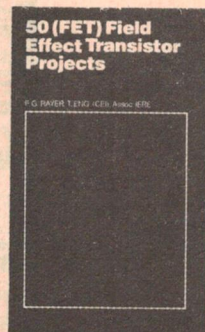



**BP 41: LINEAR IC EQUIVALENTS  
AND PIN CONNECTIONS**  
Adrian Michaels

• Essentially similar in concept to above but deals with linear integrated circuits.  
**320 pages** **Price \$10.00**

**BP 42: 50 SIMPLE LED CIRCUITS**  
R.N.Soar

• 50 interesting and useful circuits and applications using LEDs. A useful book for beginner and advanced enthusiast alike.  
**64 pages** **Price \$3.50**

**BP 44: IC 555 PROJECTS**  
E.A.Parr

• Every so often a device is made that is so useful one wonders how life went on before it! The 555 IC is one such. First made by Signetics it is now manufactured by almost everyone in the business. It is very cheap and readily obtainable.  
Included in this book are basic and general circuits, motor car and model railway circuits, alarms and noise makers plus a section on the subsequent 556, 558 and 559 devices.  
**160 pages** **Price \$6.45**

**BP 45: PROJECTS IN  
OPTO-ELECTRONICS**  
R.A.Penfold

• Opto-electronic projects of interest to all electronics enthusiasts. Included are simple circuits using ordinary LEDs as well as more sophisticated designs such as infra-red transmitters and receivers, modulated light transmission and photographic projects.  
**112 pages** **Price \$4.95**

**BP 47: MOBILE DISCO HANDBOOK**  
Colin Carson

• Most people who start mobile discos know little about equipment or what to buy. This book assumes no preliminary knowledge and gives enough info to enable you to have a reasonable understanding of disco gear.  
**128 pages** **Price \$4.95**

**BP 48: ELECTRONIC PROJECTS FOR  
BEGINNERS**  
F.G.Rayer

• This book gives the newcomer to electronics a wide range of easily built projects. Actual component and wiring layouts aid the beginner. Some of the projects may be built without using soldering techniques.  
**128 pages** **Price \$4.95**

**BP 49: POPULAR ELECTRONIC  
PROJECTS**  
R.A.Penfold

• A collection of the most popular types of circuits and projects covering radio, audio, household and test equipment.  
**144 pages** **Price \$5.35**

**BP 51: ELECTRONIC MUSIC AND  
CREATIVE TAPE RECORDING**  
M.K.Berry

• This book shows how electronic music can be made at home with simple and inexpensive equipment. It describes how sounds are created and recorded to build up a final composition. It shows how to build a small studio including mixer and various sound effects units.  
**96 pages** **Price \$4.60**

**BP 53: PRACTICAL ELECTRONIC  
CALCULATIONS AND FORMULAE**  
F.A.Wilson

• This book is for the practical person's workshop bench. It bridges the gap between technical theory and cut-and-ried methods which may work but leave the experimenter unfulfilled. There's a strong practical bias. Tedious and higher maths has been avoided where possible. Many tables are included. This one's a beauty!  
**256 pages** **Price \$8.25**

**BP 56: ELECTRONIC SECURITY  
DEVICES**  
R.A.Penfold

• Simple and more sophisticated burglar alarms using light, infra-red and ultrasonics; also other types of alarm such as gas and smoke detectors, flood alarms, doorphone and baby alarms etc.  
**112 pages** **Price \$5.35**

**ELEMENTS OF ELECTRONICS**  
F.A.Wilaon

**BP 62 — Book 1**

**BP 63 — Book 2**

**BP 64 — Book 3**

• This series provides an inexpensive intro to modern electronics. Although written for readers with no more than basic arithmetic skills, the use of maths is not avoided — all the maths is taught as the reader progresses.  
The course concentrates on the understanding of concepts central to electronics rather than continually digressing over the whole field — on the basis that once the fundamentals are mastered, the workings of most other things are soon revealed. The author anticipates where the difficulties lie and guides the reader through them.

Book 1 . . . All the fundamental theory necessary to a full understanding of simple electronic circuits and main components.

Book 2 . . . Alternating current theory.

Book 3 . . . Semiconductor technology leading to transistors and ICs.

These three books constitute a complete, inexpensive electronics theory course of inestimable value in either hobby or career.

**224 pages** **Price \$8.25 (each volume)**

**BP 65: SINGLE IC PROJECTS**  
R.A.Penfold

• All projects in this book are simple to build and are based on a single IC. A few projects use one or two transistors in addition. A strip board layout is provided for each project together with special constructional points and setting up info. The five chapters are: Low level audio, Audio power amps, Timers, Op-amps, Miscellaneous circuits.  
**128 pages** **Price \$5.50**

**BP 66: BEGINNERS GUIDE TO  
MICROPROCESSORS AND  
COMPUTING**  
E.F.Scott

• An introduction to basic theory and concepts of binary arithmetic, microprocessor operation and machine language programming. The only prior knowledge assumed is very basic arithmetic and an understanding of indices.  
**128 pages** **Price \$6.45**

## BABANI BOOKS — MAIL ORDER, DIRECT FROM ETI !

Please send me:

Book	Qty.	
160	...	BP41
202	...	BP42
221	...	BP44
224	...	BP45
225	...	BP47
227	...	BP48
BP1	...	BP49
BP14	...	BP51
BP24	...	BP53
BP33	...	BP56
BP36	...	BP62
BP37	...	BP63
BP39	...	BP64
BP40	...	BP65
		BP66

Post & handling:

1 - 4 books:	\$1.35
5 - 10 books:	\$2.70
11 - 20 books:	\$3.50
over 20 books:	\$5.00

I enclose \$ . . . . . (inc. p & h.)

Name . . . . .

Address . . . . .

. . . . . postcode . . . . .

Send to: ETI 'Book Sales', 3rd Floor,  
15 Boundary St, Rushcutters Bay NSW 2011.  
Please allow 4 - 5 weeks for delivery.

WE REGRET WE CANNOT SUPPLY NEW ZEALAND READERS




# ROD IRVING ELECTRONICS

425 HIGH STREET, NORTHCOTE 3070, MELBOURNE, VICTORIA.

## \$100 COMPUTER PRODUCTS

### 16K EPROM CARD-S 100 BUSS

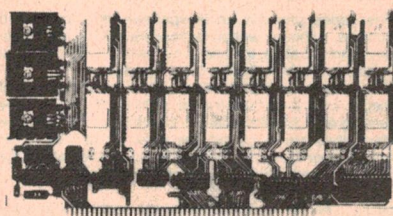

**\$89.50  
KIT**

**FIRST TIME OFFERED!  
BLANK PC BOARD - \$39**


**USES 2708's!**

Thousands of personal and business systems around the world use this board with complete satisfaction. Puts 16K of software on line at **ALL TIMES!** Kit features a top quality soldermasked and silk-screened PC board and first run parts and sockets. Any number of EPROM locations may be disabled to avoid any memory conflicts. Fully buffered and has WAIT STATE capabilities.

**OUR 450 NS 2708'S  
ARE \$8.95 EA. WITH  
PURCHASE OF KIT**

**ASSEMBLED  
AND FULLY TESTED  
ADD \$36**

### 8K LOW POWER RAM KIT-S 100 BUSS SALE

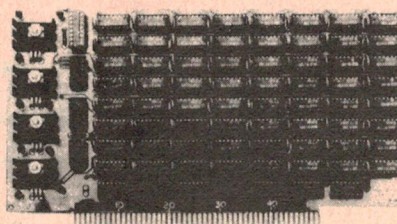

**PRICE  
CUT!**

**\$159.50**

**21L02  
(450 NS RAMS!)**

Thousands of computer systems rely on this rugged, work horse, RAM board. Designed for error-free, NO HASSLE, systems use.

Blank PC Board w/Documentation

**\$44**

Low Profile Socket Set... **13.50**

Support IC's (TTL & Regulators)

**\$13**

Bypass CAP's (Disc & Tantalums)


**\$7**

**ASSEMBLED AND FULLY  
BURNED IN ADD \$45**

**ALL ASSEMBLED BOARDS  
ARE TESTED AT 4MHZ.**

### 16K STATIC RAM KIT-S 100 BUSS

**KIT \$249  
A&T \$279**

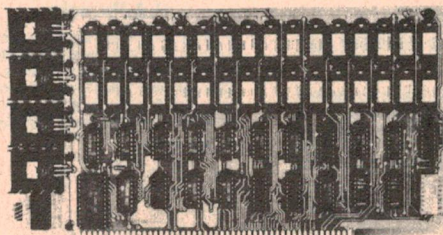

#### KIT FEATURES:

1. Addressable as four separate 4K Blocks.
2. ON BOARD BANK SELECT circuitry. (Cromemco Standard!). Allows up to 512K on line!
3. Uses 2114 (450NS) 4K Static Rams.
4. ON BOARD SELECTABLE WAIT STATES.
5. Double sided PC Board, with solder mask and silk screened layout. Gold plated contact fingers
6. All address and data lines fully buffered.
7. Kit includes ALL parts and sockets.
8. PHANTOM is jumpered to PIN 67.
9. LOW POWER: under 1.5 amps TYPICAL from the +8 Volt Buss.
10. Blank PC Board can be populated as any multiple of 4K.

**BLANK PC BOARD W/DATA \$49**

**LOW PROFILE SOCKET SET \$19**

**SUPPORT IC'S & CAPS \$27**

**ASSEMBLED & TESTED-ADD \$30**


**OUR #1 SELLING  
RAM BOARD!**

### 16K STATIC RAM SS-50 BUSS

**PRICE CUT!**

**\$279**

**FULLY STATIC  
AT DYNAMIC  
PRICES**

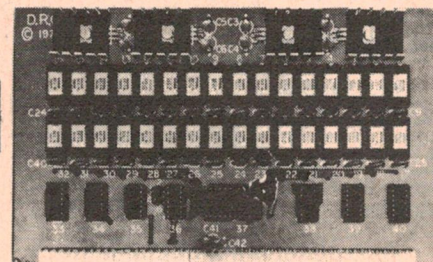

**FOR SWTPC  
6800 BUSS!**

**ASSEMBLED AND  
TESTED - \$30**

#### KIT FEATURES:

1. Addressable on 16K Boundaries
2. Uses 2114 Static Ram
3. Runs at Full Speed
4. Double sided PC Board. Solder mask and silk screened layout. Gold fingers
5. All Parts and Sockets included
6. Low Power: Under 1.5 Amps Typical

**BLANK PC BOARD— \$39    COMPLETE SOCKET SET— \$19  
SUPPORT IC'S AND CAPS— \$45**

### ITOH Model 8300 PRINTER. \$770 plus 15% sales tax.

This 80-column printer provides quiet operation, making it suitable for use in offices, classrooms and homes. Specifications include 125 cps, 60 lines per minute, paper loading from bottom or rear and Centronics-compatible, parallel interface.

A bidirectional, dot matrix impact printer with a print head designed for 100 percent duty operation, assuring a print life that exceeds 100 million characters. The precision sprocket-feed mechanism permits printing forms from 4 1/2 to 9 1/2 inches wide. A 96 ASCII character set prints in upper and lowercase with the added capability of producing double-width fonts in boldface. The vertical format unit provides preprogrammed/ programmable tab positions, top of form and bottom of form for complete formatting capabilities.

**RITRON 8 SLOT MOTHERBOARD: KIT \$65.90 inc. tax.  
BUILT & TESTED \$80.00 inc. tax.**

**RITRON COMPUTER GRADE POWER SUPPLY: +5V Reg, 10A,  
+16V Unreg. Kit of parts \$79.95 inc. tax. A&T \$99.95 inc. tax.**

Write for list of other power supplies. Tax free prices also available.

### JUST WRAP KIT - JWK-6 \$39.50


● 50ft ea. blue, white, red, yellow wire ● Just Wrap Tool ● Unwrap Tool

### S-100 Z80 CPU CARD

**Perfect for  
OEM's**

**\$199.00  
Wired &  
Tested**

**4 MHZ**

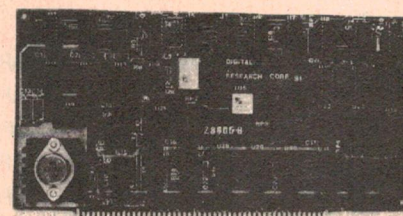

**ASSEMBLED AND TESTED! READY TO USE!** Over 3 years of design efforts were required to produce a **TRUE S-100 Z80 CPU** at a genuinely bargain price!


**BRAND NEW!**

#### FEATURES:

- ★ 2 or 4 MHZ Operation
- ★ Generates MWRITE, so no front panel required.
- ★ Jump on reset capability
- ★ 8080 Signals emulated for S-100 compatibility
- ★ Top Quality PCB. Silk Screened. Solder Masked. Gold Plated Contact Fingers

**SHUGART 5" MINI FLOPPY DRIVE: \$379.50 inc. tax.  
\$330.00 ex tax.**

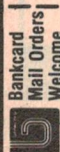Verbatim Products available. Please write for price lists.



Please debit my Bankcard.

Bankcard No. ....

Expiry Date.....

Name.....

Signature.....

General enquiries (03) 489-8131, Mail order enquiries (03) 481-1436, Ritronics Wholesale (03) 489-7099. Prices current till 7th October, 1980. Heavier items add additional postage. Extra heavy items sent Comet freight on. Prices subject to change without notice. Send 60c and SAE for free catalogues. MAIL ORDERS PO Box 135, Northcote, Vic 3070. Minimum pack and post \$1.25.





**HAS THE TASTE STOPPED  
GETTING THROUGH?**

If your present tobacco just doesn't deliver the satisfaction you want, then roll a Cannon.  
A rich new blend of medium dark cigarette tobacco that's just a little bit stronger.  
Cannon, for the taste you're missing out on now.

**CANNON.  
SLIGHTLY STRONGER.**





# What goes on in this town would fill a magazine.

## Restaurants. From China to France.

Sydney has more restaurants than you can shake a chopstick at. And each month they're reviewed. By food. By the bill. By service. And by two of Sydney's best gourmets, Ann and John Tournier.



## Gallery A to Z.

Art can be anything. And anything that is art will be in Sydney City Monthly.

From Picasso prints to Tibetan jewellery. Tucker's sculptures to Dupain's photographs. Lindsay to Whitely.



Every month Sydney City Monthly takes you around town: to the galleries, the theatre, conferences, opera, dance, concerts, rock, jazz, classical.

Every month Sydney City Monthly reveals and reviews: restaurants, exhibitions, movies, books, wine, art.

And every month Sydney City Monthly talks to the people who make this town buzz with fashion, gossip, politics, money, fun.

## Philip Marlowe is alive and well and snooping around Sydney.

Raymond Chandler created him. And someone in Sydney has brought him to life.

He's a real life private eye in the tradition of Marlowe.

He walks like Marlowe, talks like Marlowe, snoops like Marlowe. And has a gun.

Like Marlowe.

His stranger-than-fiction story is in Sydney City Monthly, November issue.

## "You look divine in pink with yellow stripes."

Fashion is fun. Fashion is expensive. Fashion is names like Trent and Carla and Flamingo.

Sydney City Monthly is in fashion, in colour.



## Three stars, two stars or overacting stars.

The movies. Good and bad. And why they're good and bad.

The plots. The stars. The hype.

Lyn Quayle reviews films worth seeing.

## It's a very good month.

Ed Joualt is almost as well known as St. Henri. And just as robust.

Each month he sniffs, swills and swallows a cellar full of vintages to bring you a page full of information.



Sydney City Monthly at your newsagent.  
\$2 BUYS A LOT OF SYDNEY.



# Lab Notes

## Transistor arrays — using the 3046/3056/3086 IC

Transistor arrays are a very useful electronic building block often overlooked by both hobbyists and professionals. This article describes a variety of circuits that can all be built using the 3046/3056/3086 — a common IC.

A transistor array consists of several transistors on the same piece of silicon. They are generally mounted in a 14- or 16-pin dual-in-line or T05 package. Because all the transistors are manufactured together, they are very well matched and because they are all on the same piece of silicon their thermal tracking is excellent.

Arrays may contain NPN transistors, 'super beta' NPNs, PNP transistors, zener diodes, transmission gates, SCRs and PUTs. The PNPs found in arrays are usually of inferior quality, having low  $\beta$ , low current handling capacity and poor frequency response. They are really only suitable for bias networks and similar low frequency applications.

### The substrate connection

All transistor arrays have a connection labelled 'substrate'. Often it is connected to the emitter at an NPN transistor, or it may simply be brought out to a pin on the IC. A cross section of two transistors in an array is shown in Figure 1. The substrate consists of P-type silicon which isolates the two transistors shown as long as the collector-to-substrate junctions remain reverse

biased. This is achieved by connecting the substrate to the most negative part of the circuit.

Beware of tricks which use the collector-to-substrate diode. They are dangerous! Figure 2 shows why. The substrate forms a PNP transistor with the base of the NPN transistor, which generates a latch. This latch can be active unless the PNP transistor is held off by taking the substrate connection to the most negative part of the circuit. Remember, when designing with arrays, **BEWARE THE SUBSTRATE CONNECTION!**

Another point to watch is that if the power supply is connected the wrong way round the collector-to-substrate diode may be forward biased, which can often destroy the array.

An internal schematic and pin connection diagram for the 3086 is shown on page xx. A similar diagram is shown in the RCA Data Book, but with one significant error! *The substrate connection is pin 13 not pin 12.*

### Current mirrors

A very useful circuit configuration that is easily implemented with arrays is

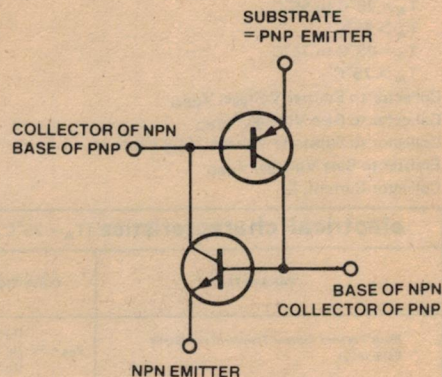


Figure 2. Beware the collector-to-substrate diode!

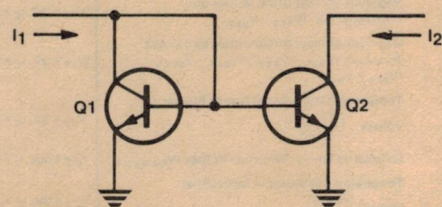


Figure 3. Basic circuit of a current mirror. Connected like this, Q1 and Q2 on the array will have identical collector currents.

the current mirror. Figure 3 shows the basic circuit.

The collector current of a non-saturated transistor depends on the base-emitter voltage. If two identical transistors have identical base-emitter voltages their collector currents will be the same. In Figure 3, Q1 is diode connected and presents a low impedance to the input current. Transistor Q2, whose collector current mirrors that of Q1, is

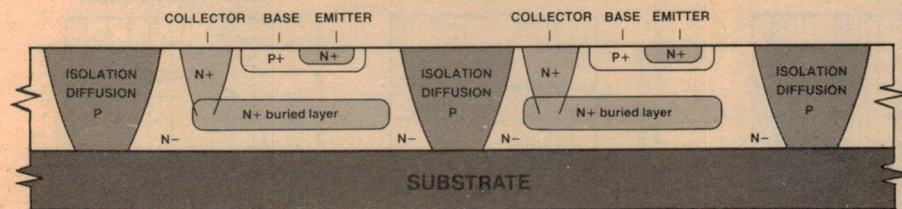


Figure 1. Cross-section of two transistors in a transistor array IC.



# Lab Notes

## SELECTED DATA ON THE 3045/3046/3086 TRANSISTOR ARRAYS

### General Description

The 3045, 3046 and 3086 each consist of five general purpose silicon NPN transistors on a common monolithic substrate. Two of the transistors are internally connected to form a differentially-connected pair. The transistors are well suited to a wide variety of applications in low power system in the dc through VHF range. They may be used as discrete transistors in conventional circuits however, in addition, they provide the very significant inherent integrated circuit advantages of close electrical and thermal matching. The 3045 is supplied in a 14-lead cavity dual-in-line package rated for operation over the full military temperature range. The 3046 and 3086 are electrically identical to the 3045 but are supplied in a 14-lead moulded dual-in-line package for applications requiring only a limited temperature range.

### absolute maximum ratings ( $T_A = 25^\circ\text{C}$ )

Power Dissipation:

$T_A = 25^\circ\text{C}$
$T_A = 25^\circ\text{C}$ to $55^\circ\text{C}$
$T_A > 55^\circ\text{C}$
$T_A = 25^\circ\text{C}$ to $75^\circ\text{C}$
$T_A > 75^\circ\text{C}$

Collector to Emitter Voltage,  $V_{CE0}$

Collector to Base Voltage,  $V_{CBO}$

Collector to Substrate Voltage,  $V_{C10}$  (Note 1)

Emitter to Base Voltage,  $V_{EBO}$

Collector Current,  $I_C$

### features

- Two matched pairs of transistors  
 $V_{BE}$  matched  $\pm 5\text{ mV}$   
Input offset current  $2\mu\text{A}$  max at  $I_C = 1\text{ mA}$
- Five general purpose monolithic transistors
- Operation from DC to 120 MHz
- Wide operating current range
- Low noise figure 3.2 dB typ at 1 kHz
- Full military temperature range (3045)  $-55^\circ\text{C}$  to  $+125^\circ\text{C}$

### applications

- General use in all types of signal processing systems operating anywhere in the frequency range from DC to VHF
- Custom designed differential amplifiers
- Temperature compensated amplifiers


3045		3046/3086		Units
Each Transistor	Total Package	Each Transistor	Total Package	
300	750	300	750	mW
		300	750	mW
		Derate at 6.67		$\text{mW}/^\circ\text{C}$
300	750			mW
		Derate at 8		$\text{mW}/^\circ\text{C}$
15		15		V
20		20		V
20		20		V
5		5		V
50		50		mA

### electrical characteristics ( $T_A = 25^\circ\text{C}$ unless otherwise specified)


PARAMETER	CONDITIONS	LIMITS			UNITS
		3045, 3046		3086	
		MIN	TYP	MAX	
Static Forward Current Transfer Ratio (Static Beta) ( $h_{FE}$ )	$V_{CE} = 3\text{ V}$ $I_C = 10\text{ mA}$ $I_C = 1\text{ mA}$ $I_C = 10\mu\text{A}$	40	100 100 54		
Input Offset Current for Matched Pair $Q_1$ and $Q_2$ $ I_{O1} - I_{O2} $	$V_{CE} = 3\text{ V}$ , $I_C = 1\text{ mA}$		.3	2	$\mu\text{A}$
Base to Emitter Voltage ( $V_{BE}$ )	$V_{CE} = 3\text{ V}$ $I_E = 1\text{ mA}$ $I_E = 10\text{ mA}$		.715 .800		V
Magnitude of Input Offset Voltage for Differential Pair $ V_{BE1} - V_{BE2} $	$V_{CE} = 3\text{ V}$ , $I_C = 1\text{ mA}$		.45	5	mV
Magnitude of Input Offset Voltage for Isolated Transistors $ V_{BE3} - V_{BE4} $ , $ V_{BE4} - V_{BE5} $ , $ V_{BE5} - V_{BE3} $	$V_{CE} = 3\text{ V}$ , $I_C = 1\text{ mA}$		.45	5	mV
Temperature Coefficient of Base to Emitter Voltage $(\frac{\Delta V_{BE}}{\Delta T})$	$V_{CE} = 3\text{ V}$ , $I_C = 1\text{ mA}$		-1.9	-1.9	$\text{mV}/^\circ\text{C}$
Collector to Emitter Saturation Voltage ( $V_{CE(SAT)}$ )	$I_B = 1\text{ mA}$ , $I_C = 10\text{ mA}$		.23	.23	V
Temperature Coefficient of Input Offset Voltage $(\frac{\Delta V_{IO}}{\Delta T})$	$V_{CE} = 3\text{ V}$ , $I_C = 1\text{ mA}$		1.1		$\mu\text{V}/^\circ\text{C}$

**Note 1:** The collector of each transistor of the 3045, 3046, and 3086 is isolated from the substrate by an integral diode. The substrate (terminal 13) must be connected to the most negative point in the external circuit to maintain isolation between transistors and to provide for normal transistor action.

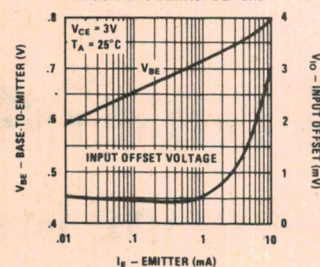
Typical Static Base To Emitter Voltage Characteristic and Input Offset Voltage for Differential Pair and Paired Isolated Transistors vs Emitter Current



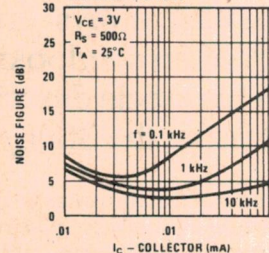
Typical Noise Figure vs Collector Current



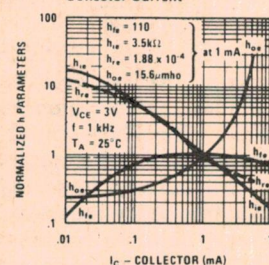
Typical Normalized Forward Current Transfer Ratio, Short Circuit Input Impedance, Open Circuit Output Impedance, and Open Circuit Reverse Voltage Transfer Ratio vs Collector Current




Typical Output Admittance vs Frequency

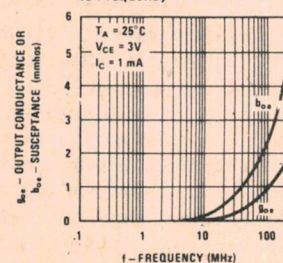

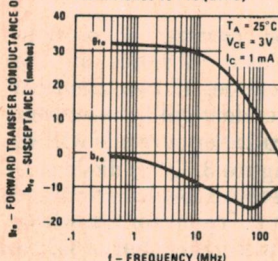
Typical Forward Transfer Admittance vs Frequency




Typical Input Admittance vs Frequency

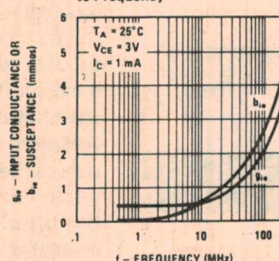

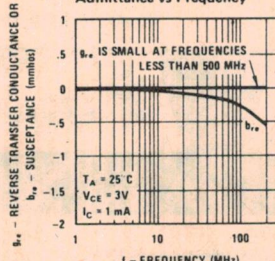Typical Reverse Transfer Admittance vs Frequency



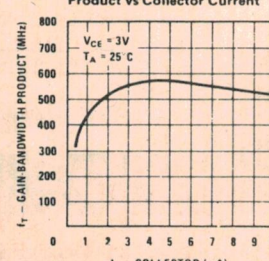Typical Gain-Bandwidth Product vs Collector Current





connected as a dc-coupled common emitter amplifier and has a very high output impedance.

Current mirrors constructed from discrete components are not nearly as accurate because two discrete transistors chosen at random will rarely be identical. Also it requires extra construction to ensure that the transistors are held at the same temperature, because transistor characteristics are very temperature-dependent.

But two transistors on an array, having been manufactured side by side and being incorporated in the same piece of silicon, are very well matched. Errors in mirrors constructed using arrays are generally less than ten per cent.

A current mirror provides a regulated high impedance current sink. Its output will generally go to 200 mV from earth before the mirror transistor saturates, making it very useful for linear ramps, biasing networks and a host of other applications.

## Voltage controlled oscillator

A circuit for a voltage controlled oscillator is shown in Figure 4. It consists of a controlled bias system with Q2 and Q3 forming a current mirror with Q1. To understand the oscillator, imagine that Q5 is turned hard on. Transistor Q2 will slowly pull Q4's emitter low until Q4 starts to turn on. As it does so it will pull Q5's base low, turning Q5 off which turns Q4 harder on. This regenerative action continues until Q4 is fully on and Q5 off. Q3 then slowly starts to turn Q5 on and the process continues.

The rate of oscillation depends on the charging time of the capacitor between the collectors of Q2 and Q3. If the current through Q2 and Q3 decreases, the charging time increases and the oscillator frequency decreases. Because Q2 and Q3 mirror Q1, varying the current through Q1 will vary the oscillator frequency.

The circuit will oscillate at about 10 MHz with 5 V on the control pin. It can be made to run at 30 MHz by placing germanium diodes between collector and base of Q4 and Q5 and increasing the control voltage. The diodes should be inserted with their cathodes to the transistor bases to stop the transistors from saturating and

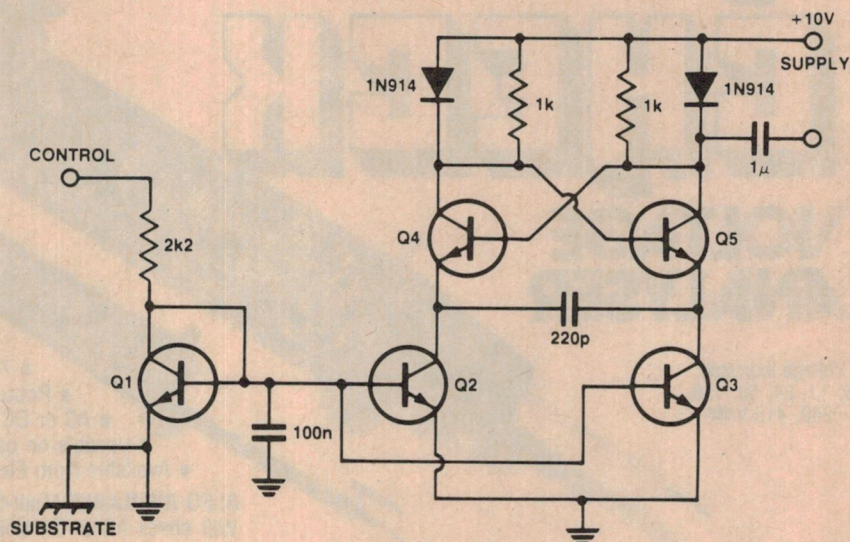


Figure 4. Circuit of a voltage controlled oscillator. Transistors Q2 and Q3 in the array form a current mirror with Q1. The voltage at the 'control' input sets the collector currents of Q2 and Q3 which controls the oscillator frequency. Circuit oscillates around 10 MHz with 5 V on the control input.

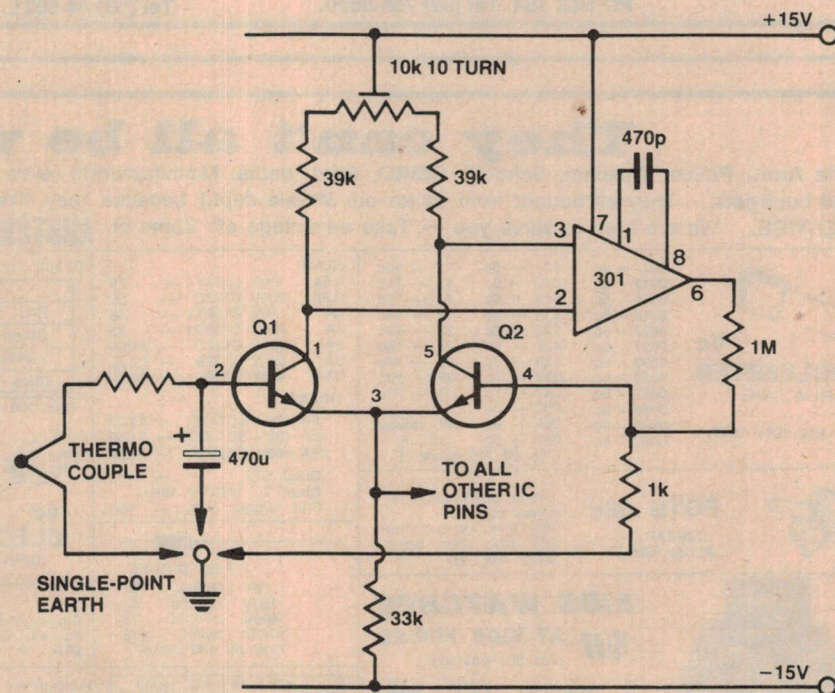


Figure 5. A useful thermocouple amplifier. Input offset nulling is independent of temperature in this circuit, unlike many circuits.

storing charge in their bases. Such charge storage slows transistors down.

## Thermocouple amplifier

Figure 5 shows a circuit for an amplifier with a gain of 1000, suitable for use with thermocouples.

The biggest problem when using op-amps as thermocouple amplifiers is the temperature drift of the input offset voltage. Most methods of nulling the input offset are ineffective if the temperature varies. This circuit solves the problem by eliminating the input offset voltage ►



# MASTER CHECK

## VOLTAGE ANALYSER

Voltage indicated:  
6, 12, 24, 50, 110,  
240, 415 V ≈



**NEW**  
**\$24** Plus 15%  
sales tax  
P & P \$2.00

### MASTER CHECK

- Cannot be over ranged.
- Indicates AC or DC Voltage.
- Automatic Voltage indication.
- Read off polarity at a glance.
- Designed for Australian conditions.
- 7 Voltage indication steps by L.E.D.'s
- Robust lightweight plastic construction.
- AC or DC Voltage Check from 6 to 415 Volts.
- Useable on battery operated devices to three phase AC.
- Available from Electrical Wholesalers throughout Australia.

**ALSO AVAILABLE** Multi-Check — Handy solid state continuity checker.  
Will check AC or DC Voltages from 4.5 to 415 Volts.

**BELL**

**BELL INSTRUMENTS PTY. LIMITED**

Garema Circuit, Kingsgrove 2208 NSW.  
PO Box 154. Tel (02) 750-6000.

74 Raglan Street, Preston 3072 Vic.  
Tel (03) 44-5021.

## They can't all be wrong:-

The Army, Police, Telecom, Schools, CSIRO, Govt. depts. Manufacturers (even Tandy & D.S. Dealers) plus 1000's of good old hobbyists. They all bought from us (or our W'sale dept.) because they like our quality, low prices and SAME DAY SERVICE. We are here to serve you — Take advantage of: Some of

### AUSTRALIA'S LOWEST COMPONENT PRICES



**4c**  
**POLYESTER**  
FILM CAPS

E12 10% 100V

.001 - 4c	.01 - 5c	.1 - 10c
.0012 - 5c	.012 - 6c	.12 - 11c
.0015 - 5c	.015 - 6c	.15 - 12c
.0018 - 5c	.018 - 6c	.18 - 14c
.0022 - 5c	.022 - 6c	.22 - 15c
.0027 - 5c	.027 - 6c	.27 - 16c
.0033 - 5c	.033 - 7c	.33 - 18c
.0039 - 5c	.039 - 7c	.39 - 19c
.0047 - 5c	.047 - 7c	.47 - 20c
.0056 - 5c	.056 - 8c	
.0068 - 5c	.068 - 8c	All values
.0082 - 5c	.082 - 9c	in uF
		10% off 100 same uF



**POTS 35c**  
(LINEAR 1/4" ALUM. SHAFT)

Linear potentiometers  
rotary carbon  
500 Ohm, 1K, 5K, 10K,  
25K, 50K, 100K, 250K,  
500K, 1M, 2M.

#### SCRs:

0.8A	30V	C103Y	—	35
0.8A	200V	C103B	—	60
4A	30V	C106Y1	—	40
4A	400V	C106D1	—	75
8A	400V	C122D	—	\$1.05
8A	500V	C122E	—	\$1.20
25A	400V	C37D	—	\$2.50

#### TRIACS:

6A	400V	SC141D	—	\$1.25
10A	400V	SC146D	—	\$1.50
25A	400V	SC260D	—	\$2.50

#### DIAC ST2

Chart to identify leads

Plus trigger info. — 10c

#### 1 Amp. DIODES

50V	1N4001 -	5c
100V	1N4002 -	6c
400V	1N4004 -	7c
1000V	1N4007 -	11c
		10% off 100 SAME

ea.	10	100	1000
1/4W	1 1/2c	13c	90c \$8
1/2W	2c	18c	\$1.40 \$10 1/4

Carb. film resistors 5% E12 values  
2.2 ohm to 4M7 good quality.  
Over stocked on less preferred E12-E6  
2.7 ohm to 3m3. Over 30 values  
premixed in 100 lots same price as  
100 above 1/4 and 1/2 W.

PROJECT BOARD 85x85mm - Price 60c  
Copper stripped P.C. Board for quick jobs  
Holes on 4mm grid. Double width 170x85mm  
available at \$1 (perforated at centre)

Quality Large LEDs well diffused wide viewing angle.

	each	10	100	1000
Red	15c	\$1.40	\$12	\$110
Green	24c	\$2.25	\$19	\$177
Yellow	27c	\$2.50	\$22	\$199
Clips	3c	all quantities		

red LEDs

\$12 a 100

15c each

Best value  
No brag Just fact

(per 100 prices in brackets) Cap.


	16V	25V	50V
0.47uF	4c(\$3 1/2)	5c(\$3 1/4)	6c(\$4)
1, 2.2, 3.3, 4.7, 10uF	5c(\$3 1/2)	6c(\$3 1/4)	7c(\$4)
22uF	6c(\$3 1/4)	7c(\$4)	
33uF	8c(\$4)		
47uF	9c(\$5)	10c(\$6)	11c(\$7)
100uF	10c(\$6)	12c(\$7)	14c(\$11)
220uF	12c(\$8)	16c(\$10)	35c(\$17)
470uF	16c(\$12)	22c(\$16)	45c(\$30)
1000uF	22c(\$18)	30c(\$25)	75c(\$50)

**4c**  
**ELECTROS**  
(UPRIGHT)

Signal Diode 1N4148  
4c ea. 35c per 10  
\$3 1/4 a 100, \$25/K

Same ohms  
No mix  
on qty. prices

1 1/2c

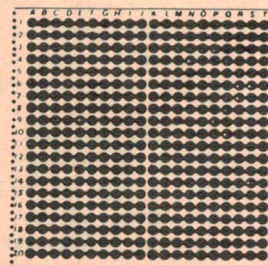

SHOWN 1/2 FULL SIZE

**DIGGERMAN ELECTRONICS**

P.O. BOX 33, CORAMBA, N.S.W. 2466

ADD ONLY 50c postage on any size  
order. All orders normally back in  
mail inside 8 hours.



# Lab Notes

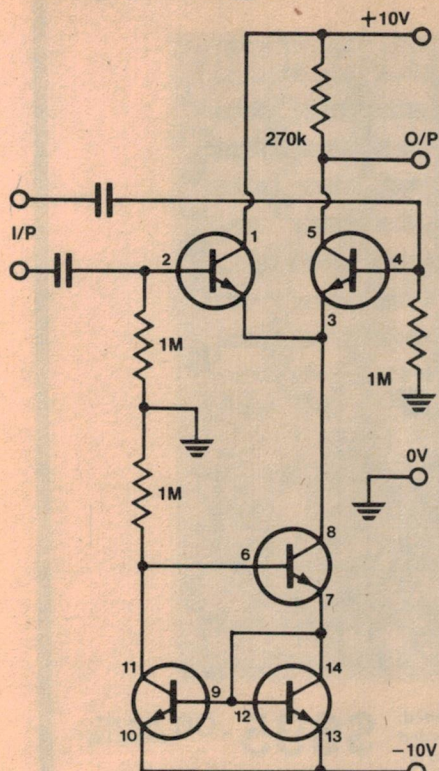


Figure 6. This differential amplifier has a very high common mode rejection ratio (cmrr). Constant current source for the differential pair is a variation on the current mirror. Circuit is suitable for bio-electronic applications such as in a cardiac monitor or EMG.

entirely. With a piece of wire replacing the thermocouple adjust the pot until the output of the amplifier is at 0 V. Since the bases of both Q1 and Q2 are at

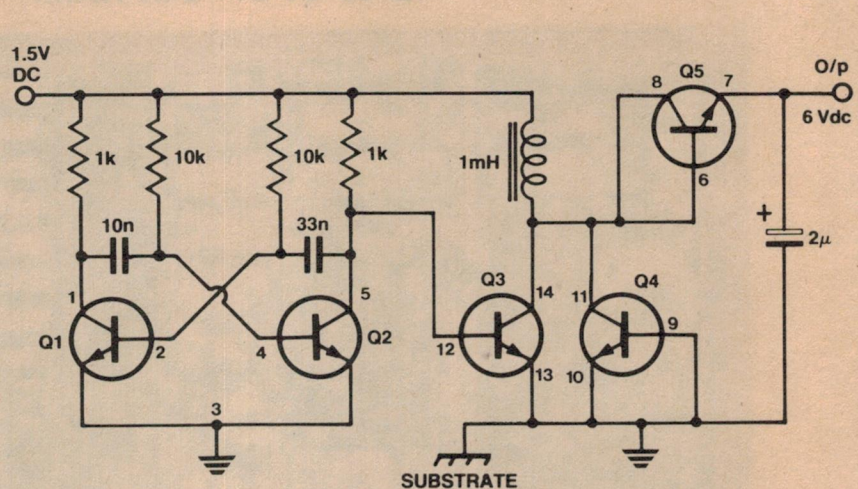


Figure 7. This ringing choke inverter is just the thing for powering CMOS circuits from a single 1.5 V cell in portable applications. Operation is explained in the text.

earth there is no input offset voltage.

This amplifier has very high open loop gain and will happily amplify any hum or other noise at its input. It will also oscillate through any capacitive coupling between output and input or between the supplies and the input. To avoid this, supplies should be well bypassed and earthing should be 'star' configured.

The substrate is not connected to the negative supply, because under extreme conditions the 20 V maximum collector-to-substrate voltage could be exceeded. However, no part of the array will ever go more negative than the sub-

strate, so the circuit is quite safe.

The other transistors on the array should not be used as they may generate temperature gradients between Q1 and Q2.

## Differential amplifier

The circuit shown in Figure 6 has a very high common mode rejection ratio and is suitable for circuits such as cardiac monitors where the desired signal may be buried in a lot of common mode noise. It's a differential amplifier biased by a variation of a current mirror that has very high output impedance to improve the common mode rejection.

## Ringing choke inverter

This is a simple circuit, illustrated in figure 7, which generates about 6 V at 50 mA from a 1.5 V battery. It could be used to power CMOS from a single pen-light battery when a compact, portable circuit is required.

Transistors Q1 and Q2 form an astable multivibrator. When Q2 turns off, Q3 turns on and current flows through the inductor from the supply. The point 'A' on the waveform diagram (Figure 8) is the point where Q3 saturates. When Q2 turns on, cutting off Q3, the inductor tries to maintain the flow of current. Q5 is connected as a diode and current will flow through it until the voltage on Q4's emitter zeners the reverse biased junction. This is point 'B' on Figure 8.

When the inductor no longer has the energy to pump current into Q4 or Q5 it starts to oscillate (or ring) with its own parallel parasitic capacitance. This is point 'C' on Figure 8. The amplitude of

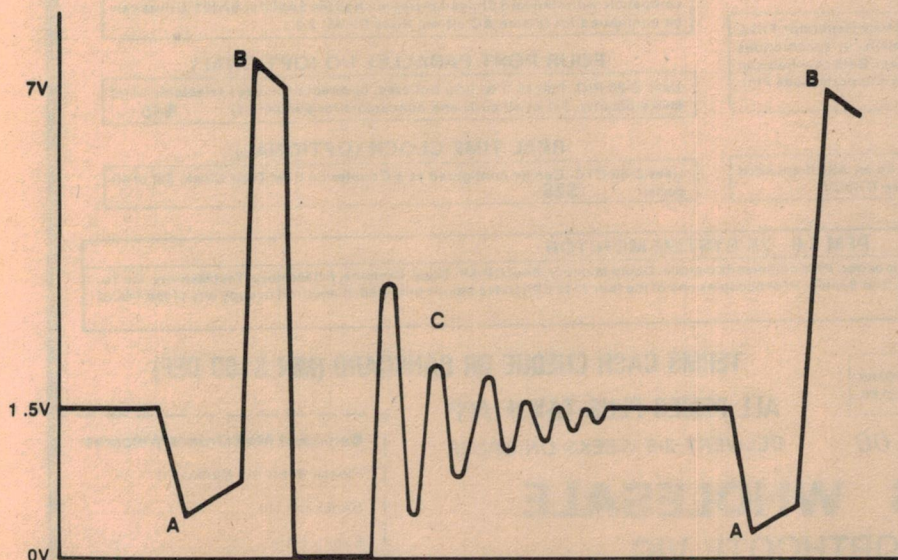



Figure 8. Typical waveform at the collector of Q3 in the ringing choke inverter.



# NEW!

## "THE BIG BOARD" OEM - INDUSTRIAL - BUSINESS - SCIENTIFIC SINGLE BOARD COMPUTER KIT! Z-80 CPU! 64K RAM!

# NEW!

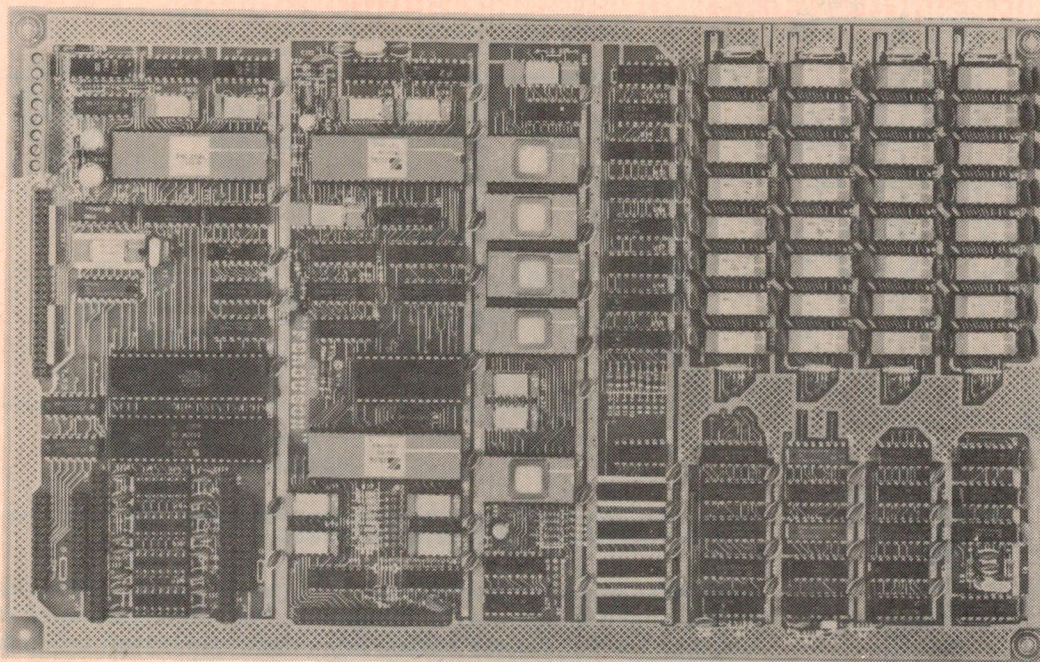

**THE FERGUSON PROJECT:** Three years in the works, and maybe too good to be true. A tribute to hard headed, no compromise, high performance, American engineering! The Big Board gives you all the most needed computing features on one board at a very reasonable cost. The Big Board was designed from scratch to run the latest version of CP/M\*. Just imagine all the off-the-shelf software that can be run on the Big Board without any modifications needed! Take a Big Board, add a couple of 8 inch disc drives, power supply, and an enclosure; and you have a total Business System for about 1/3 the cost you might expect to pay.

**\$695.00** (64K KIT BASIC I/O)

SIZE: 8 1/2 x 13 3/4 IN.  
SAME AS AN 8 IN. DRIVE.  
REQUIRES: +5V @ 3 AMPS  
- 12V @ .5 AMPS.

### FEATURES: (Remember, all this on one board!)

#### 64K RAM

Uses industry standard 4116 RAM'S. All 64K is available to the user, our VIDEO and EPROM sections do not make holes in system RAM. Also, very special care was taken in the RAM array PC layout to eliminate potential noise and glitches.

#### Z-80 CPU

Running at 2.5 MHZ. Handles all 4116 RAM refresh and supports Mode 2 INTERRUPTS. Fully buffered and runs 8080 software.

#### SERIAL I/O (OPTIONAL)

Full 2 channels using the Z80 SIO and the SMC 8116 Baud Rate Generator. FULL RS232! For synchronous or asynchronous communication. In synchronous mode, the clocks can be transmitted or received by a modem. Both channels can be set up for either data-communication or data-terminals. Supports mode 2 Int. Price for all parts and connectors: **\$95**

#### BASIC I/O

Consists of a separate parallel port (Z80 PIO) for use with an ASCII encoded keyboard for input. Output would be on the 80 x 24 Video Display.

#### 24 x 80 CHARACTER VIDEO

With a crisp, flicker-free display that looks extremely sharp even on small monitors. Hardware scroll and full cursor control. Composite video or split video and sync. Character set is supplied on a 2716 style ROM, making customized fonts easy. Sync pulses can be any desired length or polarity. Video may be inverted or true.

#### FLOPPY DISC CONTROLLER

Uses WD1771 controller chip with a TTL Data Separator for enhanced reliability. IBM 3740 compatible. Supports up to four 8 inch disc drives. Directly compatible with standard Shugart drives such as the SA800 or SA801. Drives can be configured for remote AC off-on. Runs CP/M\* 2.2.

#### FOUR PORT PARALLEL I/O (OPTIONAL)

Uses Z-80 PIO. Full 16 bits, fully buffered, bi-directional. User selectable hand shake polarity. Set of all parts and connectors for parallel I/O: **\$45**

#### REAL TIME CLOCK (OPTIONAL)

Uses Z-80 CTC. Can be configured as a Counter on Real Time Clock. Set of all parts: **\$25**

#### PFM 3.0 2K SYSTEM MONITOR

The real power of the Big Board lies in its PFM 3.0 on board monitor. PFM commands include: Dump Memory, Boot CP/M\*, Copy, Examine, Fill Memory, Test Memory, Go To, Read and Write I/O Ports, Disc Read (Drive, Track, Sector), and Search. PFM occupies one of the four 2716 EPROM locations provided. It does not occupy any of the 64K of system RAM!

#### CP/M\* 2.2 FOR BIG BOARD

The popular CP/M\* D.O.S. modified by MICRONIX SYSTEMS to run on Big Board is available for \$150.00.

### TERMS CASH CHEQUE OR BANKCARD (MIN \$100 DEP)

ALL PRICES PLUS TAX IF APP  
DELIVERY 3-8 WEEKS ON ORDER

REGISTERED PACK & POST \$5.00



## RITRONICS WHOLESALE

425 HIGH ST., NORTHCOTE VIC

481 1923

489 7099

PO BOX 235

#### Bankcard Mail Orders Welcome

Please debit my Bankcard

Bankcard No .....

Expiry Date .....

Name .....

Signature .....



# Lab Notes

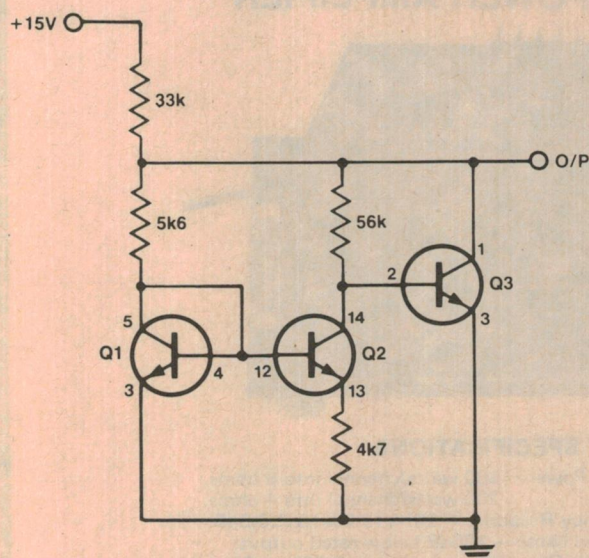


Figure 9. Typical circuit of a 'band gap' voltage reference. This has excellent long term voltage and temperature stability. Output is 1.4 V, within 7 mV from 20°C to 100°C.

the oscillation gradually decreases until Q3 is next turned on, restarting the whole process. The frequency of oscillation is a few kiloHertz.

## Band gap reference

The band gap reference shown in Figure 9 is a voltage reference circuit with excellent temperature and long term stability. Its output is around 1.4 V and it may be used as a stable reference in 5 V systems.

The voltage generated on the emitter of Q2, being the difference between Q1's and Q2's base-emitter voltages, has a positive temperature coefficient. Since the current through Q2's emitter also

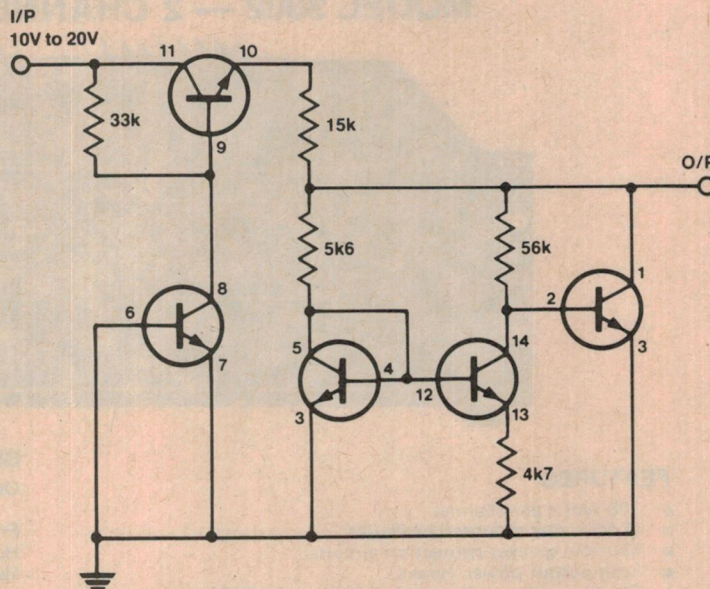


Figure 10. Improved performance can be obtained from a band gap voltage reference by adding a pre-regulator. This employs one transistor in the array as a zener and the remaining transistor as a series regulator.


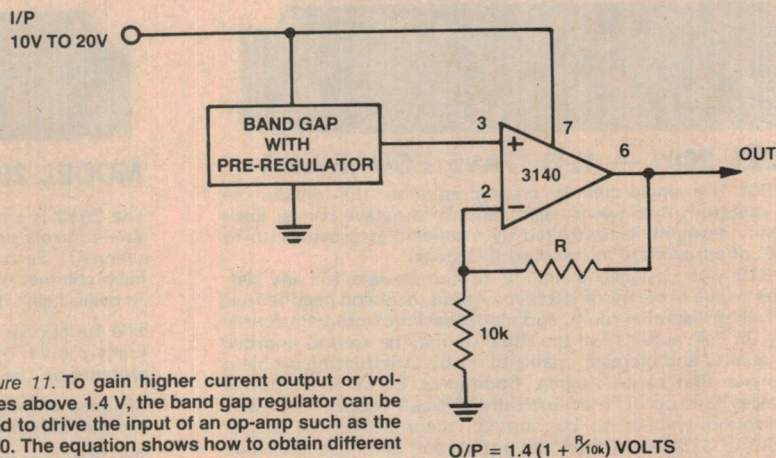


Figure 11. To gain higher current output or voltages above 1.4 V, the band gap regulator can be used to drive the input of an op-amp such as the 3140. The equation shows how to obtain different outputs.
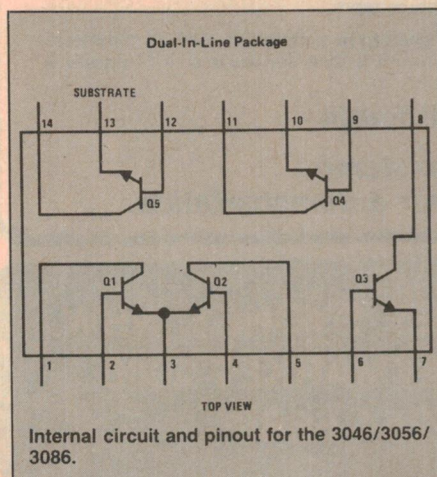
$$O/P = 1.4 (1 + \frac{R}{10k}) \text{ VOLTS}$$



flows through the 56k resistor, the voltage across this resistor also has a positive temperature coefficient. The base-emitter voltage of Q3 has a negative temperature coefficient. The values of resistors in the circuit have been chosen so that these temperature coefficients just cancel. My prototype varied by just 7 mV over the range from 20°C to 100°C.

To build a working band gap reference, high quality resistors must be used. Metal film types with 2% tolerance are best.

One problem encountered with this


circuit is that its output varies slightly with the bias current through the 68k resistor. This can be overcome by providing the circuit with a pre-regulator, as shown in Figure 10. The pre-regulator uses the two remaining transistors on the array, one of which is connected as a zener diode.

If a high drive capability, or voltages greater than 1.4 V are required, then an op-amp or a non-inverting amplifier may be used as a follower. Figure 11 shows the connections. A 3140 op-amp makes an excellent follower as it may be operated from a single supply.



# PROFESSIONAL AUDIO EQUIPMENT
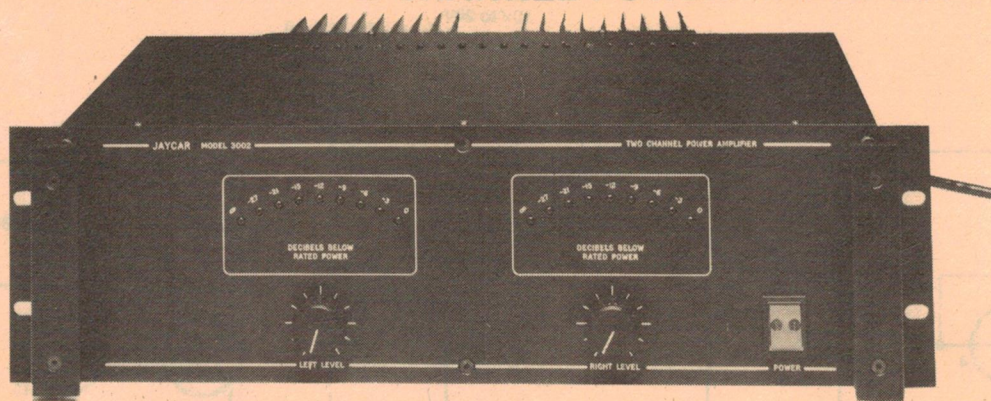
## MODEL 3002 — 2 CHANNEL POWER AMPLIFIER




### FEATURES

- 300 Watts per channel.
- Massive rear mounted heatsinks.
- Multiple speaker protection circuits.
- Peak output power meters.
- Constructed to withstand the tortures of 'On the road' use.
- Standard 19" rack mounting.
- Separate power supplies for each channel.
- Dual RCA input sockets to allow bridging to other amplifiers.
- Equally suited to Hi Fi use or P.A./Disco situations.
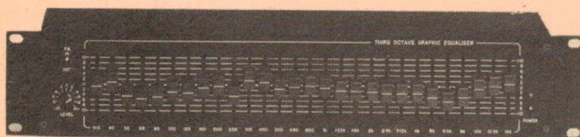
### BRIEF SPECIFICATIONS

Output Power — 300 watts/channel into 8 ohms.  
200 watts/channel into 4 ohms.  
Frequency Response — 20Hz to 20kHz  $\pm 0.5$ dB.  
Hum and Noise — 105dB below rated output.  
Harmonic Distortion — Less than 0.05% to 80 watts.  
Less than 0.15% at rated power.  
Input Sensitivity — 1.0 volts for rated output.  
Dimensions — 482mm x 133mm x 340mm.  
Weight — 20 kgs.  
**\$452.00 plus freight.**




## MODEL 2801 — 1/3 OCTAVE EQUALISER

The 2801 is a single channel graphic equaliser that divides the audio spectrum into twenty-eight one third octave bands. Each frequency segment is controlled by a slider that provides up to  $\pm 10$  dB of adjustment in standard ISO steps.

The 2810 was designed primarily to compensate for any deficiencies in the linearity of speaker systems, acoustic peculiarities of the hall or listening room, and inadequacies of program source quality. In P.A. application the equaliser may be used to improve sound quality and increase intelligibility by attenuating problem frequencies that cause ringing, boominess, or other disruptive resonances that occur in acoustically difficult rooms. The 2801 allows sound systems to be "tuned" according to the special acoustics of a room, to maximise output and minimise feedback. As a creative tool in sound recording or re-recording the 2801 allows complete freedom in contouring response over the complete audio spectrum from 31.5 Hz to 16 KHz.

**\$198.00 plus \$3.00 freight.**

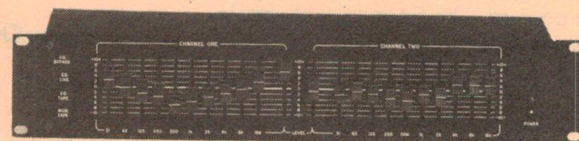

## MODEL 2010 — 2 CHANNEL EQUALISER

The 2010 is a two channel graphic equaliser featuring ten adjustable controls on octave centre frequencies (independent for each channel). Each control provides up to  $\pm 14$ dB of adjustment. Each channel is also equipped with a level match control giving an overall gain of adjustment of  $\pm 14$ dB.

The functional versatility of the 2010 equaliser is unsurpassed. Eight modes of operation are available from the push button switches on the front panel.

Included amongst these are the ability to equalise both recording and playback when dubbing tapes.

The 2010 has been designed to be compatible with all commercially available equipment and is ideal for use in a Hi Fi system or P.A. system.

**\$162.00 plus \$3.00 freight.**

*For further information, please send a 35c stamp  
for full specification sheets, or call at our showroom for a demonstration.*

**jaycar**  
PTY LTD


**380 SUSSEX STREET, SYDNEY, NSW  
P.O. BOX K39, HAYMARKET 2000  
TEL: (02) 264-6688**



# \$399

## EXPANDABLE, AFFORDABLE, LEARN AS YOU BUILD MICROCOMPUTER

CASSETTE  
INTERFACE

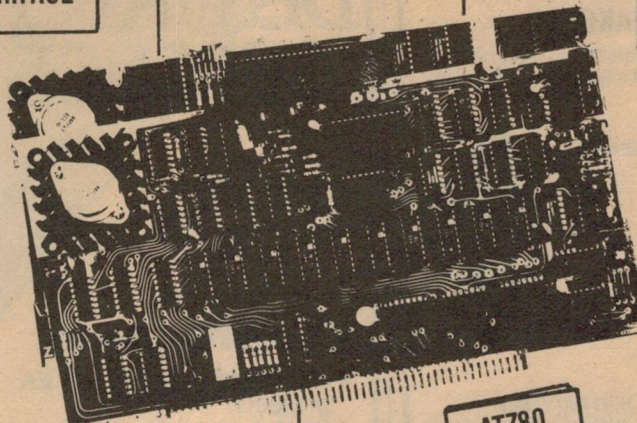

KEYBOARD

ATZ80  
OWNERS  
MANUAL

Z80  
PROGRAMMING  
COURSE

The 1980's is the age of computer technology. Update your knowledge of computer hardware and software with the ATZ80, S100 modular building blocks. Start with the basic Z80/CPU/VDU/Keyboard package and E-X-P-A-N-D later as your needs increase.

**WHY Z80?** It's the world's most powerful and popular 8-bit micro and consequently has by far the largest software support (and believe us, this counts!)

**WHY S100?** It has now evolved as the widest used standard supported by equipment manufacturers world wide. Another big plus is that each S100 card is a functional module, easy to service and, above all, easy to understand and use.

**KIT OR ASSEMBLED/TESTED.** The ATZ80 micromodular system is available in kit form or assembled and tested. By far the biggest advantage is the flexible expandability that means you build up the system you need when you need it. Start with the \$399 ATZ80/4 package and you can learn programming, build useful control systems such as a burglar alarm, time switch, robot controller, even an intelligent visual display unit (VDU). If you need more memory, add the AT16K static ram board, the SECI cassette interface controller and you can load games programs such as Target, Space Trek or Microworld Z80 Basic... even the Microworld Z80 Editor/Assembler. You now have a professional quality computer system to challenge the "ready made" systems like the TRS80, Apple and The Sorcerer at a fraction of the cost!

**NO EXPENSIVE EXPANSION INTERFACE REQUIRED!** Why spend \$500 or more for a S100 interface for the so called "popular" computers? The ATZ80 is already on the S100 bus so you can spend your expansion dollars on more powerful hardware such as floppy discs or a high speed line printer.

**THE ATZ IS VERSATILE.**... whether you want a low cost teaching machine, a word processor, a small business system, a dedicated controller or even a full process control system you can select the modular building blocks to suit your needs... and save yourself a bundle as well.

**THE ATZ80 IS A PROVEN AUSTRALIAN DESIGN,** fully supported with service and technical backup. Designed by David Griffiths, the DGZ80 was described in ETI Nov., 1979 and is the most popular single board S100/Z80 CPU in Australia. Applied Technology, leaders in microcomputer kits since 1976, selected the DGZ80 as the most suitable kit for hobbyists, but other users include Govt. Depts., Educational Institutions and industry. IBM even bought a DGZ80 for evaluation!

**SPECIAL OFFER:** \$399 ATZ80 STARTER'S KIT Package deal includes DGZ80/CPU Kit, DGOS Monitor Program in ROM, DG40/VDU kit, fully encoded ASCII keyboard, complete assembly instructions, Z80 programming course and detailed experiments/programs to run. You just connect a simple power supply (details provided) and a modified TV set or monitor.

### SUPPORT MODULES

TCT16K Static Ram Kit  
IA32K ROM (without EPROMS)  
ET1681 PCG (Graphics) Kit  
SECI Cassette Interface  
S100 Protoboard

Kit	Assembled/ Tested
\$259.00	\$ 299.00
—	\$ 110.00
\$140.00	\$ 165.00
—	\$ 27.50
—	\$ 21.75

### PERIPHERALS

Micropolis 1043/Quad Density 5" Disc system  
complete with drive, controller, cables, power  
supply and software  
8300 High Speed Printer  
12" Monitor

\$1275.00
\$ 950.00
\$ 149.50

### PACKAGING/HARDWARE

JC100 S100 Motherboard 9 slot  
JC200 Cage Kit  
EPS250 Heavy duty power supply kit  
Computer desk unit and cabinet

\$49.50
\$49.50
\$65.00


(write for details)

### SOFTWARE (SUPPLIED ON CASSETTE TAPE WITH OWNERS MANUALS)

Microworld Z80 12K Basic  
Microworld Z80 Assembler  
Games Pack 1  
Utility Pack 1

\$14.75
\$14.75
\$14.75
\$14.75

All prices include Sales Tax.

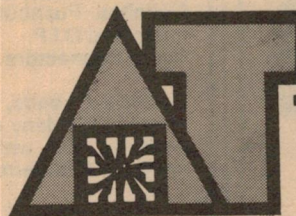

# APPLIED TECHNOLOGY PTY. LTD.

### MAIL ORDERS TO:

PO Box 311, Hornsby 2077.

Please add \$2.00 per order  
towards cost of post and packing.

### OFFICE/SHOWROOM

1a Pattison Avenue, Waitara 2077.

Hours: 9-5 Monday to Saturday  
Telephone: 487 2711

### AND NOW AT GOSFORD —

1 Debenham Road, West Gosford (behind the Pizza Hut)



AT.003





**NEW**

## RPG HI-FI & MUSICAL INSTRUMENT SPEAKERS

Manufactured to Radio Parts Group specifications by the world's largest speaker manufacturer.

### HIGH EFFICIENCY TWEETERS

H66AP45-01F 6w.....	\$5.14
E66CP45-01F 8w.....	\$5.14
B45DP70-01F 10w.....	\$8.95

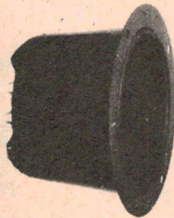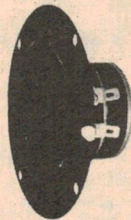


### HI-FI MID RANGE

B11EC80-02F 30w.....	\$15.79
(can back) 4 1/2 inch	
A11DP60-02F 15w.....	\$7.37
(sealed back) 4 1/2 inch	

### WIDE RANGE

4 1/2" B11EC80-01F 15w.....	\$13.49
6" A16DC61-01FW 12w.....	\$8.44
6" C16E70-01FW 15w.....	\$13.23
8" A20EP80-03FW 20w.....	\$15.04
8" A20EC70-03FW 30w.....	\$14.35

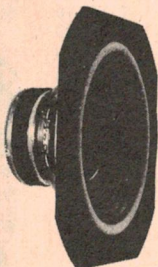


### WOOFERS

8" A20EU75-01F 30w.....	\$15.29
10" A25EP65-02F 20w.....	\$15.41
10" C25FU90-03F 50w.....	\$31.47
12" A30EU80-01F 35w.....	\$29.44
12" A30FU20-01F 65w.....	\$42.09



### MUSICAL INSTRUMENT

8" B20HP14-01F 50w.....	\$23.54
12" A30GC40-01F 100w.....	\$57.92

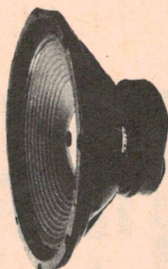

RPG Speakers are only available from:

**RADIO  
PARTS  
GROUP**

562 Spencer Street, West Melbourne.  
Phone (03) 329-7888.  
1103 Dandenong Road, East Malvern.  
Phone (03) 211-8122.

# RADIO DESPATCH SERVICE

869 George Street,  
Sydney, NSW. 2000.  
(Near Harris Street)  
Phone 211-0816, 211-0191.

## We specialise in:

- PC Boards for ETI and EA projects.
- Scotchcal labels made under order for ETI and EA projects 1979 and onwards.

## See us for all types of valves.

### Texas Calculators

	excl. S.T.	incl. S.T.
Ti.59 .....	\$265.00	\$299.90
Ti.58C.....	\$132.00	\$149.00
Ti PC 100C Printer .....	\$210.00	\$237.00
Ti.50 .....	\$36.40	\$40.30
Ti.55 .....	\$53.35	\$59.00
Ti.30 Student Pack.....	\$20.00	\$22.10
Little Professor .....	\$17.40	\$19.00
Dataman .....	\$23.63	\$26.15
Speak and Spell .....	\$68.60	\$75.95

"E-Z Circuit". Printed circuit drafting material, Pins and Hardware. Wide range in stock. Ideal for experiments and hobbyists.

L.E. Diodes. Round and rectangular. Assorted colours.

L.E.D. Diodes. Mounted Bezel assemblies. Various types.

Soldering irons and accessories — Weller, Lotring, Mico, Adcola.

Hi Fi. Record cleaners and accessories by Metro Sound. Wide range of cassette tapes, splicers, demagnetizers, head cleaners etc.

Television aerials. Indoor and outdoor plus installation, and TV accessories.

Switches. Pushbutton, toggle, rotary, micro and D.I.P.

Audio Connectors. RCA, DIN, Cannon etc.

Patchcord Leads. For audio and TV connection. Many combinations.

Batteries. For watches, calculators, radios and lanterns by Eveready and G.E.

### MAIL ORDER CUSTOMERS

\$1.00 packing plus 5 percent of order value up to \$80.00, thence a flat \$4.00 for postal items. Carrier — freight on.

OPEN: Mon-Fri 8 am to 5.30 pm.  
Thursday night late shopping till 8.30 pm. Saturday 8 am to 11.45 am.

# Ohio Scientific dealer network is Australia-wide

For more information and advice call on your local dealer to help you select the best system for your needs

AUSTRALIAN DISTRIBUTOR-TCG,  
31 Hume Street, Crows Nest, N.S.W.  
2065

### AUTHORISED AUSTRALIAN AGENTS NEW SOUTH WALES

Bambach Electronics  
NEWCASTLE 2-4996  
Compuserve Newcastle Pty. Ltd.  
HAMILTON 61-2579

Hi-Fi Gallery  
TAMWORTH 66-2525  
Macalec Pty. Ltd.  
WOLLONGONG 29-1455

Micro Visions  
KINGSFORD 662-4063  
Shoalhaven Communication Services  
NOWRA 24-444

J.G. Pearce Systems  
DOVER HEIGHTS 789-4300  
Unique Electronics  
MERRYLANDS 682-3325

### VICTORIA

Ellison Hawker Education Pty. Ltd.  
HAMPTON 596-7444

Cypher Data Systems  
MELBOURNE 86-22122  
Comprocessing Pty. Limited  
SALE 44-3399

### QUEENSLAND

Dialog Pty. Ltd.  
BRISBANE 221-4898

### SOUTH AUSTRALIA

Applied Data Control  
FULLARTON 79-9211

K Tronics  
ADELAIDE 212-5505

### WESTERN AUSTRALIA

Datas Computer Accounting Services  
SUBIACO 325-5779

Micro Data Pty. Ltd.  
EAST PERTH 328-1179

Micro Solutions  
SUBIACO 328-8372

### TASMANIA

Eastside Computers  
EAST DEVONPORT 27-8121

J. Walsh & Company  
HOBART 34-7511

### AUSTRALIAN CAPITAL TERRITORY

Minicomputer & Electronic Services  
PHILLIP 82-1774

### NEW ZEALAND DISTRIBUTOR

Computer Consultants,  
3 Wolfe St., Auckland N.Z.  
Phone: 79-8345

Computer Consultants  
Queens Rd., Lower Hutt. N.Z.  
Phone: 69-4979


**TCG**  
TOMORROW'S TECHNOLOGY TODAY

**OHIO SCIENTIFIC**


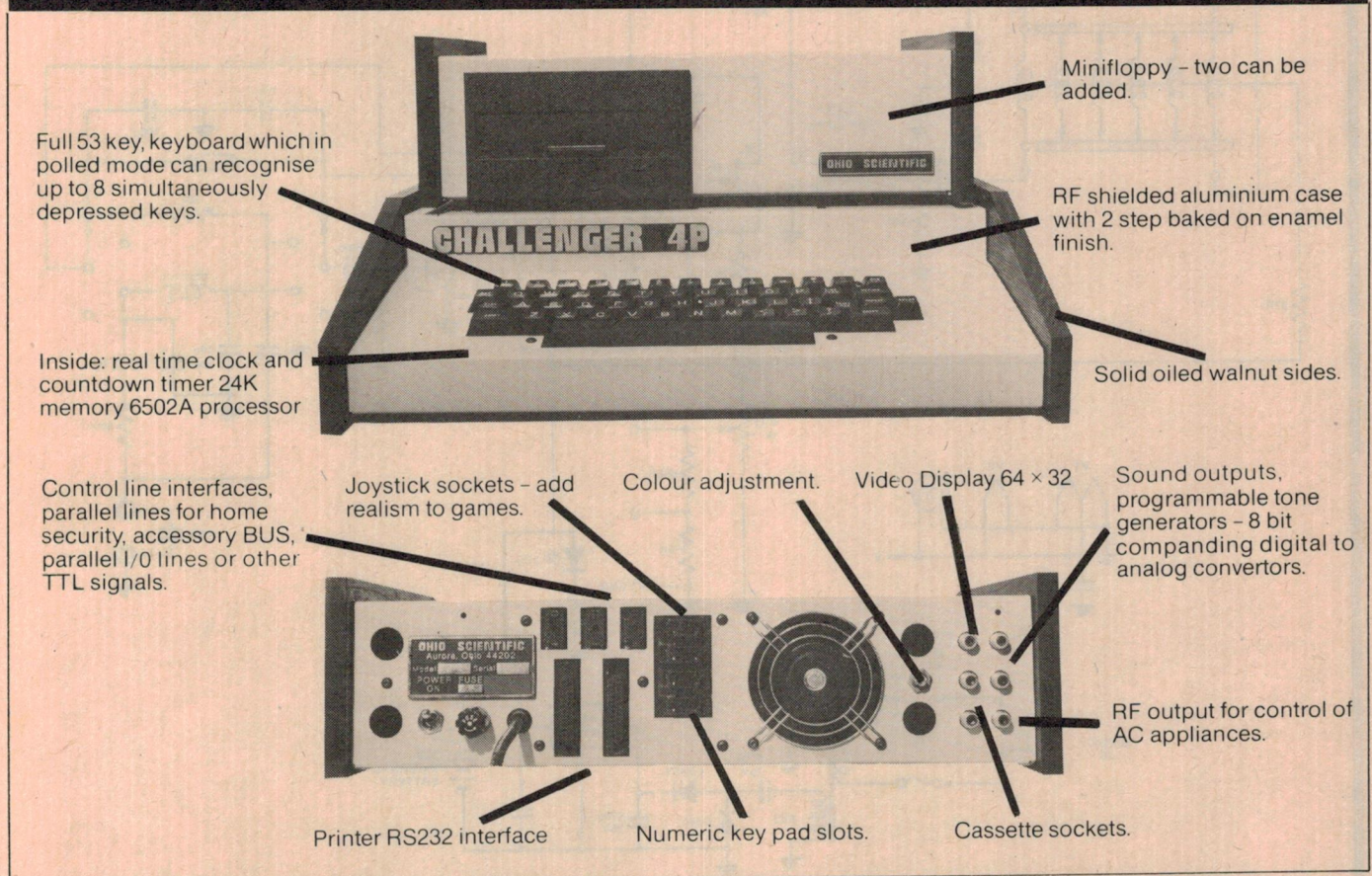
# The Challenger 4

Whichever way you look at it, no other computer offers so much for so little, and in colour!



You'd have to go a long way to get better value in a computer. It has execution speed that really separates the computers from the toys. We think the Challenger 4 is way ahead of anything you've seen so far, for a wide variety of uses including business, personal, educational and games, as well as a real-time operating system, word processor and a data base management system.

The Challenger 4 has a 2MHz 6502 processor, and if that's not fast enough we can supply the GT option with the 6502C processor, and 120 nanosecond memory which averages over one million instructions per second.

A real time clock and count down timer, a 64 x 32 display in 16 colours, including 8K memory in the cassette version, 24K for the minifloppy. A BUS structure allows easy plug in of extra memory or many more OHIO boards. The BUS means modularity. If you bought your vintage C2-4 in 1977 we can change the boards at a much lower cost than a new computer.

For the best surprise of all ask our opposition if they can provide all these facilities. When they can't, ask us!

For the complete list of dealers, please refer to listing on opposite page.

**OHIO SCIENTIFIC**  
TOMORROWS TECHNOLOGY TODAY

LOCKWOOD TCG4616 A


TCG Ohio Scientific Pty. Ltd.

31 Hume Street, Crows Nest, N.S.W. 2065

Phone: 439-6477



These pages are intended primarily as a source of ideas. As far as reasonably possible all material has been checked for feasibility, component availability etc, but the circuits have not necessarily been built and tested in our laboratory. Because of the nature of the information in this section we cannot enter into any correspondence about any of the circuits, nor can we produce constructional details.

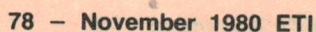





# The one-stop Microcomputer Shop for total service to TRS-80\* users

\*TRS-80 is a registered Trademark of Tandy Radio-Shack

## CISA

### NOW AVAILABLE CISA DISK PASCAL

Executes up to 60 times faster than DISK BASIC.  
HAS FULL DISK I/O FEATURES and many facilities not available on languages costing many hundreds of dollars.  
DO NOT CONFUSE WITH CHEAP CASSETTE-BASED 'TINY' PASCALS.

Systems overlays and developments will be available to registered users at a nominal charge.  
Includes the fastest and most powerful screen editor we have seen.

Will edit PENCIL, SCRIPSIT and ASCII files.

PASCAL is much easier to manipulate than ASSEMBLY, and is practically as efficient as it compiles into a true-optimized machine-code.

More efficient than currently available BASIC COMPILERS selling for twice the price.

We honestly believe that this Australian written PASCAL to be the fastest, most sophisticated and powerful high-level language available anywhere in the world for the TRS-80 Model I.

## RELEASE 1.0 \$99.00

(numbered copies to registered single-users only)

### CISA HARDWARE AND MODS

#### HEAVY DUTY POWER LINE FILTER

Essential in most domestic situations .....\$65.00

CISA LIGHT PEN (again in stock)

Includes full documentation and sample program.....\$19.95

#### CISA DATA DIGITIZER

Use this with HISPED program and you really have a business system in LEVEL 2. Requires no system modifications.....\$57.50

#### AUTOMATIC TELEPHONE DIALLER

Easy attachment to TRS-80. Requires no hardware mods. Complete with softwares and documentation.....\$57.50

#### 16K UPGRADE KITS

KEYBOARD KIT.....\$85.00

INTERFACE KIT (yes there is a difference)\$105.00

We fit — \$20.00 plus carriage \$5.00 overnight return.

#### DISK DATA SEPARATOR

These are the components that TANDY forgot. Virtually eliminates all disk I/O errors. Absolutely essential for 77 track users. We fit.....\$49.95 (sorry no kits)

#### GREEN PHOSPHOR TUBES

Not a cheap plastic overlay. We fit a genuine professional standard VDU tube with 1/4" armoured low reflective front panel. (no kits).....\$99.00 (fits old and new type Tandy VDU and current Dick Smith monitor)

#### CISA RS232 PRINTER-DRIVER

Operate any RS232 or 20MA serial printer with this Australian made unit. Includes software...\$54.75

#### LOWER CASE MODIFICATION

Get video lower-case for BOTH Scrpsit and Electric Pencil. Fitted.....\$49.95

#### VIDEO STABILISER CRYSTAL

Totally removes shimmer and wobble on your video. Highly recommended for Green Tube.

Kit.....\$19.95  
Fitted.....\$39.95

#### DUMMY PRINTER

Plug this into the parallel port of the interface and avoid system lockups if you accidentally type LLIST or LPRINT.....\$14.95

### TRS-80 SOFTWARE

#### AIR TRAFFIC CONTROLLER L2/16K

Supervise a large area of air-space in real time.....\$9.95

#### SPACE GAMES L2/16K

Five brilliant games in the classic space series.....\$14.50

#### STRATEGY GAMES L2/16K

Four fascinating games to test your judgement and logic.....\$14.50

#### ADVENTURE SERIES L2/16K

Adventure-1, The Count, Voodoo Castle. Each.....\$14.95

#### Z-CHESS

A fast and exacting opponent. 6 levels of play.

L2/16K.....\$19.95

Disk 32K.....\$24.95

DISASSEMBLER in BASIC L2/16K only

Disassembles ROM and high memory machine language routines.....\$9.95

#### TAPECHECK L2 16K plus

Checks and verifies every millimetre of a cassette tape. Also useful as cassette I/O diagnostic.....\$9.95

#### RS232 DIAGNOSTIC 32K/DISK

Interrogates, tests and reports on EVERY feature of Tandy RS232 board.....\$19.95

#### FLOPPY DOCTOR 32K/DISK

This is the most comprehensive and exacting series of memory and disk I/O tests we have seen.

From Micro-Clinic, USA.....\$29.95

#### SIMUTEK 7 separate packages

These seven packages are excellent value for any TRS-80 owner.....\$14.95 ea.

Plus many, many more.

### "HISPED" TAPE OPERATION

2K Baud PLUS for the TRS-80\*

- Save, verify and load programs up to 4 times faster than normal
- Save, verify and load array data up to 30 times faster than PRINT
- User variable hardcopy formatting (3 output routines work with most printers)

- "HISPED" is a machine language program (not a hardware add-on)

- 2 copies plus a free basic test program supplied on high quality cassette — for level 2, 16K, 32K or 48K.

MAKES STRINGY FLOPPIES REDUNDANT.

## \$24.95

Available only from Cisa and authorised agents.

### MICROPOLIS DRIVES FOR THE TRS-80\*

For the enthusiast: 192K bytes per drive.

SINGLE 77 TRACK.....\$699.00

A professional disk drive for the business user:

TWIN 77 TRACK 385K.....\$1499.00

Both complete with heavy-duty case and inbuilt power supply and free dospatch to TRSDOS.

Requires cables — 2 drive \$30, 3 drive \$40, 4 drive \$50.

MIX 'N MATCH with any 35 or 40 track drive.

SHOP WHERE YOU CAN BE SURE OF SERVICE  
BACK-UP AND YOUR WARRANTIES HONOURED.

### SOFTWARE FROM RACET

INFINITE BASIC \$49.95 L2 and DISK

Add 30 BASIC commands plus full MATRIX MANIPULATION.

Add 50 STRING functions, including high-speed sorts.

BUSINESS BASIC (requires INFINITE BASIC).....\$29.95

Another 20 functions including set printer parameters, 127 digit mathematical functions, binary array searches and hash code generator.

COMPROC Command Processor for Disk.....\$19.95

Auto your system to any sequence of DOS, machine-language or BASIC routines. Includes screen-print, auto debounce and lower-case software driver.

DSM Disk Sort and Merge Min 32K and Disk.....\$75.00

Sorts 85K diskette in less than 3 minutes.

Sorts 190K diskette in less than 6 minutes.

COPSYS for cassette systems.....\$14.95

Copy and verify virtually any machine-language program.

GSF 32K and 32K DISK.....\$34.95

18 high-speed machine-language routines including high-speed in-memory sorts.

Sorts a 1,000 element string array in 6 seconds.

### PHONE OR CALL AND BROWSE. TRADE ENQUIRIES INVITED

Trading Hours: 9am to 6pm Monday-Friday, 9am to 12.30pm Saturday.

All the above fine products are available at or can be ordered from:

**SOFTWARE-80**, Shop 11/198 Moggill Road, Taringa, Brisbane, QLD 4000. Phone: (07) 371-6996.

**SOUTH COAST COMPUTING SERVICES**, 90 Worrigea Street, Nowra, NSW. 2540. Phone: (044) 24967.

**THE BYTE SHOP**, Colbee Court, Phillip, ACT, 2606. Phone: (062) 81-5011.

**H.S. ELECTRONICS**, 104 Charles Street, Launceston, TAS, 7520. Phone: (003) 31-8942.

**WACB RADIO CENTRE**, 129 Fitzgerald Street, Perth, WA.

**TANDY ELECTRONCS**, Springers Arcade, Bowral, NSW, 2576. Phone: (048) 91-2092.

## CISA MICROCOMPUTING PTY. LTD.

159 KENT STREET, SYDNEY, NSW 2000. PHONE: (02) 241-1813.

Orders under \$100 add \$2.00 p and p. Over \$100 post free. For repairs and mods to systems — send by carrier — you pay, we pay return carriage.



# 'THE S100 BUS STOP'™


## SBC200



Z80 single board computer, 4MHz, 16K EPROM, 1K RAM, 16K EPROM, 1 serial port, 1 input & 1 output parallel port, power on jump, 2K monitor-2716 4 channel counter/timer, software controlled baud rate generator, modem look alike, vectored interrupt

KIT \$360.00 ASS & TESTED \$440.00


## MPB100

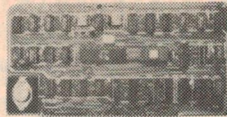

Z80 CPU board, switchable 2 or 4 MHz operation, power on jump to any 4K boundary, on board 2716 PROM socket, optional front panel provision, wait state generator, 2K monitor available, will suit dynamic rams.

Kit \$260.00 ASS & TESTED \$310.00


## 16K STATIC RAM

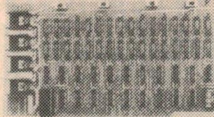

2114 low power RAM chips, 4K address boundary, standard bank select (40H) 4 MHz operation with no wait state required when using our chips, wait state generator for above 4MHz plated thru holes, solder resist, optional 300nS RAMS available.

KIT \$315.00 ASS & TESTED \$380.00

## 32-64K DYNAMIC RAM

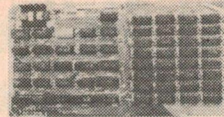

Bank select, 200 nS chips standard up to 4MHz speed, will accept 64K rams to give 256K per board, switch selectable boundaries, invisible refresh, phantom output disable, standard S100, plated thru holes, solder resist, components overlay.

KIT 32K-\$525 48K-\$670 64K-\$815  
A&T 32K-\$605 48K-\$750 64K-\$895

## 2708 EPROM



Switch selectable as 8 or 16K card 8K address boundary, wait state gen, suites industry standard 2708's standard S100, plated thru holes, solder resist.

KIT \$98.00  
ASS & TESTED \$125.00


## SERIAL-PARALLEL I/O PORT



Dual serial ports with RS232 & TTY outputs, nine programmable parallel ports, wire wrap cross link area for parallel I/O, switch selected baud rates, 9600-75 baud, 4 byte address decoding for I/O, switch selected, plated thru holes, solder resist.

KIT \$189.00 ASS & TESTED \$225.00


## SINGLE DENSITY DISK CONTROLLER

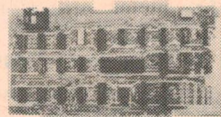

IBM 3740 soft sectored, operates standard 8" or 5" drives, single or double sided drives, utilizes FD1771 controller chip, runs CP/M disk opp software, operates with Z80, 8085 & 8080 CPU, CP/M, BIOS & diagnostic prompts to suit are available.

KIT \$258.00 ASS & TESTED \$308.00

## SINGLE/DOUBLE DEN. DISK CONTROLLER

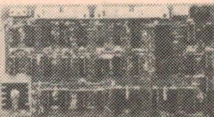

Operates with single & double den. single & double sided drives & 8" or 5" drives in any combination of 4 drives simultaneously, phase lock loop data recovery, with SDDS operating system you can run all CP/M and CDOS programmes.

KIT \$360.00 ASS & TESTED \$420.00

## 80 x 24 VIDEO



On board Z80, 80 char. x 24 lines, 7 x 10 matrix, keyboard interface, 96 up & lower character, 32 special characters, optional 128 extra char composite video, for/rev scrolling, XY address cur, blinking underline reverse video & field protect.

KIT \$380.00 ASS & TESTED \$450.00


## EPROM PROGRAMMER



2708, 2758, 2716, 2516, 2732 EPROMS switch selected, 26V generator, ZIF socket, CP/M driver program, max. time 100 sec for 16K bit EPROMS mod. available for TMS 2716 EPROMS, optional PROM based driver routines STD S100, plated thru holes.

KIT \$205.00 ASS & TESTED \$255.00

## EXTENDER/TERMINATOR

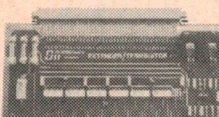

True active termination, fuse protect supply rails to extension socket, numbered test points, reset line (75) not terminated, solder resist, plated thru holes, standard S100 D.I.L. resistor packs, this board is a must for reliable operation.

KIT \$85.00 ASS & TESTED \$105.00

## WIRE WRAP PROTOTYPING BOARD



Now with plated thru holes, GND & supply rails on both sides, +5V +12V & -12V regulator provision, Hole array is .1 x .3 to suit all IC package sizes, provision for filter bypass caps, 5V reg is T03.

BOARD ONLY \$38.50


## TVI-912B TERMINAL



80 x 24 intelligent terminal, 2 page screen, printer port, dual intensity upper/lower case, 110-9600 baud, numeric pad, cursor control, XY curs block mode, self test, micro based laser siegler ADM31 look alike, full editing capabilities.

\$1295.00

## LA34 34 DECwriter

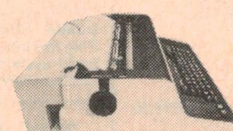

30 CPS, 128 char. set 110-300 baud 9 x 7 dot matrix, adjustable line and character spacing, opt. numeric keypad, light weight (13Ks), STD RS 232 serial com., opt. tractor feed, & paper roll holder, comes with friction feed as standard.

STANDARD VERSION \$1595.00


## Z80 STARTER KIT



Onboard keyboard & HEX display, Kansas City cassette, PROM programmer S100 interface, 2K RAM, 4K EPROM, 2K optional, 2K monitor, CTC timer, interrupts, 2x8 bit ports, wire wrap area, 120 page manual, single 5V supply, single step, breakpoints.

KIT \$350.00 ASS & TESTED \$420.00


## S-100 & 6800 CHASSIS

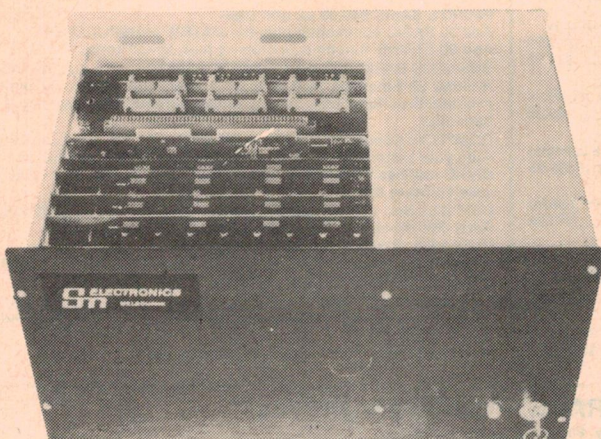

11 slot backplane, fully card guided. 15 amp power supply, fan, key switch, bench mount, rack mount, anodised aluminium. 5 edge connectors standard. S-100 Bench Kit \$345. S-100 Rack Kit \$306. 6800 Bench Kit \$370.00. 6800 Rack Kit \$330. Assembled prices add \$100.
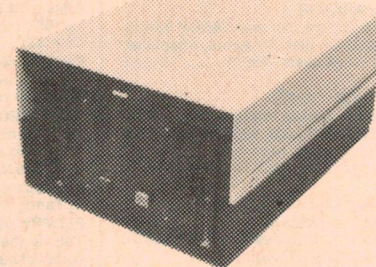
## PMS100

Introducing the PMS100 by SME Systems, an all new package microcomputer based on a Z80 CPU. This system will suit all users ranging from computer technicians, programmers and small to medium company accounting requirements.



Technical specifications are as follows:

4 Mhz Z80 CPU, 64K Dynamic memory with bank select to allow up to 8 pages of 64K each, and up to 256K of RAM on a single board, RS232 serial port and 8 bit parallel ports. Up to 16K EPROM which can be switched out after power up to allow a full 64K of user RAM per bank. Dual QUME 8" d/sided drives running at single or double density. Density selection is automatically chosen by the use of double or single density formatted disks. External Mini drives can also be interfaced to the controller. The DOS supplied is compatible with standard CP/M and CDOS to allow a wide selection of software to be used, such as MBASIC, CBASIC, COBOL, ALGOL, PASCAL, FORTRAN, ASSEMBLY LANGUAGE, WORD PROCESSING, MULTIUSER, MULTITASKING, AND ACCOUNTING PACKAGES. All of which can be supplied from SME Systems.

The PMS100 is AUSTRALIAN designed and built and can be supplied as a basic system or as a complete turnkey system including terminal, printer and software.

**Sm ELECTRONICS**  
MELBOURNE  
Ph (03) 842-3666

Trading hours: 10am-6pm Mon to Fri.

1096 Doncaster Rd, Doncaster East, Vic 3109.  
PO Box 19, Doncaster East, 3109. Telex AA37213.  
DEALER Canberra — 81-5011, Sydney — 661-9237.

Send 66c in stamps for HARDWARE CATALOGUE.  
CP — M user group software 43 volumes.  
CATALOGUE \$4.00

ALL PRODUCTS AUSTRALIAN MADE AND EX STOCK (ALMOST).  
DEALER ENQUIRIES WELCOME.  
Prices and specs. subject to change without notice.

All prices tax free, for retail prices add 15 per cent.


**bankcard**  
welcome here

Give name, number, expiry date and signature for mail order sales.

**SME**  
SYSTEMS



# Ideas for Experimenters

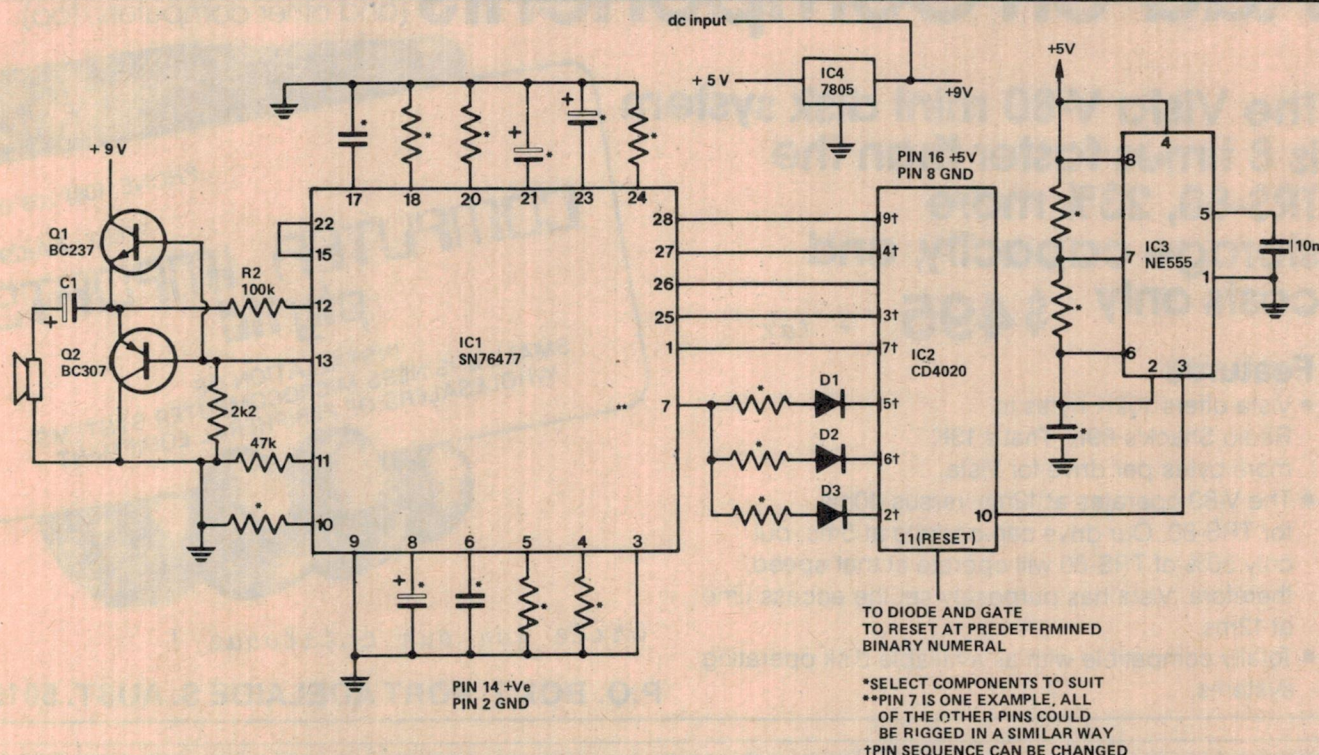

## Computer music — without the computer !

Those seemingly random musical sound effects one hears on movie tracks when a computer on screen is "thinking" are familiar to just about everyone. More recently, the sounds of 'machine music' have been heard. This circuit can be arranged to produce a whole range of similar sounds, play tunes, random notes and sounds, etc, with that familiar machine music sound.

Centred on a Texas Instruments SN76477, a 'sound synthesiser' chip, plus two other ICs, selecting the values of a group of resistors and capacitors will determine the 'sounds' you want, while selecting the speed of a 555 clock and the way the SN76477 is interfaced to a divider chip will determine the sequence of sounds to be played.

The 555, IC3, is connected as an astable multivibrator. The two timing resistors (between pins 8-7-6) and the timing capacitor determine the repetition rate. Consult the data on the 555 to select values for these components so that IC3 runs at the speed you wish (anything from say, 10 Hz to 1 kHz). The output of the 555 drives a 4020 divider and its outputs drive the SN76477 'function select' inputs. The

resistors and capacitors around the SN76477 marked with an asterisk are chosen from the data sheet and applications circuits to produce the desired sounds. Output from the SN76477 drives a simple audio power output stage (Q1 and Q2) and an eight or fifteen ohm speaker. C1 is a 1000 uF electrolytic.

So that the sound sequence repeats, the 4020 is reset using a diode AND gate. Note that the sequence of output pin connections of the 4020 can be changed around.

Pins 1, 9, 22, 25, 26, 27 and 28 on the SN76477 all require TTL level pulses (generally active high) to select the appropriate function. The table here shows what is selected when each pin is high and low (0 or 1).

G.P. Hicks (L/App) from the RAAF Base, Laverton, Victoria, who sent in the idea, says that a 4017 could be used instead of the 4020. He also notes that if the VCO resistor on the SN76477 is altered experimentally, and using a similar circuit arrangement to drive pin 7 as shown here, it may be possible to play tunes.

Pin 9 (system enable)	Pin 22 (VCO/SLF select)
0 (system enabled)	0 (VCO selected)
1 (system disabled)	1 (SLF selected)
Pin 1	Pin 28
0	0
0	1
1	0
1	1
Pin 27	Pin 25
0	0
0	1
0	0
1	0
1	1
1	0
1	1
1	1
Pin 26	Output (mixer)
0	VCO
1	SLF
0	Noise
1	SLF/noise
0	SLF/VCO/noise
1	SLF/VCO
1	inhibit

## Any ideas ?

Have you had a bright idea lately, or discovered an interesting circuit modification? We are always looking for items for these pages so naturally, we'd like to hear from you.

We pay between \$5 and \$10 per item — depending on how much work we have to do on it before we publish it.

The sort of items we are seeking, and the ones which other readers would like to see, are novel applications of existing devices, new ways of tackling old problems, hints and tips.



# The Supermarket for TRS-80\* Add-on Components (and other computers, too)

The Vista V-80 mini disk system is 8 times faster than the TRS-80, 23% more storage capacity, and costs only **\$495** + tax

## Features

- Vista offers 102K bytes to Radio Shack's 89K. That's 13K more bytes per drive for Vista.
- The V-80 operates at 12ms versus 40ms for TRS-80. Our drive can operate at 5ms, but only 50% of TRS-80 will operate at that speed; therefore, Vista has purposely set the access time at 12ms.
- Totally compatible with all available disk operating systems.



*Write for our catalogue !*

P.O. BOX 7, PORT ADELAIDE S. AUST. 5015


## Micro Computers From **INDUSTRIAL MICRO SYSTEMS** SERIES 8000: SYSTEMS WITH TIME PROVEN COMPONENTS

# SERIES 8000

Regardless of the size of machine you choose, there's room inside for up to 256k of IMS RAM with memory management. And the integrated floppy disk capacity is pretty impressive too — more than a million bytes per drive! You can start with a single 8" drive, then install one or two more when you need it — all in the same cabinet. The Series 8000 System's power supply and disk controller are made with this kind of expansion in mind so growing is simple. And our Z-80 computers have features like serial parallel I/O's, clocks, PROMS on board so that less slots are used on the S-100 12 slot motherboard, giving more space for extra RAM or special purpose boards.

Because the system is S-100 and CP/M based you can run all of the programs written for use with CP/M systems. (Like CBASIC, FORTRAN, COBOL, PASCAL, C, ALGOL, WORDSTAR etc). And you can go multi-user as well!

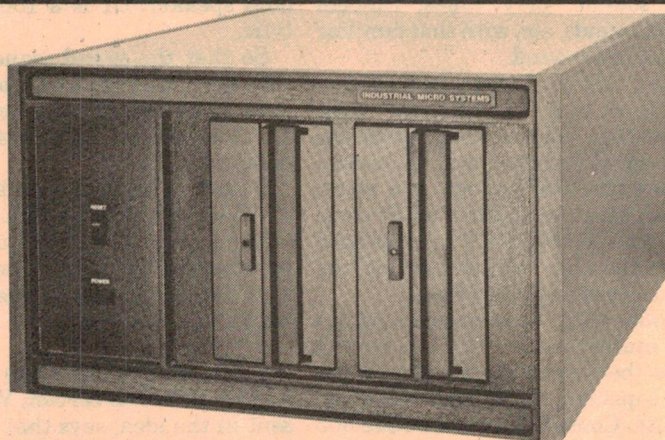CALL US FOR MORE INFORMATION ABOUT THIS SYSTEM OR IT'S LITTLE BROTHER WITH THE 5" DISKS — THE SERIES 5000.



# S.I. MICROCOMPUTER PRODUCTS PTY LTD

Formerly Sigma International Pty. Ltd.

GPO BOX 72 SYDNEY 2001

92 PITT ST SYDNEY

(02) 231 4091

232 6804



# Shoparound

THIS PAGE is to assist readers in the continual search for components, kits and printed circuit boards for ETI projects. If you are looking for a particular component or project — check with our advertisers if it is not mentioned here. Also, for a list of suppliers who stock the ETI projects published over the last few years, our "Kits for Projects" page may generally be found on the page immediately before the DREGS page (inside the back cover).

This month's projects are a mixed bag (we try to appeal to as many of the diversified readers' interests as we can each month) but little difficulty should be experienced in obtaining parts for all the projects. The only exception involves the **Takamisawa relay** specified in the Series 3000 Compact Stereo Amp.

## New Relays

The Takamisawa range of relays are a low cost, high performance line distributed here by Associated Controls Pty Ltd of 55 Fairford Rd, Padstow NSW, and 214-224 Wellington Rd, Mulgrave Vic. Of particular interest is the VB series which are almost identical to the relay type we have been using in projects over the past few years, but retail for a considerably lower price! The VB relays have either DPDT contacts rated at 5 A or SPST contacts rated at 10 A. Within the range, a whole variety of contact materials and coil voltages are available — from 3 V to 60 V.

We intend specifying these relays in projects in the future and our pc boards will be designed to accept both the older style relays and the Takamisawa VB series.

In Sydney, Radio Despatch Service, David Reid Electronics and George Brown are stocking these relays (less than \$3 over the counter at one-off prices from one supplier!). In Melbourne, the only supplier we could find was Stewart Electronics, 44 Stafford St, Huntingdale.

## The 3045/3046/3086

Those readers pursuing applications of this wonderful little transistor array IC, as featured in this month's Lab Notes, should have little difficulty in purchasing the IC in one form or another. According to the data sheet in Lab

Notes, it's not going to matter too much which number IC you choose out of the three, depending on the application. National Semiconductor (LM series) and RCA (CA series) make them.

Around Sydney, you'll be able to get the 3045/3046/3086 at Radio Despatch Service, David Reid Electronics and AWA Microelectronics (554 Parramatta Rd, Ashfield 2131).

Victorian enthusiasts are better served (lucky blighters!) as the IC can be obtained from All Electronic Components, Ellistronics, Magraths, Radio Parts, Rod Irving Electronics and Tasman Electronics.

## Projects

This month's feature project, the **Series 3000 Compact Stereo Amplifier, ETI-476**, should prove quite popular. Kits and components should be readily available, even as you read this, as we notified suppliers more than six weeks in advance of publication.

Just prior to going to press, those suppliers who indicated they would be stocking kits for this project were: All Electronic Components, Rod Irving Electronics and Tasman Electronics — all of whom are in Melbourne.

However, as we've used commonly available components throughout (except for the Takamisawa relay, but we've already told you about that), pc boards, cases, Scotchcal panels and all components will be available from the following suppliers: In Sydney — Radio Despatch Service, Electronic Agencies, David Reid Electronics; in Melbourne — Ellistronics, Magraths, Radio Parts (components, but no pc boards) in addition to those stocking kits just mentioned.

All components, printed circuit boards and Scotchcal panels will be generally available for the **Electronic Thermometer, ETI-255**, and the **Soil Moisture Indicator, ETI-247**. See October issue Shoparound, page 65, for details on the availability of Scotchcal front panels, meter scales and labels. The **ETI-475 AM Tuner**, featured in the September issue, is being stocked as a complete kit by All Electronic Components, we are advised. Printed circuit boards and all other components except the case are stocked by Radio Despatch Service. Following an unfortunate

initial delay, pot cores for this project are now obtainable.

Complete kits for October's feature project, the **ETI-568 Flash Trigger**, are stocked by All Electronic Components, Rod Irving Electronics and Tasman Electronics in Melbourne and Electronic Agencies in Sydney. All components, Scotchcal front panel and all, are available from Radio Despatch Service in Sydney.

Archeologists, treasure hunters and metal detector enthusiasts will be happy to know that All Electronic Components in Melbourne will be stocking pc boards, components and — most importantly — pot core coil kits for the **ETI-566 Metal Detector**, as revisited in Lab Notes in the October issue.

## AC output plugpacks

Most plugpack power supply units available have in-built rectifiers and filters and provide a dc voltage output. However, there are some applications where an ac output plugpack is required. The ETI-475 AM Tuner is an example.

There are several brands of 12 Vac output plugpacks on the market and you can obtain them with a 200 mA or 500 mA current rating. So far as we have been able to find out to date, the following suppliers stock one or another: In Melbourne — All Electronic Components, Rod Irving Electronics, Tasman Electronics; in Sydney — Radio Despatch Service. Dick Smith stores everywhere stock one rated at 12 V/500 mA output.

The PPB9/500 plugpack specified for the ETI-475 AM Tuner is also generally available through the same sources.

## Fastest zippy box in the west

Readers near and far, especially in West Australia, will be interested to learn that Altronic Distributors Pty Ltd of 151 York St, Subiaco 6008 W.A., has recently released a new style zippy box, as used with so many of our projects.

At first glance it looks like most other zippy boxes around — black plastic case, aluminium panel held on with four screws — but on closer inspection, it's cunningly different. They're Australian made and the inside walls are grooved to permit a pc board to be slid in vertically (in the conventional manner) but a tapered embossing with a 'stop' incorporated permits an appropriately sized pc board to be "snapped in".

The Altronic zippy boxes come in four sizes: H0101(UB1) measures 150 x 90 x 50 mm, H0102(UB5) is only 83 x 54 x 28 mm. Pricing and complete information is available from Jack O'Donnell, Altronic Distributors Pty Ltd, at the above address, or phone (09)381-7233.



# AT LAST... THE SYSTEM 80 IS REALLY A SYSTEM!

## NOW YOU CAN BUILD YOUR SYSTEM 80 INTO A SUPERB COMPUTER SYSTEM...

This is Australia's fastest selling microcomputer: the superb System 80 available only through Dick Smith Electronics (& authorised re-sellers).

However, until now, there has been a problem. The System 80 hasn't really been a system at all. Like a car without a tow-bar: useful, but limited in what you could do with it.

Now all that has changed: we're proud to announce the release of the System 80 S-100 Expansion Interface. The System 80, through its S-100 expansion interface, can now be used with hardware and software devices from over 200 different manufacturers. Just in case you didn't know, 'S-100' is the industry standard, which means you aren't tied to any one supplier for add-ons. A single supply source means that prices can be – and usually are – sky-high because there is no competition!

So now we expect the System 80 to really boom – not just to hobbyists, who've had it all their own way until now – but to businesses, to students, to housewives, to industry... There are virtually no limits to the System 80 system. All it takes is imagination.

And don't forget: software requirements for the System 80 are virtually the same as for the TRS-80: so most of the thousands of programs written for it will also run on your System 80 system!



**SAVE  
HUNDREDS OF  
DOLLARS OVER EQUIVALENT  
COMPUTERS AND HARDWARE!**

**FROM ONLY \$695<sup>00</sup>** (4K RAM,  
LEVEL II  
Cat X-4003)


**16K RAM, LEVEL II \$750<sup>00</sup>**  
MODEL (Cat X-4005)

### BUDGET MONITOR

The System 80 will run with any TV set: but in case you need a monitor, check this one out! P.S. This monitor will also work with most other micro-computers. Compare our prices and **SAVE!**

USE WITH  
ANY  
COMPUTER!

**\$149<sup>50</sup>**  
Cat X-1196

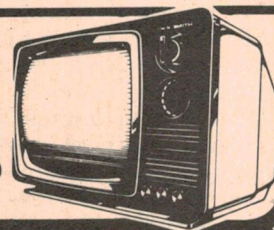


## NOW: FULL S-100 EXPANSION

Yes! It's here! Add the S-100 Expansion Interface to your System 80 for incredible versatility.

It gives you:

- All interface logic for the S-100 expansion bus.
- A floppy disk controller capable of controlling up to four single-density drives (such as our Pertec drives at right) for up to 400K bytes of storage capacity.
- A full Centronics-type parallel printer port.
- An RS-232C serial communications port, capable of communicating with modems and acoustic couplers. May also be used to drive a teleprinter or other serial printer instead of a parallel printer.
- Two vacant S-100 card sockets, to plug in further expansion items.

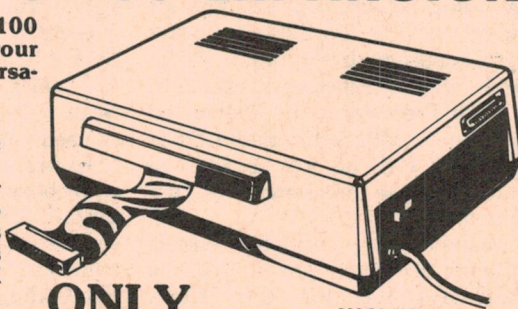

**ONLY \$499<sup>00</sup>** INCLUDING  
RS-232C  
PORT!  
Cat X-4010

### 16K (or 32K) CARD Just plugs into the expansion box...

Expand your System 80 Memory – up to 48K via the expansion interface. The plug-in card comes with 16K RAM, with room for another 16K. So with one card and our 16K expansion kit, you can have a full 48K! Much lower cost than TRS-80 expansion (currently \$220/16K!) Cat X-4016.


**\$199**  
INCLUDING  
16K RAM

**HUGE SAVING ON TANDY'S  
PRICE!**
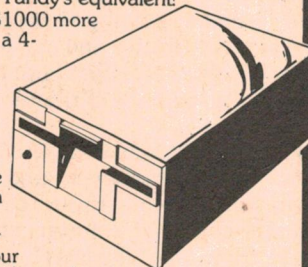
## BARGAIN PRICED MINI DISK DRIVE

\$200 less than Tandy's equivalent!

You'd pay over \$1000 more from Tandy for a 4-drive system! This incredible drive is world-famous Pertec brand; offers higher capacity than Tandy drive and will work with System 80 or TRS-80. Ask for more info. at your nearest Dick Smith store!



X-3230

**\$379**

## DISK PRICES TUMBLE!

Unbelievable prices for either hard or soft sector mini diskettes. Suit virtually all disk drives available. Buy from Dick and save a fortune!

Hard Sector (X-3505)  
Soft Sector (X-3510)

Trade enquiries  
welcome

**WERE \$5.95 EA! NOW:**  
1 – 10: \$4.95  
10 – 100: \$3.95  
100 UP: \$3.50




## ITOH 8300 BUDGET PRINTER

For budget printing, you can't go past this one! Uses standard tractor-feed paper, gives high quality print from its 7x5 dot matrix. Up to 240mm paper, prints 125 chars/sec. For either System 80 or TRS-80. Cat X-3255.

Uses Printer interface  
and cable below

**\$970**

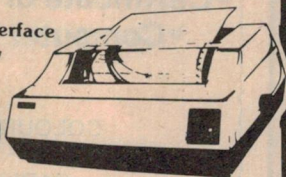

FAN-FORM COMPUTER PAPER  
TO SUIT ABOVE PRINTER. 2000 SHEETS

Cat X-1189. **\$35.00**


## LETTER QUALITY DAISY WHEEL PRINTER

For top quality print, try this: it's over \$300 cheaper than Tandy's daisy-wheel, and is capable of proportional printing! Limited stocks when they arrive.

Takes standard stationery!

DUE IN  
STOCK  
SHORTLY

Cat X-3265

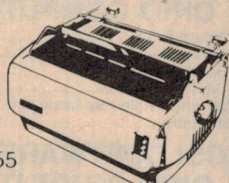


**\$1995<sup>00</sup>**

## PROGRAM CASSETTES

Popular C-10 computer cassettes (just the right size for programs!) with computer-quality tape. Suitable for all 'compact cassette' type units (which everyone uses!) Cat X-3500

**\$1<sup>95</sup>**

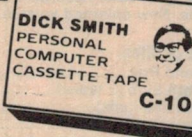

## SAVE A FORTUNE ON MEMORY IC'S

Were almost \$100 more twelve months ago! Fast 250ns 4116 RAMs, for upgrading your 4K or 8K to 16K, 16K to 32K or 32K to 48K. 8 IC's in pack. With full instr. Cat X-1186



**\$59<sup>95</sup>**

Also available individually.  
Cat Z-9310 .... \$7.90 ea.

## DON'T NEED FULL S-100 EXPANSION?

Use this parallel printer interface if you don't need full S-100 expansion. Save a bundle! Uses similar connecting cable to S-100 interface

**\$49<sup>50</sup>**

PRINTER CABLE Cat X-4013



Fitted with edge connector at one end, 57N-36 plug at other: suits virtually all Centronics-type printers. Use with either S-100 interface or parallel printer interface.

**\$39<sup>50</sup>**

Cat X-4014

## SOUND OFF

Add sound to your System 80 programs! Includes amp, programs and full instructions. You can add sound to existing programs too! Also suits TRS-80.



**\$19<sup>50</sup>**

Cat X-3648

## MICROSOFT™ EDITOR/ASSEMBLER PLUS!

Editing, assembling & debugging power you've never had before! Equivalent of Tandy's Editor/assembler and T-bug products but in one package and at less than half the price! And it's far more powerful! Suits System 80 & TRS-80.



**\$39<sup>95</sup>**

Cat X-3680

## LIGHT PEN BARGAIN! Cat X-3645

The best value around. Gives your System 80 or TRS-80 an eye. Easy to use, has simple programs

**\$9<sup>95</sup>**



## COMPUTER HOT LINE ...

Want to know more about our computers? Or are you having troubles? We've set up a special computer hot line just to help you out. Call between 9AM & 5PM on Sydney (area code 02)

**888 2002**

## SOFTWARE for System 80 or TRS-80

GAMES AND EDUCATIONAL SOFTWARE  
CURRENTLY AVAILABLE

**TIME TREK** ..... \$17.95  
You're boldly going where no man has gone before. Mind you, those pesky Klingons attack you from time to time, so you'll need fast reflexes, as well as sharp wits. Nine levels of difficulty. Cat X-3650

**STIMULATING SIMULATIONS** ..... \$17.95  
No less than 10 different games: all fascinating and original. Art Auction, Forest Fire, Monster Chase, Nautical Navigation, Lost Treasure, Business Management, Gone Fishing, Rare Birds, Space Flight and Diamond Thief. Cat X-3652

**ELECTRIC PAINTBRUSH** ..... \$17.95  
This is a special machine language graphics interpreter program, which lets you program dazzling graphics displays using simple high-level commands. Easy—and fun! Cat X-3654

**BRIDGE CHALLENGER** ..... \$17.50  
Keen on Bridge? This game never gets tired of playing with you. Ideal for practising and improving your level of play—whether you're an expert or just a beginner. Needs a 16K machine. Cat X-3656

**MICROCHESS** ..... \$22.50  
Think you're a whizz at chess? This program will put you to the test! But think out your moves carefully: the computer is out to beat you! One of the top selling chess programs in the USA. Cat X-3658

**BLOCKADE** ..... \$17.95  
You'll need fast reflexes and good co-ordination for this one. It's written in machine language so it can give really high speed graphics. Try to force your opponent into a collision with a moving wall: without running into a wall yourself! Cat X-3659

**PUNTER'S DREAM** ..... \$12.50  
Place your bets, please the race is about to start! Study the form of the various horses before placing your bets. Then the race is on! The program looks after the 'betting accounts' of up to nine punters, and can even cream off a percentage for the 'house'! You get a realistic simulation of racetrack probabilities. Use it for fun: or to improve your strategies! Needs a 16K machine. Cat X-3660

**BANDITO** ..... \$14.95  
Like playing the one-arm bandits down at the club? Here's one you can play seated at your friendly System 80! Tell the machine how much you want to spend, and it will feed it through. Watch the handle go down, the reels spin, and your money go! Then experience that familiar thrill when you hit a jackpot. Needs a 16K machine. Cat X-3661

**MATHS/SPELLING** ..... \$9.95  
Here's a great way to coach spelling and maths: imagine how much more interesting the lessons are if the computer is giving the problems! Help stamp out illiteracy and poor spelling—this great program can help you do it! Cat X-3662

**AIRMAIL PILOT** ..... \$12.95  
You're back in the early days of aviation. You must get the mail through in the shortest possible time. Your cloth-covered bi-plane must take you through unpredictable winds and electrical storms—can you make it? Cat X-3663

**INTERLUDE** ..... \$22.50  
This is the adults-only game for your computer. After the kids have gone to sleep, let the computer give you ideas for the rest of the night! It comes with a 'comprehensive' instruction manual! (Note: this program is NOT available to any person under 18 years of age). Do not purchase this program if you are easily offended. Needs a 16K machine. Cat X-3675

**SIMUTEK 1** ..... \$17.95  
Not just one, but FIVE superb space fantasy games. Includes Graphic-Trek 2000 (try to dock the Enterprise with the space station without being shot down), Invasion Worg (protect the Earth), Star Wars (get in to the Death Star, plant a Bomb and get out again!), Space Target (a battle game) and Saucers (an action graphics game). Complete with instruction book. Needs 16K. Cat X-3658

**POKER PETE** ..... \$15.95  
Like a game of poker? He's a pretty shrewd player—hard to beat, although it can be done. Has really intriguing graphics: needs 16K machine. Cat X-3664

**DEATH TRAP** ..... \$9.95  
How's your co-ordination? Escape from the minefield without getting caught: ready to try again. Only it gets tougher! This one has sound effects, too. Requires a 16K machine. Cat X-3688

**SPEED READING COURSE** ..... \$19.95  
A set of programs on two cassettes designed to help readers of all ages improve their reading skills. Written by a primary school teacher. Requires a 16K machine. Cat X-3692

**SCURVE INVADERS (Learning fun I)** ..... \$9.95  
A unique program combining basic maths drill with the ever-popular 'Space Invaders' game. Sound effects plus three levels of difficulty. Learning has never been so much fun. Needs 16K. Cat X-3694

**HANGMAN/CONCENTRATION (Learning fun II)** ..... \$9.95  
Great fun to play, but also increase familiarity with words. Two programs, can be played with two players or two teams. Requires 16K. Cat X-3696

**ALPHABET COUNTDOWN/RHYME TIME (Learning fun III)** ..... \$9.95  
Another two games which give players of any age practice in selecting and manipulating words. Gives percentage correct. Requires 16K. Cat X-3698

# DICK SMITH ELECTRONICS



SEE OUR OTHER ADVERTS IN THIS MAGAZINE FOR OUR STORE ADDRESSES AND RESELLERS



## SORCERER OWNERS!

Upgrade your existing 8K Basic with the new Software Source Mod 1.01. Makes your Basic into a Superbasic with capabilities that outstrip even some Disk Basics.

- Full input checking to eliminate unseen syntax errors and line overflows.
- Redo from start if type mismatch in input statements.
- Save numeric arrays with confidence.
- Full line editing on input — change part of line without retyping it all.
- Full selective renumbering — move your subroutines around; make a hole to insert more text.
- Delete any block of lines.
- Full recovery of program after accidental reset.

Available only for Exidy Standard Basic version 1.0.

Basic Mod 1.01 (include Rompac with order).....\$125.00

### OTHER SOFTWARE AVAILABLE

String Saver: save Exidy Basic string arrays.....\$37.50  
 Edit: merge/renumber/edit Basic programs.....\$35.00  
 Moneychart: chart cashflow of any business.....\$58.00  
 Management Report: see where & how money is spent.....\$53.00  
 Supercalc: Sorcerer becomes a 'supercalculator'.....\$12.50  
 Util 3: Use your development pac efficiently.....\$24.50  
 Life: play Conway's game superfast.....\$8.50  
 Biochart: Plot your biorhythms fast.....\$2.50  
 Grafix: Define Sorcerer graphics quickly.....\$17.50  
 MDOS: Patch Micropolis Basic for 40 percent speed increase requires your MDOS master disk.....\$24.00  
 Uploaders: Save Basic programmes easily on MDOS.....\$24.50  
 CP/M Programmes: (Lifeboat or Exidy formats on 5 1/4 Quad)  
 Q. Sorted CP/M directory.....\$24.50  
 Compare: Compare two disk files.....\$24.50  
 Fix: View/alter any byte on the disk.....\$24.50  
 Spellbinder: Super disk wordprocessor specially configured for Sorcerer.....\$299.00  
 C.10 Digital Cassette Tapes, box of 10.....\$9.50  
 16 Sector 5 1/4 Diskettes. Single Density, box of 10.....\$45.00  
 Quad Density, box of 10 plus free library case.....\$67.50  
 Software Source can offer memory expansion and disk expansion for your Sorcerer at reasonable rates. We are experts on Sorcerer, and will offer full advice on compatibility of peripherals. Talk to us first. Send cheque/money order to:

SOFTWARE SOURCE, PO Box 364, Edgecliff, 2027.

All prices inclusive. For free catalogue send SAE.  
 Need specialised software? — call us, we can help.

## SOFTWARE SOURCE

Phone (02) 33-4536

## LOOPY VIDEO

Shop: 418 Bridge Road, Richmond, Vic.  
 Mail: PO Box 347, Richmond, 3121, Vic.

Second hand video recorders and tapes, cheap. Also new.

### OSI HARDWARE FOR OHIO COMPUTERS

Superboard II.....\$367.00  
 SII Covers/VDU Stands (plastic).....\$18.95  
 RF Modulators 5/9V.....\$19.95  
 4K RAM Kits.....cheap  
 EPROM with single Key Basic and  
 Cursor control.....\$54.95

### OSI SOFTWARE FOR OHIO COMPUTERS

Almost 100 varieties for C1P/SII.  
 Many available for C2/4P; enquire.  
 Categories are: Games, Education, Business, Text, Instructions (Modifications), and Utilities.  
 K.2 Catalogue, Brief descriptions of all programs, free hints. New enlarged version. \$3.50 plus \$1.00 P&P.

#### Example of titles:

G33. Grand Prix.....\$9.95  
 G28. Death Ship (2 tapes).....\$18.95  
 U16. Filename (tape).....\$8.95  
 U19. Cursor/Editor C2/4.....\$11.95  
 U20. Mini-Assembler.....\$9.95  
 U21. Single Key Basic.....\$9.95

Now available blank digital tapes.

C10 \$1.85 ea. Less for lots of 10 or 100.

Mail orders allow postage. eg: OSI Software 1 or 2  
 \$1.00, 3-5 \$1.50, 6-9 \$2.00, 10 or more items \$2.50.

All prices INCLUDE sales tax.

Prices subject to change without notice.

## ELECTRONICS COURSES

FULL OR PART TIME

- Post Trade
- Technician
- Certificate of Technology
- Computer Service

COLOUR TV  
 AMATEUR — HOBBY

RADIO  
 COMPUTERS  
 COMMUNICATIONS  
 INDUSTRIAL CONTROL  
 MICROPROCESSORS  
 MOTOR SPEED CONTROL  
 DIGITAL

Box Hill  
 TECHNICAL  
 College

991 Whitehorse Rd  
 Box Hill 88 0691

COMPLETE COMPUTER SYSTEMS FROM \$990 TO \$90,000 — HOBBY TO PROFESSIONAL BUSINESS. TELL US YOUR NEEDS AND WE WILL BE DELIGHTED TO SUPPLY BROCHURES, FULL DETAILS, PRICES ETC.

### The CBM Computer Business System

— with standard software

also


### Commodore Pet

\$999 incl. \$153 of programs


and
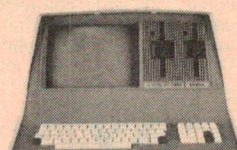
### APF Home Computers

Complete home colour system — one only left at \$990.



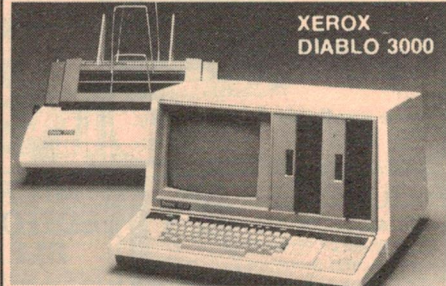INTERTEC COMPUTERS — twin Z80's using full business software plus language options of Basic, Fortran, Cobol, APL, PASCAL, etc. Hardware fully expandable.



XEROX  
 DIABLO 3000

### CALCULATORS

#### HEWLETT-PACKARD

Count on quality — use HP's

HP41C Calculator.....\$374 (\$336)  
 HP41C Accessories.....\$273 (\$245)  
 Card Reader.....\$489 (\$439)  
 Memory Modules.....\$56.40 (\$49.10)  
 Application Packs.....\$56.40 (\$49.10)  
 Solution Books.....\$15.70 (\$13.60)  
 Thermal Paper.....\$7.50 (\$6.50)  
 40 Mag Cards.....\$25.10 (\$21.80)  
 HP34C, 210 steps.....\$192.50 (\$173)  
 HP33C, 49 steps.....\$155 (\$134)  
 HP33E, 49 steps.....\$117 (\$105)  
 HP32E, Sci/Stats.....\$91.50 (\$82)  
 HP31E, Scientific.....\$66 (\$59)  
 Also HP97, HP29C, HP38C, HP38E, HP37E.  
 HP ONLY — POST FREE

### CASIO — fx502/FAI LCD PROGRAMMABLE



25 steps, 22 memories, FAI adaptor interfaces an ordinary cassette for program storage. Manual and huge book of programs. Continuous memory.

FX502P \$149 (\$135)  
 FAI \$43.50 (\$39)

### TEXAS

TI55, 32 steps, 10 mem.....\$61 (\$54)  
 TI58C 480 steps, 60 mem.....\$149 (\$132)  
 TI59, 960 steps, 100 mem.....\$299 (\$265)  
 PC100C Printer.....\$238 (\$210)  
 Module for 58C/59.....\$39 (\$34.50)  
 Pakettes for 58C/59.....\$9 (\$8)  
 Thermal Paper PC100C.....\$12 (\$10.50)  
 40 Mag Cards 59.....\$15 (\$13.50)

PACKAGE DEAL  
 FINAL WEEKS  
 TI59 and PC100C  
 \$510 (\$450)

### SPECIALS

APF 5602 LCD 40 funcs. \$21.50 (\$19) BELOW COST.

NATIONAL  
 SEMI-CONDUCTOR  
 LED,  
 RECHARGEABLE.

4650 \$21 (\$18)  
 40 funcs.  
 4640 \$29 (\$25)  
 60 funcs.  
 3 memory & RPN.

### PRICES IN BRACKETS EXCLUDE SALES TAX

Pack and Post — all LCD models \$1.50 anywhere in Australia (except Casio fx502p). Otherwise \$4 for registered post in NSW, \$5 elsewhere.



Sales Tax forms available.

Copy and complete  
 Please debit my Bankcard \$.....  
 No.....Expiry Date.....  
 Signature.....  
 Name.....  
 Address.....

CALCULATOR AND COMPUTER DISTRIBUTORS  
 INCORPORATING ELECTRONIC CALCULATOR DISCOUNTS

PHONE (02) 624-8849  
 PO BOX 106, BAULKHAM HILLS  
 2153



# LETTERS

**Dear Sir,**

As dedicated manufacturers of high fidelity amplifiers we were pained by your September editorial. We wholeheartedly agree with you that tariffs ought not to be used to protect insignificant industries, hi-fi not excepted, but why must you assume that our hi-fi industry is bound to stay 'miniscule'? Does this sort of attitude advance Australia?

If you employed the reverse attitude and gave a little publicity to the forty-plus companies in Australia currently manufacturing audio amplifiers and the substantially greater number producing loudspeakers and ancillary equipment, perhaps these companies could become large enough either to merit the tariff protection they are now receiving or not to need such assistance at all. This is not to say that Australian companies could ever compete with cheap budget equipment, but they could easily perform well at the middle and high end of the market.

We venture to suggest that, like us, other manufacturers are experiencing acceptance from overseas markets and heavy going within Australia.

A little 'intelligent investigation' might reveal an industry waiting to burst into life, given a little media coverage and awareness. How about publishing a series of articles on Australian domestic hi-fi equipment? It might provide interesting reading for many enthusiasts and be an example of positive thinking by the media which would eventually filter down to all Australians.

**Peter A. Stein  
ME Sound Pty Ltd  
Dyers Crossing, NSW**

*Taking last things first, we are always delighted to publish articles on Australian made domestic hi-fi equipment. You, and the readers of like mind, should be delighted with the review of the Audiosound AM101 tuner on page 138 of this very issue.*

*Where are the "forty-plus" companies that comprise "our" domestic hi-fi industry? Why do you all hide your collective lights under a bushel... or a wool bale, or whatever? Don't be bashful. If you're proud to be Australian, tell everybody. Let us know what you're doing — regularly. To put the ball back in your*

*court, why have you never submitted any of your equipment to us for review? Why don't we have a file of press releases or news items from you? We don't get any, that's why. If we don't get anything, we can't print anything. If we don't print anything, nobody gets to hear about you. If nobody gets to hear about you, nobody knows who you are... etc. If you succeed at exporting, clearly you've put some effort into it. Have you put the same effort into local promotion? If you've had little result from local promotion, do you know why?*

*We don't say the local 'domestic hi-fi' industry (miniscule or not) doesn't deserve tariff protection — but you're going to have to promote yourselves if you want recognition.*

**Roger Harrison  
Editor, ETI**

**Dear Sir,**

Your illustration of the Sinclair DFM in the August issue of ETI was to me like the proverbial red rag to a bull.

Sinclair used to market quite good expensive hi-fi units world-wide until it switched into the more profitable field of computers and suchlike. When it abandoned the hi-fi business, what did it do about the many thousands of Sinclair amplifiers and FM units already in the hands of consumers? Quite simply, it washed its hands of all responsibility!

When my Sinclair amp broke down I wrote to Sinclair requesting semiconductor specifications as the required transistors could not be physically identified. I received a duplicated letter in reply, which said in effect, "Sorry, we are no longer in the market and therefore cannot assist".

I wrote to an English magazine, complaining bitterly, and they must have forwarded my letter to Sinclair because eight months later I received a reply from Mr Clive Sinclair's office. Sinclair Radionics did not exist any more and Mr. S was busy launching his new computer!

It's not unreasonable to suppose that if Sinclair doesn't make a success of DFMs and computers it will give that away too with the same 'devil take the hindmost' attitude.

If a company goes bust, then that's just bad luck — these things happen. But to

merely shift emphasis to an allied field and wipe the slate clean in respect of service responsibilities is downright diabolical!

I would be gratified if this matter could be aired in your magazine. There are still many ardent hi-fi buffs who swear by the products of the 'mother country' from manufacturers like KEF, SME, Rogers and Quad for example. But it's no wonder that as a nation we now buy most of our products from Japan. The Japanese give service!

**Ian Stuart  
North Balwyn, Vic.**

*We can understand your anger at being 'caught' with a now-useless piece of equipment and sympathise wholeheartedly. The editor was caught himself, in a similar fashion, some years ago. The history of some of the Sinclair enterprises has certainly been "chequered", to put it mildly.*

*However, there is no reason for you to transfer your anger or anxieties about the situation to Sinclair instruments, calculators and computers. These are marketed in Australia by Consolidated Marketing, under the banner of Sinclair Equipment (Australasia) Pty Ltd, of 308 High St, Kew, Vic 3101; phone (03) 861-6224. The company provides after-sales service on all the Sinclair products distributed here by them. They are, in fact, Sinclair service agents for the Australasian-Pacific region, according to Mr Julian Barson whom I rang before composing this reply.*

*It is easy to understand your reluctance, and that of other consumers, about buying products from a company or companies where there has been a history of collapse and no follow-on service. It may not be peculiar to British products, but the availability of local service, and particularly long after the product has been superseded, does wonders for the image and goodwill of a company. As you say, this is where the Japanese companies excel, and consumers give them the custom. The message is clear — he who gives the service gets the repeat custom.*

**Roger Harrison,  
Editor, ETI**

**Dear Sir,**

The Electromyogram biofeedback project that David Tilbrook designed (Sept/Oct 1979) has proved to be most useful to me and is in daily use.

I find it is particularly helpful in teaching relaxation techniques to patients and in encouraging active movement in poorly functioning muscle groups.

**Margaret Goldfinch  
Prince Henry Hospital, Sydney**



# TRANSFORMERS for MICROPROCESSORS



**PF4405**  
9 Volts @ 10 Amps  
Two Windings each  
15 Volts @ 1 Amp

**PF4354**  
9 Volts @ 10 Amps  
9 Volts @ 1 Amp  
Two Windings each  
15 Volts @ 1 Amp

**PL158/15VA**  
8 Volts @ 500mA  
Two Windings each  
14 Volts @ 400mA

**PL30-9/40VA**  
9 Volts @ 3 Amps  
Two Windings each  
15 Volts @ 500mA

**PL30-9/60VA**  
9 Volts @ 5 Amps  
Two Windings each  
15 Volts @ 550mA

**PL161/5VA**  
8 Volts @ 200mA  
12V-0-12V @ 150mA  
*Designed to suit standard PCB grid  
— pins centred at 0.1 inch.*


SEND FOR A DATA SHEET

**FERGUSON**

FERGUSON TRANSFORMERS PTY LTD  
331 High Street  
CHATSWOOD, NSW. 2067  
Tel: (02) 407-0261  
Melbourne: (03) 329-6415

**AUSTRALIAN MADE**

## S/09 -the mighty micro-mini

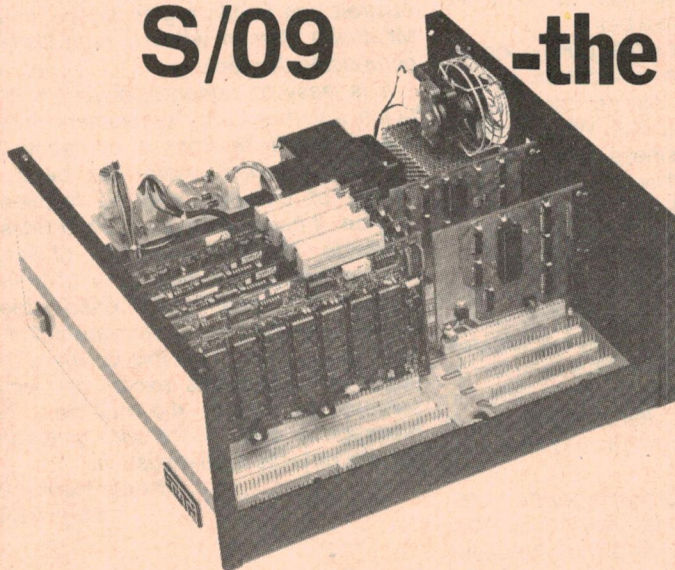

### MC 6809 PROCESSOR — 20-BIT ADDRESS BUS DIRECTLY ADDRESSES UP TO 768K OF RAM


- Uses Motorola MC 6809 processor — 8 bit general purpose MPU.
- 24 indexing submodes.
- 20-bit address bus enables direct addressing of up to 768K of memory on RAM.
- "Built-in" multi user capability.
- The dual-bus motherboard design used in the S/09 makes adding I/O ports to the system quick and economical.
- All serial I/O cards may be quickly programmed to run at standard baud rates from 110 to 38,400.
- Basic, Pascal and Assembler immediately available.
- Edit and Debug programmes available for Systems Development.

S/09 with 128K bytes of RAM memory, one parallel and two serial I/O ports .....\$3,350  
Prices plus Sales Tax if applicable, subject to change without prior notice.



**SOUTHWEST TECHNICAL  
PRODUCTS CORPORATION  
OF AUSTRALASIA**

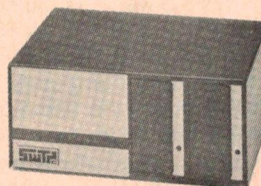7a BURTON STREET, DARLINGHURST, NSW. TEL (02) 357-5111.




**D-5** Two double sided, double density, 5" disk drives with a total on line capacity of 720,000 bytes of data. Includes cabinet, power supply, connecting cable and controller. Controller will operate up to four drives. \$1,395



# READER OFFER

## computer books

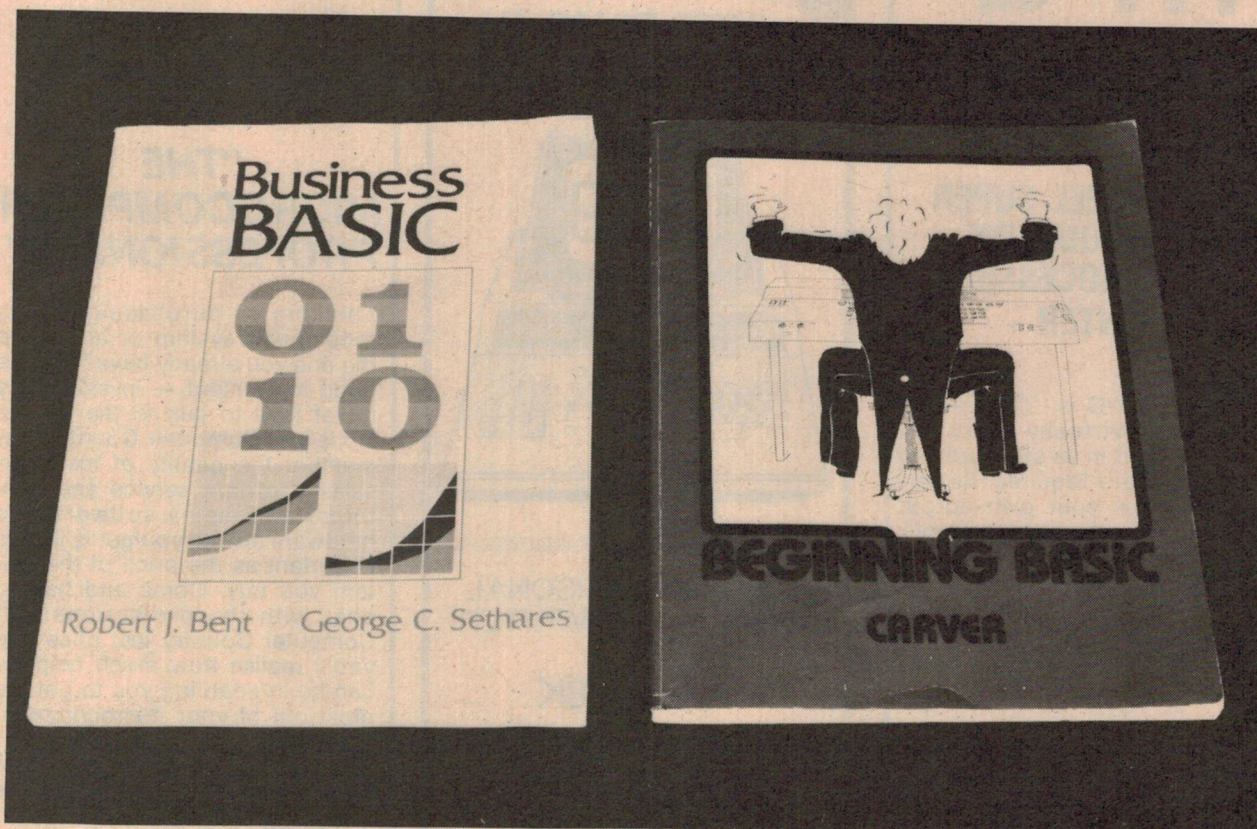

### Beginning BASIC

Carver

Beginning BASIC is not *just* another programming text. It is "... written for the true beginner in the world of programming. The important concepts are explained simply, yet with enough detail to enable the reader to understand why a particular programming technique is used. Short, simple and, for the most part, *nonmathematical* examples illustrate each programming idea or BASIC statement. In addition, flow charts have been used extensively throughout the book to illustrate the logic of various programming methods. These flow-charts, in conjunction with sample programs and narrative, provide the student with multiple means of assimilating the ideas of programming."

The above is a precis of the author's introduction to the book and neatly sums up what it's all about. Nine chapters, 200 pages; 280 x 215 mm.

**PRICE:** **\$10.95**  
post & handling \$1.50

### Business BASIC

Bent & Sethares

"This is great for the first-time business user with no previous computer or programming experience. There's a brief look at hardware and software, leading on to exercises in problem solving and the first program. Small business users who have ingested the contents of this book will be able to converse on much more equal terms with slick salesmen and white-coated experts."

The above is a review of this book by ETI staffer Elaine Ray, published in the September 1980 issue, page 89. Fifteen chapters, 223 pages; 280 x 215 mm.

**PRICE:** **\$11.95**  
post & handling \$1.50

NOTE: This offer is made by Wadsworth Publishing Co. (A'Asia) and ETI is acting as a clearing house only. Cheques or money orders should be made payable to **COMPUTER BOOKS OFFER** and sent, together with this coupon (or photostat) to "Computer Books Offer", ETI magazine, 15 Boundary St, Rushcutters Bay NSW 2011. We will process your order and pass it on to Wadsworth who will send you the goods. Please allow up to four weeks for delivery.

Enclose cheque or money order to total value and mail this coupon to:

#### COMPUTER BOOKS OFFER,

ETI Magazine, 15 Boundary St, Rushcutters Bay NSW 2011

Beginning BASIC (Carver) ..... (\$10.95) .....

Business BASIC (Bent & Sethares) ..... (\$11.95) .....

Post and handling (\$1.50 per book) .....

TOTAL \$ .....

Cheque or Money Order No: .....

Signature .....

(Please *print* name and address clearly)

Name .....

Address .....

..... Postcode .....



# XYMEC HY-Q 1000

**DAISY WHEEL SUPER  
LETTER QUALITY  
WORD PROCESSING  
PRINTER**

The XYMEC HY-Q is "Tomorrow's Printer" with virtually every advancement built in as standard. No other options are required. Its versatility matches your own output format and it can be used as an off-line typewriter with all the same capabilities.

Software select:  
Normal print  
Normal print, underlined  
Bold print  
Bold print, underlined  
**Reverse print**

Sample shown of the XYMEC HY-Q 1000 above is actual size.

**\$3250**  
including tax

**COMPUTERWARE**  
305 La Trobe Street,  
Melbourne, Vic, 3000.  
Telephone (03) 602-1006.

**THE  
MICROCOMPUTER  
HOUSE PTY. LTD.**

19 William Street, Alexandria,  
NSW 2015. Phone (02) 699-4334.

**JUST PLUG IN  
AND COMPUTE!**



**PET** PERSONAL  
COMPUTER

**USER 8K  
USER RAM  
CASSETTE  
MONITOR**

**\$999** complete

Call in and see our

### Microcomputer House

- Specialised custom software for all your business applications
- Software development
- Conversion from 16K to 32K
- Sound units
- Exciting range of executive furniture for microcomputers from \$285.00
- Extensive range of technical publications for 6502
- All microcomputer supplies

Sole NSW agents for  
**DATASOFT**

- Business programmes covering a wide variety of standard business applications — accounts, estate agent pack, hotel database, portfolio management, Wordpro II and III
- Games and simulations — fast moving, quick thinking, exciting. See our extensive range.

**TEACH YOUR PET NEW TRICKS**  
Select your software and try now.

*Computer  
Country  
Pty. Ltd.*

## "THE MICROCOMPUTER PROFESSIONALS"

Thinking of purchasing a microcomputer system or adding to the one you already have? Make a good investment — invest a little bit of time to talk to the professionals at Computer Country. Remember the quality of the after-sales hardware service and continual after-sales software and hardware advice you get is just as important as the price of the system you buy. Come and have a chat with the professionals of Computer Country just once and you'll realise how much help we can be in enabling you to get the most out of your microcomputer system.

Computer Country stocks a wide range of microcomputer hardware including the Apple, Northstar, Commodore, Texas Instruments, NEC, Impact Data and many more. We carry a wide range of software for many systems including the TRS-80. We can also help you in customising software for your specific application.

Our service department not only completely backs up all hardware purchased from us, but invites enquiries from those who have purchased elsewhere and have hard-to-fix problems.

**MAKE A SMART MOVE  
— COME TO**

*Computer  
Country  
Pty. Ltd.*

**338 QUEEN STREET,  
MELBOURNE, VIC 3000  
(03) 329-7533**



# Print-out

## The Compucolor II microcomputer

After putting this machine through its paces we're not surprised it's America's fourth best selling small computer.

**A fully integrated system based on the 8080A microprocessor, the Compucolor is a sophisticated and very usable machine that represents good value for money.**

Its most attractive feature is obviously its colour graphics capability. Eight 'primary' colours can be selected by keys at the left of the keyboard, namely red, green, blue, magenta, cyan, yellow, white and black, and by using various combinations of these basic colours the makers say that as many as 56 different 'secondary' colours can be generated. Sixteen PLOT functions make it easy to generate an astonishing variety of patterns without getting involved in complex programming. For example to draw a straight line it is only necessary to specify the end points. There are 16384 separately addressable plotting blocks arranged in a 128 x 128 array.

The 33 cm screen can also display 32 lines of 64 characters. The 64 standard ASCII characters are formed in a 5 x 7 dot matrix within a 6 x 8 dot pattern and there are also 64 special characters, including chess symbols and playing card suits, which use the whole 6 x 8 dot matrix.

The keyboard is standard ASCII, four level coded with 132 codes. Seventy two crossbar commercial keyswitches are provided, including CPU reset and automatic (single chip driven) disk loading.

The built-in minifloppy disk drive uses double-sided, segmented 40-track disks with a density of approximately 19 tracks per cm, giving a total storage capacity of 51.2K per side. Transfer rate is 76.8 kilo-

bytes per second and access time is 200 milliseconds.

The Model 5 Compucolor II has 32K of user RAM, against the 8K and 16K provided on the Models 3 and 4, but these two can both be expanded up to 32K by means of extra RAM modules.

The CPU clock period is set at two microseconds and there are a total of 512 input/output ports, of which only 25 are implemented in the standard unit, leaving 487 spare ports, which obviously give the Compucolor considerable scope for applications involving lots of peripherals.

The disk operating system includes a comprehensive range of file control commands. For example, pressing the AUTO key instructs the system to search for a 'MENU' program on the disk, load it and run it to display a list of disk contents. The 'DIRECTORY' command lists all the files on one side of a disk, detailing their names, addresses and lengths.

At the back of the unit is an RS-232 interface for connecting a printer or modem. The baud rate at this interface can be independently software controlled on a range of seven rates between 110 baud and 9600 baud.

BASIC, Fortran and Assembler languages are all contained in ROM. There are 25 statement types, five command types, 18 mathematical functions and nine string functions. The disk file commands include copy, device, directory (mentioned above), initialise, load, print, read, re-name, save, run and write.

A wide range of video games software is available and new items are being introduced all



the time. Real time colour games obviously make the Compucolor very attractive to children, which is one reason why it's probably the best small computer for use in schools. Any intelligent child, even a six-year-old, should be able to make the transition from games to programming without any difficulty.

The Compucolor's ability to display statistical information in the form of bar graphs, histograms or two-dimensional curves make it a very useful educational aid in the sciences and especially in the social

sciences. Since it's very easy to 'boot up' the machine, to load it and to reset it, it's clear that there's a great future for it in the classroom. Here at last is something that turns children's obsession with the TV screen to educational advantage.

The Compucolor II is distributed by Anderson Digital Equipment Pty Ltd, P.O. Box 322, Mt Waverley Vic 3149; (03) 543-2077. Our review machine came from The Logic Shop who are at 212 High St, Prahran Vic 3138 and 91 Regent St, Chippendale NSW 2008. Phone (03) 51-1950 or (02) 699-4910.

Elaine Ray

## Microcomputer Handbook

**Recently published by Computer Reference Guide of Chatswood, NSW, the "Australian Microcomputer Handbook" has 11 chapters on microcomputers and micro systems plus detailed summaries on the range of micros and desktop computers sold in Australia.**

The first section covers everything from Architecture of the CPU to Word Processing, BASIC programming to User markets. The second section covers all the machines from A1 Electronics to Zenith and Zilog. The book sells for \$22, including post and handling.

Last month's issue carried a loose insert on this book. If you missed it, a copy can be obtained from Computer Reference Guide, Suite 204, 284 Victoria Ave, Chatswood NSW 2067. (02) 411-2567. Mention ETI.



## Portable micro has unique features

The Findex microcomputer is a completely integrated, portable system that weighs only 14 kg, and features bubble memory and gas plasma display.

**Not much larger than a portable electric typewriter, it contains a CPU, keyboard, floppy disk drive or bubble memory, gas plasma display and plain paper printer. You can obtain an acoustic coupler as an option and a built-in rechargeable battery that gives enough power for one hour's use.**

The system is built around the Z-80 microprocessor, with a clock rate of 2.8 MHz, but it can also be supplied with the 4 MHz Z-80A. Standard dynamic RAM provision is 48 kilobytes, expandable to 2 megabytes, and there is 1K of static RAM. The ROM capacity is 8 kilobytes, expandable to 32K.

The model 100TD has a single minifloppy disk drive that holds 200k bytes with an access time of 40 to 75 milliseconds. There is also an option for a built-in dual disk drive.

Instead of the disk storage, the model 128TD has 128K of magnetic bubble memory, which can be expanded to two megabytes on the same controller (but only half a million can be accommodated inside the case). Access time to the bubble memory is claimed to be only eight milliseconds!

The gas plasma display panel has six rows of 40 or 80 characters each, formed on a 5 x 7 dot matrix. If necessary it can be interfaced to a full CRT screen. The printer is a dot matrix impact type that can print up to 135 columns per line at 25 lines per minute on multi-copy plain paper.


Findex uses CP/M as its operating system. In addition to the disk operating system it includes a monitor, text editor, assembler and debugger. When interfaced to an external hard disk drive it can address up to

128 megabytes with 8M per file.

We had an all-too-brief 'play' with the machine shortly before press deadline and were most impressed with the boot-up speed of the Findex. The display is well formatted and very clear — it's visible under almost any lighting conditions, ideal for field applications. The printer is a real convenience. Construction is very rugged, obviously designed to take a 'beating' in expected applications 'out in the field'.

Retail price of the Findex is around \$14 000, depending on which options are chosen. For more information contact the distributors, Mensa Computers Pty. Ltd, Suite 3, 454 St Kilda Road, Melbourne, Vic 3004. (03) 26-5683.

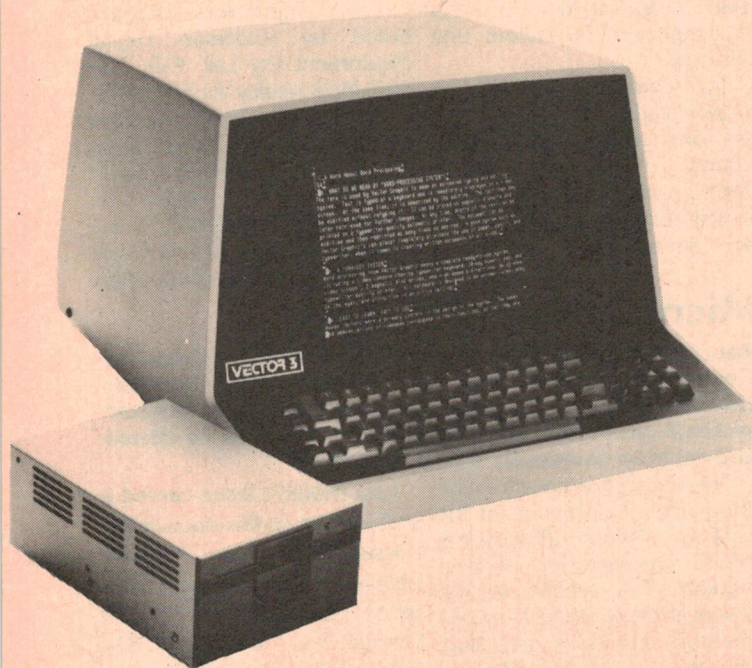We think the Findex micro is such an interesting machine that we've arranged to borrow one and try it out thoroughly for ourselves. Watch for our review in a forthcoming issue of ETI.



## New Vector systems

**The Vector 3 integrated video console is the basis for two new small business microcomputer systems from Vector Graphics.**

Their System 2800 offers two megabytes of mass storage on 200 mm disks, with formatting that is IBM compatible. The dual disk drive has an access time of 91 milliseconds and a transfer rate of 500K bits per second.

Built into the Vector 3 console are a Z80 MPU, 64K of dynamic RAM (of which 56K is usable) and a video board that can handle displays of 24 lines of 80 characters, using an 8 x 10 matrix font.

Standard software on System 2800 is CP/M, Microsoft BASIC-80, RAID debugger and SCOPE editor. Software packages available as options include general ledger, accounts payable and receivable, inventory control and word management.

The Vector Intelligent Partner

(VIP) is a low cost system aimed at businesses that have not previously used a computer. It uses the same Vector 3 video console as the System 2800 but has less scope for mass storage — just a single 130 mm disk drive. Nevertheless it can still run the same standard software and if a second minidisk drive is added the VIP can cope with all the optional accounting and word processing packages.

Suggested retail price for the System 2800 is \$8500 and for the VIP \$4300 (plus tax in both cases).

More information about Vector products is available from the NSW distributors, Dicker Data Projects Ltd, 31 Cawarra Road, Caringbah, NSW 2229. (02) 525-4707.



# ANNOUNCING A DAISY WHEEL TYPEWRITER FOR YOUR TRS-80 OR SYSTEM 80!!! \* ONLY \$1995 \*

MICRO-80 has converted the new OLIVETTI ET-121 DAISY WHEEL typewriter to work with the TRS-80 and SYSTEM 80 or any other microcomputer with a Centronics parallel port. The ET-121 typewriter is renowned for its high quality, fast speed (20 c.p.s.), quietness and reliability. MICRO-80 is renowned for its knowledge of the TRS-80/SYSTEM 80 and its sensible pricing

policy. Together, we have produced a dual-purpose machine:- an attractive, modern, correcting typewriter which doubles as a correspondence quality Daisy-Wheel printer when used with your micro-computer.

How good is it? :- This part of our advertisement was typeset using an ET-121 driven by a TRS-80.

## 77 TRACK DISK DRIVES DOUBLE YOUR CAPACITY

**DD-7S** ... .. \$775  
Micropolis Floppy Disk, 77 Track, 100% larger capacity than most mini-floppy drives, complete with cable, power supply, chassis, and includes NEWDOS '80.

**DD-7** ... .. \$649  
Same as above but no cable or Newdos '80.

**DC-4** ... .. \$45  
4 drive connector cable.

## \* \* SPECIAL \* \* MPI DISK DRIVES ONLY \$339!!

40 track bare drive for TRS-80. Only requires readily available 5 volt 0.7 amp and 12 volt 1 amp power supply to be up and running. Can be mounted in simple cabinet or used bare.

## DISKETTES FOR TRS-80

**BASF single side/single density** ... \$4.50 ea  
**BASF double side/double density** ... \$5.90 ea  
**VERBATIM 77 track** ... .. \$6.99 ea  
Minimum Order 10

## EXATRON STRINGY FLOPPY

**\$352.50 incl p&p**

15 times faster than cassette, infinitely more reliable. Completely under computer control, the stringy floppy is easier to use than disks and is a very much cheaper alternative. Will save and load any L2/16K software. Special software also available.

**Wafers for Stringy Floppy**  
**\$3.50 ea. Any Size**

## MICRO-80 MAGAZINE

**ANNUAL SUBSCRIPTION** ... \$24.00  
Monthly Magazine dedicated to TRS-80 and System '80 users. Every issue contains at least 6 new programs, plus problem solving columns, hardware articles, readers' letters, hints, etc., etc.

## AUSTRALIAN SOFTWARE

**BMON (L2/16K) \$19.95 plus 50c p&p**  
The ultimate program to assist BASIC programmers.

**TOUCHTYPE (L2/4K) \$19.95 plus 50c p&p**  
22 lessons to teach you to type on your own keyboard and screen!

**RPN CALCULATOR (L2/16K & 32K)**  
**\$14.95 plus 50c p&p**  
Turns your computer into a \$600 calculator. Ideal for Architects, Surveyors, Engineers, Teachers, Scientists, etc.

**U-BOAT (L2/16K) \$7.50 plus 50c p&p**  
You're the Commander, read all the guages, fire the torpedoes, crash dive, get the enemy before his depth charges get you!!

**MMM-1 GAMES PACK (L2/4K)**  
**\$7.50 plus 50c p&p**  
3 fast moving games - INDY 500, SUB-HUNT, KNIEVEL

## ANNOUNCING SYSPAND 80 FOR THE SYSTEM 80 \$99.00

SYSPAND 80 is a self-contained module which connects to the expansion port on your SYSTEM 80 and gives you a CENTRONICS parallel port to drive a printer PLUS the TRS-80 40 line bus. SYSPAND 80 allows you to connect all Tandy peripheral, including the expansion interface, disk drives, MICROTEK MT-32 memory expansion unit and the fabulous EXATRON STRINGY FLOPPY.

Price shown is for a built-up and tested unit. SYSPAND 80 is also available in kit form, call or write for details and price.

## TRS-80 MEMORY EXPANSION UNIT MT-32 ... \$149.00

The MT-32 is manufactured by MICROTEK Inc., USA. It provides a CENTRONICS printer port and sockets for up to 32K of dynamic RAM. It comes complete, ready to plug into the expansion port of your Level II 16K machine. (Will also work with your SYSTEM 80 via SYSPAND 80).

**MT-32A without RAM** ... .. \$149.50  
**MT-32B with 16K RAM** ... .. \$214.50  
**MT-32C with 32K RAM** ... .. \$274.50

## 16K MEMORY EXPANSION KIT ONLY \$65 incl. p&p

These are prime, branded, 200 ns (yes, 200 ns!) chips. You will pay much more elsewhere for slow, 350 ns. chips. Ours are guaranteed for 12 months. A pair of DIP shunts is also required to upgrade the CPU memory - these cost an additional \$4.00. All kits come complete with full, step-by-step instructions, no soldering is required. You don't have to be an electronic type to instal them.

## FREE SOFTWARE OFFER

**\$40 WORTH OF SOFTWARE FOR TRS-80 AND SYSTEM '80 WITH EVERY NEW SUBSCRIPTION TO MICRO-80!**  
Every new subscriber will receive on cassette, ready to load, 3 x Level I and 3 x Level II programs (includes our fabulous household budget program), with a regular retail value of at least \$40.

## THE FABULOUS NEWDOS 80 IN STOCK NOW!

**ND-80** ... .. \$149  
The disk operating system that gives:

- New basic commands that support variable record lengths up to 4095 bytes long.
- Mix or match disk drives - supports any number of tracks from 18 to 80. Use 35, 40 or 77 track 5" mini disk drives or 8" disk drives, or any combination.
- A security boot-up for basic or machine code programs. User never sees "Dos-ready" or "Ready" and cannot "break" clear screen or issue any direct basic statement including "List" ... .. and much, much more

**ND-35+** ... .. \$99  
Newdos+ for 35 track drives

**ND-40+** ... .. \$110  
Newdos+ for 40 track drives

## SCOTCH BRAND PERSONAL COMPUTING CASSETTES

**C-10 pack of 10** ... \$26.00 incl. p&p  
**C-30 pack of 10** ... \$28.00 incl. p&p

**To: MICRO-80**  
**P.O. Box 213, Goodwood, S.A. 5034**

Please rush me the items checked below:

- ☐ 12 month subscription to MICRO-80 and my free software cassette ... .. \$24.00
- ☐ 12 month subscription to MICRO-80 and the cassette edition, plus my free software cassette ... .. \$60.00
- ☐ The latest issue of MICRO-80 ... .. \$2.50


**PLUS THE ITEMS LISTED BELOW**

DESCRIPTION	PRICE
TOTAL ENCLOSED	

Name .....

Address .....

Post Code .....

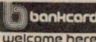 No .....

Please debit my Bankcard \$ .....

Expiry date .....

Signature .....

ETI

## MICRO 80 PRODUCTS

(08) 272 0966

284 GOODWOOD ROAD,  
CLARENCE PARK, ADELAIDE





# MENSA COMPUTERS PTY. LTD.

Suite 3, 454 St. Kilda Road, Melbourne, 3004. Telephone: (03) 26-5683, 26-6150.

## FINDEX — The Real Computer



### THE WORLD'S FIRST PORTABLE MICROCOMPUTER Battery or mains operated

RAM 48K to 2 megabytes, bubble memory to 2MB, gas plasma display, optional audio, printer, mass storage mini floppys to 800K bytes, hard disk to 195 megabytes, acoustic coupler, S-100 bus, battery optional, CPU with real time clock. For dynamic businessmen on the move. Ideal for real estate agents, insurance brokers and accountants.

## SUPERBRAIN™ SERIES

## BUSINESS SYSTEMS

Priced competitively from as low as \$45.00 p.w. lease cost including sales tax and software.



Powerful, multi-purpose microcomputer systems.

## TYPICAL APPLICATIONS

Debtors ledger and statements, creditors ledger and remittances, general ledger and trial balance, order entry/invoicing, sales analysis, payroll/wages, enquiry, word processing, mailing, record keeping, ledger card, doctors office, real estate, agency accounting, hotel/motel accounting, branch office accounting.

Facilities management consulting.

Software and computer sales.

Computer data preparation.

## OPAL 1000

The OPAL 1000 is an 8 slot S-100 system conforming to the new IEEE standards. A Delta Products Z80a 4 MHz CPU card, with 2 RS232c serial and 3x8 bit parallel ports, is used in conjunction with the Delta Products Disk Controller. Memory is provided by a 4MHz 64k dynamic RAM Board by Measurement Systems and Control. The memory board is fully bank selectable and is designed for upgrading to a multi-user system. Disk drives are 2x8" Shugart SA801R running at double density (480k/disk) and fitted with our exclusive Disk Saver which prolongs the life of the drives and floppy disks by turning off the AC power to the drives 14 seconds after the last drive select and thus reduces routine maintenance. The Disk Saver also reduces the risk of data loss due to power failures. The software is CP/M version 2.2 with Delta Product's utilities which include DTEST (for testing drives and floppy disks) and M2 (a comprehensive memory test program). The Delta PROM monitor enables fault finding to be carried out independently of the Disk Drives. The system is mounted in an attractive pressed Aluminium housing with a cast front panel fitted with reset button and key operated on/off switch.

Dealers for Opal in Victoria.

Sole Distributor for Findex, Victoria and NSW.

## SUPPLIERS FOR NDKS S-4000

### MATHEMATICS

$$F(\omega) = aT \frac{\sin \omega T/2}{\omega T/2} e^{-j\omega T/2}$$

$$e_{rms}^2 = 4KTR(f_2 - f_1)$$

$$L_1 = 10 \log \frac{1}{80} \times S_n \text{ (dB)}$$

$$A^2 + B^2 = C^2$$

$$A^2 + B^2 = C^2$$

$$F(\omega) = aT \frac{\sin \omega T/2}{\omega T/2} e^{-j\omega T/2}$$

$$e_{rms}^2 = 4KTR(f_2 - f_1)$$

$$L_1 = 10 \log \frac{1}{80} \times S_n \text{ (dB)}$$

$$A^2 + B^2 = C^2$$

$$A^2 + B^2 = C^2$$

$$F(\omega) = aT \frac{\sin \omega T/2}{\omega T/2} e^{-j\omega T/2}$$

$$e_{rms}^2 = 4KTR(f_2 - f_1)$$

$$L_1 = 10 \log \frac{1}{80} \times S_n \text{ (dB)}$$

$$A^2 + B^2 = C^2$$

$$A^2 + B^2 = C^2$$

$$F(\omega) = aT \frac{\sin \omega T/2}{\omega T/2} e^{-j\omega T/2}$$


$$e_{rms}^2 = 4KTR(f_2 - f_1)$$

$$L_1 = 10 \log \frac{1}{80} \times S_n \text{ (dB)}$$

$$A^2 + B^2 = C^2$$

$$A^2 + B^2 = C^2$$



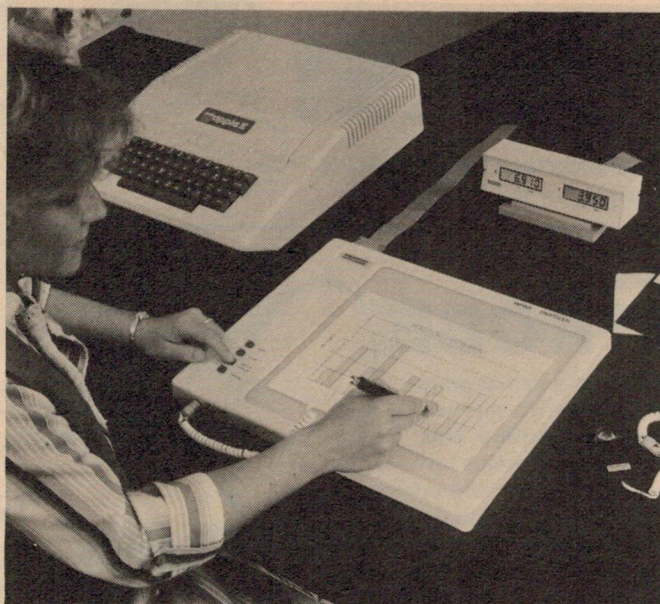

## Apple II digitiser updated

**The new DT-11A version of the HI PAD digitiser includes a slot interface card for the Apple II, a floppy disk software package, stylus and menu overlay.**

Functions supported by the software include Draw, Line, Area, Background, Pen Colour, Separate, Catalogue, Save, Load and Shape. A plastic overlay that serves as a menu allows the user to select from these functions to generate a variety of manipulable colour graphics displays.

Features of the DT-11A include slot independence, BASIC and Pascal compatibility, assembler driver code, user

controls and an optional cursor. For use with the Apple II it requires a 48K system and the Applesoft firmware card, but no magnetic blanking is needed and the digitiser is not oversensitive to static.

All up price for the digitiser with interface, software overlay and stylus is \$995 plus tax. More information from Anderson Digital Equipment Pty Ltd, P.O. Box 322, Mount Waverley, Vic 3149. (03) 543-2077.

## New User groups

**We've recently been told about three new computer users groups in different states.**

The first is the Victorian O.S.I./6502 users group. Interested people are asked to contact Ian Eyles at 10 Forbes St, Essendon, Vic. 3040 or phone (03) 375-3478 after hours.

Then there's the 'Queensland Sorcerer Users' or QSU, whose secretary is Ian Branch at 41 Chuter St, Stafford Heights, Qld 4053; (07) 350-2889. QSU say they have no plans to publish a newsletter at this stage but they will be issuing "Hints and Kinks" sheets on an occasional basis.

In South Australia there's now a Commodore Computer Users Association, whose address is P.O. Box 60, Clarence Gardens, SA 5039. The group meets at 7.30 pm on the first Tuesday of each month, usually at the Adelaide University Union Building. More information from Earle Rowan on (08) 297-7253.

## Avoid the 15% surcharge

**A practice has come to light recently where certain US microcomputer suppliers add a 'surcharge' to products bought from outside the country.**

Catalogues carry a note requesting the payment of a 15% surcharge on items exported.

It turns out that it is not necessary to pay the surcharge and potential customers are advised to 'buck'. Offer to pay postage or freight and everybody gets a fair deal. If they won't come to the party, shop somewhere else.

First to try the surcharge stunt was Jade, followed more recently by QT Computer Systems.

Many thanks to a reader from JT Microcomputers for the information.

## Japanese business micro

**A Japanese-made desktop microcomputer aimed at business users has just been released in this country.**

The PALM RL-800 is based on the Z80A microprocessor. It has 64K of internal RAM and mass storage is provided by an integral dual floppy disk drive system which has a total capacity of 736 kilobytes on double-sided double-density disks.

The built-in 300 mm monochrome video screen can display up to 24 lines of 80 characters, using a 7 x 9 dot matrix font. Cursor control, edit and auto-repeat are among the functions incorporated in the 89 key detachable keyboard unit.

The RL-800 can be used with a wide variety of printers, because in addition to two parallel

Centronics standard I/O interfaces it also has two serial synchronous or asynchronous I/O interfaces with variable modulation rates which comply with the RS232C/CCITT-V24 specifications.

Application software includes programs for accounts receivable and payable, general ledger, invoicing, inventory control, payroll, order entry and word processing.

For more details contact the national distributors, GFS Electronic Imports, 15 McKeon Road, Mitcham, Vic 3132. (03) 873-3939.

## Matrox video boards


**A new range of colour graphics controllers from Matrox are built on cards compatible with LSI-11 and PDP-11.**

The boards display a 256 x 256 raster with four bits per pixel, which allows sixteen colours or scales of grey. Boards may be combined to provide more bits per pixel with no extra hardware. For example two boards operated together will provide 256 colours.

Sync may be derived internally or from an external master, allowing the boards to be integrated into existing facilities.

Next month's ETI will probably contain a review of one of these boards.

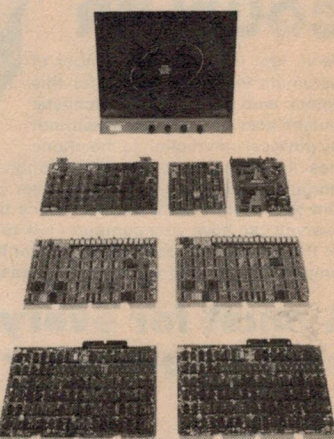For more information about Matrox products, contact the distributors, Measuring and



Control Equipment Pty Ltd, P.O. Box 78, Epping NSW 2121. (02) 86-4060.




# BUILD NOW FOR CHRISTMAS!

Get ready for the Christmas festivities and save \$\$\$! You'll be surprised at how easy a Dick Smith Kit is to build; and your Christmas bill won't cost you a fortune!!!



## NEW EA CHASER

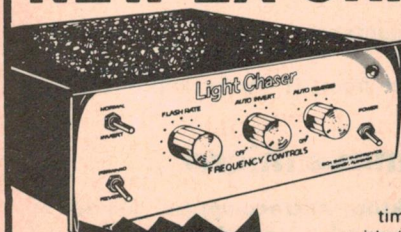

What a way to add life to your next Christmas party with this incredible Light Chaser.


Features include reverse/forward chasing, variable flash rate control plus an invert/normal switch. This switch can make two lights appear to move instead of one at a time. The versatility is increased with 'auto reverse' & 'auto invert' functions. When either control is switched on, the unit will automatically inverse or reverse the display at any set rate. All this makes it a worthwhile project that will save

\$\$\$ and give hours of entertainment.

**\$69<sup>50</sup>**

Cat. K-3145

## ETI STROBE

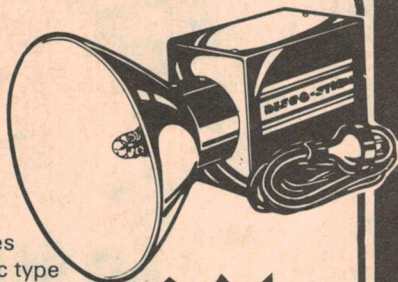


Get your Christmas party swinging with this superb Disco Strobe. This popular kit contains up-to-date circuitry and comes complete with photographic type reflector, perspex safety guard and instructions. Vary the flash rate to the beat of your music.

**\$34<sup>50</sup>**

Cat. K-3152

## EA MUSIC COLOR

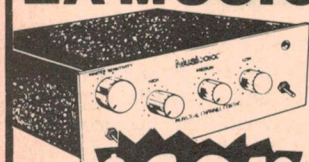

K-3140

Turn your music into a light show. This unit will accept an audio

input from almost any amplifier and uses the information to control 3 channels of colour. The ideal unit for your Christmas or New Year's party, disco, bands etc etc. Also makes an ideal present.

**\$69<sup>50</sup>**

## COLOURED GLOBES

Ideal for discos, parties etc. Use with your Musicolor. Available in 4 colours: yellow, red, blue, & green.

**\$79<sup>50</sup>ea**

Cat. S-3850/52/54/56



SWIVEL BASE Globe Holder attaches to wall or ceiling.

**\$3<sup>50</sup>**

Cat. P-5620

## HOLD IT!

Line socket for bayonet mount lamps makes it ideal for running wander light leads for loft & outside. Ideal for holding standard colour globes for parties, Xmas decorations outside etc.



**95c**

P-5510

## OTHER EXCITING DICK SMITH KITS...

## ACOUSTIC COUPLER



We've lost count of the number of customers who have asked for this project: well here it is! This acoustic coupler acts like a modem without any physical connection to the phone lines. It uses your standard telephone handset, placed over a small microphone & speaker in the coupler case, & transfers the information from your computer by sound. Hence the name, acoustic coupler.

Now you can have your computer talk to another across the street, across the town - even across the country (or further!) It is a must for all serious computer users, and we hope to release the kit soon.

**A must for everyone with a computer**

**\$75<sup>00</sup>**

Cat. K-3605

## LEDS & LADDERS GAME



**NOW ONLY**

**\$15<sup>75</sup>**

One of our most popular kits of the past was the intriguing 'LEDS & LADDERS' game described in EA in 1975. Now EA have come up with a new version of the game which is not only easier to build, it is also easier to play! Can you climb out of the well without being plummeted down again?

**AND NOW FOR THE BEST NEWS:** This kit is actually \$1.00 cheaper than it was in 1976 - despite 4 years of inflation! Makes an ideal gift.

**Was \$16.75 in 1976**

Cat. K-3390

# DICK SMITH ELECTRONICS

SEE OUR OTHER ADVERTS IN THIS MAGAZINE FOR OUR STORE ADDRESSES AND RESELLERS





# Print-out

## For 2650 fans

This column has been written by Brian Young of the 2650 Enthusiasts Group. It's the first of an occasional series that he'll be contributing for the edification and entertainment of 2650 users.

This is a DUMP and LOAD program for the 2650 micro-computer that will allow storage on tape at approx 3000 baud (six seconds per 1k). A very simple interface is required to operate this program. It uses the first five bytes of memory (immediately after the program) as its own scratchpad. It was written by Max Crisp for his RCA-1802 and modified by Max and myself for the 2650.

The LOAD program is from 0F00-0F59, and the DUMP is 0F5A-0FDE.

Use as follows:-

LOAD ... Type GF00(CR).

Now switch the sense input to the output of the squaring op-amp. When the LOAD is successful, a 'P' will be printed. If you don't get a 'P', rewind the tape and try again. You must press 'RESET' to exit from the LOAD program ...


DUMP ... Type GF5A(SP)(AAAA)(SP)(XX)(CR).

Where AAAA is the Start Address of your DUMP and XX is the number (in hex) of 256-Byte blocks you wish to DUMP. Be sure you have your tape running on RECORD before you press 'CR'.

These programs are extremely reliable and well worth using. There are two listings given so you can put it above your programs depending on how much memory you have. I will be pleased to relocate it anywhere in memory if necessary.

If you would like more information about this program, please write to me at the 2650 Enthusiasts Group, 115 Grey St, Traralgon, Vic 3844.


Brian Young

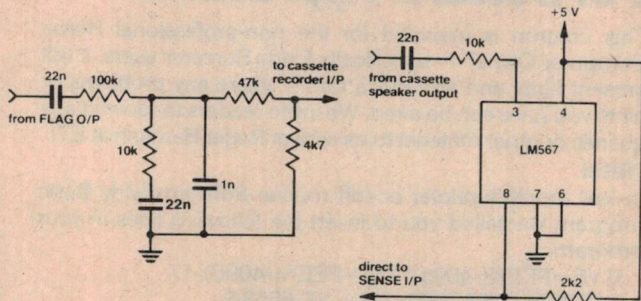

0F00	20	CC	0F	E1	75	08	05	00	06	FF	20	86	00	18	02	FA
0F10	00	B4	80	18	7C	07	21	FB	7E	B4	80	18	6E	5A	67	3B
0F20	35	58	13	3B	22	CC	0F	E0	3B	1D	C2	3B	1A	CE	EF	E0
0F30	81	C1	DA	77	1B	54	21	50	84	50	3F	02	B4	3F	00	8A
0F40	1B	44	B5	01	14	1B	02	04	01	B4	80	18	7C	07	21	FB
0F50	7E	80	B4	80	18	6C	64	01	1B	78	3B	87	CD	0F	E0	CE
0F60	1F	E3	3F	02	DB	CE	0F	E2	75	08	20	C1	0E	0F	E3	CC
0F70	0F	E1	3B	3E	F9	7C	04	01	3B	38	0F	0F	E2	18	27	A7
0F80	01	CF	0F	E2	3B	31	0C	0F	E0	3B	27	02	3B	24	14	0E
0F90	EF	E0	C3	81	C1	03	3B	1F	DA	75	0F	0F	E0	87	01	CF
0FA0	0F	E0	3B	12	1B	50	01	64	01	3B	0C	DB	7E	D8	7C	1F
0FB0	00	00	07	07	1B	03	C0	07	04	80	64	01	FB	7E	B5	01
0FC0	18	04	07	18	1B	03	07	31	14	CF	0F	E4	76	40	FB	7E
0FD0	74	40	0F	0F	E4	A7	16	FB	7E	80	07	0D	58	5E	17	FF
0FE0	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF

1F00	20	CC	1F	E1	75	08	05	00	06	FF	20	86	00	18	02	FA
1F10	00	B4	80	18	7C	07	21	FB	7E	B4	80	18	6E	5A	67	3B
1F20	35	58	13	3B	22	CC	1F	E0	3B	1D	C2	3B	1A	CE	FF	E0
1F30	81	C1	DA	77	1B	54	21	50	84	50	3F	02	B4	3F	00	8A
1F40	1B	44	B5	01	14	1B	02	04	01	B4	80	18	7C	07	21	FB
1F50	7E	80	B4	80	18	6C	64	01	1B	78	3B	87	CD	1F	E0	CE
1F60	1F	E3	3F	02	DB	CE	1F	E2	75	08	20	C1	0E	1F	E3	CC
1F70	1F	E1	3B	3E	F9	7C	04	01	3B	38	0F	1F	E2	18	27	A7
1F80	01	CF	1F	E2	3B	31	0C	1F	E0	3B	27	02	3B	24	14	0E
1F90	FF	E0	C3	81	C1	03	3B	1F	DA	75	0F	1F	E0	87	01	CF
1FA0	1F	E0	3B	12	1B	50	01	64	01	3B	0C	DB	7E	D8	7C	1F
1FB0	00	00	07	07	1B	03	C0	07	04	80	64	01	FB	7E	B5	01
1FC0	18	04	07	18	1B	03	07	31	14	CF	1F	E4	76	40	FB	7E
1FD0	74	40	0F	1F	E4	A7	16	FB	7E	80	07	0D	58	5E	17	FF
1FE0	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF
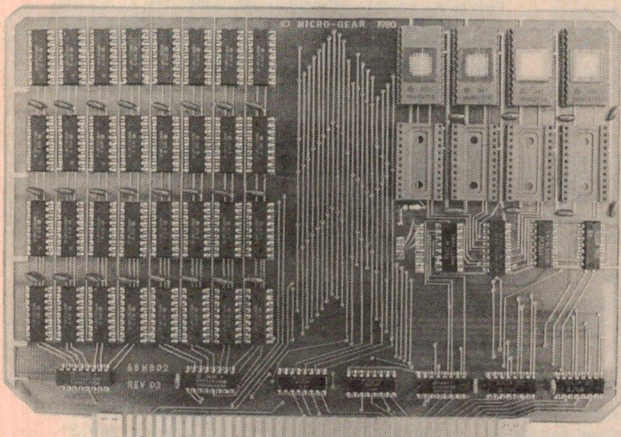
## TWO BOARDS IN ONE WITH OUR 68MB02 16K RAM/16K EPROM MEMORY BOARD



- Ideal for Motorola D2 kit expansion.
- 16K RAM (2114) expandable in 1K increments.
- 16K EPROM (2716, plus 5V) expandable in 2K increments.
- Two 8K RAM blocks selectable in 8K increments.
- Two 8K EPROM blocks selectable in 8K increments.
- Fully buffered address and data lines.
- High quality double sided PCB.
- Plated through holes and solder resist mask.
- Motorola Exorciser Bus compatible.
- Gold plated edge connector.

**SPECIAL INTRODUCTORY OFFER  
PCB AND INSTRUCTIONS ONLY \$55**

(P&P \$2 Add 15 percent if sales tax applicable)

**MICRO GEAR** 3 Coora Place, Churchill, Vic. 3842. Phone (051) 67-1498 AH (051) 22-1157.



# Printout

## For Sorcerer Apprentices

This column is intended for the non-professional Home Computer Owner — specifically Exidy Sorcerer users. It will present hints and tips and a forum where any problems or hints you have can be aired. We invite readers to forward any queries or other material to us care of Roger Harrison at ETI.

### Note:

In last month's printer on/off routine from an Exidy Basic program we asked you to insert the following lines in your program:

```
0 VE=PEEK(-4095)*256+PEEK(-4096)-47
1 IF VE>32767 THEN VE = VE-65536
```

We omitted to explain why these specific numbers had to be used. Theoretically you could have used another method, e.g. calculating the number (VE) before writing the program and then simply nominating VE with a statement such as VE=12345 or whatever you might have calculated VE to be. However, if you expand your memory or run the program on a different sized system the value of VE changes and your routine will not work any longer.

This is the reason that we used the 'long hand' method. The same principle applies for the following examples.

### Hint:

Ever wanted to change the speed of your cursor in the middle of your program (as the Monitor command SE S=10)?

Insert the following lines in your program:

```
0 VS=PEEK(-4095)*256+PEEK(-4096)-48
1 IF VS>32767 THEN VS = VS-65536
2 SP=10
3 POKE VS,SP: REM SP=Speed 0 to 255
```

Naturally, you can now use the value of 'VS' anywhere in your program without having to calculate it again.

### Assembler program:

Here now is a listing of a rather useful program which was supplied to us by Claude Almer. He writes:

"It is good to see that ETI have started to publish this column. I am sure it will prove to be very interesting and useful to us Sorcerer owners. Having worked on a similar project myself, I know how good it is to get some feedback from

readers. I would like you, if you think it is worth it, to publish the little program below. It must be loaded from F002 (HEX) onwards as the printout shows. When you have keyed it in, "GO F002". You will see that the normal prompt is changed into a question-mark. Also, the TOP OF RAM and STACK BEGINS will be displayed. This is to inform you that the stack has been moved down a bit. When you key in any command in Monitor and want to repeat that same command after completion, simply press "CTRL" and "X" simultaneously. If you want the command to be repeated permanently, key in the command and press "CTRL" and "I". "RUN/STOP" will let you exit this mode.

"For example: SE X=F002 (return)

SA KEYRP F002 F07F "CTRL" & "I"

This will immediately display the same command and then execute it. When finished executing, it will display it again and execute it again and so on until you press "RUN/STOP".

ADDR 0 1 2 3 4 5 6 7 8 9 A B C D E F

```
F000:      CD A2 E1 FD E5 2A 00 F0 01 D9 FF 09 22 00
F010: F0 E1 CD A2 E1 FD F9 FD E5 D1 01 6E 00 ED B0 21
F020: 3A F0 01 28 00 ED B0 2A 00 F0 FD 75 41 FD 74 42
F030: FD 36 44 3F 21 A7 E3 C3 CB E0 CD 18 E0 28 FB FE
F040: 09 CA 62 F0 00 00 00 00 00 FE 18 C0 CD A2 E1 FD
F050: E5 E1 E5 3E 0D BE 23 20 FC 36 00 E1 CD BA E1 C3
F060: F9 E0 CD A2 E1 FD 36 36 41 76 FD 42 F0 33 33 E1
F070: E5 3B 3B 36 0D C9 CD 15 E0 28 D1 CD A2 E1 18 A7
```

"Locations F044H to F048H are free for the user to insert a compare and jump to his liking."

P.S: As long as you don't use the Development Pac or that area of RAM this program will remain there, even after a reset and all you have to do to get it active again is "GO F002".

**Claude Almer, Hornsby, NSW**

Thanks a lot Claude. We've tested the program, and it seems to work well. Perhaps you could write and let us know in a little more detail just how the program works. As you know, we intend to educate our readers as well as supplying them with little goodies such as your program. Incidentally, it might be worth mentioning to readers that the bytes F000 and F001 must NOT be used, as the Monitor always uses them.

**A.P.F. Fry**

## microtrix



Microprocessor Systems,  
Development,  
Sales & Servicing.

**MICROTRIX,**  
**PO Box 158 Hurstbridge,**  
**Vic., 3099.**  
**Ph. (03) 718-2581 AH.**

We strive to present only top quality boards and systems at competitive prices. Our own card cage and floppy disc subsystem are now ready, so we can supply all your requirements from a single board to a complete microcomputer system. In terms of quality and value for money, you will find

our products most impressive. Prices are tax free; add 15 percent sales tax if applicable. For built and tested prices, add \$50 to those shown. Mail orders are welcome; and \$3 for postage. Please write for our catalogue, or for specific information on any product.

## \$100 PRODUCTS

### SBC 200 SINGLE BOARD COMPUTER

Z-80 based 4 MHz microcomputer with 1K RAM and sockets for 8K/16K PROM, synchronous and asynchronous serial I/O port with software programmable baud rate generator, RS232 interface, parallel ports, four channel counter/timer, power-on jump, and vectored interrupt operation. Kit with monitor in 2716 PROM \$350.

### EXPANDORAM 2 DYNAMIC RAM

A single dynamic RAM card that will hold 64K. Expandable to 256K with the latest chips. Page mode operation allows the use of up to eight boards for multiuser applications. Supplied with 200 nS 2116's for 4 MHz operation. Ideal for use with the SBC 200 and Versafloppy 2. Kit 16K \$360, 32K \$440, 48K \$520, 64K \$600.

### VERSAFLOPPY 2 DISC CONTROLLER

State-of-the-art controller operates with all combinations of drive types in single or double density modes, and has PLL data recovery circuit. Operates with SDOS or CP/M 2.2. Kit \$350.

### VERSAFLOPPY 1 DISC CONTROLLER

Low cost controller will operate with either mini or full size drives, single or double sided, in single density. Operates with CP/M or SDOS and is Remex or Shugart compatible. Kit \$250.

### PROM 100 PROM PROGRAMMER

Capable of programming all popular EPROMs such as 2708, 2758, 2716 and 2732. Zero insertion force socket is standard. Kit \$199.

### VDB 8024 VIDEO DISPLAY BOARD

On-board Z-80 and CRT 5037 controller. I/O mapped, 80 x 24 lines plus programmable characters. Kit \$370.

### \$100 CARD CAGE

Attractive sprayed aluminium, complete with 12 slot motherboard, cooling fan, and 20A power supply. Fully assembled and tested. \$350.

### FLOPPY DISC SUBSYSTEM

In a matching cabinet to our card cage, complete with twin double-headed Remex or YE Data drives. Fully assembled and tested with cable. \$1850.

Rack mount cabinet and mother board available soon. Some other cards in design stage. Add \$50 to prices for built and tested. For mail order add \$5 for reg. post. Please write for more info on any product.



# Color your thinking with Compucolor 11



...The Renaissance Machine

- Color Graphics Display
- Tutorial Software
- Financial Software
- Computer Games
- Personal Data Base
- Fortran, Basic, Assembler
- Text Editor, Utilities

The Renaissance Machine is a "one-of-a-kind" system for the "one-of-a-kind" person who demands, and will not settle for anything less than, the best.

The color machine with the black and white price

Available from

**ANDERSON DIGITAL EQUIPMENT PTY. LTD.**



DEALER ENQUIRIES  
WELCOME

MELBOURNE: 1 Expo Court, Mt. Waverley. (03) 543-2077.  
 SYDNEY: 9 Pioneer Ave, Thornleigh. PO Box 341, Pennant Hills, NSW 2120. (02) 848-8533.  
 Your local dealer:  
 Melbourne: Logic Shop (03) 51-1950. Sydney: Logic Shop (02) 699-4910.  
 Newcastle: DGE Systems Pty Ltd (049) 69-1625. Canberra: ADE (062) 58-1811.  
 Brisbane: ADE (07) 59-6436. Adelaide: Applied Data Control Pty Ltd (08) 79-9211.  
 Perth: WJ Moncrieff Pty Ltd (09) 325-5722. Hobart: Management Technology (002) 34-4522.  
 Darwin: Direct TV and Electronic Services (089) 81-9313.  
 NEW ZEALAND:  
 Wellington: ADE 69-3008. Auckland: ADE 66-3833. Christchurch: ADE 79-0210.  
 NEW GUINEA: Komputel Systems 42-3924.



# FREDERICK & HOWARD

PTY. LTD.

HEAD OFFICE

Directors:  
James F. Frederick  
Gordon P. Howard  
Ralph J. Griffiths

## ASSOCIATES:

Terry S. O'Brien

Peter W. Howard

Alfred D. Lane

Barry T. Read

Ralph J. Griffiths

## McWilliam's Bin Seventy Seven Traminer Riesling ...it's ready when you are.

Success doesn't happen overnight. It takes time. Just as it takes time to truly appreciate the subtle qualities of a fine white wine. But like success, once you've got a taste for it, you're ready to move on to bigger and better things. Take McWilliam's Traminer Riesling, for instance. It's a superb blending of the Traminer and Rhine Riesling grape varieties



grown in the Riverina District of New South Wales. The distinct spicy flavour of the Traminer complements the crisp acidity and freshness of the Rhine Riesling to give a wine with complexity and excellent balance. McWilliam's Traminer Riesling is ready for you right now...whenever you're ready for it.





from  
**PARAMETERS<sup>PTY LTD</sup>**  
*"Perfection in Measurement"*  
 Sydney 439 3288 Melbourne 90 7444

*Available from selected dealers*

N.S.W. Sydney Martin de Launay 29 5834; George Brown 519 5855; Radio Despatch 211 0191; Dick Smith Stores 888 3200; Tech Rentals 438 2199. Newcastle D.G.E. Systems 69 1625; Elektron 2000 26 2644. Wollongong Macelec 29 1455; Hundell Engineering 74 0278. QLD. Brisbane Audiotronics 44 7566; L.E. Boughen 36 1277. VIC. Melbourne Browntronic 419 3986; J.H. Magrath 663 3731; Ellistronics 602 3287; Radio Parts 329 7888; Douglas Radio 211 1698; G.B. Telespares 328 4301; Ritronics 489 8131; Edible Electronics 41 5708; Tech Rentals 51 1303. Geelong Teleparts 21 7288. N. Ballarat Ballarat Electronic Supplies 31 1947. S.A. Adelaide Trio Electrix 51 6718; K.D. Fisher 269 2544; Gerard & Goodman 223 2222. W.A. Perth Hincro Engineering 381 4477; Electrical Equipment (Rablec) 381 2866; W.J. Montcrieff 325 5722. TAS. Hobart Imbros Surpath Systems 23 2892; George Harvey Electric 34 2233; Launceston Imbros Surpath Systems 31 7160; George Harvey Electric 31 6533.



# Owners of Nikon, Pentax, Olympus, Minolta, Canon, Leica... improve your images.

↑  
4"  
↓



← 6" →

Kodak Elite 35 Prints set a new standard of excellence in color reproduction for 35mm camera owners.

1. Kodak Elite 35 Prints measure 15cm x 10cm (6" x 4") have a finely-textured matt finish, and square corners.
2. Kodak Elite 35 Prints are processed from negatives individually assessed by computer.
3. Kodak Elite 35 Prints are subject to extremely strict quality controls.

4. Kodak Elite 35 Prints are returned to you with the negatives in special plastic sleeves for complete protection.

Kodak Elite 35 Prints take slightly longer to process and cost a little extra, but that's what you'd expect for wanting the best.

Kodak Elite 35 Prints are available from all C41 compatible 35mm color negative film.

KODAK (Australasia) PTY. LTD.



KO/6163/Y/KSB





# SOUND

## **FEATURES:**

- **BOSE CONTEST (JULY) WINNERS** 106
- **POWER MOSFETS — THE TECHNOLOGY, THE TECHNIQUES** 114
- **GREAT MARUNI CONTEST** 125
- **AUDIOSOUND AM101 TUNER** 138
- **SOUNDOUT S400 200W/CH STEREO AMP** 146

## **REVIEWS:**





# sound engineering





## Hitachi's Digital Synthesizer and Super-Linear Circuit

**Tuning with quartz stability  
and power amplification  
without switching distortion.**

### **Together in the HTA-7000 Tuner/Amplifier.**

The digital synthesizer tuner is sound engineering. And so is the super-linear circuit. They work together to bring in the correct oscillation and amplify with remarkable clarity. In the Hitachi HTA-7000 Tuner/Amplifier they are the essence of a trend-setting new component package.


The tuner's quartz crystal reference oscillator delivers the most stable frequency standards available. That's the reason so many professional broadcast facilities use them. Hitachi's PLL synthesizer utilizes this advance to achieve a tuner that really stays locked-in to stations — regardless of changes in temperature, humidity or line voltage.

That oscillation accuracy is further amplified by the Hitachi super-linear circuit. It's a totally new way to bias the transistors.

Instead of the on/off delay distortion that occurs during signal-phase changes in a conventional system, the Hitachi circuit keeps the transistors idling on alternate half cycles. So the waveform stays smooth. And even at high frequencies the absence of switching distortion makes the sound refreshingly clean.

The Hitachi HTA-7000 Tuner/Amplifier also features a programmable memory. Preset up to six AM and six FM stations for recall at the push of a button. FM band scanning is automatic, so every station is perfectly tuned. Rated amplifier output: 55 watts total RMS with less than 0.02% THD at 8 ohms from 20 Hz to 20 kHz.

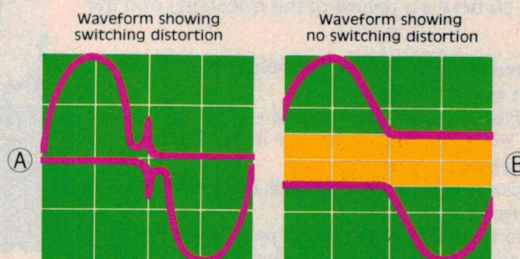Hitachi tuner technology and amplifier technology are at work to deliver accuracy and purity. The new HTA-7000 Tuner/Amplifier with digital synthesizer and super-linear circuit is the result of those efforts. Listen to the soundness of Hitachi engineering today.



(A) Conventional Class B amplification  
(B) Hitachi's super-linear amplification

Graphic illustrations are reconstructed from Hitachi Toyokawa audio laboratory data.

**Professional sound through sound engineering**

# HTA-7000





## Bose car stereo contest results

Pictured here receiving their prizes of Bose 1401 car stereo systems are two of the winners (and a proxy) of the contest featured on pages 100-101 of our July issue.

**Nobody answered all the questions correctly, but five people got all but one correct. Since there were exactly five prizes, the questions proved a perfect filter.**

The winners were **Jim Cumming, Geoff Bickham and Ian Haynes** from NSW and **Brian Connors and Jim Cerini** from Victoria.

The rest of you are no doubt wondering just where you went wrong in your entries, so here's a review of the questions and the correct answers.

**Q1:** To double the perceived sound level obtainable from a 10 watt car stereo what power would you need?

**A:** The human ear has a logarithmic response — hence to double perceived sound levels the power has to be increased ten times. Most entrants answered this correctly.

**Q2:** What is the approximate peak power in watts generated by a one metre diameter bass drum?

**A:** Measured at three metres from the drum, peak levels approach 115 dB (referenced to the threshold of hearing). This corresponds to a peak power of 25 acoustic watts. About 20% of entrants answered this question correctly.

**Q3:** Two cars are standing side by side with their engines revving hard. Do they make twice as much noise as one car... or?

**A:** This is of course related to Question 1. The correct answer is less than one and a half times: in fact the increase would be only barely perceptible! Most entrants answered this correctly.

**Q4:** Some problems occur in reproducing music below certain limiting frequencies in small areas — such as a car interior. Which of the following is the primary problem?

**A:** The required answer was that "sounds reflecting off far surfaces cancel those heard directly". The equaliser used in the Bose system helps offset this phenomenon. About 25% of entrants got this one right.

**Q5:** Bose's fundamental speaker design concept is that only a small part of the sound in a concert hall is perceived directly — most is reflected. So they design their speakers to work in the same way. What percentage of sound does Bose feel is direct?

**A:** 11%. Most people answered this correctly.

**Q6:** What is the model number of Bose's best known domestic speaker?

**A:** 901. Almost all entrants answered this correctly. Bose must be delighted!

**Q7:** What total harmonic distortion level do Bose claim for their 1401 car stereo?

**A:** 0.09%.

**Q8:** What was a 'Housekeeper seal'?

**A:** This was a method of sealing base metals through glass. Its development enabled the anode of a valve to be part of the vacuum envelope, allowing the outer surface of the anode to be cooled directly. This led to the development of high-power transmitting valves. Most entrants were stumped by this question!

**Q9:** This measuring device was in use during the very early days of electromagnetic communications. What was it called?

**A:** This was a bit of a tricky question! The device was called a Cymoscope, a term which covered any instrument which enabled the user to see the effect of electrical waves to detect their presence. When the device was held close to a short wave transmitter a spark would jump across the gap, provided the wavelength was appropriately adjusted. The device was **used** by Hertz but was never known



ETI's Editor, Roger Harrison (far left) and David Bell of Bose (far right) present the prizes to Geoff Bickham, Ian Haynes and Steven Williams (for Brian Connors) at a function turned on by Bose just before we went to press.

as a 'Hertzian loop'. Less than 20 entrants answered this question correctly.

**Q10:** "Music has charms to sooth the savage breast — but...". Who said the above?

**A:** Sorry folks but neither ETI nor Bose give stereos away **that** easily! This question was intended as an eliminator and succeeded very well indeed. Almost all entrants picked William Congreve, but Congreve's version was "Music hath charms to sooth a savage breast, to soften rocks or bend a knotted oak" (some editions read "Music has charms").

The correct answer is Alexander Chase, whose **parody** of the original reads "Music has charms to sooth the savage breast — but not the unmusical one. The quote is from Chase's 'Perspectives' (1966). All the prize winners answered this correctly. Well done!

## More efficient headphones

**New electrostatic headphones from Sennheiser feature two-part membranes that are claimed to give twice the sound output with no increase in input power and no decrease in quality.**

The sound radiating membranes of the Unipolar 2002 headphones have an inner circular section, which radiates preferentially in the middle to high frequency ranges and an outer ring-shaped section which is tuned to lower frequencies.

The purchase price of \$345 includes a control unit with two broadband transformers to produce the relatively high voltages needed by electrostatic head-




phones. Output sockets on the control unit have been specially constructed to prevent non-electrostatic headphones from being inadvertently connected.


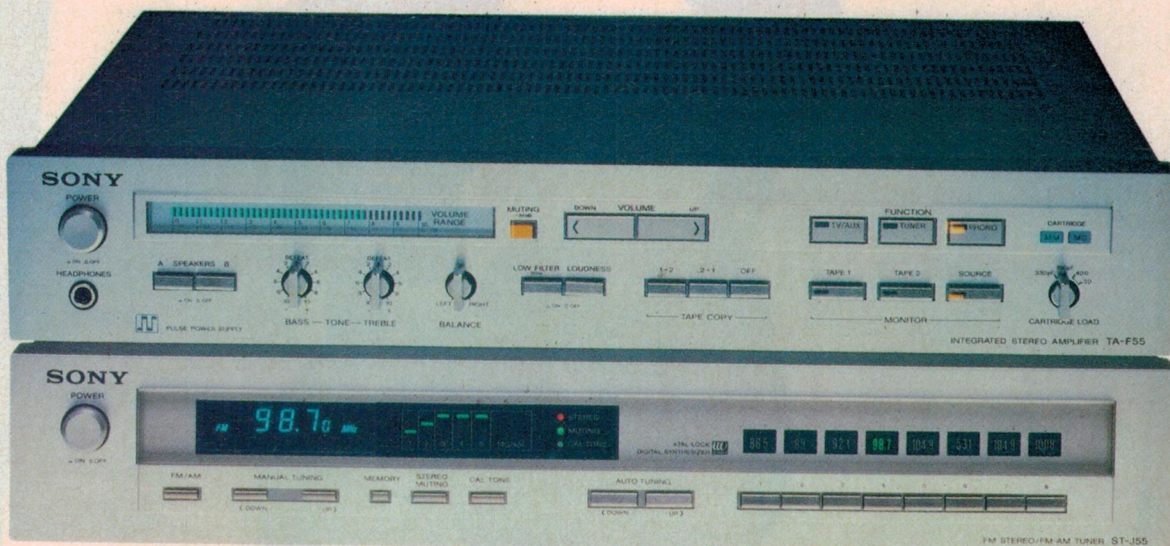
# Sony's inseparable separates.

Sony's new ST-J55 tuner and TA-F55 amplifier come in elegant matching designs. Separately, they're

straight signal processing circuit construction, revolutionary Heat Pipe, and Pulse Power Supply, providing



TA-F55

ST-J55

outstanding. Together, they're out on their own, both in appearance and performance.

The J-55's tuner is frequency synthesized and quartz locked. A neat line of feather-touch switches gives a choice of Memory, Auto, or manual tuning.

The J55's incredible electronic MNOS memory tuning lets you preset your 8 favourite AM/FM stations – including reception adjustments like muting or mode pre-set.

The other half of the team, the 65W F55 Amplifier, features an electronic motor driven volume control,

extremely clean and noise-free sound quality.

The F55 operates with almost any type of MC and MM cartridge; has gold-plated phono jacks, oxygen-free copper wiring, metallized film resistors and polypropylene capacitors.

You won't find better engineering than these. Not even from Sony.

## SONY®



**THE INCREDIBLE STUDIO 1000**



*N.B. MARUNI microphones take some beating too!!!*

**MARUNI**

SUPERLATIVE HEADPHONES AND MICROPHONES

THE **MARUNI** CORPORATION

297 WILLIAMSTOWN ROAD, PORT MELBOURNE, 3207 • TELEPHONE, 645 2079 • TELEX 32571



## At last — the bionic tonearm!

For reasons best known to themselves, Sony have chosen the name Biotracer for their motional feedback controlled tonearms.

**The name, however, is the only silly thing about them. Sony have opted for straight low mass arms made of a special aluminium alloy, eight times stronger than the usual alloys, which allows a 35% reduction in effective mass.**


To prevent excessive movement of the arm, the Biotracer has two inbuilt sensors which measure horizontal and vertical velocity, a microprocessor to interpret their signals and two linear motors to apply corrective forces.

Among the benefits claimed for this feedback control system are reduced resonance, better

channel separation, lower inter-modulation distortion and less wow and flutter from warped records.

A lateral position sensor, (comprising a LED, a slotted plate and a CdS photo-detector) detects the horizontal angle of the tone arm so that the anti-skating force can be varied as it tracks toward the centre of a record.

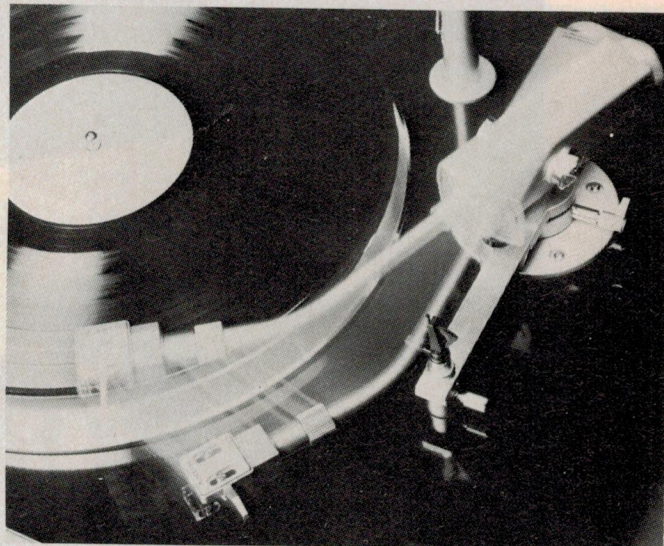For those who are disturbed by the noise associated with touchdown and liftoff of the stylus, the Biotracer has a muting circuit which automatically disconnects the audio output during these operations.



## But does it make coffee ?

**A recently released 'sound centre' unit appears to do just about everything except make "the morning cuppa".**

The Model PS 2000, distributed in Australia by Unitrex, incorporates — all in a single unit — an AM tuner, a stereo FM tuner, a stereo cassette deck (with record and playback facilities), a clock radio and an alarm (... pause for deep breath).

The unit has two inbuilt speakers for stereo reproduction and provision for external speakers. Power output is rated at 2 W. Two microphones are supplied with the unit for recording, plus you can tape direct from the AM/FM tuner or an external source (tape, turntable etc).

The clock/alarm can be set to wake you with a tone or the radio set to your favourite station (... or 2BL with Clive Robertson...). You get the usual 'snooze' button too. In addition, you can be soothed into sleep with the radio which will turn off one hour after you set the 'sleep' button.

The PS 2000 will be marketed through department stores and specialist shops. Recommended retail price is a little under \$200. More details from Unitrex at P.O. Box 176, Blackburn, Vic 3130. (03) 877-2922

## Low cost hi-fi speakers



**A new range of L & D loudspeakers came on the market recently.**

Designed to give good quality reproduction at a modest price, the range extends from 200 mm three-ways at \$199 per pair to 300 mm four-way systems at \$399 the pair.

The systems feature horn and dome tweeters, wide dispersion

midrange units and bass drivers with high power handling capability. Dividing networks are 6 dB per octave inductive filters.

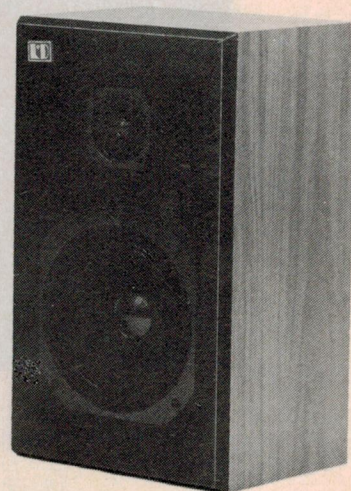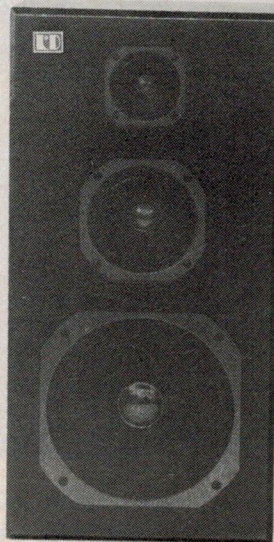More details are available from L & D Audio Distributors, 24 Enterprise Avenue, Padstow, NSW 2211; (02) 771-3999.







A dream come true  
demands music  
as true as the dream  
- Nakamichi





For further information contact Convoy International Pty Ltd 4 Dowling Street Woolloomooloo NSW 2011

Telephone (02) 3582088



# The instant upgrade.


The new Bose® 901® IV  
Direct/Reflecting® speakers  
help your stereo sound better.



If you are thinking of upgrading your music system, Bose has the fastest way to do it.

The new Bose 901® Series IV speaker.

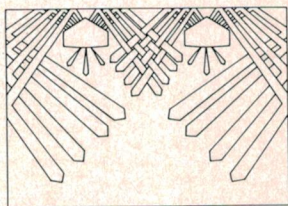Since the speaker has more to do with the sound you hear than any other part of your music system, you



can improve the quality of your sound by improving your speakers.

The new Bose 901® IV speakers

are the answer. You can drive these speakers with as little as 10 watts per channel. And they are durable enough to handle any non-commercial amp. So you can match them to your system, no matter what the system.

The Bose 901® Series IV speaker. The best regardless of size or price.

## **BOSE®**

BOSE AUSTRALIA INC., 11 MURIEL AVENUE, RYDALMERE, NSW. Tel: 684-1022, 684-1255.

**DEALERS AND DISTRIBUTORS:**

**HI FI HOUSE** Wollongong NSW, **D.M.E. HI FI** Sydney NSW, **APOLLO HI FI** Marrickville NSW, **HI FI COUNTRY** Engadine NSW, **NITRONICS** Coffs Harbour NSW, **BROWN AND JOLLIE** Lismore NSW, **HABERECHTS RADIO** Albury NSW, **DURATONE HI FI** Phillip ACT, **STEREO SUPPLIES** Brisbane QLD, **DENMAN AUDIO** St. Kilda VIC, **BELMONT STEREO SYSTEMS** Geelong VIC, **NORTHERN ELECTRONICS** Coburg VIC, **SOUND FACTORS** Dandenong VIC, **PROUDS AUDIO** Bendigo VIC, **TEAK HOUSE** Hobart TAS, **AUDIO WHOLESALE** Burnie TAS, **BLACKWOOD SOUND** Blackwood SA, **THE AUDIO CENTRE** West Perth WA.

111689-9/78-11



# The dawn of a new recording era

## Auto Azimuth Alignment

Undoubtedly the most advanced and sophisticated cassette recorders in the world today, the ZX Series launches a new era in high-fidelity cassette recording. These revolutionary transports feature exclusive Nakamichi Discrete-Head technology, 4-Motor, Dual-Capstan, Asymmetrical, Diffused-Resonance Transport, Random Access Music Memory, and Auto Azimuth Alignment. For the first time, you can be assured of perfect azimuth alignment – on any cassette – at the touch of a button. Unprecedented frequency response – to 22kHz at standard speed, to 15kHz at half speed! The culmination of Nakamichi's commitment to excellence in the fine art of recorded sound.



### 680ZX

The premier Model 680ZX – half-speed response that rivals that of other decks at full speed! And, at standard speed, a full 22kHz! High-resolution wide-range FL level indicators and 18 program RAMM. Choose your speed, choose your program. The 680ZX does it all!

### 670ZX

Full off-tape monitoring facilities with Double Dolby and two complete sets of electronics. Single-speed operation to an astounding 22kHz! Nine program RAMM and wide-range peak-responding meters. Outstanding performance.



For further information contact Convoy International Pty Ltd 4 Dowling Street Woolloomooloo NSW 2011 Telephone (02) 3582088



# Power MOSFETS — the technology, the techniques

A state-of-the-art MOSFET amplifier project will be the highlight of a forthcoming issue. This introductory article explains what MOSFETs are and how they have developed into high power devices.

## Brian Dance

IN 1976 Siliconix startled the semiconductor world with a new type of power MOSFET device. Recently other manufacturers have produced many other types of MOSFET products which are challenging power transistors and Darlingtons.

The name MOSFET stands for Metal Oxide Silicon Field Effect Transistor. Field effect transistors (FETs) are essentially voltage controlled devices, unlike conventional transistors in which the small base current controls a larger collector output current. FETs have very high input impedances so that very little input current is required to control their output current.

The input impedance of MOSFETs is especially high because they have an insulating film of silicon dioxide between the input gate electrode and the channel through which the output current flows. The gate electrode is therefore essentially completely insulated and virtually no input current can flow.

Various types of small MOSFET devices have been available for many years. Internally they contain a very small silicon chip on the surface of which the MOSFET device has been fabricated. Any current passes through these devices in a horizontal direction through the very thin surface layers and therefore the maximum current is quite low; maximum power dissipation in such devices is not normally over 1W.

### VMOS devices

In the so-called VMOS devices, developed by Siliconix about four years ago, the current flows vertically through the semiconductor material — hence the name VMOS. This name is also associated with the V-shaped groove formed in the surface of the semiconductor material of such devices. Figure 1 shows a cross-section of a VMOS transistor.

If the gate electrode is connected to the source and the drain contact at the bottom of Figure 1 is made positive rela-

tive to the source, no appreciable current will flow from drain to source, since the internal diode formed between the p and n type materials will be reverse biased. If, however, the gate electrode is made positive with respect to the source, the electric field produced by the gate potential creates a channel in the position shown in Figure 1. A current can now flow upwards from the drain through the channel to the source. As the gate becomes more positive, the width of the channel increases and the current from drain to source increases.

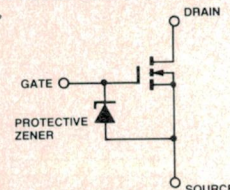


Figure 2. Zener protection of the gate.

If small changes in the gate voltage are to produce the required channel depth, the insulating layer must be extremely thin, which results in an appreciable gate input capacitance (typically some 50 pf). The thin layer also imposes a limit to the maximum voltage which can safely be applied to the gate without the risk of breaking down this thin layer and thus destroying the device. As the gate input resistance is so high (often of the order of a million megohms), it is very easy for small stray electrostatic charges to be picked up on the gate and produce voltages which can puncture the insulating film.

In some devices a small zener diode is connected between the gate and the source, as shown in Figure 2. If the gate to source voltage exceeds the zener voltage, the zener conducts and shorts out the voltage, protecting the MOSFET. However, the maximum zener current is quite small, so the zener can easily be damaged. The maximum input voltage

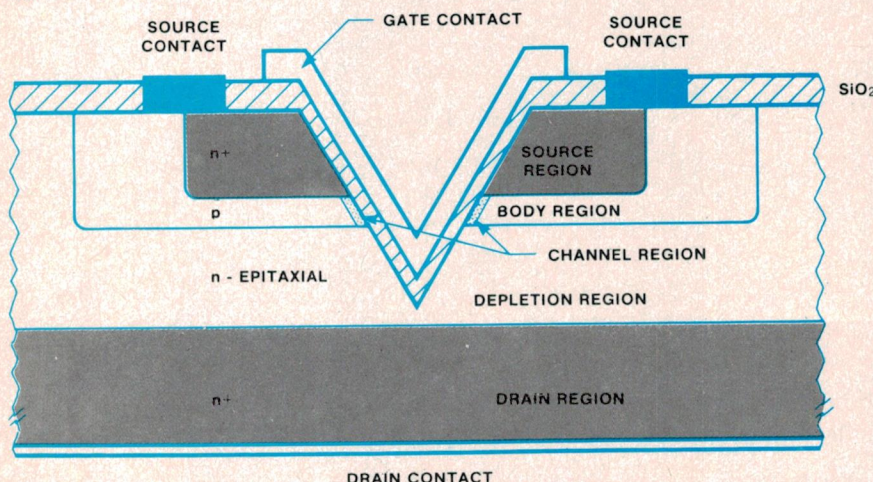


Figure 1. Structure of the VMOS device developed by Siliconix. With the gate biased positive with respect to the source, current flows from the drain region to the source via the channel region indicated. As the gate is biased more positive, the channel region increases, increasing the drain-source current. VMOS FETs are majority-carrier devices and can switch current in less than 10 ns. Bipolar transistors cannot compete as they suffer from minority carrier storage in the base region.



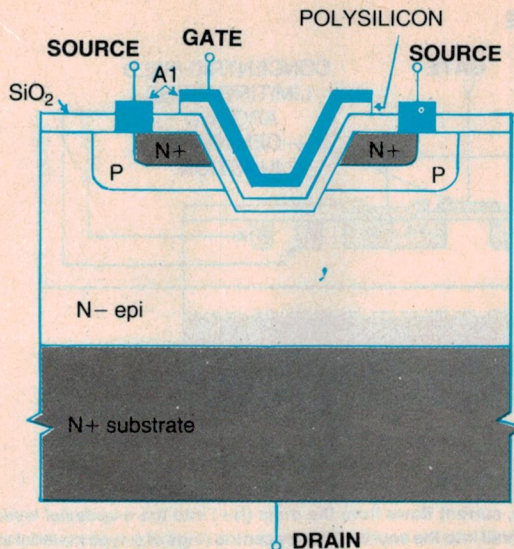


Figure 3. The U-groove device, introduced by Intersil, reduces problems associated with the intense electric field at the edge of the V-notch in VMOS devices. The polysilicon layer prevents migration of sodium impurity ions through the gate oxide layer, a source of chip failure in VMOS.

'in circuit' should not exceed the zener voltage so that the zener is used to provide protection against electrostatic charges only.

If the gate becomes more than a fraction of a volt negative with respect to the source, the zener will conduct in its forward direction. If one wishes to operate a MOSFET with the gate voltage negative with respect to the source at any part of the duty cycle, a device not containing a zener should be selected, but then one must take precautions to avoid electrostatic charge pick up.

The first VMOS devices marketed were n-channel devices, with an n-type channel formed in the p-type material shown in Figure 1. Siliconix still only market n-channel devices, but some other manufacturers offer both p-channel and n-channel types.

### Comparison with bipolars

As the early VMOS devices could not handle so much current or so much applied voltage as conventional transistors, yet were more expensive than the latter, they obviously had some advantages or their manufacture would not have been a viable proposition.

Ordinary bipolar transistors suffer from the disadvantage of minority carrier storage in the base region. VMOS products are majority carrier devices and can therefore switch a current in less than 10 nanoseconds and operate up to several hundred megahertz. For example, the 2N6657 can switch 1 A on or off in less than 4 ns, this being 10 to 200 times faster than a comparable bipolar device.

'Secondary breakdown' is another problem with bipolar transistors. If the

current density increases at one point, the temperature rises in this region, leading to a still greater current density — a positive feedback effect which can lead to the rapid destruction of the device. In VMOS devices, an increase in the current density in the channel produces an increased temperature which results in a lower current density in that region, so that the current density automatically equalises itself throughout the chip without the formation of hot spots.

It follows that it is possible to connect two or more VMOS devices in parallel (often without any additional components), since the total current is automatically shared equally between the devices. Any device passing more current than the mean will become hotter and this will reduce the current somewhat in that device.

Apart from their higher cost, one of the disadvantages of VMOS devices is that their saturation voltage (typically 2V, maximum 4V for some devices when passing 1A) is much greater than for bipolar transistors. Although the V-shaped groove utilises the silicon area quite efficiently, the relatively sharp bottom of the groove is a disadvantage, since a strong electric field can be developed at this point between the gate and the drain where the insulating layer tends to be thinner than elsewhere. This results in a limited operating voltage capability owing to the possibility of gate to channel breakdown.

A perfect switching device would have an infinite resistance in the off state, but the drain current of many VMOS devices is in the nA region when

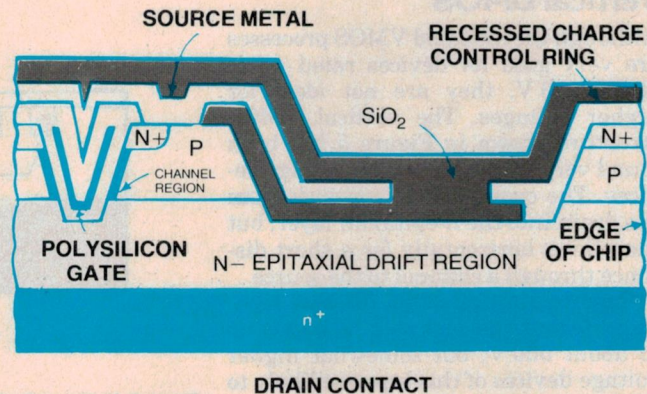


Figure 4. Having introduced power MOSFET technology, Siliconix have gone on to improve the devices. The tri-planar construction shown here allows much higher packing densities on the chip, the smaller size resulting in lower on state resistance. Polysilicon gates are buried in the oxide layers allowing source metallisation to cover a greater fraction of the chip area.

in the off state with gate and source voltages equal. The resistance in the conducting state is normally a few ohms instead of the zero resistance of the perfect switch. This on-resistance is greater for devices with higher voltage ratings.

### U-groove devices

The problem of the relatively intense electric field at the edge of the V-shaped notch of VMOS devices has already been mentioned. Intersil, followed by some other manufacturers, reduced this problem by producing devices with the structure shown in Figure 3, where the bottom of the groove is flat. Note that there is an additional layer of phosphorus-doped polycrystalline silicon between the gate and the insulating layer of silicon dioxide. This overcomes another problem of the early VMOS devices, namely the migration of sodium impurity ions through the gate oxide layer, which can cause reliability problems.

### Other VMOS products

In 1980 Siliconix announced an improved triplanar VMOS process with the device structure shown in Figure 4. The source, the gate and the drain are each fabricated in a different plane. It is stated that this type of structure allows much higher packing densities on the chip and the smaller size will enable lower on state resistances to be obtained. Polysilicon gates are buried under the oxide layers so that the source metallisation can cover a greater fraction of the chip area.

Another major improvement from the triplanar structure arises from the use



of thin low-resistivity doped layers and from a re-arrangement of the V grooves for optimum use of the epitaxial layers.

## Vertical DMOS

Although the modified VMOS processes are very good for devices rated up to about 150 V, they are not ideal for higher voltages. The vertical DMOS structure shown in Figure 5 has been found very suitable for high voltage devices. The current flows upwards from the drain into the n-epitaxial layer, but then flows horizontally for a short distance through a channel to the source.

Supertex of California use this technique to make devices with ratings of up to about 500 V, but somewhat higher voltage devices of this type are likely to become available. Figure 5 shows how the main junction region is surrounded by a concentric second junction which is in turn surrounded by a third junction. Apart from high voltage capability, this process can produce devices with a very low on-resistance (down to 0.05 ohm). In addition the devices are very fast, owing to the low gate capacitance. For example, a 1A device can operate at about 2 GHz and a 10 A device at about 500 MHz.

The Ferranti Company of Oldham, England have co-operated with Supertex to develop vertical DMOS devices, both n-channel and p-channel, with ratings up to 650 V and drain currents up to 16 A continuous.

Figure 5. In the vertical DMOS device, current flows from the drain (N+) into the n-epitaxial layer (N-) then flows horizontally through a channel into the source. The concentric rings of p-type material around the main junction help improve the current capability and reduce the on-resistance. This form of construction achieves significantly higher voltage and current ratings compared to prior power MOSFETs.

## Hitachi devices

Hitachi has developed a MOSFET device with the structure shown in Figure 6. The gate oxide layer is designed to handle only 20 to 30 V, so a field plate is provided to prevent high electric fields from forming near the gate. This type of device is most suitable for audio frequencies and for operation at up to a maximum of a few MHz. Both p-channel and n-channel types are available with ratings of up to 200 V and 8 A.

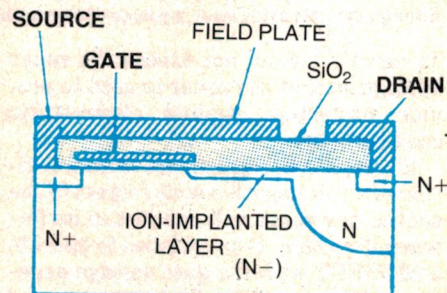


Figure 6. Hitachi MOSFET construction.

## HEXFET devices



In mid-1980 International Rectifier introduced a range of devices named HEXFET after the hexagonal structure of the source cells which are connected by a common silicon gate (see Figure 7). The density of these source cells is over half a million per square inch.

HEXFET devices are available in both p-channel and n-channel polarities and can handle high power levels. They have voltage ratings of up to 500 V and continuous current ratings of up to 25 A. Values of channel resistance as low as 0.05 ohm can be obtained in the on state.

Some of the main applications for HEXFETs include servo motor control, RF induction heating, welding control equipment, audio amplification and other uses where the control of high power is required.
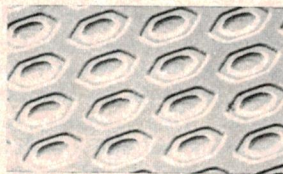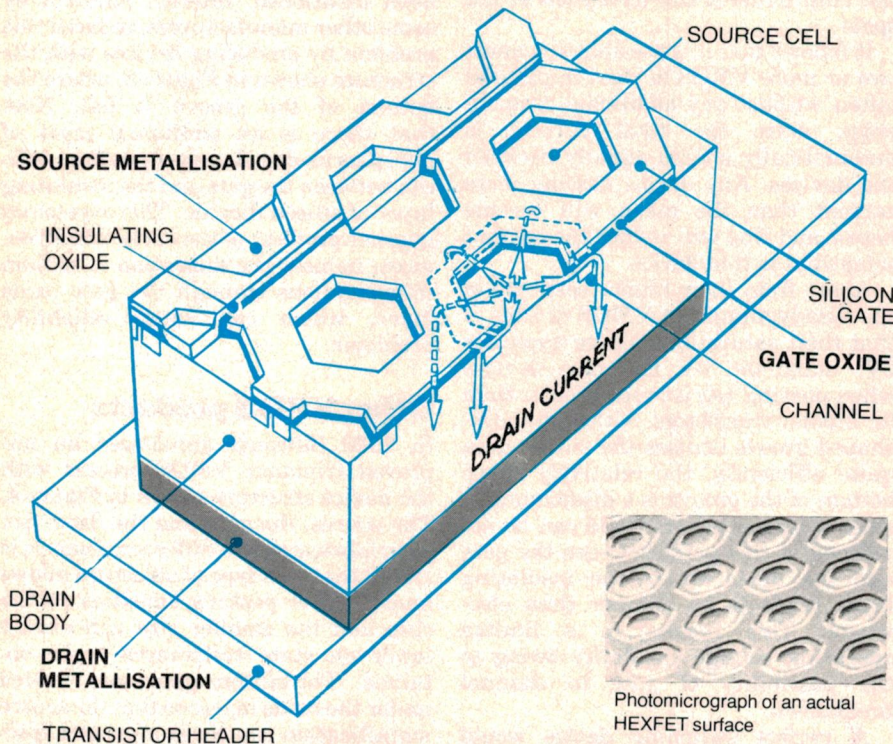
## SIPMOS

The latest technology to emerge in the power MOSFET field is SIPMOS from Siemens of West Germany, which is an extension of the vertical DMOS technique. Siemens have used this technique to fabricate the first 1000 V MOSFET device, the BUZ 54, which can handle 5 A. It is expected to have wide



Photomicrograph of an actual HEXFET surface

Figure 7. Construction of the HEXFET device introduced by the International Rectifier company in mid-1980. The hexagonal source cells (hence the name) are connected by a common silicon gate. Claimed advantages include high voltage and current ratings plus very low on-resistance.



# "I have always wanted a really good loudspeaker system."

Today the cost of excellent turntables, cartridges, tape decks and amplifiers has fallen to the point where the average family man can afford equipment of a quality and performance-level that was impossible ten years ago.

But good loudspeakers have remained extremely expensive and, in most domestic hi-fi systems, the rest of the equipment can dramatically outperform the speaker.

Electronics Today International magazine, in co-operation with Philips Elcoma Division, set out to correct this imbalance and designed the ETI 4000/1 speaker system.

The Series 4000/1 is available in kit form which means you save money by assembling it yourself.

A total kit, including:

- 8 loudspeaker drivers (4 per box)



- 22 element crossover networks
  - pre-assembled boxes.
- For around \$798.00 per pair. (\$300.00 less, if you build your own boxes)!

The Series 4000/1 is comparable to systems selling for twice the price.

See your Philips dealer today or send for complete details including a free reprint of the original construction article. Further information on Philips loudspeakers; a list of Philips dealers and a free 4-speed stroboscope card for checking the speed accuracy of your turntable.

#### Philips Electronic Components and Materials

P.O. Box 50  
LANE COVE, N.S.W. 2066

Please send me complete information on the Series 4000/1 loudspeaker system plus my free 4-speed stroboscope card and further information on loudspeakers.

NAME \_\_\_\_\_  
Please Print

ADDRESS \_\_\_\_\_

STATE \_\_\_\_\_ P'CODE \_\_\_\_\_

ETI



**Electronic  
Components  
and Materials**

# PHILIPS

AHEARN EL37

ETI November 1980 - 117



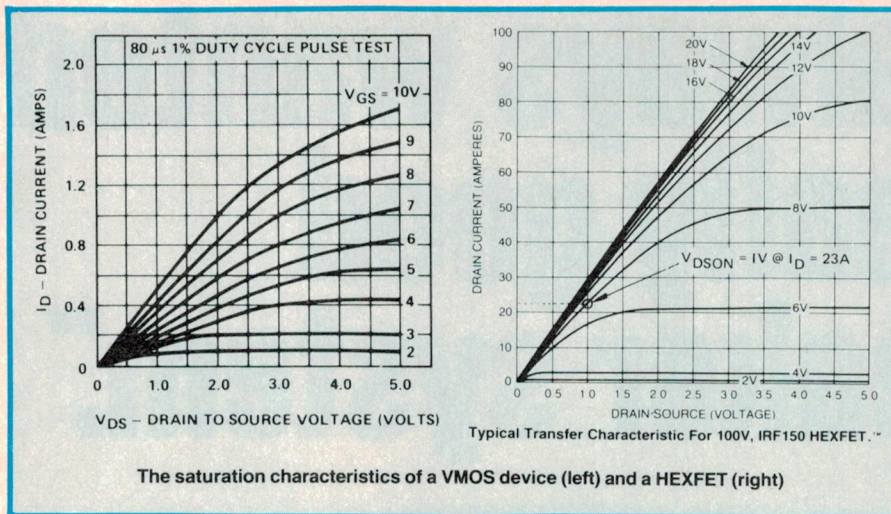


Figure 10. Capacitive touch switch will cycle on and off if finger is held on the sensor.

Figure 10 shows another touch switch designed by IIT Semiconductors, only a single touch point being used for on/off operation. When power is first switched on, T1 will conduct and T2 is kept non-conducting. Touching the sensor contacts will cause T2 to conduct and feedback from the drain of this device through the 4M7 resistor to the gate of T1 will keep the latter device in the non-conducting state. The 470nF capacitor now becomes charged.

If the sensor is touched again, the positive potential from this capacitor is transferred to the gate of T1 and the latter device is switched to conduction, whilst T2 is turned off. If the sensor is touched for longer than about one second, the circuit will operate as a relaxation oscillator which changes its state about once per second. The load impedances employed in this circuit need not be identical, any values from about 10 ohm to 10k being suitable.

## CMOS Interfacing

The 4000 series of CMOS logic devices can provide only small output currents, but sometimes one wishes to use the output from such a device to control a relay or other load which requires a relatively large current. A VMOS device can conveniently be employed to match the high output impedance of a CMOS device to a relatively low load


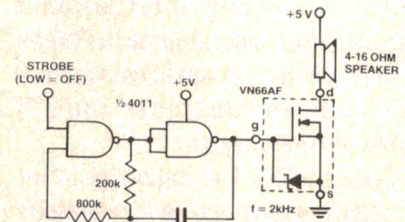
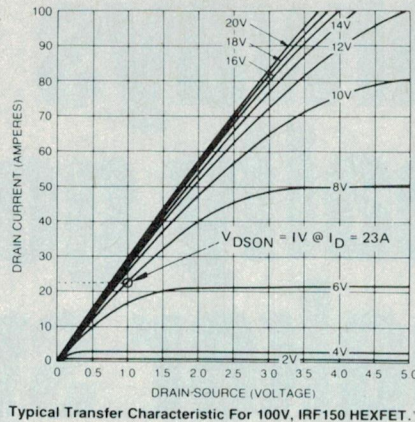


Figure 11. Audio alarm.

impedance such as a tungsten filament lamp.

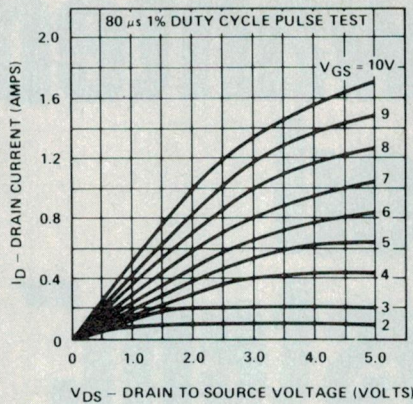An example is the audio alarm circuit of Figure 11. Two of the four logic gates of a CD4011 device are connected as a standard 2 kHz oscillator. Any appreciable current taken from the output of this oscillator affects the operation of the circuit, but the VN66AF requires negligible current and forms an ideal



Typical Transfer Characteristic For 100V, IRF150 HEXFET. \*

The saturation characteristics of a VMOS device (left) and a HEXFET (right)

uses in switching mode power supplies.

Other SIPMOS devices have ratings in the range of 50 V to 500 V, all being n-channel types. SIPMOS transistors can switch loads of up to 5 kW using inputs to the gate of less than 1 mA at 5 V. Maximum drain currents of up to 30 A can be handled, while on-resistance values can be as low as 0.03 ohm.

## Applications

Power MOSFET devices can be used as alternatives to power transistors and power Darlington devices in many applications, but they are generally more expensive than the latter and the circuit designer must decide which types of device are most suitable for his own application.

The use of power MOSFET products is particularly attractive when one can take advantage of their high switching speed or their high frequency capability. Although they may be somewhat more expensive than other transistors, the use of these new devices may simplify circuitry and reduce the overall costs. For example, a conventional power transistor requires a considerable current at its input and one or more driver stages may be required to provide this current, whereas the high input impedance of the power MOSFET enables the latter to operate with such small input currents that power driver stages can usually be eliminated.

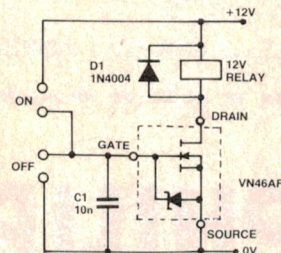


Figure 8. Simple touch switch.

## Simple touch switch

The circuit of Figure 8 shows how the very high input impedance of a VMOS power MOSFET can be employed in a simple touch switch. When the circuit is first switched on, the capacitor C1 is normally fully discharged, so the VN46AF VMOS device passes negligible drain current.

When the upper pair of contacts is touched, current flows from the +12 V line through the person's skin and charges C1. The VN46AF device is thus biased to conduction and the relay closes. If a finger is now placed across the lower touch contacts, C1 discharges and the VN46AF is turned off, opening the relay. The diode D1 is used to bypass the transient voltages formed when the current ceases to flow through the relay coil — such voltages can destroy MOSFETs.

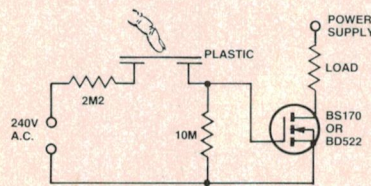


Figure 9. Capacitive touch switch.

## Capacitive touch switch

The gate circuit impedance of VMOS devices is so high that circuits can be designed as touch switches in which no part of the circuit is actually touched. In Figure 9 (designed by IIT Semiconductors), the presence of a finger just above the plastic material at the point of separation of the electrodes under the plastic is sufficient to cause current to flow in the load.

The capacitance between each of the electrodes and the finger allows a small alternating current to flow through the 2M2 safety resistor to the gate circuit of the small BS170 or the larger BD522 n-channel device.



interface device between the CMOS oscillator and the loudspeaker.

When the upper input of the left hand CMOS gate is connected to the +5 V line, oscillation takes place, but when this input is connected to ground, oscillation ceases. Thus a high impedance logic output can be used to switch the oscillator on and off through the use of this input to the left hand gate.

Figure 12 is an interesting variation of the circuit of Figure 11 in which the four gates of a 4011 device are used to form two oscillators. The two left hand gates form a sub-audio frequency oscillator which modulates the audio oscillator formed by the two right hand gates of Figure 12. Thus one obtains a much more impressive two-tone alarm sound than with the simpler constant-note circuit of Figure 11.

The timer circuit of Figure 13 is another example of VMOS interfacing between a CMOS device and a relay. In the quiescent state, the upper input to the left hand gate will be low and the output from this gate high. Thus the output from the right hand gate will be low and the relay will remain open.

If the start switch is momentarily closed, the high input applied to one input of the left hand gate will cause the output from this gate to go low, while the output from the right hand gate goes high and switches the VN46AF to conduction. Thus the relay closes.

The capacitor between the two gates charges slowly through the fixed and variable resistor from the positive supply line. When the inputs to the right hand gate become sufficiently high in potential, the output of this gate goes low and by feedback to the left hand gate the circuit switches back rapidly to its quiescent state in which

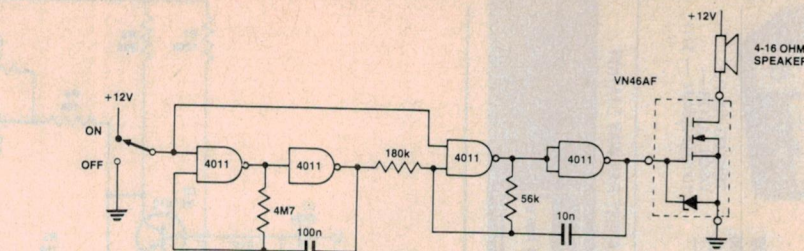


Figure 12. This two-tone alarm is a variation of the Figure 11 circuit.

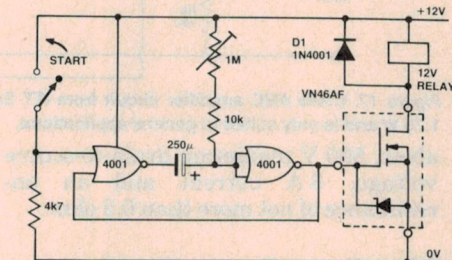


Figure 13. Simple timer has a variable range from a few seconds to a few minutes. The 1M pot sets the time the relay holds in.

negligible current passes through the relay. The length of time for which the relay remains closed can be set by the 1M pot or by altering the value of the capacitor connected between the two gates. When the values shown are used, times obtained range from a few seconds to a few minutes as the variable resistor is moved.

## Delay switch

A simple VMOS delay switch is shown in Figure 14. When the switch is closed for a moment, the capacitor becomes fully charged and the VN46AF passes current through the load. The capacitor slowly discharges through the 10M resistor, so the gate voltage of the VN46AF will eventually fall to a value where very little current can pass through the load.

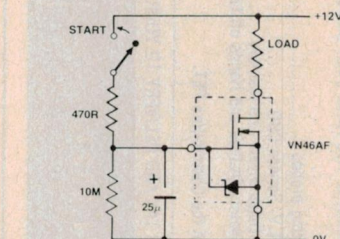


Figure 14. Simple delay timer. The load could be a lamp, relay or whatever.

## Auto applications

The fast switching ability of MOSFET devices renders them very suitable for use in vehicle electronic ignition systems. Timing pulses from a magnetic or other contactless pickup may be fed to an IC which provides a voltage output for the control of a MOSFET device. The latter switches the current through an ignition coil to provide the required high voltage.

An automobile circuit using a SIPMOS transistor as a power switch is shown in Figure 15. As in so many applications of MOSFET devices, the high input impedance of the SIPMOS device is utilised here, since it can be voltage driven by a suitable IC. This circuit is for an automobile alternator voltage regulator and has been designed for a SIPMOS device rated at ▶

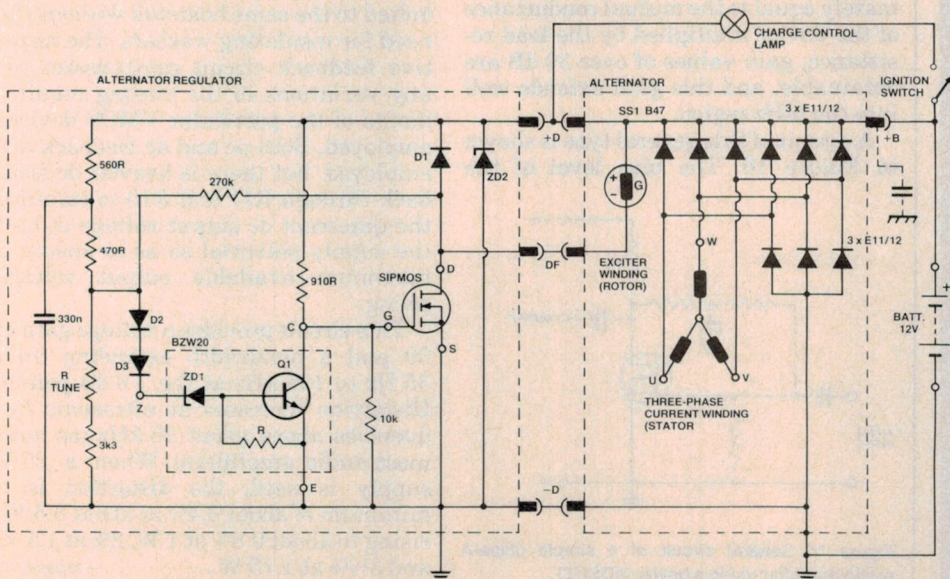


Figure 15. The latest power MOSFET development, SIPMOS, has already found application in automotive electronics. This circuit is an alternator regulator and employs a SIPMOS device rated at 500 V/8 A and an on-resistance not greater than 0.2 ohm.




### CHEAP LIFE INSURANCE

EARTH LEAKAGE PROTECTED POWER OUTLETS. These units detect leakage of current out of the circuit (possibly through your body!) and cut off power before a fatality can occur. If you have ever received an electric shock you must realize the worth of these units. From \$116. THE CHEAPEST LIFE INSURANCE YOU HAVE EVER BOUGHT.
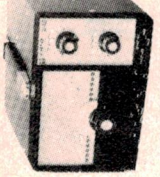
### SPECIALS

- TRIO CS-1560A II including probes ..... \$660.00
- TRIO CS-1572 30 MHz T.V. Service CHO ..... \$1095.00
- Telephone Press Button Dialer insert with memory ..... \$45.00.
- Wireless Telephones, Memory Dialers and Hands off telephones — prices on application.
- Ask about our special on the Commodore PET.



TRIO SG-402 R.F. OSCILLATOR — \$111  
100KHz-30MHz


### NEW-FEELINGS

Now your computer can Sense the Real World with sixteen 8 bit Analog inputs with our DAM (Data Acquisition Module). Measure Temperature, Light, Pressure, Distance, Db, etc., etc. — it's an experimenter's delight while being a useful tool for Computer Control and Measurement.

COMPLETE SET FOR PET (including power supply and interface modules) \$449.00 including tax.

Sets for other computers and sensors available shortly . . . prices on application.

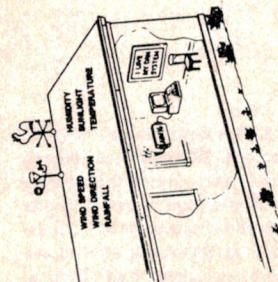P.S. We handle the complete Commodore Computer, Product range and Trendcom Printers (at competitive prices).



WIND SPEED  
WIND DIRECTION  
HUMIDITY  
BRIGHTNESS  
TEMPERATURE  
RANGE ALL

P.O. BOX 1053.  
RICHMOND NORTH, 3121.  
PH.(03)415708

**ADIBLE ELECTRONICS**

### Simple audio applications

The excellent linearity of VMOS devices has attracted considerable interest in their possible use in the audio field but the relatively high price of these devices and their previously limited power handling capability retarded their adoption until recently. They may be used in simple, low-power circuits, but moderately high power ultra-low distortion circuits have also been designed using VMOS devices. The very fast switching ability of VMOS devices also makes them very suitable for Class D pulse width modulation circuits.

To operate a VMOS device as a simple class A amplifier, it is only necessary to provide a bias network so that the device operates in its linear region without cutoff. The gate is connected to a tap on a resistive potential divider across the power supply lines and the input signal is capacitively coupled to the gate. The gain will be approximately equal to the mutual conductance of the device multiplied by the load resistance; gain values of over 30 dB are obtainable, and this gain extends well into the MHz region.

A circuit of this general type is shown in Figure 16. The bias level of the

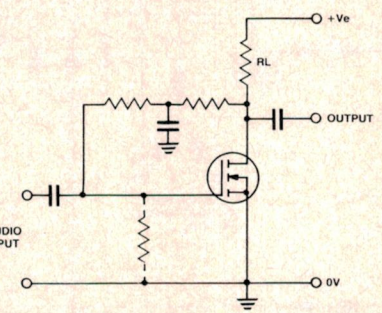


Figure 16. General circuit of a simple class-A audio amplifier using a power MOSFET.

### Class ABC amplifier circuit

The circuit shown in Figure 17 is a Class ABC amplifier. It consists of a BC107C transistor (Q1) in the input stage, followed by a BD512 p-channel VMOS device (Q2) in the output stage. The circuit includes various resistors (R1-R11) and capacitors (C1-C3) for biasing and coupling. The output is connected to a 15 OHM SPEAKER. The power supply is +Ve and the ground is 0V.

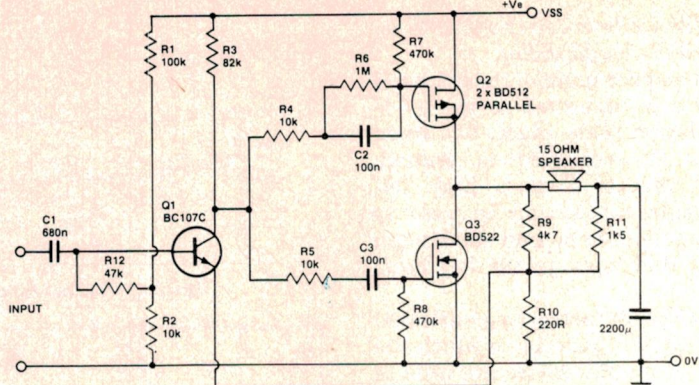


Figure 17. Class ABC amplifier circuit from ITT Semiconductors is simple but has 3½% distortion at 1.75 W and is only suited to general applications.

about 500 V maximum drain-to-source voltage, 8 A current and an on-resistance of not more than 0.2 ohm.

VMOS device is stabilised by means of negative voltage feedback from the drain to the gate circuit.

Figure 17 shows a particularly interesting circuit from ITT Semiconductors which they call a class ABC amplifier, since it is basically a Class B amplifier, but one of the transistors is more in Class A, while the other is definitely in Class C. It is a simple circuit not designed for particularly low distortion.

The output stage is unusual in that it comprises two BD512 p-channel VMOS devices in one part and a complementary BD522 single device in the other part. This is because hole mobility in the p-channel BD512 is only half that of the electron mobility in the n-channel BD522s so two p-channel devices are required to obtain about the same mutual conductance as that provided by the single n-channel device. As explained earlier, MOSFETs can be connected in parallel without extra circuitry because they automatically share the current.

As the drain electrodes of the VMOS devices in Figure 17 are connected to the device tabs, all of the tabs can be bolted to the same heatsink without the need for insulating washers. The negative feedback circuit compensates for any variations in the biasing requirements of the particular VMOS devices employed. Both ac and dc feedback are employed, but there is heavier dc feedback through R11 and R10 to stabilise the quiescent dc output voltage at half the supply potential so as to ensure a maximum available output voltage swing.

This circuit provides a voltage gain of 30 and a bandwidth extending from 35 Hz to 125 kHz at the -6 dB points. Distortion increases at ultrasonic frequencies above about 25 kHz (as with most audio amplifiers). When a 25 V supply is used, the distortion is a minimum of about 0.4% at about 0.5 W, rising to about 0.8% at 1 W, 2% at 1.5 W and 3½% at 1.75 W.

— to page 135 ►



# Technics SL-10

*Sounds  
Alive*

Quartz-Phase-Locked  
Control Direct-Drive  
Turntable with Linear Tracking  
Tonearm



## Marking the 10th anniversary of the direct-drive turntable.


It has been 10 years since Technics introduced the world's first direct-drive turntable, the SP-10. When it was introduced this turntable had less wow and flutter and better speed accuracy than the cutting lathes used to make records. And because the drive system did not use rubber parts like belts and idler wheels, it insured that its excellent specifications would be retained for a long time.

Six years after the introduction of the SP-10, Technics brought out an improved version, with higher torque and quartz control. Today, more than 1500 of these SP-10MKII's are used by broadcasters in 27 countries around the world. In the past two years, Technics has added quartz synthesizer control to various models, permitting the precision of quartz to be retained in speeds above and below the standard 33-1/3, 45 and 78 rpm.

More significant to the consumer, Technics has also developed direct-drive turntables which have a very high degree of precision, yet cost much less than the professional grade models. It is possible to get numerous Technics direct-drive turntables in the popular price range, yet with specifications that were obtainable only in very expensive equipment a few years ago. With the SL-10, Technics continues to lead the industry in turntable innovation. This new turntable represents as radical a departure from conventional design as did the SP-10 ten years ago.

It has the same width and depth dimensions as an LP record jacket, yet within the compact package are an amazingly precise drive system, a gimbal suspended linear-tracking tonearm, a high-grade moving coil cartridge, plus extensive control systems which permit even a complete hi-fi novice to use the SL-10 without any problem. Nearly every operation is automated, with the upper and lower halves of the cabinet closed during record play. And the tonearm is designed so that the system can be stood vertically without any sacrifice in tracking accuracy. The SL-10 marks as great a step forward in convenience as did the development of cassette tapes versus the open-reel format. Yet there is absolutely no loss in reproduction quality. On the contrary, numerous factors in the SL-10's design will significantly enhance the sound from records.
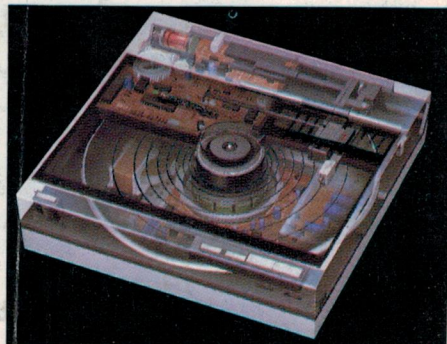
## Technics changes the face of turntable technology . . . again.




# Technics

For further information contact The Technics  
Advisory Service,  
P.O. Box 319, North Ryde 2113

TT2.80


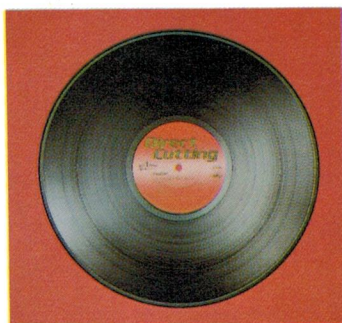
# UNTIL WE DEVELOPED THE STEREO GROOVE, HI-FI WAS PRETTY HO-HUM!



The world of hi-fi owes a lot to the original and continuing innovation of JVC. Few companies, if any, have done as much to help turn records and record-players into the virtual musical instruments they are today . . . or to lead the way in developing so many *firsts* in the more recent concepts of sound amplifiers, cassette decks and computer-designed speaker

systems. Hi-fi, as we know it today, had its beginnings in 1956, with JVC's development of the 45°/45° groove for stereo records. The fact that this system still remains as the world standard is, in itself, outstanding testimony to the technology of JVC. The development revolutionised not only the record-making industry, in which we've been involved since 1930; it also paved the way for enormous advancement in the design and engineering of record-playing equipment. Now, hi-fi has expanded to



R-S77. Super-A FM/AM Stereo receiver

embrace a wealth of highly-sophisticated electronic equipment; and it's not surprising that JVC has continued to play a leading role in so much of its development.




HR-3660 EA. VHS Colour Video Cassette recorder

## THAT WASN'T OUR ONLY FIRST, EITHER.

We also pioneered Japan's television industry, introducing their first TV receiver just over 40 years ago. A more recent innovation is VHS, the home video recording system now gaining world-wide acceptance as *the* system for such equipment. In the course of staying ahead, we've introduced a number of world *firsts* of radical importance: the Quartz Lock turntable is one of them.
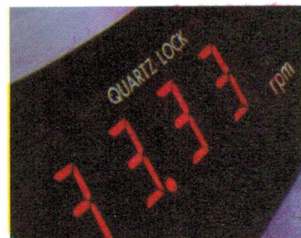
## THE QUARTZ LOCK TURNTABLE. MANY TIMES MORE ACCURATE.

It stands to reason that if your equipment is at the top end of the range, then your turntable must be capable of comparable performance. Only Quartz Lock ensures this, tying the speed of the turntable to the unvarying pulse of the atom, and providing a level of accuracy far in excess of conventional turntables.



## MORE MILESTONES IN HI-FI.

To match the superb quality of Quartz Lock, we produced the S.E.A. graphic equalizer system. Then we refined it to such a degree it even compensates for the effect your furniture has on sound when it leaves the speakers! To expand the capabilities of tape, we designed ANRS and




SEA-80. Stereo Graphic Equalizer

Super ANRS — automatic noise reduction systems which not only reduce distortion and 'hiss' but actually extend the dynamic range of the tape. Similarly, with speakers: at JVC we employ computers in their design to help provide the ultimate in sound reproduction.
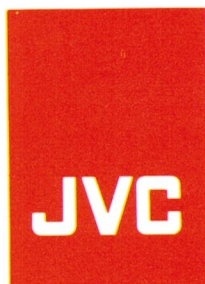
## AND NOW, SUPER-A.

In its own way, as significant a hi-fi development as the stereo groove. Imagine an amplifier which combines the *best* features of the two recognised amplifier classes (A and B) . . . an amp which combines the *efficiency* of one with the *low distortion* of the other. Some engineers said it couldn't be done; but not those at JVC. Enter the Super-A amplifier . . . the *latest JVC first!*

Distributed and Serviced by...  
**HAGEMEYER**



the right choice

## THE FUTURE.

It's already with us. For instance, we were so far ahead in the new metal tape technology that our cassette decks were metal-compatible before the tapes were generally available. And now there's the JVC Electro-Dynamic Servo Tonearm, damping tonearm resonance by means of a purely electronic system and two 'thinking' linear motors. Who was it who dubbed JVC, 'the innovators'?





## Chicken little rides again!

Our page 8 story (News Digest) on the Earth's magnetic field flipping should bring a rash of 'chicken little' doom predictors out of the woodwork of Nostradamus's coffin. Not because they've read ETI — the original report was in Science News, 117:407, 1980 — but because it's been widely reported in the scientific press and has just begun filtering through the fringe "scientific phenomena" press.

This declining trend in the Earth's magnetic field goes way back to 1830 when Gauss himself had a few words to say on the subject. The geological record certainly registers a long history of magnetic field decline-and-reversals (the science of paleomagnetology covers the field). Coincident with these reversals is geological/paleontological evidence of great biological changes and it is this that sets the doomsayers off. If any readers are around in about 1200 years time, I'd like to know what happens (assuming retrospective communications has been invented — we've already allocated Project Number 435 678 to it).

Two papers in a recent issue of that erudite and widely respected journal, Nature, should send the chicken litters into paroxysms of 'I-told-you-so's. Kenneth Hsu's paper titled "Terrestrial

Catastrophe Caused by Cometary Impact at the End of Cretaceous", Nature 285:201-203, 1980, attributes the extinction of large terrestrial animals (dinosaurs to you) to the effects of a cometary impact with the Earth heating the atmosphere and releasing cyanide. What a way to go! The second paper, by Smit and Hertogen, titled "An Extraterrestrial Event at the Cretaceous-Tertiary Boundary", Nature 285:198-200, 1980, takes a look at planktonic and nanofossils (nF?) in the sedimentary record and finds their extinction is coincident with enrichments of iridium and osmium, attributed to an extraterrestrial source such as the impact of a large meteorite.

Let's hope Halley's Comet — due 1985 — isn't off course. We won't know until it gets within the vicinity of the solar system. It returns roughly every 76 years (so far). If Halley's comet remains reliable then perhaps we should start sweating over Tempel 2, due 1988.

Maybe it's all too remote. We've probably got more to worry about at home. Like some radical group getting a homemade atom bomb together. Did you see the April 1979 issue of Analog magazine? Aptly timed was an article on the ins and outs of making your own atom bomb. Precis is — forget it, you should live that long! I note

the same article made it into New Scientist earlier this year and is beginning to appear in the fringe press. No doubt Dick Smith (tongue firmly in cheek distorting that well known grin) will shortly offer a kit (say, \$20 million?).

If it wasn't for Dregs, Spike Milligan books and The Goon Shows etc, your Editor would have taken up mysticism long ago.

## Awful Puns Competition

All you awful punsters out there are giving us a veritable paroxysm in the penultimate page. This contest is so crazy, even the **staff** are entering. William Fisher (see column one, page 8 this issue) contributed one with a real 'electronics flavour': "What do you get if you poke a resistor into each end of a Jelly Bean? — ohm-sweet-ohm!". Sorry William, but this month's penultimate page pun prize goes to young Bruce Harris of Goroke in Victoria, who sent in no less than six, the best/worst being a possible newspaper headline: "Bright Spark Discharged in Power Dispute". A copy of Test Gear 2 is on its way Bruce.

Keep those entries coming. See this page in the July issue for details. Send entries to: The Great Dregs Awful Puns Competition, ETI Magazine, 15 Boundary St, Rushcutters Bay NSW 2011.





Editor  
**Roger Harrison VK2ZTB**

Technical Editor  
**David Tilbrook VK2YMI**

Project Manager  
**Phil Wait VK2DKN**

Editorial Staff  
**William Fisher B.Sc. (Hons)**  
**J.B. Scott B.Sc./B.E. (Hons)**  
**VK2YBN**

**Jan Vernon B.A.**

Art Direction and  
technical photography  
**Ivy Hansen**

Layout  
**Bill Crump**

Reader Services  
**Jan Collins**

Managing Editor  
**Collyn Rivers**

Acoustical Consultants  
**Louis Challis & Associates**

Editorial and Sales Office  
**4th Floor, 15 Boundary St**  
**Rushcutters Bay NSW 2011**  
**Ph: 33-4282; Tlx: 27243**

Sales Manager: **Bob Taylor**  
Sales Admin: **Jan Collins**  
(address as above)

**Melbourne**  
Bill Philpott  
150 Lonsdale St  
Melbourne Vic 3000  
Ph: 662-1222; Tlx AA34543

**New Zealand**  
Geoff Collins  
P.O. Box 39163  
Tel: (9)760-150  
Auckland NZ

**Adelaide**  
Admedia Group  
24 Kensington Rd  
Rose Park SA 5067  
Ph: 332-8144; Tlx AA82182

**United Kingdom**  
Australian Consolidated Press  
Ludgate House  
107 Fleet St  
London EC4A 2AL  
Ph: 353-1040; Tlx: 267163

**Brisbane**  
Geoff Horne Agencies  
60 Montanus Drive  
Bellbowrie QLD 4070  
Ph: 202-6229

**Japan**  
Genzo Uchida  
Banchō Media Services  
15 Sanyei-cho  
Shin juku-Ku  
Tokyo 160  
Ph: 359-8866  
Cable: Elbanchorito

**Perth**  
Aubrey Barker  
133 St Georges Terrace  
Perth WA 6000  
Ph: 322-3184; Tlx: AA93810

**USA**  
Peter Samuel  
Australian Consolidated Press  
444 Madison Avenue  
New York NY 10022  
Ph: 751-3383; Tlx: 620892

Electronics Today International is published by Modern Magazines (Holdings) Ltd, 15 Boundary St, Rushcutters Bay, NSW 2011. It is printed (in 1980) by Wilke & Co, Browns Rd, Clayton, Victoria and distributed by Gordon and Gotch. Recommended retail price only.

### Reader Enquiries

**By Mail:** There is no charge for replies but a foolscap-size stamped addressed envelope **must** be enclosed. Queries relating to projects can **only** be answered if related to the item as published. We cannot advise on modifications to projects, other than errata or addenda, nor if a project has been modified or if components are otherwise than specified. We try to answer letters as soon as possible. Difficult questions may take time to answer.

**By phone:** We can only answer readers' technical enquiries by telephone **after 4.30 pm**. In enquiring by telephone about back issues or photostats, please ask for the "Subscriptions Department". **33-4282**

### ORDER FORM

I enclose \$ . . . . . for (tick appropriate box/es):

NAME . . . . .

ADDRESS . . . . .

. . . . . POSTCODE . . . . .

- ☐ Subscriptions \$21.50 per year within Australia \$ . . . . .  
\$27.00 overseas (surface mail) \$ . . . . .  
Airmail rates on application.
- ☐ Back issues (\$2.50 from April 1977 on)
- ☐ or photocopies (\$2.50 per article per issue)

Project No. . . . . Month . . . . . Year . . . . . \$ . . . . .  
Project No. . . . . Month . . . . . Year . . . . . \$ . . . . .  
Project No. . . . . Month . . . . . Year . . . . . \$ . . . . .  
Project No. . . . . Month . . . . . Year . . . . . \$ . . . . .

\* Please attach a list if more than four required.

- ☐ Binders No. . . . . @ \$6.10 each in NSW \$ . . . . .  
No. . . . . @ \$7.50 each other states \$ . . . . .

### ALL PRICES INCLUDE POSTAGE

Send orders to: **ETI, 4th Floor, 15 Boundary St,**  
**RUSHCUTTERS BAY NSW 2011 Phone: (02)33-4282**



# KITS for projects

WE GET MANY enquiries from readers wanting to know where they can get kits for the projects we publish. This list is a guide to suppliers of kits and components for ETI projects.

We have listed here most of the projects published over the last few years which are either available as kits or can still be made up by shopping around for components. Suppliers listed against a particular project will either stock it as a kit or stock the pc board plus the other components.

## Printed circuit boards

Those suppliers listed against specific projects here are able to supply pc boards for those projects. Printed circuit boards for every project ever published in ETI are available through the following companies (to the best of our knowledge):

RCS Radio      Radio Despatch Service  
651 Forest Rd    869 George St  
Bexley NSW      Sydney NSW 2000

For current projects and a more comprehensive list of pc board suppliers refer to the Shoparound page in this and previous issues. This list will be updated roughly every four months.

## Key to Companies

- A Applied Technology Pty Ltd, 1A Paterson Avenue, Waitara, NSW 2077. Ph. (02) 487-2711.
- B Electronic Agencies, 115 Parramatta Road, Concord 2137. Ph. (02) 745-3077
- C J.R. Components, PO Box 128, Eastwood, NSW 2122. Ph. (02) 85-3385.
- D Dick Smith Electronics P/L, Cnr Waterloo & Lane Cove Roads, North Ryde, 2113. Ph. (02) 888-3200.
- E All Electronic Components, 118 Lonsdale Street, Melbourne, Vic 3000. Ph. (03) 662-3506.
- F Tasman Electronics, 12 Victoria Street, Coburg, Vic 3058. Ph. (03) 354-5062.
- J Jaycar Pty Ltd, PO Box K39, Haymarket, NSW 2000. Ph. (02) 211-5077.
- K S M Electronics, 10 Stafford Court, Doncaster East, Vic 3109. Ph. (03) 842-3950.
- L Ellistronics, 289 Latrobe Street, Melbourne, Vic 3000. Ph. (03) 602-3282.
- M Mode Electronics, PO Box 365, Mascot, NSW 2020. Ph. (02) 666-6324.
- N Nebula Electronics Pty Ltd, 15 Boundary Street, Rushcutters Bay, NSW 2011. Ph. (02) 33-5850.
- O Orbit Electronics, PO Box 7176, Auckland, New Zealand.
- P Pre-Pak Electronics, 718 Parramatta Road, Croydon, NSW 2132. Ph. (02) 797-6144.
- R Rod Irving, PO Box 135, Northcote, Vic 3070. Ph. (03) 489-8131.
- V Silicon Valley, 23 Chandos Street, St. Leonards, NSW 2065. Ph. (02) 439-4655.
- W Willis Electronics, 993 Hay Street, Perth, WA 6000. Ph. (09) 321-7609.
- Y Trilogy, 40 Princes Highway, Fairy Meadow, NSW 2519.

## Project Electronics

- 041 Continuity Tester ..... W,R,D,B,Y,L
- 042 Soil Moisture Indicator ..... R,B
- 043 Heads or Tails Circuit (Oct 76) ..... W,R,D,E,A,F,B,Y,L
- 044 Two Tone Door Bell (Oct 76) ..... W,R,D,E,O,A,F,B,Y,L
- 045 500 Second Timer ..... W,D,E,A,B,Y,L
- 047 Morse Practice Set ..... W,D,O,A,B,Y,L
- 048 Buzz Board ..... W,D,A,B,Y,L
- 061 Simple Amplifier (Oct 76) ..... W,R,D,E,A,B,Y,L
- 062 Simple AM Tuner (Mar 77) ..... W,D,E,B,Y
- 063 Electronic Bongos ..... R,D,A,B,Y,L
- 064 Simple Intercom (Nov 76) ..... W,A
- 065 Electronic Siren ..... W,R,D,E,O,A,B,Y,L
- 066 Temperature Alarm (Dec 76) ..... W,D,E,A,B,Y,L
- 067 Singing Moisture Meter ..... D,B,Y
- 068 LED Dice Circuit (Oct 76) ..... W,R,D,E,A,B,L
- 070 Electronic Tie Breaker (Jan 77)
- 071 Tape Noise Limiter (Jun 78) ..... R,E,F
- 072 Two-Octave Organ (Jun 78) ..... W,D,B,Y
- 081 Tachometer (Mar 77) ..... W,E,O
- 082/
- 528 Intruder Alarm ..... W,R,E,A
- 083 Train Controller ..... W,R,E,L
- 084 Car Alarm ..... W,R,D,E,A,B,Y,L
- 085 Over-rev Alarm ..... W
- 086 FM Antenna ..... W
- 087 Over-LED ..... W,E
- 088 Hi-Fi Speaker ..... W

## Test Equipment

- 132 Experimenter's Power Supply (Feb 77) ..... E,O
- 133 Phase Meter (Apr 77) ..... E
- 134 True RMS Voltmeter (Aug 77) ..... E
- 135 Digital Panel Meter (Oct 77) ..... E
- 136 Linear Scale Capacitance Meter (Mar 78)
- 137 Audio Oscillator (May 78) ..... W,D,E
- 138 Audio Wattmeter (Nov 78) ..... E,B
- 139 SWR/Power Meter (May 78)
- 140 1GHz Frequency Meter-timer (Mar 78)
- 141 Logic Trigger (Jan 79) ..... E
- 142 High Current Power Supply (Feb 79) ..... W,E
- 143 Curve Tracer (Jan 79) ..... W
- 144 Expanded-scale RMS Voltmeter (Jun 79) ..... E
- 148 Versatile Logic Test Probe (Jul 79) ..... E,L

## Simple Projects

- 243 Bip Beacon (Apr 77)
- 244 Alarm Alarm (Feb 77) ..... F
- 245 White Line Follower (Nov 77) ..... F
- 246 Rain Alarm (Apr 78) ..... F
- 248 Simple 12V to 22V Converter (Jul 78) ..... W
- 249 Electronic Combination Lock (Apr 79) ..... E
- 252 The Passionmeter (Aug 79)
- 253 Electronic Grenade (Hot Potato) (May 79)
- 254 Egg Timer (Jun 79) ..... W

## Motorists' Projects

- 316 Transistor Assisted Ignition (May 77) ..... W,E,O,K
- 317 Rev. Monitor Counter (Jul 77) ..... E
- 318 Digital Car Tacho (Jul 78) ..... W,E,K
- 319 Variwiper MK II (Sep 78) ..... W,E,O
- 320 Battery Condition Indicator (Apr 79) ..... E,L

## Audio Projects

- 448 Disco Mixer (Nov 76) ..... W
- 449 Balanced Microphone Amp (Nov 76) ..... W,D,E,J,F,Y
- 450 Bucket Brigade Audio Delay Line (Dec 77) ..... W,E
- 451 Hum Filter (Jul 79) ..... D,E,F
- 470 60 W Amp Module (May 79) ..... W,R,E,F,B,P,L,A,V
- 471 High Performance Stereo Preamp Control Unit (Jun 79) ..... W,R,E,F,B,P,A,V,L
- 472 Power Supply — the Series 4000 Stereo Amp (Jul 79) ..... W,R,E,F,B,V,L
- 473 Series 4000 Moving-coil Cartridge Preamplifier ..... F,J
- 480 50-100 Watt Amp Modules (Dec 76) ..... A,W,R,D,E,J,O,Y,L
- 481 12V 100 Watt Audio Amp (May 77) ..... R,E
- 481 High Power PA/Guitar Amp (Jun 77) ..... W
- 482 Stereo Amp (Jan 77) ..... O,E
- 482 Stereo Amp Part 2 (Feb 77) ..... O,E
- 483 Sound Level Meter (Feb 78) ..... E
- 484 Simple Compressor Expander (Jul 77) ..... A,E
- 485 Graphic Equaliser (Jun 77) ..... W,E,J,O
- 486 Howl-round Stabiliser (Nov 77) ..... J
- 487 Audio Spectrum Analyser (Feb 78) ..... E
- 489 Audio Spectrum Analyser 2 (Apr 78) ..... E,J
- 490 Audio Compressor (Dec 78)
- 491 Simple Graphic Equaliser (Mar 79) ..... W,E
- 495 Transmission Line Speakers (Aug 77)

## Miscellaneous

- 546 GSR Monitor (Mar 77) ..... W,E
- 547 Telephone Bell Extender (Jun 77) ..... E
- 548 Photographic Strobe (May 77) ..... W,E
- 549 Induction Balance Metal Detector (May 77) ..... W,D,E,L
- 550 Digital Dial (Aug 78) ..... E,O
- 551 Light Chaser (Sep 78) ..... W,E,O
- 552 LED Pendant (Sep 78) ..... A
- 553 Tape/Slide Synchroniser (Oct 78) ..... E
- 556 Wind Speed/Direction Indicator (Dec 78)
- 557 Reaction Timer (Feb 79) ..... E
- 558 Mast-head Strobe (Feb 79) ..... E
- 559 Cable Tester (Mar 79)
- 575 Portable Fluorescent Light Wand for Car, Camping (Aug 79) ..... W
- 577 General Purpose Power Supply ..... J
- 581 Dual Power Supply (Jan 77) ..... W,E,Y
- 582 House Alarm (Jul 77) ..... W,E,O,A
- House Alarm — Installation Instructions (Aug 77) ..... W
- 583 Marine Gas Alarm (Aug 77) ..... D,E,M
- 585 Ultrasonic Switch (Sep 77) ..... R,D,E,O,F
- 586 Shutter Speed Timer (Oct 77) ..... E
- 587 UFO Detector (May 78)
- 588 Theatrical Lighting Controller (Nov & Dec 77 Jan & Mar 78) ..... N
- 589 Digital Temperature Meter (PCB135) (Dec 77) ..... E
- 590 LCD Stopwatch (Oct 78) ..... O,N
- 591 Up/Down Presettable Counter (Jul 78) ..... D,E
- 592 Light Show Controller (Aug 78) ..... E
- 593 Colour Sequencer (Dec 78)
- 594 Development Timer (Apr 79) ..... E
- 595 Aquarium Lamp Controller (May 79)

## Electronic Music

- 602 Mini Organ (Aug 76) ..... W,D,E,A
- 603 Sequencer (Aug 77) ..... W
- 604 Accentuated Beat Metronome (Sep 77) ..... E
- 605 Temp Stabilized Log-exponential Converter (Sep 78)

## Computer Projects

- 630 Hex Display (Dec 76) ..... E,A
- 631 ASCII Keyboard (Dec 76) ..... W,E,O,A
- 631 Keyboard Encoder (Apr 77) ..... W,E,O,A
- 632 Video Display Unit (Jan 77) ..... A,E,O
- 633 TV Sync Generator (Jan 77) ..... A,E
- 634 8080 Educational/Prototyping Interface (Jul, Aug 78)
- 635 Microcomputer Power Supply (Sep 77) ..... O
- 637 Cuts Cassette Interface (Jun 78) ..... V,E,A
- 638 Eprom Programmer (Jul 78) ..... W,E,A
- 639 Computerised Musical Doorbell (Mar 78)
- 640 S100 VDU (Apr, May, Jun 78) ..... W,O,A,V
- 641 S100 Printer (Sep 78) ..... O
- 642 16k S100 RAM Card (Feb 79) ..... K
- 650 STAC Timer (Nov 78) ..... A,E,L
- 651 Binary to Hex Number Converter (Jun 79) ..... E

## Radio Projects

- 712 CB Power Supply (Jun 77) ..... W,E
- 713 Add-on FM Tuner (Sep 77)
- 714 VHF-Log-Periodic Antenna (Feb, Mar 78)
- 715 VHF Power Amplifiers (Nov 77)
- 716 VHF Power Amplifiers (Jan, Feb 78)
- 717 Crosshatch Generator (May 78) ..... W,D,E,A,Y
- 718 SW Radio (Oct 78) ..... E
- 719 RF Field Strength Indicator (Nov 78)
- 720 2m VMOs Power Amp (Jan 79)
- 721 Aircraft Band Converter (Mar 79) ..... W,E
- 722 Antenna for Aircraft Band Converter (May 79)
- 724 Microwave Oven Leak Detector (Jul 79) ..... D,E,B
- 725 Simple SSB Generator employs Polyphase Network using Standard Components (Aug 79) ..... E,L
- 730 Get Going on Radioteletype (Aug 79) ..... E,L

## Electronic Games

- 804 Selectagame (Nov 76) ..... O
- 804 Selectagame (Rifle Project) (Mar 77) ..... O
- 805 Puzzle of the Drunken Sailor (Oct 77)
- 806 Skeet (Jan 78) ..... O
- 810 Stunt Cycle TV Game (Jun 78) ..... D,O
- 811 TV Tank Game (Oct 78) ..... O
- 812 Wheel of Fortune (Dec 78)
- 813 Race Track Game (Jan 79) ..... O
- 814 The 'Dinky-Die' (Aug 79)





## Because it's hard enough getting a home together, we've put all this cover together.

Six insurance covers in one.

It's called the AGC Insurance Executive policy for homeowners and householders.

And it saves you dealing with six different insurance companies and worrying about six different policies.

You get one simple policy.

Up to six kinds of cover.

It's a policy that's never been beaten.

### **Your home itself.**

AGC provides insurance cover for your home. Even garages, out buildings and swimming pools.

And we also offer you the New Rebuilding Cover alternative.

These days there is generally a big difference between the current value of your home and what it would cost if you had to rebuild.

AGC's Rebuilding Insurance protects you automatically against inflation. And the increased cost of building materials.

### **The contents of your home.**

We'll cover household goods and personal effects of every description.

No depreciation on goods or articles less than 5 years old. (Excluding linen and clothing.)

### **Specified personal property anywhere in Australia**

We'll also cover the special things you value.

Very valuable objects such as furs, jewellery, paintings and the like.

### **Other essential protection.**

Your AGC Executive policy can also give you cover against Personal Legal Liability

Death of nominated person by accident.

And, if you employ domestic help, workers' compensation (not applicable in Queensland).

With AGC's Executive policy you're not only covered by up to six different types of insurance.

You're covered by a big name – **AGC Insurances.**

Sydney: Phillip & Hunter Streets.

Melbourne: 31 Spring Street.

Brisbane: Tank Street & North Quay.

Adelaide: 10 Pulteney Street.

Perth: 165 Adelaide Terrace.


Hobart: 161 Collins Street, and offices throughout Australia.

AGC (Insurances) Limited. A division of Australian Guarantee Corporation Limited in which the Bank of New South Wales is the major shareholder.

AGC 994 FCB


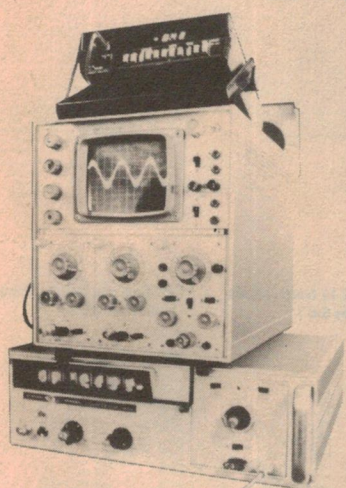
# How to crack a highly paid job as an electronics technician.



We'll give you  
excellent training  
- as good as you'll  
get anywhere in  
Australia.

We'll give you  
free medical,  
dental and hospital  
treatment.

We'll provide plenty of good tucker  
and a comfortable place to stay.

We'll give you substantial leave,  
and on top of all that, we'll pay you well  
while you're training.

On your side, you'll give us a period  
of hard, but interesting and rewarding  
work. And, when eventually you leave  
us, you'll find yourself a fully qualified  
and experienced Electronics  
Technician. Not a bad  
thing to be, these days.

So, if electronics is your  
idea of a great career and  
you are (at time of entry)  
approx. 15 to 17 for apprenticeship

and over 17 for an Adult Trainee,  
join the Navy, Army or Air Force.

Phone us at:

Adelaide 223 2891. Brisbane 226 2626.

Canberra 822 333 Hobart 34 7077.


Melbourne 61 3731. Perth 325 6222.

Sydney 212 1011.

Write to either the Navy, Army  
or Air Force Electronics Technician  
Counsellor, GPO Box XYZ in your  
nearest State Capital City (please

include your  
date of birth).

**Learn  
Electronics  
with us.**

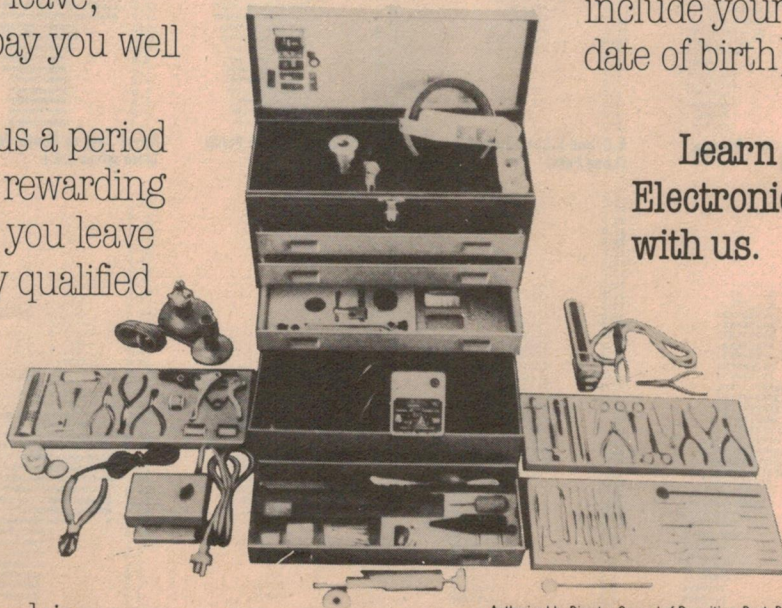

Authorised by Director-General of Recruiting, Dept. Defence.  
TSAP15.FP.48




# PREDICTIONS

DECEMBER 1980

Covering 3 MHz to 40 or 60 MHz, these predictions show the times radio contact is possible between the areas designated beneath each graph, as well as the possible 'mode' and reliability. Vertical columns indicate time — commencing at 0000 UT on the left, to 2300 UT at right. For reliable predictions follow the times and frequencies indicated by the F character.

Complete information on using these predictions can be obtained by sending a stamped, self-addressed envelope to:-

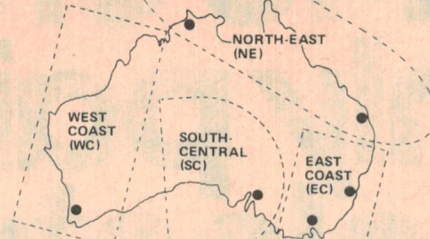ETI — Predictions  
3rd floor 15 Boundary St  
RUSHCUTTERS BAY NSW 2011.



These GRAFEX style computer generated predictions are provided courtesy of the Australian Ionospheric Prediction Service, Dept. of Science & the Environment.

## KEY TO SYMBOLS

\*See page 153 about changes

A blank area means no normal propagation is possible.

● . . . path open less than 50% of days in month.

% . . . path open 50-90% of days in month.

F . . . path open at least 90% of days in month.

X . . . complex mixture of modes. Expect abnormal propagation.

M . . . propagation possible by both 1st and 2nd F-layer modes. Expect strong fading.

S . . . propagation possible by 2nd mode (also 3rd and mixed E and F modes). Expect strong fading, weak signals.

A . . . High absorption indicated. Expect weak signals.

60.0 58.5 57.0 55.5 54.0 52.5 51.0 49.5 48.0 46.5 45.0 43.5 42.0 40.5 39.0 37.5 36.0 34.5 33.0 31.5 30.0 28.5 27.0 25.5 24.0 22.5 21.0 20.0 18.5 17.0 15.5 14.0 12.5 11.0 9.5 8.0 6.5 5.0 3.5 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0 11.0 10.0 9.0 8.0 7.0 6.0 5.0 4.0 3.0 2.0	40.0 39.0 38.0 37.0 36.0 35.0 34.0 33.0 32.0 31.0 30.0 29.0 28.0 27.0 26.0 25.0 24.0 23.0 22.0 21.0 20.0 19.0 18.0 17.0 16.0 15.0 14.0 13.0 12.0
--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--



# Spotlight on precision.



The Sanwa name has long been associated with high quality reliable test instruments and has gained wide acceptance in many areas including Telecom, military establishments, research, educational, trade and hobbyists. The above represents a selection of some of the more popular instruments from the comprehensive Sanwa power line up.

## The "NO SWEAT" Insulation and Low $\Omega$ Meter

### PDM 500c

- One man operation—no handle to crank.
- No wearing parts—solid state for long trouble-free life.
- Large easily read scale.
- Simple push-button operation.

## High Performance—Rugged Construction

### 460 ED

- 10 $\mu$ A movement in a heavy-duty case.
- 12A A.C./D.C. measurement capability.
- Maintenance simplified with detachable indicator block.
- Polarity reversal switch.

## Top of the Line—for Lab and Bench

### N501

- VTVM performance with constant 1M $\Omega$  impedance on A.C.V. ranges.
- 2 $\mu$ A taut band suspension movement.
- High resolution of 0.05 $\mu$ A/1mV
- Fuse and diode protection.

## Hot Favourite for Temperature Measurement

### TH-510

- Thermometer measuring—50°~300°C in dual ranges.
- N-1 type accompanies a pointed tip probe. S2 type a flat tip probe for surface temperature.
- Constant voltage IC circuit.
- Minimal current consumption (3mA) increases service life of battery—150-hour continuous use.

## Low Cost 3-in-1 Logic Pulse Scale

### YX-380TR

- Instant L.E.D. indication of pulses in excess of 0.5 VRMS. 0-30MHz (using optional probe).
- DC and AC simultaneously indicated on meter and logic probe.
- Multitester function may be expanded with optional hFE adaptor and HV probe.

## Versatility Plus Sensitivity

### BX808M


- High sensitivity 30 $\mu$ A meter movement.

- Simultaneous measurement of A.C. and D.C. signals.
- A.C. signals may be measured even when mixed with D.C.
- Provides logic pulse analysis facilities with pulse and DCV range.
- Instant L.E.D. indication of pulses exceeding 0.5 RMS 0-30 MHz.

## Popular Choice of Hobbyists & Servicemen
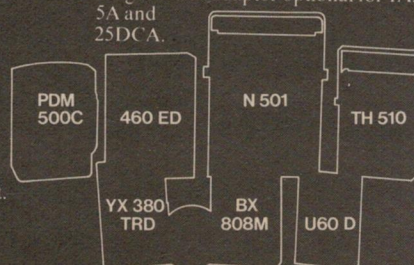
### U-60D

- Easy to read wide scale.
- 44 $\mu$ A diode protected movement.
- Optional temperature probe for -30° to 150°C.
- Plug in shunt adaptor optional for 1A, 5A and 25DCA.



Available nationally from



# WARBURTON FRANKI

• ADELAIDE (08) 356-7333 • BRISBANE (07) 52-7255 • HOBART (002) 28-0321  
 • MELBOURNE (03) 699-4999 • PERTH (09) 277-7000 • SYDNEY (02) 648-1711  
 • AUCKLAND N.Z. (09) 77-0924 • WELLINGTON N.Z. (04) 69-8272



## Singapore shake up

Earlier this year, the former Radio Singapore was converted into the new "Singapore Broadcasting Corporation". Recently the SBC has expanded its services in English on shortwave.

**Radio Singapore was operated as part of the government structure, under the authority of the Department of Broadcasting in the island republic.**

The new Singapore Broadcasting Corporation is a separate statutory corporation, independent of the direct control of the government. The Corporation is still reliant on government finance to a large degree, although this is supplemented by fees from radio licences and commercial advertising over the SBC.

The Singapore Broadcasting Corporation has recently added a new channel on shortwave for relays of the Home Service in English. The new outlet of 15 200 is used in parallel with the usual outlets of 11 940, 5052, and 5010, during the time span 2230 to 1630 daily.

Best reception of the new 15 200 outlet is from sign-on at

2230 up to about 2330, and again during our late evenings.

Best of the other frequencies is 11 940, currently well heard from about 0800, while both 5010 and 5052 sometimes give good signals later in the evenings, from about 1230.

Singapore also has programmes for Malay and Chinese speaking listeners, both of which are relayed on shortwave. The Malay service uses 6155 and 7250 between 2115 and 1630, with best reception noted on 6155 from about 1000 in our evenings.

Meanwhile, the Chinese language network uses 9635 and 6000, between 2230 and 1630, with easily the best reception being on 9635 in the 31 metre band, from fade-in at around 0830 in our early evenings.

The 6000 frequency suffers strong co-channel interference from the Chinese Peoples Liberation Army station in Fuzhou.

## English from Bangladesh

**Radio Bangladesh in Dacca currently broadcasts to South East Asia in English daily from 1230 to 1300.**

Current frequencies for this service are 21 770 and 15 285. Best reception is generally on the former frequency, with 15 285 suffering interference in the crowded 19 metre band. Programmes begin with a bulletin of world and regional news, followed by a news commen-

tary, and features of Bengali music and current happenings. Radio Bangladesh currently has on order two new shortwave transmitters, each of 250 kW, to be used for external service broadcasts. These will be installed at Kabirpur, near the capital, Dacca.

## Kathmandu calling

**Radio Nepal in Kathmandu operates a daily English language programme which is usually well received in east Australia.**

Current schedule for Nepal's English programme is 1435 until 1520, on both 3425 and 9590. Best frequency is the former, as the 31 metre band

outlet suffers interference from other, more powerful, transmitters on this crowded band. The main English news bulletin is heard from 1450 until 1505.

## Peak time for Bhutan

**The very limited time span of broadcasts from this tiny Himalayan kingdom, plus the very low power of the transmitter used, make Bhutan one of the hardest countries to hear on shortwave.**

Nevertheless, the summer months are peak reception time here for this choice DX signal.

The station is operated by the National Youth Association of Bhutan (NYAB) in the capital city Thimphu and the transmitter used is a former amateur rig rated at 300 watts. However, due to frequent irregularities in the local power supply, the transmitter power output is often very much lower than this.

Australians have two opportunities to pick up the NYAB station. These occur on Wednesday and Friday evenings, when the Thimphu station operates between 1230 and 1400, on 4692, just below the 60 metre band. The last half hour of these broadcasts is in English.

The northern hemisphere winter months mean that sig-

nals from Asian locations such as Bhutan will tend to fade in earlier in our evenings, due to earlier sunset times in most of Asia.

An indication of propagation conditions on any evening from South Asia into your location can be gained by checking the fade-in times for stations such as All India Radio at Hyderabad on 4800, Burma Broadcasting Service (Rangoon) on 5040 and 4725, or Sri Lanka Broadcasting Service on 4940.

Should these stations be well heard by 1200 or shortly after, then conditions should be at an optimum to receive the low powered Bhutan station.

NYAB will verify all correct reception reports with a detailed QSL card, and reports could be sent to: Radio NYAB, Box 1, Thimphu, Bhutan.

## Kampuchea in English

**The Voice of the People of Kampuchea in Phnom Penh provides reliable signals on most evenings, commencing with an English programme at 1200 until 1215 using both 11 938 and 9695.**

Programmes continue with a French broadcast at 1215, then a programme in Thai from 1230 to 1245. There is also an English programme during our mornings, from sign-on at 0000 until 0015, followed by 15 minutes each of French and Thai. This broadcast is not so well heard at present, and reception of the morning programme is usually confined to our winter months.

The Phnom Penh station has recently started to reply to reception reports from listeners world wide. Several DXers in both Australia and in Europe have recently received verification letters from the Head of the

Foreign Service in Phnom Penh.

There is currently no mail service direct to Kampuchea, and all mail goes first via Hanoi in Vietnam.

**NOTE!** All times are given in Greenwich mean time (GMT). To convert to Australian Eastern Standard Time, add 10 hours (11 hours during Daylight Saving Time, November to February). To convert to Central Standard Time, add 9.5 hours and Western Time add 8 hours.

All frequencies are given in kHz.

These notes are compiled by Peter Bunn on behalf of the Australian Radio DX Club (ARDXC). Further information on DXing or the activities of the ARDXC may be obtained from P.O. Box 79, Narrabeen, NSW 2101, for a 22c stamp.



# EXTENDED BY PUBLIC DEMAND!

Woops! We're sorry! We give up! We will extend the deadline!

When we announced our Dick Smith-Yaesu Win a Fantastic Trip to Hong Kong competition, we completely forgot about all the new Yaesu models.


Little did we realise that the new models would be so popular that they would sell out immediately: and anyone who waited for the next shipment would be too late to enter!

And then there were the customers who wanted the brand new models: the ones that hadn't even arrived yet!

Scores of customers have asked: 'Hey! What about us. Why should we miss out on winning the trip just because you guys ran out of stock!'

You're right, of course! So to give everyone a fair chance, we've decided to extend the deadline until the end of February 1981. So now you can have your new Yaesu - and still be in the running for the fabulous contest prize!
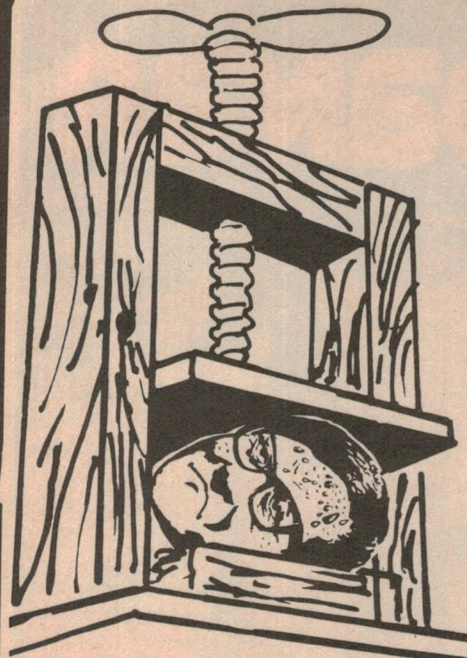
## SO NOW YOU CAN BUY YOUR NEW YAESU: AND STILL BE ELIGIBLE!




**\$543<sup>00</sup>**

OR FROM \$63 DEPOSIT  
AND \$26.28/MONTH  
(24 MONTHS)
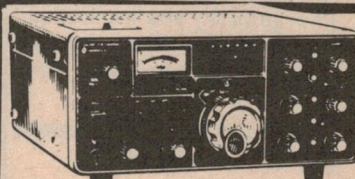
### NEW FT480

- All mode 2 metre SSB/CW/FM!
- Microprocessor controlled!
- Digital display!
- 30 watts PEP

This is the one they're all talking about: the fabulous new 2 metre all-mode transceiver from Yaesu. Offering outstanding performance and ease of controls, it must be the transceiver of the eighties! Cat D-2887



### SAVE ON FT625!

WAS \$795.00 ..  
NOW ONLY

**\$695<sup>00</sup>**

OR FROM \$75 DEPOSIT AND  
\$20.48/MONTH (48 MONTHS)

We've knocked an incredible \$100 off the price of these popular all-mode 6 metre rigs. There's still plenty of good DX out there on 6 - and the FT-625 is just the transceiver to get it! Cat D-2886



**\$735<sup>00</sup>**

OR FROM \$75 DEPOSIT AND  
\$22.48/MONTH (48 MONTHS)

### NEW FT707

- All HF bands!
- AM/SSB/CW!
- Tiny Size!
- True digital display
- New WARC bands!

They've been pretty hard to get: and small wonder! The superb FT-707 packs a huge punch from its tiny size: 240W DC! It's the ideal rig for mobile, base or portable work. Cat D-2869

### SUPERB FT-207

- Microprocessor controlled hand held giving full 144-148 band!
- Digital display.

For today's active ham, this is the set to take with you. Takes up virtually no room, but really gets out! Make contacts wherever you go with the FT-207R.

**\$358<sup>00</sup>**

Cat D-2888

OR FROM \$38 DEPOSIT AND  
\$17.52/MONTH (24 MONTHS)



**\$1278<sup>00</sup>**

OR FROM \$138 DEPOSIT AND  
\$38.32/MONTH (48 MONTHS)

### NEW FT107M

- The ultimate!
- WARC bands
- All solid state
- Variable IF bandwidth!
- Speech proc.

It must be every amateur's dream to own one of these! You can: and take full control of the bands. Whatever you want from your transceiver, the FT-107 offers it! Cat D-2871

### BUDGET FT-101Z

We throw in a digital display kit worth over \$100! This turns the FT-101Z into an FT-101ZD!

More hams have 'cut their teeth' on one of the famous '101' series than any other rig! Rugged and reliable, with all the features you really need. Cat D-2862

OR FROM \$85 DEPOSIT AND  
\$23.19/MONTH (48 MONTHS)



**\$775<sup>00</sup>**

WITH BONUS DIGITAL  
DISPLAY WORTH \$139!!

ANY TERMS OFFERED ARE TO APPROVED, PERSONAL APPLICANTS ONLY. ORDER BY MAIL: USE YOUR BANKCARD!

# DICK SMITH ELECTRONICS

SEE OUR OTHER ADVERTS IN THIS MAGAZINE FOR OUR STORE ADDRESSES AND RESELLERS





## State of the Art contest results

The revived State of the Art contest, featured on these pages in the July issue, attracted a small band of dedicated entrants and the organisers have deemed the revival a success.

The contest ran over 19 July to 3 August, the scoring period being any 10 days between those dates. The object of the contest is to promote operation on the available VHF/UHF/SHF bands with the object of promoting the more 'difficult' scatter techniques, satellite operation and UHF/SHF activity. Judging by the entries, that aim has been fulfilled.

First place goes to G. MacDonald, VK2YHZ, with 10 230 points all gained from 144 MHz troposcatter contacts. He will receive a \$50 open order on Radio Despatch, donated by the organisers, the NSW VHF & TV Group.

Second place goes to Rod Preston, VK4ZRQ, with 8386 points gained from working Oscars 7 and 8, plus 146 and 432 MHz troposcatter.

The entries this time contrast to previous contests which were

dominated by 52 MHz meteor scatter operation. The Oscars were well used and the effort by Geoff Campbell, VK2ZQC, is worthy of mention. He gained 1200 points just working Oscar 8. If Oscar 9 had not met such an unfortunate demise earlier this year, things would have been different, I'm sure.

Flying the flag on SHF were Jeff Pages, VK2BYY and Doug Morrison, VK2ZYM who gained 3050 points with contacts on 10 GHz (F3 modulation) over an 18 km path.

That's not a bad result, seeing as the last time the NSW VHF & TV Group attempted to run this contest, there were no entries! Prior publicity was low key and not far in advance, but even so, there was one entry from Queensland.

Dates for next year's contest are to be announced.

## Predictions change

The Ionospheric Prediction Service of the Department of Science and the Environment has made a few alterations to their GRAFEX predictions we publish each month.

Firstly, some charts now cover the range from 3 MHz to 60 MHz, extending the top range from the previous limit of 40 MHz. This change has been effected as a result of increased solar activity.

Secondly, a change in the symbols used on these charts has been made. The letter 'B', signifying "propagation possible via E and F layers over 90% of days. (Overrides 'F')", has been replaced by the letter 'X'. This symbol signifies "complex mixture of modes. Expect abnormal propagation."

The latest preliminary monthly smoothed sunspot figures we have to hand at ETI indicate that we may have reached the peak of this cycle early this year, contrary to many reports in the technical press that we passed it October/November last year. The DX is good for a few years yet!

CITIZENS RADIO EMERGENCY SERVICE TEAMS - AUSTRALIA INC.  
SYDNEY DIVISION

☐ **VOLUNTEERS** REQUIRED FOR TRAINING AS... **MONITORS** ☐

YOU WILL BE REQUIRED TO...


1. UNDERTAKE A FULL TRAINING PROGRAM IN EMERGENCY RADIO PROCEDURES.
2. MONITOR THE EMERGENCY CHANNEL ON THE CITIZENS RADIO SERVICE AND PASS INFORMATION TO THE APPROPRIATE AUTHORITIES.

FOR FURTHER PARTICULARS  
WRITE TO...

SECRETARY SYDNEY CREST  
P.O. BOX 380, GLADESVILLE, 2111

# SOANAR

PW SERIES

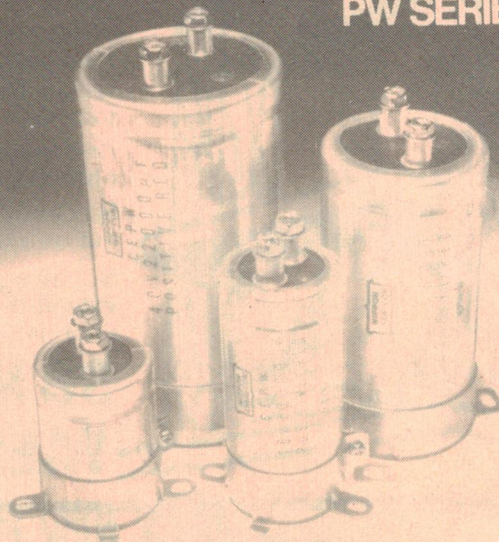

## COMPUTER GRADE ELECTROLYTICS

PW Series Capacitors are particularly suitable as power source filters for computers, inverters, high current power supplies, high output power amplifiers and control equipment.

Despite their small size, these capacitors have exceptionally large capacity and are capable of handling high ripple currents. Miniaturisation has been achieved by the use of new electrode foils developed from a technique of high magnification etching.

Construction includes an aluminium can which is sealed with a long life, heat resistant resin and heavy duty screw terminals for handling the high currents involved. Mounting clamps are supplied as standard equipment.

**2,900uF TO 100,000uF**  
**16 Volt TO 40 Volt DCW**

Available ex stock all States

**SOANAR ELECTRONICS PTY.LTD.**

A MEMBER OF THE A+R-SOANAR ELECTRONICS GROUP  
30 Lexton Road, Box Hill, Vic. 3128, Australia. Telex: 32286  
SALES VICTORIA 89-0661 STH AUST 51-6981 WEST AUST 381-9522  
OFFICES NSW 789-6733 QUEENSLAND 52-5421 TASMANIA 31-6533







## Tiny, synthesised 2m handheld packs a big punch

It is clear from an examination of the products, and their sales success, that when Icom set out to produce a product, they do their homework carefully.

**The Icom IC2A 2m FM handheld transceiver is the company's first entry into the 'handheld market'.**

There've been many before them — who doesn't remember the famous Ken KP2A? (they still fetch remarkably high prices secondhand). There's been plenty of talk on the air and at club meetings about this rig since it appeared earlier this year. Let's see what Icom have packed into a remarkably small package.

First, the size. The rig measures 65 mm wide by 35 mm deep by 16.5 mm high (depending on which way you hold it!) and weighs a mere 470 grams, depending on the battery pack. Two battery packs are available, the BP-5 which gives around 2 W output, and the BP-6 which gives 5 W output, according to Icom.

It has a 400 channel synthesiser, operated by a thumbwheel

switch, with  $\pm 600$  kHz repeater offset switching, and a  $+5$  kHz switch (giving '800 channels'). Duplex/simplex switching and hi/lo power switching is also provided.

Standard volume and squelch controls are provided and there are jacks for an external speaker and external microphone. The antenna connector is a conventional BNC socket. The familiar "rubber ducky" antenna is provided with the unit.

I note from the handbook that one model of the IC2A (IC2AT) has a tone encoder pad on the front panel, below the speaker. It's not available here, but it's interesting to note.

Circuit-wise, the IC2A has a PLL 'heart' that provides 72 to 73.9975 MHz to the transmit multiplier stages, and 66.6525 to 68.65 MHz to the receiver 1st mixer. Four diode-switched crystals provide either simplex,  $+600$  kHz,  $-600$  kHz or  $+5$  kHz

offsets. The thumbwheel switches program a divider in the PLL feedback chain to select 10, 100 and 1000 kHz frequency increments giving 400 channels between 144 and 147.995 MHz. The modulation is 'true' FM (not PM as is common in other

quoted as more than 60 dB, which it quite happily exceeds, and audio power output is given as 300 mW.

The transmitter delivered 1.8 W on the BP-5 battery pack supplied but we had no equipment to measure the low power output. Maximum deviation is quoted as  $\pm 5$  kHz and spurious emissions as better than 60 dB below carrier, but we had no way to measure either. Frequency stability is given as within  $\pm 1.5$  kHz and measured better than 150 Hz.

On the air reports with both solid and slightly noisy signals gave the rig 'good' audio. Using a dipole mounted inside our Rushcutters Bay offices (a 'not good' QTH) I was able to key up four local repeaters plus Wollongong. With a little help from the ETI-720 VMOS power amp (20 W out), the IC2A could just about 'talk' as well as it could 'hear'.

Operation with the flexible antenna is handy, but don't expect much in the way of performance. Still, I was surprised on occasions.


The inbuilt electret microphone takes a little practice to get things 'right', but once you work it out, all goes well. Receiver audio is OK for the tiny speaker in the rig, remarkable when connected to a good external speaker.

The unit is supplied with a plugpack battery charger for the 8.4 V battery pack, but charges from a 13.8 V supply so you can charge from a vehicle battery.

Overall, the unit is delightfully simple to operate but the lack of an S-meter is disconcerting. The IC2A packs a lot of punch for its small size and light weight. At \$279, one is sorely tempted!

Our review unit was kindly supplied by Vicom, 68 Eastern Rd, South Melbourne, Vic 3205. (03) 609-6700.

**Roger Harrison VK2ZTB**

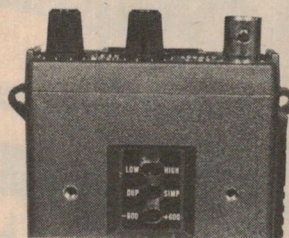

schemes) as the PLL VCO is modulated directly.

The receiver has a cascade bipolar RF stage before the FET 1st mixer, followed by IFs at 10.695 MHz and 455 kHz. A single IC incorporates the 2nd mixer and conversion oscillator, the 455 kHz IF amps, limiter, detector and noise amp for the squelch. The squelch uses four transistors and a single IC audio stage follows.

Overall, the unit contains 43 transistors, three FETs, five ICs and 21 diodes. They sure pack a lot in there!

Receiver performance is quoted as 26 dB SINAD at 1  $\mu$ V, less than 0.5  $\mu$ V for 20 dB quieting with a squelch sensitivity of 0.4  $\mu$ V. On measurement the unit exceeds those specs by more than 6 dB and can quite happily hear the leakage from our HP8654B signal generator (below  $-130$  dBm or 0.07  $\mu$ V)! Spurious response rejection is



**TNT**  
COURIER


# AUSTRALIA WIDE SATCHEL.

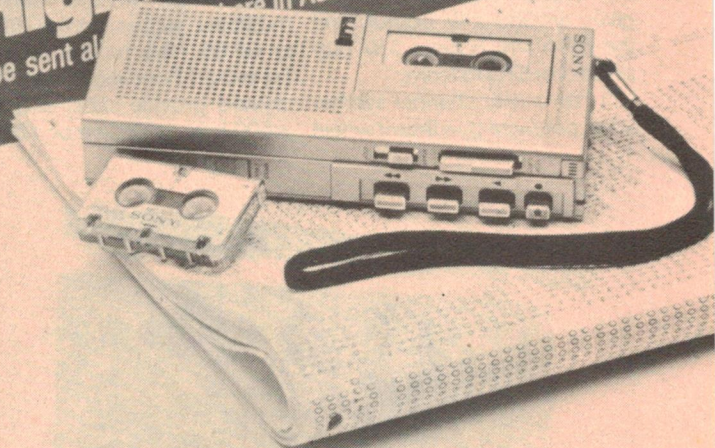**URGENT!**



**\*anywhere in Australia  
overnight.**

\*Anything which fits inside this satchel may be sent almost anywhere in Australia, overnight.



## Now your newsagent can solve your urgent parcel problems.

This TNT Courier Overnight Satchel has just turned your friendly newsagent into an air freight depot. For \$8.75 you can send anything that fits inside to almost anywhere in Australia. Overnight. You don't have to wrap a thing. The bag is tough, waterproof and tear resistant.

You can buy TNT Satchels at most newsagents throughout Australia. (At present in N.S.W., they are

available only in Sydney, Newcastle, Wollongong, Gosford and A.C.T.). Just address the satchel and leave it with your newsagent. TNT Courier collect it, air freight it overnight and deliver the next morning.

The TNT Courier Suburban Satchel is for overnight local deliveries in all mainland capitals (and soon Hobart) for just \$5.00.

**TNT Courier Overnight Satchels.\*Anything, anywhere, overnight.**



A Speedy Communications product. \*Anything which fits inside the satchel may be sent almost anywhere in Australia, overnight.



# Bill Edge's ELECTRONIC AGENCIES

115-117 PARRAMATTA ROAD, CONCORD 2137.  
(Corner Parramatta Rd & Lloyd George Ave)  
Telephone 745-3077, 2 lines.

## MAIL CHARGES

\$5 - \$9.99	\$1.00
\$10 - \$24.99	\$2.00
\$25 - \$49.99	\$3.00
\$50 - \$99.99	\$4.00
\$100 or more	\$5.50

All heavy or bulky items (over 20 kg) sent  
"freight on" through carrier.  
Bankcard welcome - by mail, telephone,  
or over the counter.



BILL EDGE is now handling a very large range of the famous Plessey Foster Speakers. These speakers are world renowned and we are offering them at a very attractive price for a short period only - in order to introduce them to ETI readers.

All have an 8ohm nominal impedance

## WOOFERS MIDRANGE

ONLY  
\$29.95



C300L05 (300mm, 12 inch)  
Maximum Power: 50(W) RMS  
Resonant Frequency: 25 ± 5(Hz)  
Effective Freq. Range: fo ~ 3500(Hz)

ONLY  
\$9.95



C100M02 (100mm, 4 inch)  
Maximum Power: 30(W) RMS  
Resonant Frequency: 600 ± 90(Hz)  
Rated Freq. Range: 1000 ~ 10000(Hz)

ONLY  
\$24.95



C250L07 (250mm, 10 inch)  
Maximum Power: 40(W) RMS  
Resonant Frequency: 32 ± 5(Hz)  
Effective Freq. Range: fo ~ 6000(Hz)

ONLY  
\$16.00



C130M08 (130mm, 5 1/2 inch)  
Maximum Power: 60(W) RMS  
Resonant Frequency: 205 ± 31(Hz)  
Rated Freq. Range: 600 ~ 10000(Hz)

ONLY  
\$8.95



C100K03 (100mm, 4 inch)  
Maximum Power: 10(W) RMS  
Resonant Frequency: 80 ± 15(Hz)  
Effective Freq. Range: fo ~ 17000(Hz)

ONLY  
\$11.50



C130M06 (130mm, 5 1/2 inch)  
Maximum Power: 30(W) RMS  
Resonant Frequency: 600 ± 90(Hz)  
Rated Freq. Range: 1200 ~ 15000(Hz)

C200L09 WOOFER ONLY \$12.00  
(Not illustrated)

## TWEETERS

ONLY  
\$6.50




C065N05 (66mm, 2 1/2 inch)  
Maximum Power: 25(W) RMS  
Resonant Frequency: 1230 ± 190(Hz)  
Rated Freq. Range: 3000 ~ 15000(Hz)

ONLY  
\$11.50



D025N15 (25mm, 1 inch)  
Maximum Power: 30(W) RMS  
Resonant Frequency: 1300 ± 240(Hz)  
Rated Freq. Range: 2600 ~ 22000(Hz)

ONLY  
\$6.95

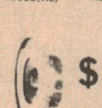

C050N08 (50mm, 2 inch)  
Maximum Power: 60(W) RMS  
Rated Freq. Range: 3000 ~ 20000(Hz)

ONLY  
\$17.00



H016N17  
Maximum Power: 50(W) RMS  
Rated Freq. Range: 5000 ~ 40000(Hz)



CITY & SHOWROOM: 649 George St, Sydney, NSW.  
(02) 211-0531.

POSTAL: PO Box K21, Haymarket, NSW 2000. Cable: Emtron Sydney.

## NEW SUPER RECEIVER NRD 515 from JRC



\$1927

• PLL digital VFO • Digital tuning system • 24 channel frequency memory unit (option) • Continuous coverage, all mode reception • Up-conversion type double superheterodyne • Effective pass band tuning • Electronic tuning and electronic switching • All solid state • Completely modular construction • Easy to operate, small and rugged • Built-in accessory circuits • Operation in combination with the NSD 505 transmitter.

WRITE FOR COLOUR BROCHURE AND SPECS



## KENWOOD R-1000

Communications receiver of the year. Digital and analog dial, digital clock, automatic timer, three selectivity positions and many other features.

We also stock Australia's largest selection of scanning receivers. You can listen to aircraft, marine, police and other transmissions.



BEARCAT 210  
BEARCAT 220FB  
BEARCAT 250FB  
BEARCAT POCKET SCANNERS  
SX-200 etc.

WRITE FOR PRICES AND SPECS

## SHORT WAVE LISTENERS PLEASE NOTE

We stock the largest range of communications receivers in Australia - JRC, Kenwood, Yaesu, Grundig, National Panasonic, Mark, etc. We also stock SWL accessories such as antenna tuners for receivers, active all band antennas, low noise preselectors, active audio filters and many others.

WRITE FOR OUR VERY LATEST 1981 CATALOGUE

# Now you can breathe easier!

## NEGATIVE IONS.

For more than 20 years Medical research has been demonstrating the amazing benefits of negative air ions. They clear the air of smoke and dust, reduce fatigue and increase alertness, reduce up to 75% of airborne bacteria and much more.

In natural surroundings they are abundant but in stale or polluted air they quickly become depleted. Now an inexpensive device to alleviate this condition is being manufactured in Australia.

The "Aironic" negative ion generator electrically produces safe, natural levels of negative ions. Stale odours and smoke are removed from the room and the air becomes fresh and invigorating once more.



**Aironic**  
NEGATIVE ION GENERATOR

See your health food shop or natural therapist or post coupon to:

## BELLE LUMIERE PTY. LTD.

SYDNEY: P.O. BOX 216, Lane Cove, NSW. 2066. Tel: (02) 428 1334  
MELBOURNE: 5/47 Fitzroy St., St. Kilda. Vic. 3182. Tel: (03) 534 7493  
BRISBANE: P.O. BOX 184, Toowoong. Qld. 4066. Tel: (07) 371 3645

☐ Home/office model. \$85 each.

☐ Deluxe wood casing. \$95 each.

Add \$2.00 for postage and packing.

I enclose cheque/money order for .....

NAME .....

ADDRESS .....

POSTCODE .....

Bankcard Mail Orders Welcome.

Expiry Date .....

Signature .....

☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐

Send SAE for further literature on negative ions.



The use of tip and sleeve sockets may be acceptable in the UK, but most professionals and amateurs in this country prefer XLR connectors. This is not a trivial point because one of the biggest hassles for most rock groups is the plethora of different plugs, and connectors they have to cope with.

The most significant attribute of this amplifier is its sensible weight which any professional will quickly appreciate when he compares it to the 'lead lined' amplifiers he is accustomed to carrying around.

## Conclusion

The Soundout S400 amplifier is a well

designed, rugged and low weight unit with a performance that is better than one could reasonably expect for the modest price, although at a recommended price that works out around \$1.7 per watt this is not the cheapest professional amplifier on the market. However, price is not necessarily the most important factor — the overall weight of 16 kg is probably a more important consideration.

Most professionals would be prepared to swallow the small differential in price to save having to lug around an amplifier with almost twice the weight, especially after that late, late show. When you add the sensible protection

circuits into the equation this amplifier can be seen to have more than the average number of pluses.

## SOUNDOUT S400 STEREO AMPLIFIER

Dimensions: 482 mm wide x 145 mm high x 380 mm deep

Weight: 16 kg

Price: \$680

Manufactured by: Soundout Laboratories Ltd, London UK.

Absolute copyright in this review and accompanying measurements is owned by Electronics Today International. Under no circumstances may any review or part thereof be reprinted or incorporated in any reprint or used in any advertising or promotion without the express written agreement of the Managing Editor.



MEASURED PERFORMANCE OF SOUNDOUT S400 STEREO AMPLIFIER  
SERIAL NO. 10814

Louis A Challis and Associates Pty Ltd

### FREQUENCY RESPONSE:

(-3dB re 1 watt, 0.5V Left 3.5Hz to 130kHz  
Input to Aux.) Right 3.4Hz to 115kHz

### SENSITIVITY:

Left Right  
(for 1 watt in 8Ω) Aux. 80mV 80mV

### INPUT IMPEDANCE:

Left Right  
Aux. 6.0KΩ 7.0KΩ

### OUTPUT IMPEDANCE: = -16 milliohms (@ 1kHz)

### NOISE & HUM LEVELS:

(re 1 Watt into 8Ω) AUX. -70dB(Lin) 82.5dB(A)  
(with volume control set for 1 watt  
output with,  
0.5V input (Aux.)

### MAXIMUM OUTPUT POWER AT CLIPPING POINT:

(IHF -A - 202)

(20ms burst repeated at 500ms 88V P-P  
intervals) = 242 Watts  
Dynamic Headroom = 1.6 dB (re 200 watts)

### TRANSIENT INTERMODULATION DISTORTION: 0.16%

(3.15kHz square wave and  
15 kHz sine wave mixed 4:1)



### HARMONIC DISTORTION:

(A) (At rated power of 200 watts into 4Ω = 28.3 volts)	100Hz	1kHz	6.3kHz
2nd	-61.1	-64.7	-63.4 dB
3rd	-60.6	-58.8	-59.0 dB
4th	-73.5	-73.2	-75.2 dB
5th	-	-	- dB
THD	0.13	0.13	0.13 %



(B)	100Hz	1kHz	6.3kHz
2nd	-64.0	-74.0	-71.3 dB
3rd	-60.0	-59.3	-59.6 dB
4th	-72.6	-74.3	-71.2 dB
5th	-	-	- dB
THD	0.12	0.12	0.11 %

(C) (At rated power of 1 watt into 4Ω = 2.83 volts)	100Hz	1kHz	6.3kHz
2nd	64.5	79.9	76.9 dB
3rd	68.1	75	71.6 dB
4th	76.1	-	- dB
5th	78.4	79.8	- dB
THD	0.07	0.02	0.03%

(D)	100Hz	1kHz	6.3kHz
2nd	67.0	81.8	79 dB
3rd	68.2	68.5	67.5 dB
4th	79.1	88.8	- dB
5th	74.2	73.4	- dB
THD	0.06	0.05	0.04%

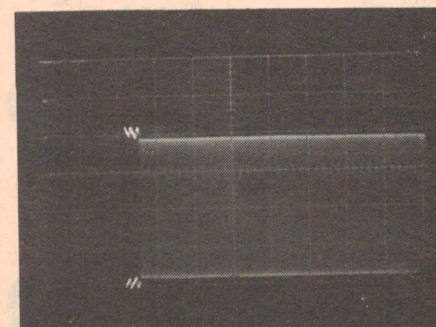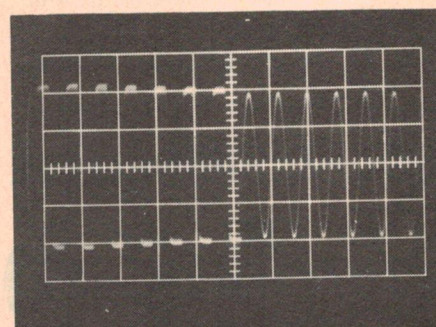

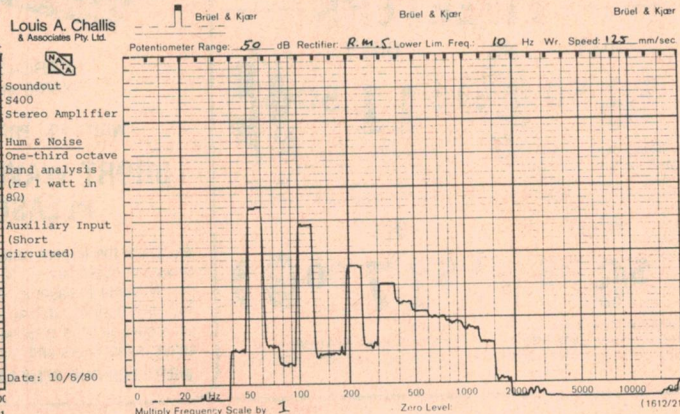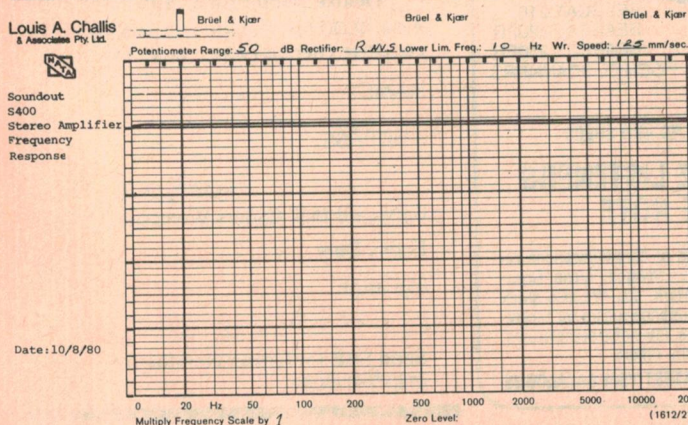Transient overload recovery test (IHF-A-202).  
Top: 1ms/div., bottom: 50 ms/div. Overload of  
10 dB re rated power into 8 ohms, both channels  
driven. Overload duration: 20 ms; repetition  
rate: 512 ms.





# WHEN IT COMES TO SOUND . . .

We've been hiring, for the last 5 years, sound systems to many local, interstate & international groups & artists. Now our expertise in equipment knowledge goes into selling the right sound equipment to you! Talk to us first, we'll get your act together!


RIGHT FROM THE:  
MICROPHONES (BEYER/SHURE)  
STANDS/CABLES  
MIXERS (JANDS)  
MXR GRAPHIC EQUALIZERS  
DBX COMPRESSOR/LIMITERS  
CROSSOVER (JANDS)  
POWER AMPS (JANDS)  
JBL SPEAKERS  
'W' BINS  
MID CABINETS  
JBL HORNS  
JBL TWEETERS

MISCELLANEOUS:—  
CANNONS  
PIEZOS  
GAFF  
DI BOXES  
SESSIONS  
CATCHES/CORNERS  
MUFFIN FANS  
MODIFICATIONS  
RACK/ROAD CASES  
ETC. ETC.

**SALES & HIRE**  
**DROP IN OR GIVE US A CALL!**

**DSA CONCERT SYSTEMS**  
156 GIVEN TCE, PADDINGTON 4064  
PHONE (07) 36 6367

## PHILIPS HI-FI SPEAKER KITS

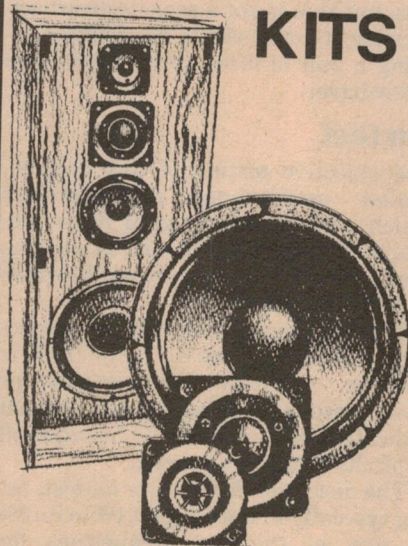

**FREIGHT FREE**  
**SA, VIC, NSW, NT**  
(nearest bus/rail station)

PHILIPS ETI 4000/1 4 way 100w speakers and C/O \$459.00  
PHILIPS ETI 4000/2 3 way 100w speakers and C/O \$350.00  
12K12 12" 3 way 40w complete kit veneered boxes, lining, C/O speakers \$299.00

140T8 Tweeter	\$12.00 ea. ....
162T8 Tweeter	\$13.50 ea. ....
1610T8 Tweeter	\$16.00 ea. ....
5060sq8 Midrange	\$22.00 ea. ....
210sq8 Midrange	\$32.00 ea. ....
2160sq8 Midrange	\$33.00 ea. ....
12650/W8 Woofer 60w	\$54.00 ea. ....
12100/W8 Woofer 40w	\$55.00 ea. ....
12200/W8 Woofer 80w	\$73.00 ea. ....
12250/W8 Woofer 100w	\$78.00 ea. ....
80652/W8 8" Woofer 50w	\$26.00 ea. ....
70601/W8 7" Woofer 30w	\$20.00 ea. ....
4060/W8 4" Woofer	\$19.00 ea. ....
ADF3000 Crossover	\$12.00 ea. ....
ADF500/4500/8" Crossover	\$21.00 ea. ....
ADF600/4000/8" Crossover	\$32.50 ea. ....
ETI4000/1	\$85.00 ea. ....
ETI4000/2	\$55.00 ea. ....

Goods sent at purchaser's risk. Insurance extra \$5.00.

**WORLD IMPORTS**  
232 RUNDLE STREET, ADELAIDE, S.A.  
5000. Phone (08) 223-6539.



Name .....

Address .....

.....P/Code.....

or debit my Bankcard.

Signature .....

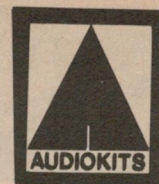 


## Mail Order KEF Drivers & Kits

CERTIFIED MAIL  
DELIVERY THROUGHOUT  
AUSTRALIA  
& NEW ZEALAND  
Bankcard accepted

**KEF**  
**B1139**

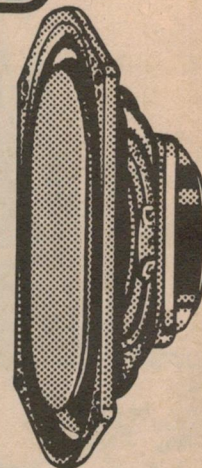Superb 30 x 21cm bass driver, with solid flat diaphragm of unique construction, acting as a perfect rigid piston, to give clean, distortion-free bass over the frequency range 20-1,000Hz. The KEF range also includes mid range and high frequency units, with dividing networks designed to link them into compatible systems.



*the no-compromise approach  
to uncoloured sound*

For full information, write to:  
AUDIOKITS  
PO BOX 553  
BROOKVALE NSW 2100





one that they use in their 200 watt mono amplifier. The result is a classically simple design, using one superior design of transformer and a simple reliable construction which would be particularly hard to beat.

All the electronic components are mounted on a single high quality printed circuit board which is mechanically fixed to the side of the sub chassis, with the filter capacitors braced off the base of the sub chassis to provide positive and effective support. The unit makes use of colour coded wiring harnesses to connect components, sockets and fuses to the transformers and rear panel connections, which is normal practice in professional equipment of this type. All adjustable bias controls are positioned near the tops of the boards, with some wheel type controls that don't need a screwdriver. One fuse on each chassis is located in a rather inaccessible position between the mains transformer and one of the filter capaci-

tors, but this is not a serious drawback because it could easily be replaced by using a pair of forceps or a finger and screwdriver.

### On test

The objective testing of this unit revealed performance characteristics which were generally good for a professional amplifier but not as good as would now be called for by most serious or dedicated amateurs.

The frequency response is impeccable, extending from 3.5 Hz to 115 kHz and the sensitivity of 80 millivolts for 1 watt into eight ohms for each channel indicates that 1 volt would be required to produce 200 watts output.

The distortion figures are modest, being typically in the range 0.1% to 0.13% at any of the test frequencies for 200 watts input and 0.02% to 0.07% at the 1 watt level. Transient intermodulation distortion is good at less than 0.16% and the hum and noise levels


are -82 dB A-weighted and -70 dB unweighted at the 1 watt level.

At 200 watts the unit has a dynamic headroom of only 1.6 dB and hence is a genuine 200 watt per channel amplifier. There are electronic protection circuits which the makers say preserve the output transistors from destruction in the event of open or short circuit conditions. We tried to disprove this claim but did not succeed.
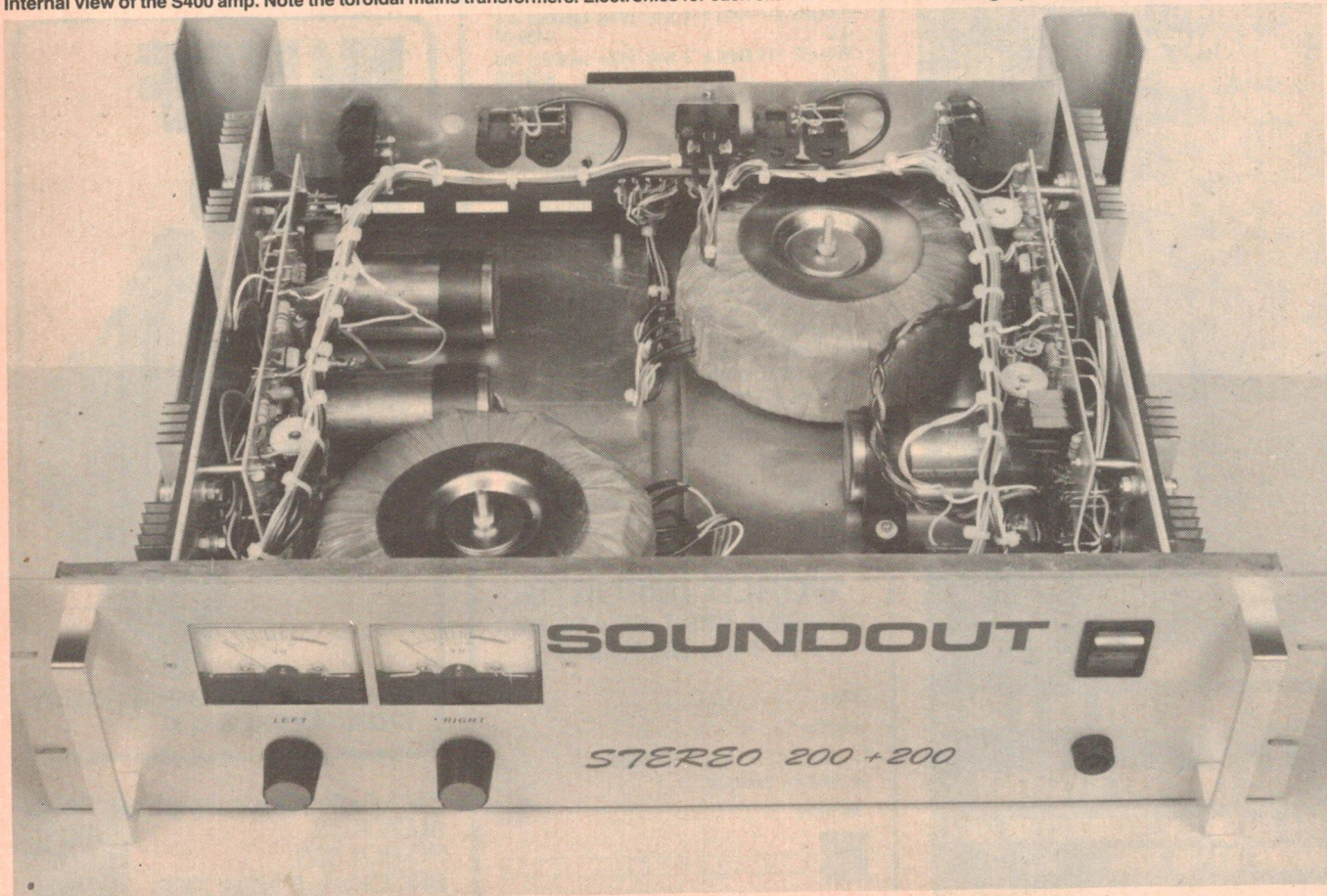
### Subjectively

The performance of the Soundout S400 is typical of a high quality professional amplifier. It can produce rollicking rock and high level classical music into professional speaker systems without distress or audible distortion. Whilst the transient performance is not as good as that of some other amplifiers we have tested, we should point out that these amplifiers cost much more and do not have some of the attributes of the Soundout. ▶

Internal view of the S400 amp. Note the toroidal mains transformers. Electronics for each channel is mounted on a single pc board.







## Soundout S400 stereo amplifier

Low weight, modest price and effective protection circuits make this professional 200 W per channel amplifier an attractive item.

THE PROBLEM with most high powered amplifiers for professional use is that they weigh too much, have questionable reliability and many other less obvious deficiencies that only show up in the field.

Like most manufacturers, Soundout Laboratories of the UK are aware of these problems and they have tackled them in a sensible and pragmatic manner. The Soundout S400 stereo amplifier is a particularly good example of how some of the usual drawbacks can be avoided by adopting a good engineering approach.

### Design

The amplifier is designed for mounting in a standard 19 inch (48 cm) rack and features a brushed satin finish aluminium front escutcheon with two lifting handles on either side. The escutcheon contains two rectangular VU meters for the left and right channels,

with the associated input level controls located immediately below. On the right hand side of the panel is a large illuminated main switch, below which is the mains fuse.

The chassis is an unusual all-welded monocoque construction with ventilation slots along sides and rear and a recess at the back which houses the input and output jacks and the IEC mains socket. A separate ventilated steel cover screws onto the chassis, making the whole structure extraordinarily rugged.

The sockets for input and output are all tip and sleeve to standard IEC and Post Office dimensions. Each input socket is actually a parallel pair of sockets to allow parallel feed into other equipment and there are two output sockets for each channel for multiple speaker connections.

The inside of the unit is a trifle unconventional. First of all the mains

transformers are toroidal types, which really reduce the weight problem so that the S400 weighs far less than other amplifiers in the same power range and less even than many rated at half the power.

Another feature that cuts down on weight is the heatsink system, which for each channel consists of an L-shaped aluminium sub chassis onto which the output stage finned heatsinks are directly mounted. This results in a far more effective power dissipation and a consequent overall reduction in weight. Each sub chassis is directly attached to the main chassis, which further improves the thermal dissipation characteristics and reduces the weight.

Soundout have exercised a little lateral thinking and designed each sub chassis so that the same standard module is used for both channels. This of course keeps the price down, all the more so because this module is also the



# No car is complete without one



**Gregory's** Will get you there.

# Do-it-yourself money saving maintenance



Gregory's S.P. car service and repair manuals.

**Gregory's**  
will get you there - safely

# B&W DM12

## THE UNOBTRUSIVE REVOLUTIONARY

We could have built something smaller, but we were determined to build a miniature speaker that rises way above the limitations hitherto imposed by a small enclosure. In particular, we wanted to achieve wider response and more realistic sound levels in the low frequency range. We also wanted safe power-handling capacity. Thanks to our unique resources in computer and laser technology and the sheer creativity of our design team, DM12 achieves all this and more.



**B&W**  
LOUDSPEAKERS



**It's certainly small.**  
Just 355mm (14 in) high x 220mm (8¾ in) wide x 270mm (10½ in) deep.

**106dB.**

That's the surprising peak sound pressure level DM12 produces from its 12 litre enclosure.

**Monitor standard.**

Frequency linearity + 2 dB 85 Hz to 20kHz.

**APOC-protected.**

B & W's exclusive audio-powered overload circuit protects against accidental damage or overload.

For further information see your B & W dealer or contact  
Convoy International Pty Ltd  
4 Dowling Street Woolloomooloo NSW 2011  
Telephone (02) 3582088



**NEW  
NEWS!**

# Australian Business is not written with an ohm and watt.

Australian Business means business; pure and simple. It exists because business in Australia has come of age, and there has been no topical quality news magazine to report its affairs. Now there is.

Every second Friday, Australian Business will report the top business stories — for every kind of business at every level. The kind of people who need it most are the people with the least time to spare. We understand that.

We would like you to become a subscriber. For \$35 a year you will receive 26 issues delivered, post free, to any address you nominate. \$35 is a saving of a few dollars on news-stand price and your sub is probably tax deductible.

It could be smart business to fill in the coupon right now.

An associate publication of THE BULLETIN

**Australian  
BUSINESS**

For a year's subscription to Australian Business at just \$35, fill in this coupon and post today to:  
**Murray Distribution Services Box 4088 GPO SYDNEY 2001.**

Tick box to indicate payment.

Diners Club ☐ American Express ☐

Bankcard ☐ Cheque ☐



Credit Card No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Card Expiry Date

NAME:

ADDRESS:

STATE:

POSTCODE:

COMPANY:

POSITION:

SIGNATURE:

(unsigned orders cannot be accepted)

Please make cheques payable to: Murray Distribution Services.

J596



—from page 139.

manufacturer, should this be required.

Low noise field effect transistors are used in the mixer and BF494 transistors in the IF stages. The detector stage is followed by a 9 kHz whistle filter which provides effective attenuation of the beat frequency components between distant stations transmitting on adjacent frequencies. This feature is particularly important at night.

## In the lab

Objective testing proved to be a little more complex than we expected. Firstly, the balanced coupling requirements for the input aerial tuning plug are a little different from the normal 75 ohm or dummy aerial configurations which have been the basis for our receiver testing over the last 25 years. As a result of this, some measurements may appear to be different from the manufacturer's. Audiosound do not provide a specification for the dummy aerial configuration used in sensitivity testing, so we resorted to connecting our signal generator directly to the aerial terminals.

With 30% modulation the tuner has a 1.6 microvolts sensitivity in the sharp position and 7.2 microvolts sensitivity in the broad position, for a 6 dB signal to noise ratio. The corresponding figures for a 26 dB signal to noise ratio are 25 microvolts and 60 microvolts. At 60% modulation the 26 dB signal to noise ratio is achieved at a 10 microvolts sensitivity in the sharp position.

Intermediate frequency rejection is a very satisfactory 53 dB and the image rejection is 46 dB. The maximum signal level that the tuner can cope with is 52 millivolts, at which point severe overloading occurs. Signals at or above this level would require an attenuator at the aerial input.

The distortion characteristics of the unit are quite good, being less than 1%

for 30% modulation and well under 2% for 60% modulation. We had some difficulty in obtaining these figures because our signal generator was designed in a bygone era when distortions of less than 5% were regarded as more than adequate for AM reception.

The bandwidth in the broad position is 12 Hz to 7.6 kHz and in the sharp position it is 12 Hz to 2.6 kHz. The notch frequency of the whistle filter is 8.98 kHz, which is near enough to the specified 9 kHz.

The circuitry contains one other unusual feature which is worthy of comment. This is the incorporation of a simulated stereo output stage. The designers provide very little information apart from five lines in the well presented 15 page handbook, which describe this circuitry as being "an elegantly designed, 90° all-pass phase network designed by Thiele". This simulated stereo stage is apparently intended to provide a spatial distribution of the monaural AM sound when the output of the tuner is fed into a stereo amplifier.

## To the ear

My subjective evaluation of the tuner proved that the manufacturer's statements and his faith in the quality of AM transmission are well founded. On a simple A-B comparison test anyone can tell the difference between conventional ereo receivers and the Audiosound AM101 (even in the sharp selectivity setting). Obviously that test is too easy.

A more difficult subjective test was to compare the quality of an ABC station on AM and FM. Here the extra bandwidth of the FM station gave it the edge, but there was not such a significant difference as I would have expected between the signal to noise ratios. The FM stations have signal to noise ratios of only about 50 dB (although with effective quieting this may approach 60 dB).

The Audiosound AM101 provided signal to noise ratios of better than 46 dB in my home during the day and slightly less at night when more distant stations were received on long distance skip propagation.

The quality of the sound produced by the AM101 tuner was particularly good and the ability of the aerial to either selectively receive or selectively reject signals and stations was particularly gratifying. Even the simulated stereo effect was a success and would generally satisfy most listeners.

## AUDIOSOUND AM101 AM TUNER

Dimensions: 357 mm wide x 108 mm high x 280 mm deep

Weight: 4.5 kg Price: \$249;+ \$38 for 'stereo'.  
Manufactured by: Audiosound, NSW.

Absolute copyright in this review and accompanying measurements is owned by Electronics Today International. Under no circumstances may any review or part thereof be reprinted or incorporated in any reprint or used in any advertising or promotion without the express written agreement of the Managing Editor.



## AUDIOSOUND AM101 AM TUNER

Tuning Range: 560-1750kHz

Sensitivity:

Signal to noise measured at 760kHz. Modulation 30%.

Signal to noise

Ratio	Sharp	Broad
6dB	1.6µV	7.2µV
10dB	2.9µV	14µV
20dB	10µV	25µV
26dB	25µV	60µV

at 60% modulation 26dB occurs at 10µV

IF Rejection: 53dB

Image: 46dB

Maximum Signal Input: At 760kHz 52mV

Distortion:

30% modulation "Sharp" <1% "Broad" <2%

Output at set: 30% modulation 50mV

Whistle Filter dip frequency: 890Hz

Audio Bandwidth response (-3dB):

"Broad" 12Hz-7.6kHz "Sharp" 12Hz-2.6kHz

Louis A. Challis  
& Associates Pty Ltd

AUDIOSOUND 101

AM TUNER

Simulated AM

Stereo Circuit

Showing phase

differences

between Right


(upper curve)

and Left

(lower curve)

outputs

Date: 17/8/80

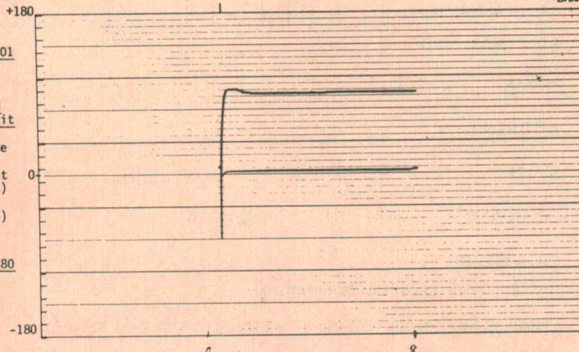

Louis A. Challis  
& Associates Pty Ltd

AUDIOSOUND 101

AM TUNER

Overall Response

Upper Curve -

"BROAD"

Lower Curve -

"SHARP"

Input


Frequency = 1kHz

Modulation

= 30%

Output = 50mV

Date: 17/8/80

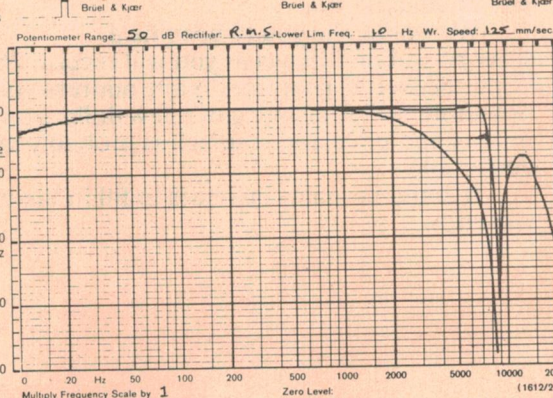



# BRIAN BAMBACH ELECTRONICS

## THE ELECTRONIC KINGS OF THE HUNTER VALLEY

- QUARTZ-LOCKED
- AUTO RECORD SIZE DETECTOR
- RUMBLE BETTER THAN 68dB
- WOW AND FLUTTER .03 PERCENT



**SHARP OPTONICA**

### RP-7100H

RING REVERSE CHARGES  
FOR OUR SPECIAL  
CHRISTMAS DISCOUNT  
PRICE.

#### THE WORLD'S FIRST APLD/DIRECT DRIVE


Select any track by the touch of a solenoid controlled button. If you wish jump further tracks for playing and recording ease. Also has a repeat function.

NO DEPOSIT FINANCE FOR APPROVED APPLICANTS.

**672 HUNTER STREET, NEWCASTLE, NSW 2300**  
**Telephone (049) 24-996**


# AUDIO DESIGN

## professional audio products

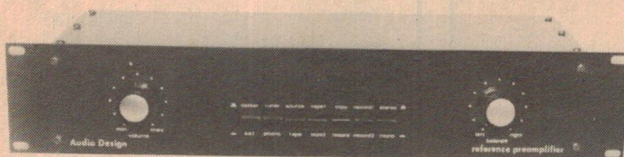
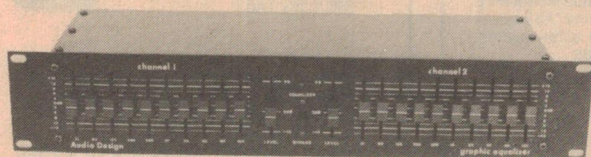
#### REFERENCE PREAMPLIFIER

This new class A preamplifier eliminates cartridge interaction common mode and slewing induced distortions, and provides accurate and extended bass response with 18dB/octave subsonic filtering below 15Hz. Noise reduction unit links and record/playback/copy facilities for two tape decks are provided. 20Hz-20KHz  $\pm 0.25$ dB(RIAA); <0.01% THD at 1V out (20Hz-20KHz) 10V/ $\mu$  phono slewing rate; 90dBA signal/noise below 10mV in 40dB overload margin (20Hz-20KHz) . . . . . \$395




#### OCTAVE BAND GRAPHIC EQUALIZER

A high slewing rate, ultra low noise, wide bandwidth design. 20Hz-20KHz  $\pm 0.25$ dB; <0.01% THD at 1V out; 100dBA signal/noise  $\pm 15$ dB control range (adjacent filters at  $\frac{1}{2}$ ) . . . . . \$395

Please contact

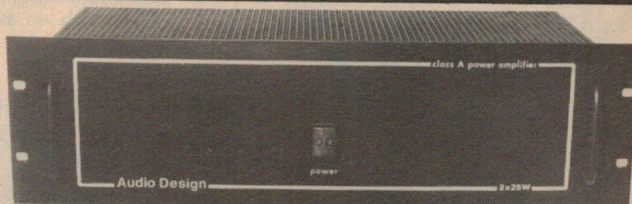
## AUDIO DESIGN

3/7 Harvton Street, Stafford 4053. Phone (07) 356-9191 or  
Sydney 597-3492, Adelaide 272-6606, Perth 322-4606.


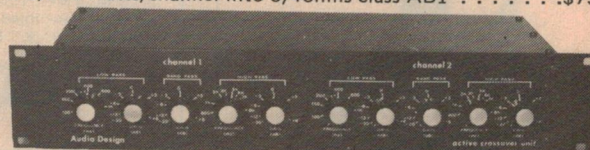
#### 4 POWER AMPLIFIERS

The amplifiers all feature high slewing rates and will drive 8 ohms  $\pm 400$  load phase angles to full output. Avoidance of output coupling zobel networks eliminates frequency response aberrations with reactive loading. 20Hz-20KHz  $\pm 0.25$ dB; <0.05% THD at 1dB below clipping (typically 0.02% 1KHz).  
25 Watts/channel into 8 ohms CLASS A . . . . . \$595  
50/75 Watts/channel into 8/4ohms class AB1 . . . . . \$350  
100/150 Watts/channel into 8/4ohms class AB1 . . . . . \$550  
200/300 Watts/channel into 8/4ohms class AB1 . . . . . \$750



#### ACTIVE CROSSOVER UNIT

This 2/3 way unit features a phase and amplitude coherent class A design. Variable 100Hz-1KHz, 8Hz-8KHz crossover frequencies. 5V/ $\mu$ s slewing rate; 100dBA signal/noise ratio; <0.01% THD at 1V out; 26dB gain range. . . . . \$395  
NEW SUBWOOFER CROSSOVER 18dB/octave;  
150Hz nominal . . . . . \$250

OTHER PRODUCTS INCLUDE compander, active cross-over/amplifier combination, moving coil amplifier, disco mixer, 12 into 2 microphone mixer, loudspeaker systems, passive Crossovers.



# BAD T.V. RECEPTION

IMPROVE YOUR PICTURES BY FITTING AN AMPLIFIER, PLUS A GOOD QUALITY CABLE. SUCH AS:

**ECRAFT Double Screened Coaxial cable**  
2045 3.5 dB loss at 216 Mhz per: 30 M 47c per metre.  
2063 2.05 loss at 216 Mhz per: 30 M 1.08 per metre.  
Open-wire feeder 1.5 dB loss at 200 Mhz per 30 M 70c per metre.

## MAST HEAD AMPLIFIERS

HILLS	Input	Output	Gain	Ratio
Mh.1	300	300	10 dB	3.1
Mh.2	300/75	75	20 dB	10.1
Mh.4	300/75	300/75	25 dB	17.1

MH.4/10 or 20dB down on Ch's 3-4-5A

## KINGRAY

MH20	300	75	20 dB	10.1
MH20WN	300	75	20 dB	10.1

## LABGEAR


6060	75	75	28 dB	25.1
6059	75	75		

approx. 15 dB down on Ch's 0-6

## ECRAFT Line Amplifiers VHF-UHF

Type	Outputs	Gain per Outlet
175D16	1	16 dB
275D12	2	12 dB
375D10	3	10 dB
475D10	4	10 dB
175D25	1	25 dB
275D21	2	21 dB
375D19	3	19 dB
475D19	4	19 dB

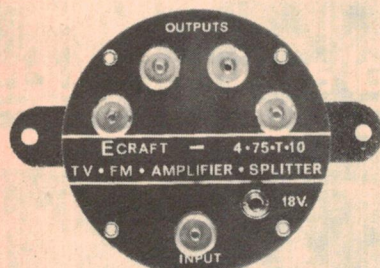These Amplifiers are suitable for installation of extra points in your home. Please phone for prices.



**ELECTROCRAFT PTY LTD**

68 Whiting Street, Artarmon NSW  
Telephone 438-4308 ext. 6  
or 438-3266 ext. 6.

WE ARE SPECIALISTS

30 years in the antenna business.  
Hours: 8am to 5pm

Prices subject to alteration without notice.

**Sm ELECTRONICS**  
MELBOURNE  
Ph (03) 842-3666

Trading Hours: 10am-6pm Mon to Fri.

**SME SYSTEMS**

## are on the move again


Due to an incredible increase in business, we have been forced to look for larger premises.

Consequently we will soon be moving into a new 4,500 sq. ft. air conditioned office and factory.

For our new phone number and address, watch this space in next months' issue.

Until then we are open for "BUSINESS AS USUAL" at the address at the bottom of this page.


## S-100 I/O PORT BOARD

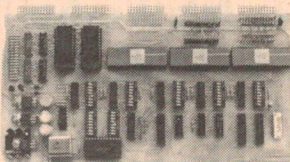

Now with dual serial ports

**DUAL SERIAL I/O CARD** Features:- dual independently controlled serial ports with TTY and RS232 outputs and inputs. Nine programmable parallel ports, crystal controlled baud rates fully buffered and address decoded. Plated through holes & solder resist mask.  
Price: Kit \$189. Ass. \$225.

## UV EPROM ERASER

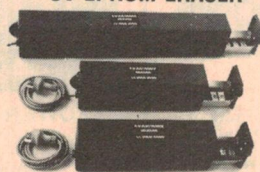

New product range. Model LEE/T 15W tube, 120 min timer, up to 40 EPROMS will erase in 10/15 mins. Model MEE/T 8W tube 120 min timer, up to 10 EPROMS will erase in 20/30 mins. Model MEE is same as MEE/T but with no timer. All erasers are fully assembled and have a safety switch.  
LEE/T \$125. MEE/T \$105. MEE \$85.

**SME SYSTEMS**

1096 Doncaster Rd, Doncaster East, Vic 3109.  
PO Box 19, Doncaster East, 3109. Telex AA37213.  
DEALER: Canberra - 81-5011, Sydney - 661-9237.

Send 66c in stamps for COMPUTER PRINTOUT CATALOGUE for more details.

ALL PRODUCTS AUSTRALIAN MADE AND EX STOCK (ALMOST).  
DEALER ENQUIRIES WELCOME.

Prices and specs. subject to change without notice.

All prices tax free, for retail prices add 15 percent.



**NORTRONICS**

## AUDIO & DIGITAL TAPE HEADS

for long life extended response

- Replacement heads for cassette decks, reel to reel decks, cartridges and cassette recorders. Also professional recorders and duplicators.
- Will fit AMPEX, SCULLY, TEAC, ATC, GATES, PENTAGON and many more.
- Specification sheet of all Nortronics heads available on request.
- Complete range of Alignment tapes for cassette, reel to reel and cartridge decks.
- REGULAR MAINTENANCE ENSURES CONTINUED OPTIMUM PERFORMANCE. Nortronics manufacturers a full range of audio care products.

MAGNETIC TAPE DEVELOPER



ALIGNMENT TAPES



SPlicing BLOCKS



TAPE HEAD CLEANER



SPlicing TABS

- NORTRONICS audio care products are designed to care for and maintain your valuable recording equipment.
- SEND TWO 22c STAMPS FOR OUR FREE BROCHURE ON THE COMPLETE NORTRONICS ACCESSORIES RANGE.

**E.I. EMAC INDUSTRIES Pty. Ltd.**


2 Bengal Crescent, Mount Waverley, Vic. 3149. Ph: (03) 277-9989.



ENTER THE 80's NOW WITH

# UNI-BOARD

## THE "UNIVERSAL" CIRCUIT BOARD

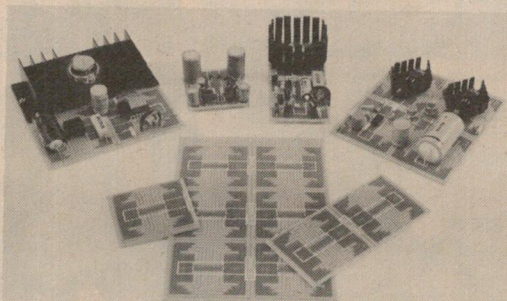

### BUILD ALMOST ANY CIRCUIT

- AMPLIFIERS
- REGULATED POWER SUPPLIES
- LINEAR IC CIRCUITS
- DIGITAL IC CIRCUITS
- PRE-AMPS, TONE CONTROLS
- STANDARD 6 PACK UNI-BOARD (41" x 6 1/2") HAS SOME 2,800 HOLES SO IT CAN EASILY ACCOMMODATE EVEN 40 PIN IC's
- MANY, MANY MORE!

### ECONOMY PLUS!

UNIBOARD WILL SAVE YOU MONEY.

- NO WASTE — SURPLUS BOARD CAN BE USED ON ANOTHER PROJECT
- USE AGAIN & AGAIN
- LOW COST "BREAD BOARDING"
- PROTOTYPE LAYOUTS CAN ALSO BE USED FOR YOUR "UNI-BOARD" PRODUCTION RUN
- BOARD EASILY CUT OR TRIMMED TO SUIT THE SIZE OF YOUR PROJECT.

### PRICE LIST

UNI-BOARD SINGLE MODULE PACK (STANDARD GRADE) .....	\$2.20
UNI-BOARD SINGLE MODULE PACK (PROFESSIONAL GRADE — F/GLASS) .....	\$2.60
UNI-BOARD TWIN PACK (STANDARD GRADE) .....	\$3.20
UNI-BOARD TWIN PACK (PROFESSIONAL GRADE — F/GLASS) .....	\$3.80
UNI-BOARD SIX PACK (STANDARD GRADE) .....	\$7.97
UNI-BOARD SIX PACK (PROFESSIONAL GRADE — F/GLASS) .....	\$9.90

TO: ADVANCED ELECTRONIC SYSTEMS PTY LTD  
3 STANILAND GROVE, ELSTERNWICK 3185

PLEASE SUPPLY ..... UNI-BOARDS AT \$ .....EA.  
I ALSO ENCLOSE 70c P&P.

NAME .....

ADDRESS .....

POSTCODE .....

— PTY. LTD —  
**DELSOUND**

BRISBANE

### NEW PRODUCTS

#### TOGGLE SWITCHES

1. 250V 10A
  2. AC 1500V
  3. More than 100M  $\Omega$  at DC 500V
  4. Less than 50m  $\Omega$
  5. More than 20,000 times
- R6-7A S.P.D.T. 0.99 each  
R6-7D D.P.S.T. 1.49 each  
R6-7E D.P.D.T. 1.76 each  
R6-7F D.P.D.T. 3 position 1.82 each



#### TOGGLE AND LEVER SWITCHES

1. 120V 5A & 240V 3A
  2. AC 1000V
  3. More than 100M  $\Omega$  at DC 500V
  4. Less than 50m  $\Omega$
  5. More than 20,000 times
- R6-8B S.P.D.T. 0.88 each  
R6-8C S.P.D.T. 3 position 1.09 each  
R6-8E D.P.D.T. 0.99 each  
R6-8F D.P.D.T. 3 position 1.09 each



#### TOGGLE AND LEVER SWITCHES

1. 120V 5A & 240V 3A
  2. AC 1000V
  3. More than 100M  $\Omega$  at DC 500V
  4. Less than 50m  $\Omega$
  5. More than 20,000 times
- R6-8H S.P.D.T. 0.76 each  
R6-8I D.P.D.T. 0.82 each



#### PUSHBUTTON SWITCHES

1. 250V 3A
  2. AC 1500V
  3. More than 100M  $\Omega$  at DC 500V
  4. Less than 50m  $\Omega$
  5. More than 20,000 times
- A-push "ON" and push "OFF"  
B-push "ON"  
R7-3A Push on push off. 0.80 each  
R7-3B Push on 0.63 each



#### A TYPE FUSE HOLDER

- 6.4 x 30mm  
Net weight: 12.5gr.  
R1-2A 3AG type 0.40 each  
R1-2App 3AG approved 1.50 each





#### PLUGS, JACKS AND CLIPS

- Diamond Type  
Colour  
Lamp  
Net Weight: 16.4gr.  
M, E, S, Multi facet  
bezel red 0.45 each


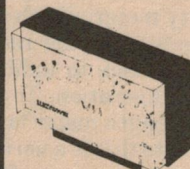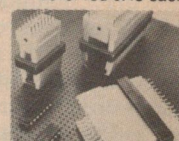
#### I.C. TEST CLIPS

- Gold plated, 3 models  
14-16, 26-28 and 40 way  
from \$6.00 each



- LED VU METER**  
Power supply 12-15V DC  
Current 40 mA  
Frequency response 20Hz to 100 KHz  
Sensitivity 770mV = 0dB  
Rise & Decay Adjust  
1mFD to 10mFD \$24.00 each


Above shows only part of our huge range, customers special requirements our speciality. All prices plus tax. Prices and availability subject to deliveries, stocks and fluctuations.

For further information, local agents and wholesale prices, write to the Australian Importers:
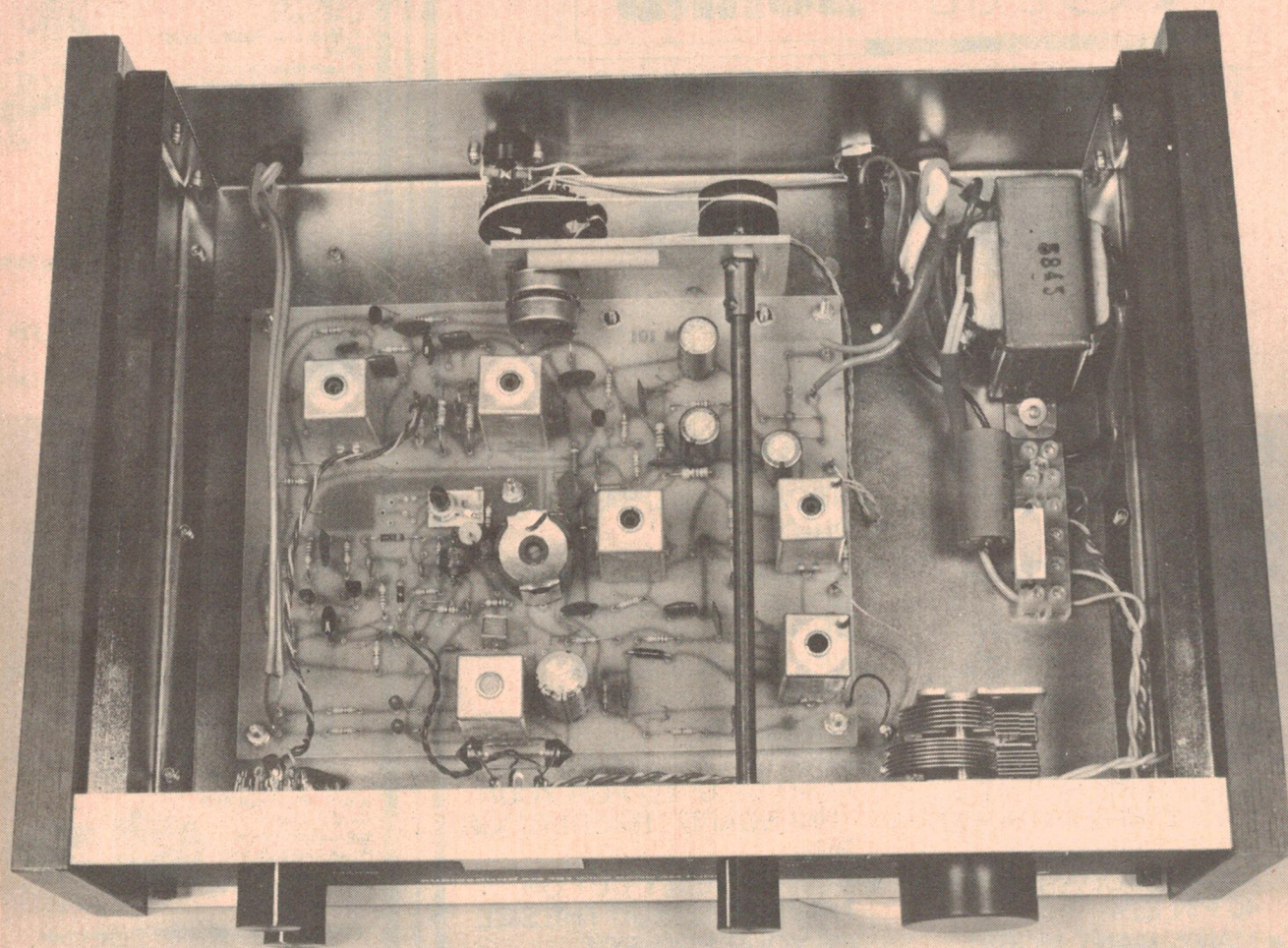
### DELSOUND PTY. LTD.

1 Wickham Tce. (Cnr. Wharf St.)  
Brisbane. Phone 229-6155.  
Wholesale and Retail suppliers of  
Electronic Hardware and  
Components.





panel. At the top left is a selectivity control for nominal bandwidths of 30 Hz to 9 kHz in the broad position and 30 Hz to 2.5 kHz in the narrow band position. Below the sensitivity switch is a rotary mains on/off switch and to the right of this is the sensitivity meter, which has five calibration levels with the range 2.5 to 4.5 marked in black to indicate the preferred area of operation. To the right of the signal strength meter is the gain control and next to this is a vernier tuning dial covering the range from 560 kHz to 1750 kHz. The vernier control on the dial provides a simple but effective 1.5 to 1 magnification of the rotational movement, making accurate tuning quite easy.

At the rear of the tuner are a mains lead, a fuse holder, a permanent one metre long output signal lead terminated in two RCA coaxial sockets and a balanced, low noise antenna socket for which an antenna is separately pro-

vided. The antenna works on the same principle as the simple tuning loop directional antenna developed over 50 years ago for radio direction finding. It overcomes some of the limitations of the integral ferrite loopstick antenna found in virtually all tuner and tuner/amplifier units manufactured today. Its major advantages are a better signal strength capture radio, general freedom from electrostatic field induction and the fact that the loop can be made smaller or larger as a means of controlling the pickup level to suit any given situation.

The antenna is cleverly designed in the form of a simple figure eight cable with the outer ends electrically connected. By opening out the gap between the ends of the leads it is possible to create any size loop within the limitations of the length of antenna cable supplied. The box even contains a number of drawing pins with which the

cable can be fixed to the wall or furniture and precise instructions on its installation and optimisation. Conceptually the idea is novel, although we doubt whether many people will find it aesthetically appealing.

The external aerial is supplemented by an input filter trap-tuned to 455 kHz and connected directly to the rear of the aerial socket inside the tuner. The appearance of this filter unit is a little ungainly but it performs its task very well and we were unable to fault it.


The main circuitry is neatly laid out on a quality printed circuit board and has the professional appearance of the other Audiosound products that we have previously reviewed. The circuitry is simple, featuring a two-gang tuning capacitor with oscillator and mixer stage (no RF stage), three very carefully designed intermediate frequency stages and sufficient space for servicing and alignment by either the owner or the

—to page 143.


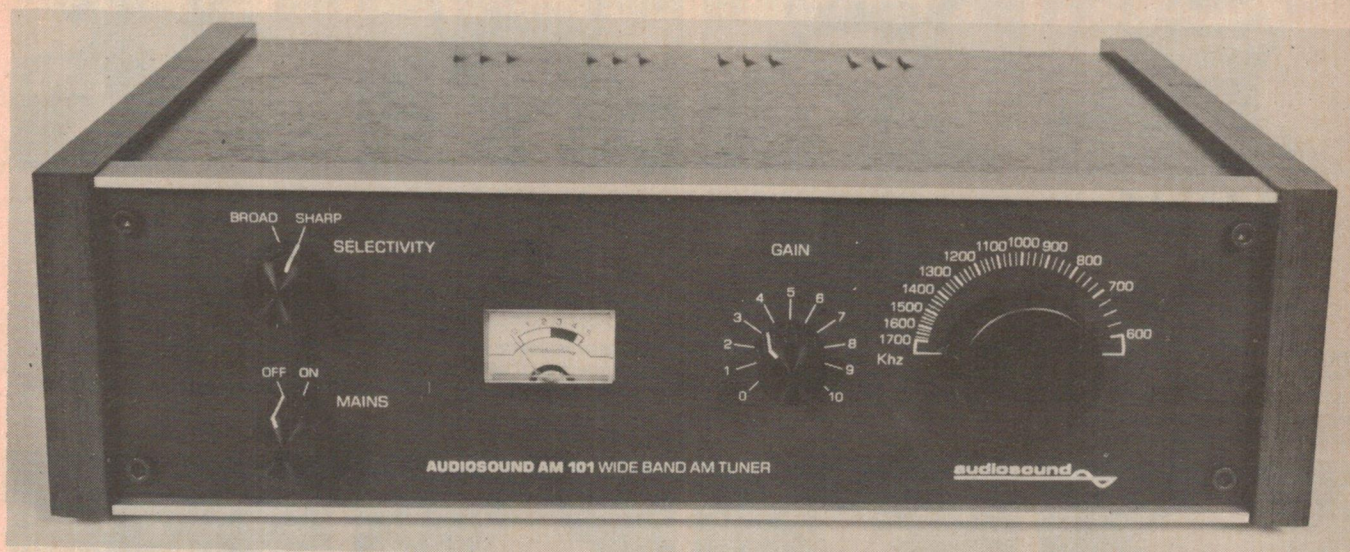
## Audiosound AM101 AM tuner

Designed in Australia to suit the unusually wide bandwidths of our AM broadcast stations, this tuner was much appreciated by our reviewer, Louis Challis.



IN THE LAST few months Australia's capital cities have seen the introduction of a number of new FM stations. In Sydney for example there are almost twice as many as there were at the beginning of the year. This is good news for people with FM tuners and receivers who are able to appreciate the medium, but it further emphasises AM's status as broadcasting's 'Cinderella'.

AM transmissions in this country have bandwidths of up to 15 kHz, much wider than in most countries of the world. Equally important, the quality of most AM broadcast studios is excellent — the majority of those that I have observed are vastly superior both acoustically and architecturally to the new breed of FM studios being built right now.

The second class status of AM has come about largely because the overseas manufacturers, who produce most of our receiving equipment, design

tuners and receivers to meet the technical performance requirements of the world's less fortunate countries, where the airwaves are truly crowded with stations and the maximum practical bandwidth is invariably more restricted than it is here.

So the majority of Australians are tricked into believing that the quality of sound being transmitted by our AM stations is vastly inferior to what is produced by the FM stations and that consequently we must have FM if we want to listen to high quality transmissions.

AM broadcasting does suffer from some limitations, notably its susceptibility to electrical interference and the tendency of some of the newer and less august stations to use an unreasonable degree of peak compression (to get the maximum signal to noise ratio on rock and pop music). However the ABC and some other stations still produce ex-

cellent programmes with sound quality rivalling that of the best FM stations and radiated power levels which all but swamp out electrical interference.

Audiosound and a few other equipment manufacturers have realised this problem and have responded to the market requirements. Or maybe they have read my continuing complaints and criticism of imported tuners in this magazine!


### Design

The AM101 is a neatly designed free standing or stacking type unit with a black anodised front escutcheon with white stencilled lettering, framed at top and bottom by strips of aluminium moulding. The sides of the unit are wood veneered particle board and the ventilated metal top has a simulated wood grain finish.

There are only four controls and a signal strength meter on the front


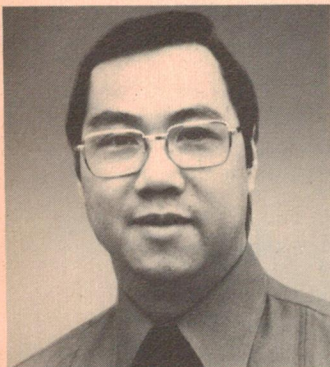
# Eight of the leading tape deck manufacturers talk frankly about TDK cassettes.




**AIWA®**

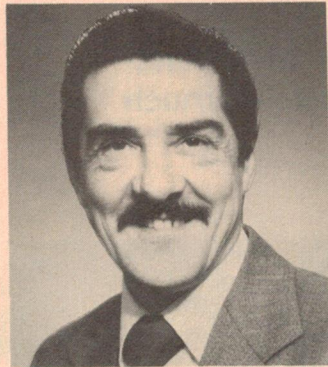**William Lam**

Product Manager  
Aiwa Australia Pty. Limited

*"We recommend TDK cassettes as they compliment the fine bias adjustment that all current model AIWA tape decks are equipped with, enabling optimum recording results."*




**KENWOOD HI-FI**

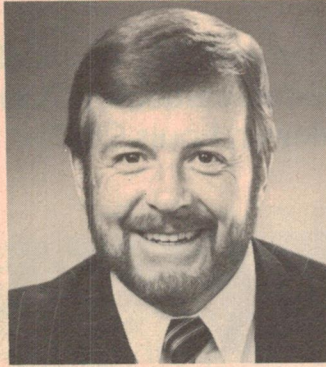**Reg. J. Hall**

National Sales Manager  
Trio-Kenwood (Australia) Pty. Ltd.

*"TDK tape is consistently accurate in quality reproduction, to the degree of being classified by Kenwood as our reference standard."*




**marantz®**

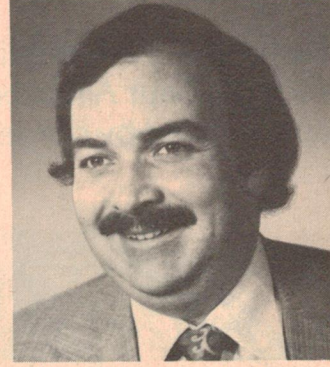**Ted Fawle**

Managing Director  
Marantz (Australia) Pty. Limited

*"The combination of Marantz two-speed cassette decks and TDK tape provides a new dimension in home recordings comparable to professional performance standards."*




**Nakamichi**

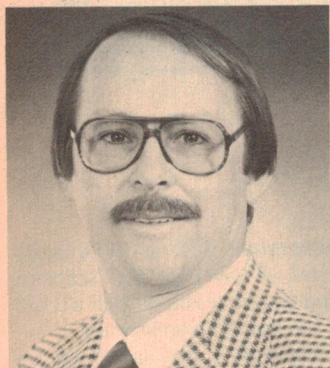**Geoff Matthews**

Marketing Director  
Convoy International Pty. Ltd.

*"We recommend TDK for Nakamichi cassette decks for two reasons. The first, for sonic performance and second, for the precision engineered, high stability cassette housing."*




**OPTONICA**

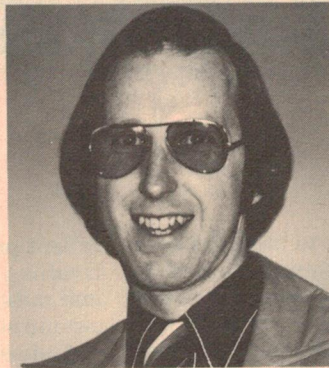**Geoff J. Muir**

Marketing Manager - Audio  
Sharp Corporation of Australia Pty. Ltd.

*"We at Sharp believe that TDK tapes add to the performance of our tape decks; you should have this improvement also."*




**PIONEER®**

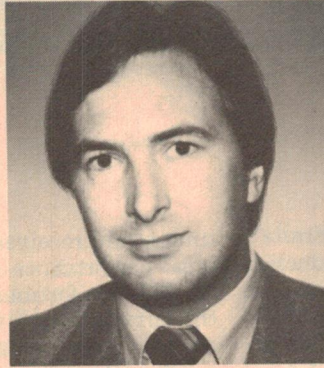**Graham Ham**

Products Manager Hi-Fi  
Pioneer Electronics Australia Pty. Ltd.

*"Pioneer and TDK engineers constantly work to set new standards of tape performance - and TDK delivers the wide frequency response typical of Pioneer decks."*




**Sansui®**

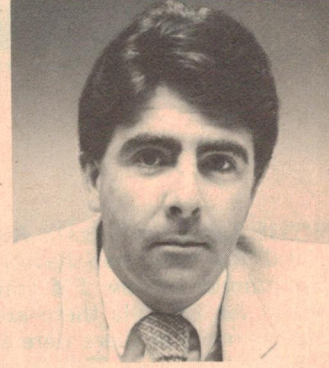**Geoff Brown**

Marketing Director  
Vanfi (Australia) Pty. Ltd.

*"We have had a long and close association with TDK, commencing when we first introduced our cassette decks in 1972 and have always recommended TDK cassettes."*



**YAMAHA**

**John R. Fahey**

Marketing Manager - Audio  
Rose Music Pty. Ltd.

*"When you put a five year warranty on the deck and a lifetime guarantee on the heads, you encourage the purchaser to use the best tape available...and that means TDK."*

For trade enquiries contact



**TDK®**

**TDK (AUSTRALIA) PTY. LTD.**  
4 Dowling Street, Woolloomooloo, NSW 2011  
Phone: (02) 358 1877 Telex: AA 70174



Write or phone for your FREE copy of the new revised "Guide to better recording".

Name \_\_\_\_\_

Address \_\_\_\_\_

Note: Any person practising tape recording should observe the provisions of the Copyright Act 1968.

TDK8073



# THE LOUDSPEAKER DILEMMA EXPLAINED.



Unlike **brand X**, the "Executive Monitor" has been designed to handle the whole content of the incredibly precise direct cut recordings, not just stand around on one leg and bounce around what is left.

Unlike **brand Y**, the "Executive Monitor" is anything but a speaker kit mercilessly put together from a box of bits and pieces.

And unlike **brand Z**, which is imported, the "Executive Monitor" has a price indicative of high quality and performance, not just a large mark-up by the importer.

The "**Executive Monitor**" will delight you with its performance, its looks, its finish and its 5 year warranty.

Chadwick take tremendous pride in their "Executive" range of speakers: "Executive Monitor" (\$990 a pair), "Executive 12" (\$499 a pair) and "Executive 10" (\$449).

Years from now you will wonder why a Chadwick speaker wasn't your first choice. For more information phone Chadwick today on (02) 647 1103.



Chadwick Audio Furnishings Pty. Ltd.

GM + ASSOC/Eti/11/80

## PHILIPS LOUDSPEAKERS

### PROFESSIONALLY DESIGNED SPEAKER KITS

If you are in the market for a \$2000 set of speakers with only a few hundred dollars in your pocket, we could have just what you want. The ETI 4000 Series Speakers — using Philips Drivers — compare very favourably with speakers costing twice to three times as much. If you are on a really tight budget you could consider the Philips AD12K12 kit — a 70 watts r.m.s. per channel 12" 3-way system — which you assemble completely in about 2 hours. A steal at under \$300 per pair. You can buy all components with or without boxes, any way you like. We have both the ETI 4000-I and II on display, as well as other Philips Kits. Come in for an audition, or write for further information.



northpoint hi-fi

 **WAGNER ELECTRONICS**  
SALES & SERVICE

100 Miller St, North Sydney.  
Ph 922-7780.

305 Liverpool Rd, Ashfield.  
Ph 798-9147.



## High fidelity

In 1976 Siliconix published a circuit for a high quality 40 W amplifier using VMOS devices, but each half of the output stage required three VMP12 (now designated 2N6658), 90 V TO-3 devices in parallel. Thus, twelve of the devices were required in a stereo amplifier providing 40 W per channel. Rather cumbersome — and costly. However, distortion at the mid-frequency range was only about 0.04% at the 40 W level and about 0.025% at the 1 W level. Only 22 dB of feedback was needed to obtain a response flat to 4 MHz and the slew rate was 100V/ $\mu$ s!

One of the advantages claimed for VMOS amplifiers is the lack of transient intermodulation (TIM), because the power bandwidth exceeds the small signal bandwidth. For any frequency below 500 kHz, the amplifier simply overloads before TIM appears.

Taking things a step further, the circuit in Figure 18 is a simple power amplifier first published in the Hitachi MOSFET application notes. The 2SK133 and 2SJ48 have an on-resistance of roughly two ohms, so that at 7 A peak output current you can expect a voltage drop of about 14 V across each device. With the power supply voltages shown the circuit is capable of around 50 W.

Transistors Q1 and Q2 form an input differential pair that compares the input signal with the output signal of the amplifier. The difference between these two signal voltages is fed to a second differential pair, Q4 and Q5. This ensures that the open-loop voltage gain of the amplifier is high and allows a fairly high feedback factor when negative feedback is applied. A relatively large amount of negative feedback is essential when using MOSFETs like this in audio amplifiers to linearise the MOSFET characteristics which have, on average, 10 times the distortion of a typical bipolar transistor of similar

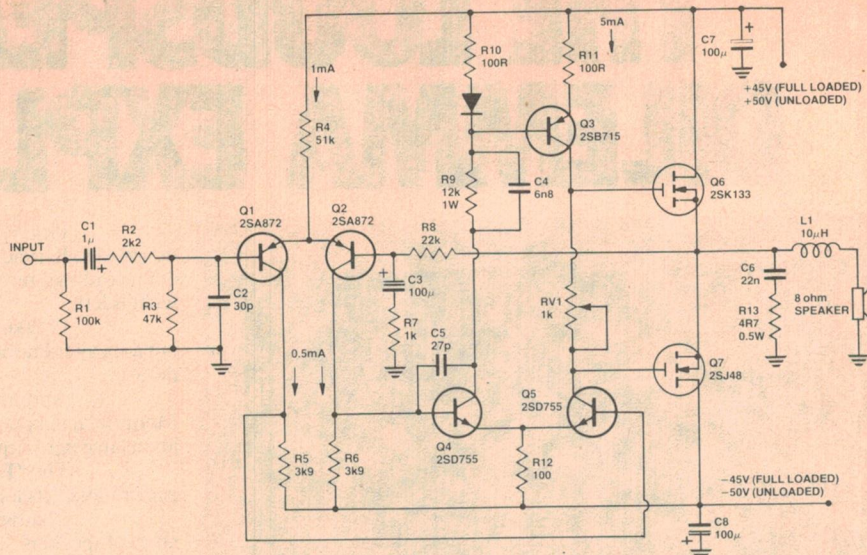


Figure 18. Circuit of a 50 W hi-fi amplifier from the Hitachi MOSFET application notes. Performance is quite good but dependent on the driver transistors.

power capabilities.

The transistors forming the driver stage, Q3 and Q5, have been specially designed by Hitachi to drive MOSFETs. They're superb devices, having a  $V_{ce0}$  of 100 V and a typical gain ( $h_{FE}$ ) of around 500. With these transistors the distortion characteristics shown in Figure 19 can be expected. Unfortunately, these transistors are not available in Australia at the present time and substituting alternative available transistors degrades performance considerably. A BD139/BD140 complementary pair for instance, with typical  $h_{FE}$  of around 50, is not capable of providing the necessary open-loop gain, especially at high frequencies. An experimental circuit we built with BC177s and BD139/BD140s gave less than 0.02% at 1 kHz at full power, rising to as much as 0.1% or more at 20 kHz. So, MOSFETs with all of their advantages have disadvantages too — mainly due to the fact that the forward transconductance is only a fraction of that of a good bipolar transistor.

In order to design an extremely high quality amplifier employing MOSFETs, we are really faced with a new set of problems to solve, but with the promise of performance that makes it worthwhile. Such a design is coming off our drawing board as you read this. Don't miss it! (This section on Figure 18 inserted by David Tilbrook ... Ed.). ●

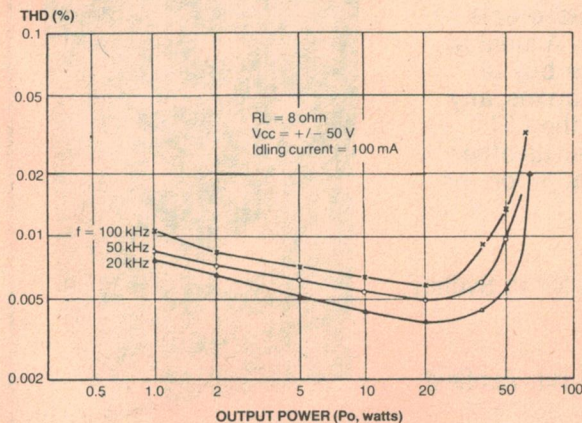


Figure 19. Distortion characteristics of the circuit in Figure 18.

## DO YOU WORK IN ELECTRONICS BUT PREFER IT AS A HOBBY ?



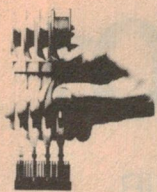
## WANT TO GET PAID TO PURSUE THAT HOBBY ?

Then we'd like to speak to you. We're looking for someone to join our project design team here at ETI. If you think you have the ability to design projects like you've never seen in ETI then write or phone us now. Age and qualifications are of secondary importance to ability and experience. Pay and working conditions are comparable to or better than generally found in the industry.

Phone, or write to:  
**Roger Harrison, Editor ETI**  
**15 Boundary St**  
**Rushcutters Bay NSW 2011**  
**(02)33-4282.**






## JUST WRAP™ WIRE WRAPPING TOOL

WHY CUT? WHY STRIP? WHY SLIT?  
WHY NOT JUST WRAP?

JW-1-B	BLUE WIRE
JW-1-W	WHITE WIRE
JW-1-Y	YELLOW WIRE
JW-1-R	RED WIRE

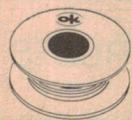

## JUST WRAP REPLACEMENT ROLLS

R-JW-B	BLUE WIRE	50 ft. Roll
R-JW-W	WHITE WIRE	50 ft. Roll
R-JW-Y	YELLOW WIRE	50 ft. Roll
R-JW-R	RED WIRE	50 ft. Roll



## UNWRAP TOOL FOR JUST WRAP

JWU-1	UNWRAPPING TOOL
-------	-----------------



## JUST WRAP KIT

JWK-6	JUST WRAP KIT
-------	---------------



## "HOBBY" WIRE WRAPPING TOOL BATTERY POWERED

Use "C" size NICAD Batteries, not included. Bits not included.

BW-2630	FOR AWG 26-30
BT-30	BIT FOR AWG 30
BT-2628	BIT FOR AWG 26-28

## HOBBY WRAP TOOLS

WSU-30	REGULAR WRAP
WSU-30M	MODIFIED WRAP


STRIP

WRAP


UNWRAP
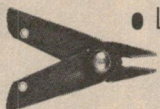
# XURON CORP.

Cutters have a new patented shearing action



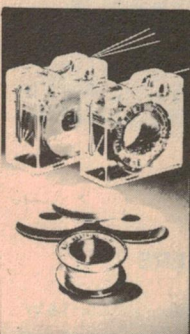- Very thin profile
- Low operator fatigue
- Low cost
- Long life



## TRI-COLOR DISPENSER

WD-30-TRI	TRI-COLOR DISPENSER
-----------	---------------------

R-30-TRI	REPLACEMENT ROLLS
----------	-------------------

## WIRE DISPENSER

WD-30-B	BLUE WIRE
WD-30-Y	YELLOW WIRE
WD-30-W	WHITE WIRE
WD-30-R	RED WIRE

## DISPENSER REPLACEMENT ROLLS

R-30B-0050	30-AWG BLUE 50 FT. ROLL
R-30Y-0050	30-AWG YELLOW 50 FT. ROLL
R-30W-0050	30-AWG WHITE 50 FT. ROLL
R-30R-0050	30-AWG RED 50 FT. ROLL


\*KYNAR-PENNWALT



## PRB-1 DIGITAL LOGIC PROBE

- DC to > 50 MHz
- 10 Msec. pulse response
- 120 K $\Omega$  impedance
- Automatic pulse stretching to 50 Msec.
- Automatic resetting memory
- Open circuit detection
- Automatic threshold resetting
- Compatible with all logic families 4-15 VDC
- Range extended to 15-25 VDC with optional PA-1 adapter
- Supply O.V.P. to -70 VDC
- No switches/no calibration

PRB-1	DIGITAL LOGIC PROBE
-------	---------------------

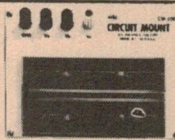

## PROTOTYPE BOARD CM-100

TERMINALS: 1,020 TEST POINTS. 188 separate 5 point terminals, plus 2 horizontal bus lines of 40 common test points each.

SIZE: 6 1/2" Wide, 5" Long.

CM-100	MODULAR PROTOTYPE BOARD
--------	-------------------------



## PROTOTYPE BOARD CM-200

TERMINALS: 630 TEST POINTS. 94 separate 5 point terminals, plus 4 bus lines of 40 common test points each.

SIZE: 6" Wide, 3 1/2" Long.

CM-200	MODULAR PROTOTYPE BOARD
--------	-------------------------




## PROTOTYPE BOARD CM-300, CM-400

CM-300 and CM-400 have two separated rows of five interconnected contacts each. Each pin of a DIP inserted in the strip will have four additional tie-points per pin to insert connecting wires. They accept leads and components up to .032 in. diameter. Interconnections are readily made with RW-50 Jumper Wire. All contact sockets are on a .100 in. square grid (1 1/4 in. wide).

CM-300	MODULAR PROTOTYPE BOARD
--------	-------------------------

CM-400	MODULAR PROTOTYPE BOARD
--------	-------------------------

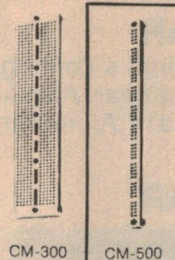

## MODULAR BUS STRIP

CM-500 is a bus strip to be used in conjunction with CM-300 and CM-400 for distribution of power and common signed lines. Two separate rows of common terminals, grouped into clusters of five. All contact sockets are on a .100 in. square grid.

CM-500	MODULAR BUS STRIP
--------	-------------------



## DIP IC INSERTION TOOLS WITH PIN STRAIGHTENER


Narrow profile. Pin straightener built into tool. Automatic ejector.

INS-1416	14-16 PIN DIP/IC INSERTER
----------	---------------------------

## MOS, CMOS-SAFE

GROUND STRAP NOT INCLUDED

MOS-1416	14-16 PIN, MOS CMOS SAFE INSERTER
MOS-2428	24-28 PIN, MOS CMOS SAFE INSERTER

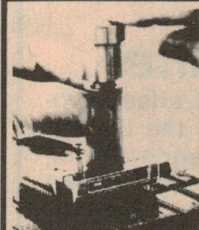


## 36-40 PIN CMOS-SAFE IC INSERTION TOOL

Aligns bent out pins. Includes terminal lug for attachment of ground strap.

GROUND STRAP NOT INCLUDED


MOS-40	36-40 PIN CMOS SAFE INSERTION TOOL
--------	------------------------------------

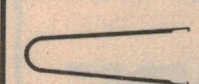

## DIP IC EXTRACTOR TOOL

Extracts all LSI, MSI and SSI devices of from 8 to 24 pins.

EX-1	EXTRACTOR TOOL
------	----------------

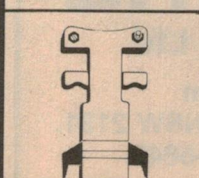

## 24-40 CMOS-SAFE EXTRACTOR TOOL

Removes 24-40 pin IC's, .600" centers. C-MOS safe. Includes terminal lug for attachment of ground strap.

GROUND STRAP NOT INCLUDED

EX-2	CMOS SAFE EXTRACTOR TOOL
------	--------------------------

AMPEC ELECTRONICS PTY. LTD. 1 Wellington Street, Rozelle, 2039. Tel. (02) 818-1166. Available from: NSW David Reid Electronics, 29-6601. Radio Despatch Service, 211-0191. Electronics (Distributors), 636-6052. Martin De Launay, 29-5834. Applied Technology, 487-2711. Vic. Radio Parts, 329-7888. Stewart Electronics, 534-3733. Ellistronics, 602-3282. Davred Electronics, 602-4673. Qld. L.E. Boughen, 36-1277. N.S. Electronics, 36-5061. W. Aust. Reserve Electronics, 275-2377. Taimac Electronics, 328-1988.



**YOU'LL LOVE OUR A.S.S.  
(After Sales Service)  
ON ALL OUR LIGHT AND  
SOUND GEAR.**

**OUT NOW  
INFINITY PANELS**

All shapes and sizes made to order — all new original designs. Ideal for discos and displays.

**SATURN 4 CHASERS**

The latest sound activated light chaser — Energy Authority approved. (Approval No. N/1385). 4 x 1000W per channel plus Snakelight connection.



**FRUNT P.A. GEAR**

12 into 2 mixers — 16 into 4 coming soon. All professional gear. Also a large range of guitar amps and P.A. mixer amplifiers.

**SOUNDOUT DISCO GEAR**



New range of units including Panther and Leopard.

**ALSO OUR OLD FAVOURITES**

Strobes, Mirrorballs (round and oval), effects projectors and accessories (including the Dynagraph), Snakelights, illuminated dance floors, turntables, pyrotechnics, bubble machines and accessories.

Brochures and price list on request.  
Mail Orders accepted.

**CASH-MORE**

**Enterprises Inc. Pty. Ltd.**

Offices and Showroom  
356 Liverpool Road, Ashfield, NSW 2131.  
Phone: (02) 797-7022, 798-5647.

**SALES — HIRE — A.S.S.**

Also Sound Stage Studio for TV commercials and full band facilities.



# B&W 801

**TO CREATE OUR  
SERIES 801  
WE BROKE THE RULES**

With the B & W 801, the design brief was brief. In fact, the required performance was summarised in just four telling words; full professional monitor requirements.

To qualify as a monitor by B & W standards, a system must have linear free-field amplitude response from 30Hz to 20kHz, with minimal deviation horizontally and vertically. It must be free from distortion and colouration and have an audio-powered overload circuit to protect against accidental damage or overload.

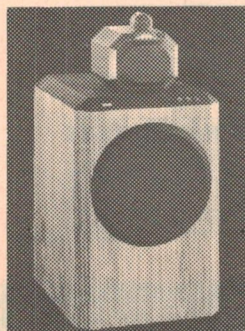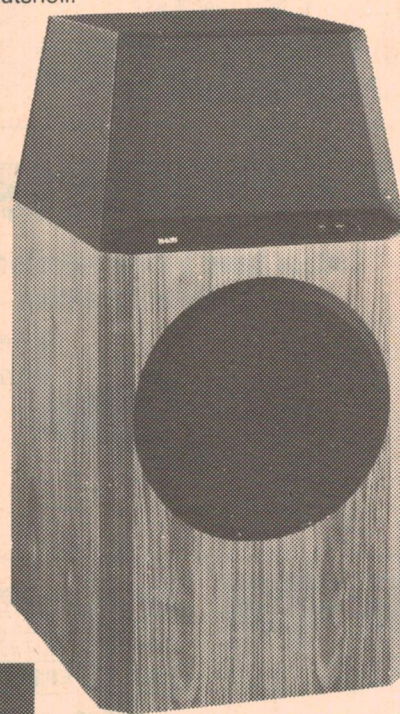This is the Series 80 concept in a nutshell.




**B&W**

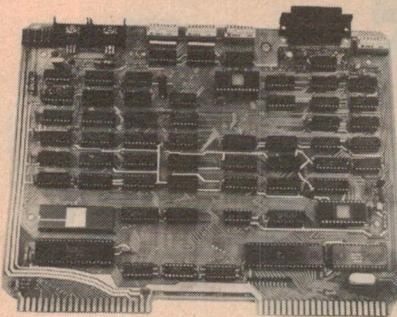**LOUDSPEAKERS**

For further information see your B & W dealer or contact  
Convoy International Pty Ltd  
4 Dowling Street  
Woolloomooloo NSW 2011  
Telephone (02) 3582088





### VIDEO PLUS II FOR AIM, SYM

Programmable display of up to 136 x 30; MC6845 supports hardware scrolling, programmable cursor, light pen, reverse video, ACIA; keyboard interface; full software on 2716. \$315.00 A&T.

**DRAM PLUS** 16K expansion to 32K, 16K EPROM space, EPROM programmer, 50 x 20 mm W/W area, S/W on cassette. \$353.00 A&T. **PROTO PLUS II** 1K add, decode, data buffers. \$64.00 A&T. **MOTHER PLUS II** buffered and decoded, 5 additional boards. \$108.00 A&T. **CARD CAGE PLUS** compatible with Mplus anod. aluminium. \$28.00. **MUSIC SYNTHESIZER** four voices; D/A filter and amp \$55.00 A&T. Music Synthesizer S/W for AIM or SYM on cassette. \$25.00



PO BOX 6502, GOODNA 4300  
PHONE (07) 288-2757

Prices subject to change without notice.

SAE for  
Datasheet

### SYDNEY OPERA HOUSE ELECTRONICS TECHNICIAN, Grade III Position No. S 311

#### SALARY:

\$14,470 range \$14,781.

#### QUALIFICATIONS:

**Essential** — Several years practical experience in operation and maintenance of professional electronic equipment. Possession of Electronics and Communications Certificate, Television Operators Certificate or equivalent.

Applicants should have a thorough knowledge of electronic circuits together with an understanding of electronics systems. An ability to construct electronic projects and work with colour-coded components is required.

**Desirable** — Experience working with Television Audio Systems.

#### DUTIES:

The successful applicant will be required to maintain to specification a wide range of audio, video and digital electronic equipment, sometimes under operational conditions.

#### CONDITIONS:

40 hours per week. Non-continuous shift work may be required for which appropriate allowances will be paid. Four weeks annual leave, Superannuation benefits (subject to certain conditions).

#### INQUIRIES:

(02) 20588 ext. 271 (Mr. G. Wilson) or ext. 296 (Mr. R. Hill).

Application forms may be obtained by phoning the Employment Officer, Sydney Opera House on (02) 20588 and are to be returned to this office by 14th November, 1980.

### HERE'S VALUE !

## TOP PROJECTS

FROM ELECTRONICS TODAY INTERNATIONAL  
VOLUME 5 PRICE \$3

Over 20 of our top projects for the princely sum of \$3 ! A collection of some of the 'Best from ETI' projects, including: The Induction Balance Metal Detector; Accentuated Beat Metronome; Marine Gas Alarm; Shutter Speed Timer; CB Power Supply; Ultrasonic Switch; Photo Strobe; House Alarm & many more ! How do you get it ! . . . . .

Send \$3.00, plus 65 cents post and handling, for your copy to:

ETI, Subscriptions Department  
3rd Floor, 15 Boundary St,  
Rushcutters Bay NSW 2011

# SEVLEN

# LIGHTING PTY. LTD.

MANUFACTURERS OF LIGHTING CONTROL SYSTEMS

Office: 4 Weldon St., Burwood. 2134 N.S.W.

Tel. (02) 74 8905

## HERE NOW! Saturn 4 Chasers & Snakelights....

The most portable, economical and adaptable low priced lighting system ever invented, a must for clubs, displays, windows and dance venues.


Connected to the "STARCHASER" controller, an amazing sequence is produced all within a tube.

Up to 300 metres of scintillating, pulsating chase.

No complicated connections, bend it, shape it, take it anywhere, anytime. (Each snakelight is 10 metres long). 12 different colours available.


The price will amaze you.  
Find out more - now!

DISTRIBUTOR AND TRADE ENQUIRIES WELCOME

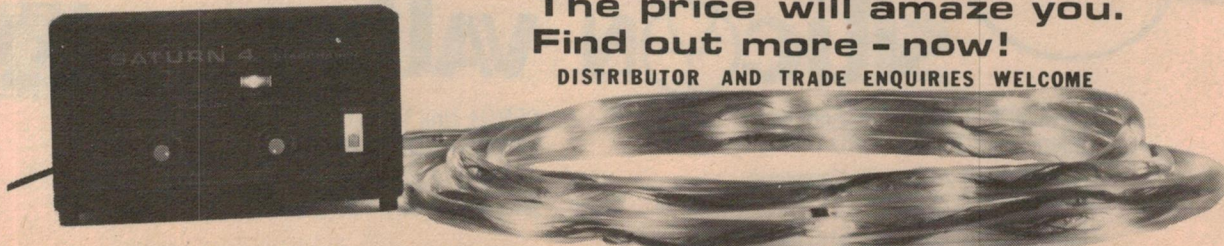



# CHRISTMAS SPECIALS

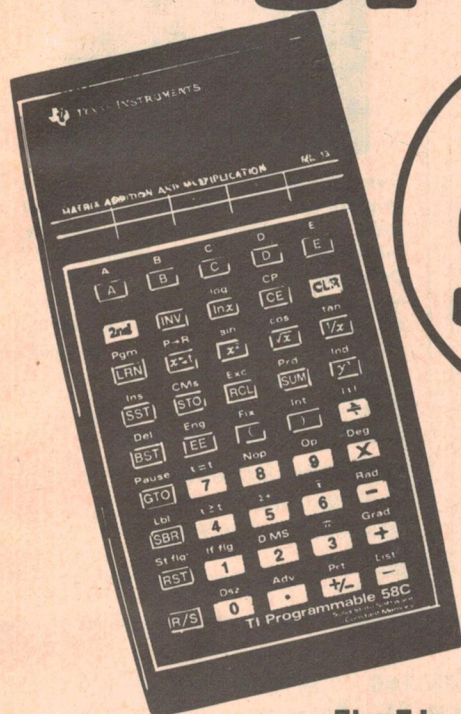

Save  
near  
**\$24**

## TI Programmable 58C

Here's a programmable calculator that offers more power, flexibility and capability and features TI's exclusive Solid State Software. With Master Library module with 25 programmes in math, statistics, and finance you can choose from 12 optional libraries. You can also programme the TI programmable 58C right from the keyboard. TI's Constant Memory feature retains data or programme information even when the calculator is turned off.

It has up to 480 programme steps or 60 memories with 4 types of display testing with independent test or "Y" register and 10 additional test registers.

Over 170 functions and operations in scientific, engineering, and statistical fields. Complete editing and error correction capabilities with single-step and back-step keys.

The TI Programmable 58C gives hard copy when used with the PC-100C thermal printer/plotter.

**\$122.99 + TAX = \$141.44**



Saving  
**\$32.66**

## The T.I. Programmable 59

A revolutionary new personal programmable calculator. 960 programme steps or 100 memories. Master library module plug in feature. 25 different programmes in key areas. Four types of display up to 10 additional test registers. 72 useful labels. Up to 6 levels of sub routines. Complete programme editing. Operates with PC-100C printer. Optional solid state software libraries.

**\$276.99 + TAX = \$318.54**



Save  
Over  
**\$23**

**\$198.99 + TAX = \$228.84**

## PC-110C

The PC-110C printer plotter turns your programmable T.I.58C or T.I.59 into a high speed quiet printer calculator that prints, lists and traces your programme.

TEXAS INSTRUMENTS  
INCORPORATED

**silicon valley**



ADELAIDE: 170 Sturt St, Adelaide.  
Telephone (08) 51 4080

BRISBANE: 22 Ross St, Newstead.  
Telephone (07) 52 1339

MELBOURNE: 208 Whitehorse Rd, Blackburn.  
Telephone (03) 877 5311

PERTH: Unit 1, 25 Brisbane St, East Perth.  
Telephone (09) 328 8091

SYDNEY: 23 Chandos St, St. Leonards.  
Telephone (02) 439 2965

NOTE: Offer closes 24th December, 1980



# MINI-MART

## Where readers can advertise — For Sale/Wanted/Swap/Join.

• We'll publish up to 24 words (maximum) totally free of charge for you, your club or your association. Copy must be with us by the 1st of the month preceding the month of issue. Please — **please** — print or type adverts clearly, otherwise it may not turn out as you intended! Every effort will be made to publish all adverts received however, no responsibility for so doing is accepted or implied. Private adverts only will be accepted. We reserve the right to refuse adverts considered unsuitable.

• **Conditions:** Name and address plus phone number (if required) must be included within the 24 words. Reasonable abbreviations, such as 25 W RMS or 240 Vac, count as one word. Adverts must relate to electronics, audio, communications, computing etc — general adverts cannot be accepted. Send your advert to:  
**ETI Mini-Mart, Modern Magazines**  
15 Boundary St,  
Rushcutters Bay NSW 2011

### AUDIO

**FOR SALE:** Two Byer transcription turntables, no tone arms, the lot \$100 o.n.o. Write to R. Saunders, P.O. Box 54, Adamstown, NSW 2289.

**COLLECTORS:** I have for sale one Tandberg Model 6 reel to reel tape recorder (valve), including service manual. Phone Paul (042) 61-5451.

**SPEAKER** Systems to your specs. 6" auto systems to 16" thumpers. Top quality finish. Contact Andrew Hutchison, 10 Janner Street, Bargara, Qld 4670. Phone (071) 79-2430.

**FOR SALE:** Phase Linear amplifier 400 series 200 Wrms mounted in fan cooled power rack. Cannon connections completely overhauled suit disco work \$650 o.n.o. Phone (03) 88-1795.

**TECHNICS SL-10 TURNTABLE**, with moving coil cartridge and pre-pre amp, like new, \$375. Denon 103 cartridge, new \$80. Phone Tim (02) 888-2622.

### COMMUNICATIONS

**Kenwood TR 7625 2M transceiver**, as new \$300. **Astro 200 HF transceiver**, good condition \$500. R. Hunter, 67 Wilks St, Cairns, Qld 4870. Phone (070) 54-2385.

**SELL:** 50m long wire shortwave antenna, \$360. Complete with Realistic DX300 receiver, 10kHz - 30MHz AM/SSB; new condition, packing. Wayne Wolfgang, "Pendennis", Denman, NSW 2328. Phone (065) 47-2330.

**FOR SALE:** Transceiver. IC22 with an assortment of crystals. \$120. Phil Wait, ETI. (02) 33-4282.

**SALE:** Power supply 13.8Vdc 10A peak \$90. Teleprinter Model 15 recently overhauled \$50. 115Vac transformer suit above \$20. Loop supply for Teleprinter \$20. Phone Craig (02) 74-0316 a.h.

**SHORTWAVE** listeners and DXers: Join Australia's national "Southern Cross DX Club". Details for 22c stamp from Grantley Williams, 19 Wicklow Av, Athelstone, SA 5076.

**SELL:** Erlang meter model ECSQ 144/2 as new. Range 1 max 10mA. Range 2 max 50mA. 6" square face. Can be converted. Suitable most hobbyists. Best offer secures. CB Clarion raider 18ch Transceiver. Complete with mike in good condition. Best offer. Brynley Bennett (07) 208-1860.

**COLLINS R391/URR receiver** in very good condition with some spare valves \$500. Also instruction manual. John Bies, 38 Carbine St, Kerang, Vic 3579.

**AUSTRALIAN Radio DX club** for shortwave, mediumwave DXers. For a sample copy send one 50c stamp to P.O. Box 79, Narrabeen, NSW 2101, mentioning this ad.

**WANTED:** Realistic SX-190 or AX-190 and Barlow Wadley ECR30 Mk2. N. Glaros, 11 Norman St, Underdale, SA 5032. Phone (08) 43-4981.

### COMPUTERS

**TECHNICO TMS 9900, 2K RAM, 2K EPROM**, instant input assembler, complete manuals and drawings, \$400. R. Hunter, 67 Wilks St, Cairns, Qld 4870. Phone (070) 59-2385.

**S100 12K PROM/RAM board**, as new 2708 or 2704 PROMS may be used. Power on reset jump feature. Full documentation. \$125. Phone (02) 887-1686.

**16K RAM card, S-100 buss, \$250. Video RAM card, S-100 buss, \$350. EPROM (2716) \$14. Mail order acceptable.** Clifford Kobayashi, 205/76 Roslyn Gardens, Elizabeth Bay, NSW 2011. Phone (02) 358-1806.

**S100 Motherboard** with 8 goldplated slots and selected lines terminated. \$25. M. Morton, 104/2 Artamon Rd., Willoughby, NSW 2068. Phone (02) 411-1892.

**VDU ETI-632 32 x 25 well constructed, boxed and tested.** Circuit diagrams included. \$70. M. Morton, 104/2 Artamon Rd., Willoughby, NSW 2068. Phone (02) 411-1892.

**Z80 STARTER KIT**, assembled, onboard keyboard and hex display, cassette interface, PROM programmer, 2K monitor, 2 x 8 bit ports, documentation. \$250 posted. Kevin Wilson, 72 Tweeddale Rd, Applecross, WA 6153. Phone (09) 326-6795 b.h., (09) 364-2843 a.h.

**COPYRIGHT:** The contents of Electronics Today International and associated publications is fully protected by the Commonwealth Copyright Act (1968).

Copyright extends to all written material, photographs, drawings, circuit diagrams and printed circuit boards. Although any form of reproduction is a breach of copyright, we are not concerned about individuals constructing projects for their own private use, nor by pop groups (for example) constructing one or more items for use in connection with their performances.

Commercial organisations should note that no project or part project described in Electronics Today International or associated publications may be offered for sale, or sold, in substantially or fully assembled form, unless a licence has been specifically obtained so to do from the publishers, Modern Magazines (Holdings) Ltd or from the copyright holders.

**LIABILITY:** Comments and test results on equipment reviewed refer to the particular item submitted for review and may not necessarily pertain to other units of the same make or model number. Whilst every effort has been made to ensure that all constructional projects referred to in this edition will operate as indicated efficiently and properly and that all necessary components to manufacture the same will be available no responsibility whatsoever is accepted in respect of the failure for any reason at all of the project to operate effectively or at all whether due to any fault in design or otherwise and no responsibility is accepted for the failure to obtain any components parts in respect of any such project. Further, no responsibility is accepted in respect of any injury or damage caused by any fault in the design of any such project as aforesaid. The Publisher accepts no responsibility for unsolicited manuscripts, illustrations or photographic material.

**WANTED:** Floppy or mini floppy drive(s). Also a printer, 300 baud (or faster), with lower case. Contact Geoff Cohen, 72 Spofforth St, Holt, ACT 2615. Phone (062) 49-2688 b.h., (062) 54-7608 a.h.

**SELL:** EA2650.2K, fully working, documentation, software; BASIC, games. I will expand sys. if wanted. \$175. R. Curtain, 12 Esplanade, Williamstown, Vic 3016. Phone (03) 397-5968.

**CROMENCO Z2 computer** 4MHz 48K 8 inch Persci dual disk drives, BASIC, Z80 assembler, word processor. \$3900. R. Butcher, 4 Summit Drive, Bulleen, Vic 3105. Phone (03) 850-5880.

**MUST SELL 2650 May EA version!** Every IC socket gold. Only three decoder ICs. All other parts. Otherwise finished. \$25. 48A Malton Rd, Beecroft, NSW. Phone Ben (02) 848-8141 after 6pm.

**WANTED:** EUY-10E023LE printer mech. for the ETI-641 S100 printer. T. Menzies, 320 Pallas St, Maryborough, Qld 4650. Phone (07) 22-1143 a.h.

**ZX-80 Sinclair computer** for sale. Programs, basic, video VHF or UHF output. Used two hours, perfect working condition. Giveaway \$199. Phone (02) 337-2317.

### MISCELLANEOUS

**WANTED:** Novus 650 mathsbox calculator. Must be in good working condition. Will pay \$5 o.n.o. R. Petronio, 11 Coppleridge Drive, Elizabeth Vale, SA 5112. Phone (08) 255-5403.

**SELL:** PCB resistors, 390K ½W, 50c per 100, 500K trimpots, \$9 per 100, M. Sully, 61 Newman St, Niddrie, Vic 3042. Phone (03) 379-2879.

**WANTED:** Mullard circuit for stereo amp using ECL86 6GW8 valves. A.W. Hurrey, 4 Eagle Av, Burleigh Heads, Qld 4220. Phone (075) 35-1098.

**DIGITAL** Frequency counter — constructed EA2 project, not suitable for my requirements \$120 o.n.o. Frank Collins, 14 Durant Way, Brentwood. Phone (09) 364-5715.

**NONSTOP MUSIC System.** 3M Cantata tape player. Suit motel, office, home. Includes popular music tape. Good condition. Cost \$1100, sell for \$450. Phone (08) 261-5904.




**SELL:** Power supply 1.2A 20 Volts plus fixed 5V supply. Two large meters for volts and amps, two scales, short-circuit proof. Sell for \$45, which is less than the cost of components. George Skarbek, 879 High St, Glen Waverley, Vic 3150.

**SELL:** Telequipment D66 dual trace 25MHz CRO with manual and two probes. Good condition, \$650 o.n.o. G. Spiers, Brisbane (07) 376-1484.

**SELL:** Gemtronics GTX-3325 23 ch. SSB CB, S/8 ground plane aerial with cable. Phone (02) 631-0116 before 8.00 a.m. or after 3.30 p.m. \$165 or any reasonable offer.



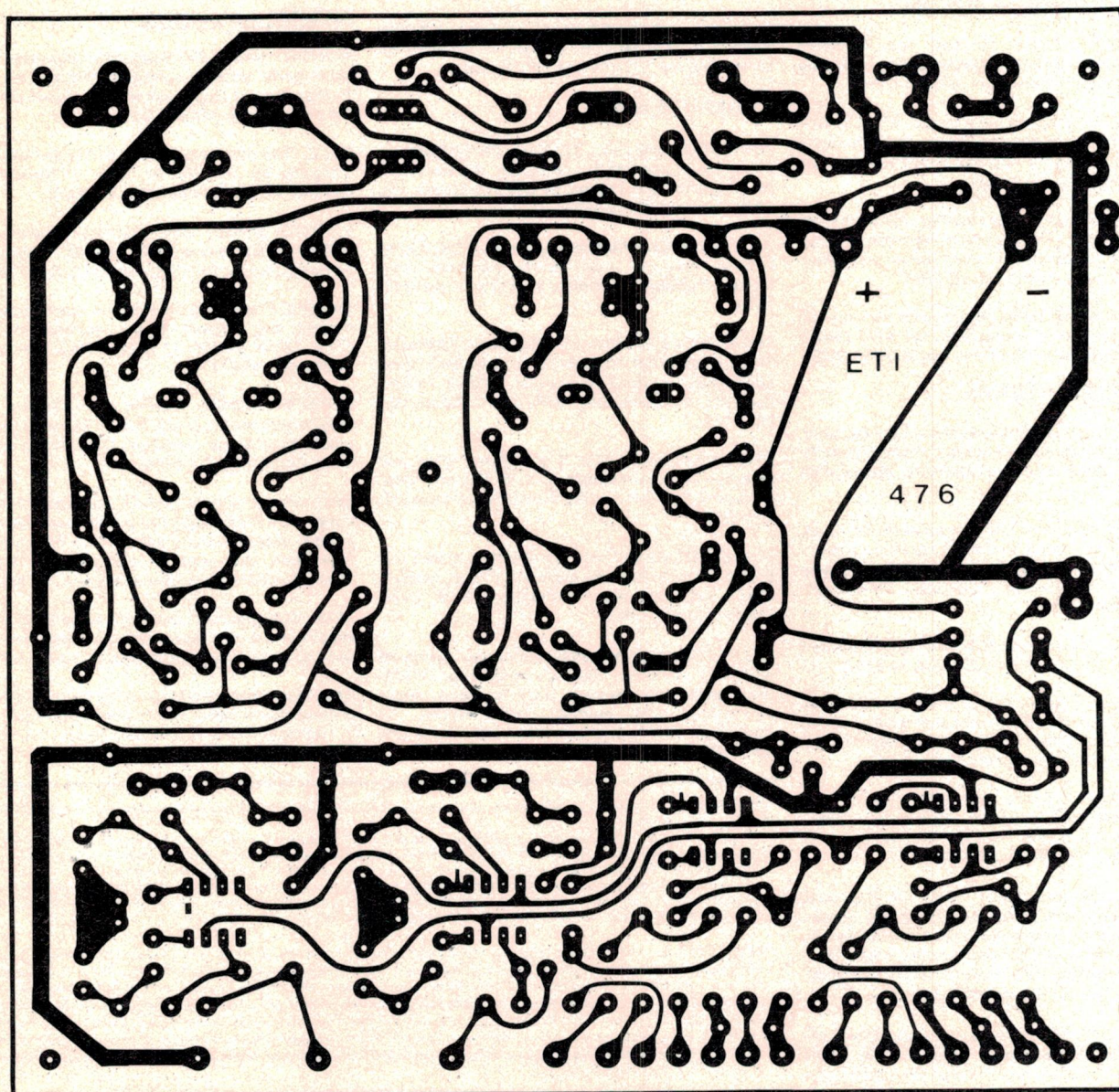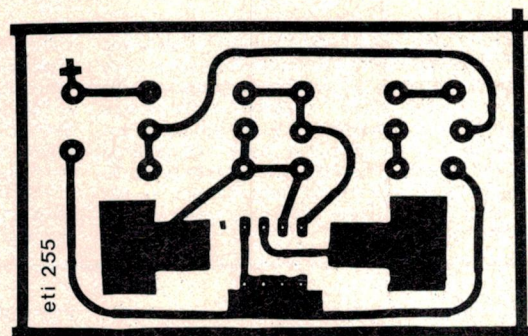
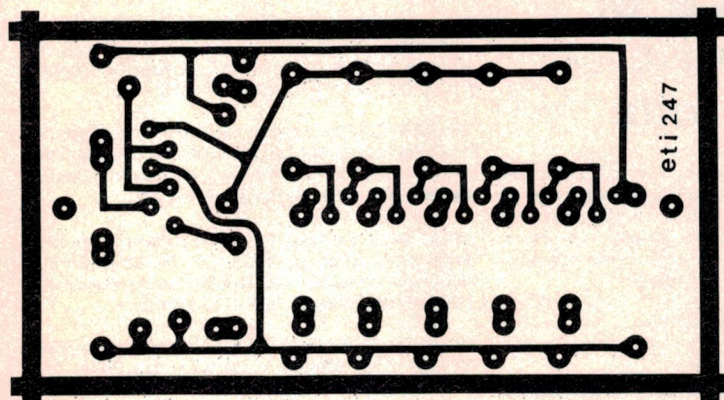
Instructions on how to make your own pc boards using the Scotchcal method and exposing through this page may be found on page 113 of the March '80 issue.




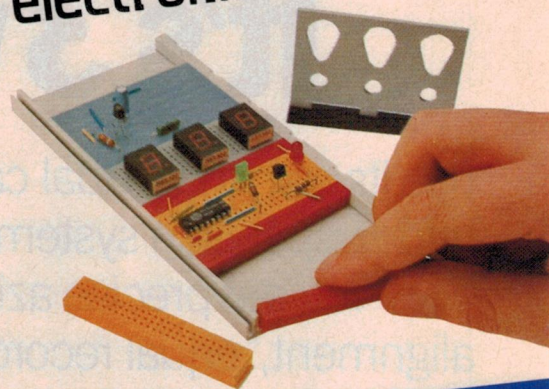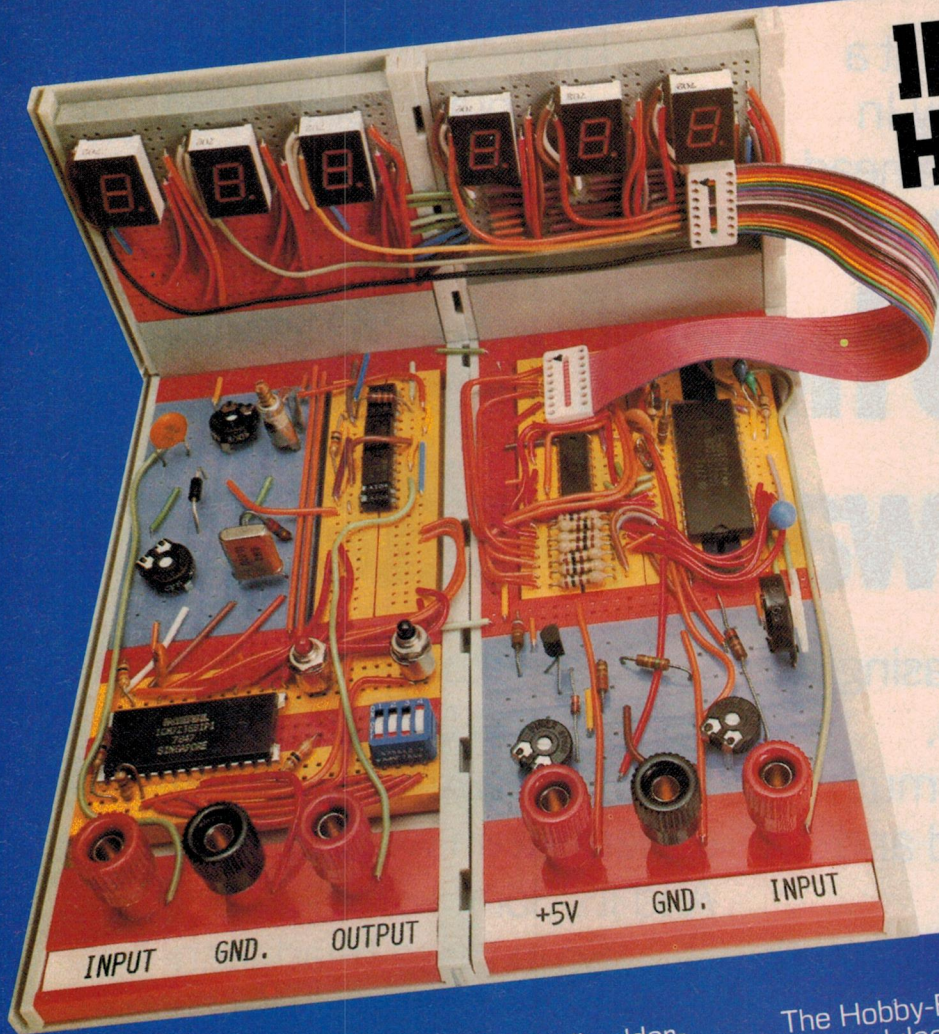
# INTRODUCING HOBBY-BLOX™

The new modular circuit building system designed especially for electronic hobbyists.



Until now, you had to buy "professional" solderless breadboards for your projects and pay "professional" prices. Now there's Hobby-Blox, a totally new circuit-building system that's not only economically priced but offers many more advantages to the hobbyist.

At the core of the system are two expandable starter packs, one for discrete component projects, the other for integrated circuit projects. Each comes with a number of Hobby-Blox modules that fit into a tray and an illustrated project booklet. In addition, the system includes 14 separate component packs you can purchase individually — terminal, distribution and bus strips, speaker panels, binding posts, etc.

The Hobby-Blox system is easy to use because the modules are color-keyed and letter/number indexed. It's time-saving, because they're solderless. It's compatible with DIP's of all sizes and a wide variety of discrete components. And you save money, because the parts can be reused again and again.

How far can you go with the Hobby-Blox system? Take a look at the example above. Then you'll know why we say, "your only limit is your own imagination!"

Patents Pending  
© A P PRODUCTS INCORPORATED 1980



A P PRODUCTS INCORPORATED  
1359 West Jackson Street  
Painesville, Ohio 44077  
(216) 354-2101

**For a free catalog,  
contact your local  
HOBBY-BLOX™ dealer:**

N.E.T. PTY. LTD.  
92 Woodfield Boulevard  
Caringbah, N.S.W. 2229  
TEL: 525-6090

RIFA PTY. LTD.  
P.O. Box 485  
Cross House, 2 Cross Street  
Hurstville, N.S.W. 2220  
TEL: 570-8122

RIFA PTY. LTD.  
P.O. Box 95  
202 Bell Street  
Preston, Victoria 3072  
TEL: (03) 480-1211



It's a better system, at a better price, and it's Sony. In Sony's new TC-K81 three head cassette tape deck, each head

The new TC-K81 also has microcomputer control and feature-touch operation, and LED Peak Programme Meter,

# Sony's 3 head system. It's 3 ways better.

has its own individual casing and suspension system.

You get precise azimuth alignment,\* equal record and playback head-to-tape pressure, and reduced magnetic leakage flux.

It's a unique three-head system, with two-motor, closed-loop dual capstan drive with metal tape compatibility.

bias and record level calibration system, and Dolby\*\* NR.


It's an exceptional new system, at an excellent price. And it's Sony.

So in three-head technology, we're three-ways better.
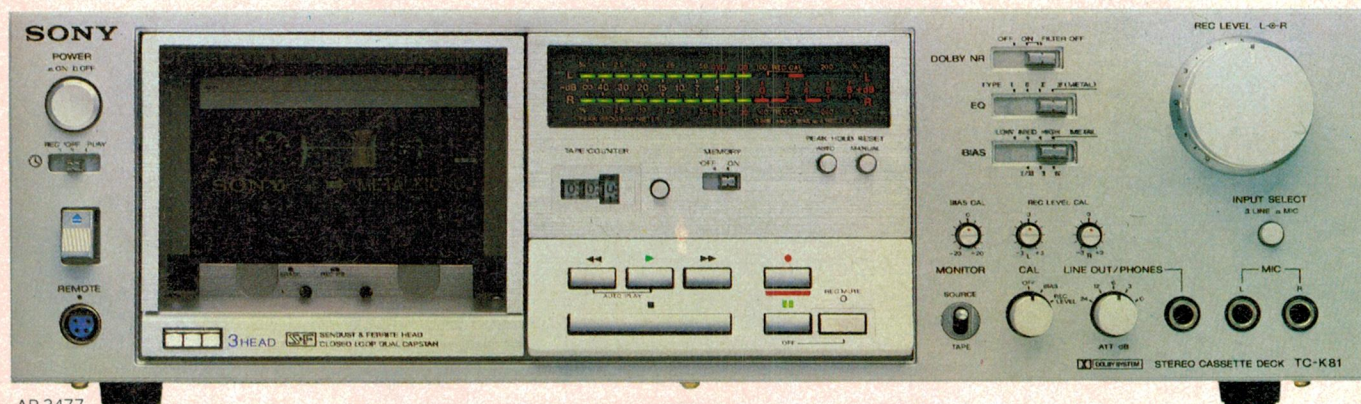
## SONY®

\*Factory aligned.

\*\*Dolby is a registered trademark of Dolby Laboratories.






# Introducing a totally new concept in stereophones.

The new Koss HV/X high velocity stereophone represents a remarkable breakthrough in hear-thru stereophone design and performance. For the first time, Koss engineers have been able to create a lightweight, hear-thru stereophone that combines the transparency of high velocity phones with the superior bass performance of closed-type phones. The result is a breathtaking musical experience.
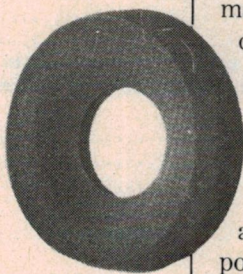
## CONTOURED VARIABLE-DENSITY EARCUSHIONS


While most lightweight, hear-thru stereophones have earcushions that fit against the ear, the new Koss HV/X features a unique, contoured, variable-density cushion that fits around the ear. Not only does this unique earcushion design create a far more comfortable stereo-  
phone but it has also allowed Koss engineers to create a dramatically better element



design as well.

These new variable-density earcushions are made up of a very porous material that is acoustically transparent at the perimeter of the earcushion yet compressed toward the center region. This varies the pattern of acoustic resistance over portions of the earcushions creating the proper seal for specific bass frequencies while al-

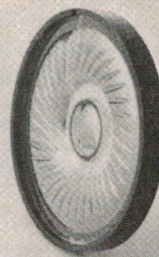lowing the flow of middle and high frequencies at the perimeter of the earcushions.



## LIGHTWEIGHT ELEMENT

The uniqueness of the new variable-density earcushions made it possible

for Koss engineers to design a lightweight element that reproduces a Sound of Koss you have to hear to believe. Incredibly, even though the overall weight of the element was reduced, Koss engineers were able to develop a magnet with enough magnetic density to drive an extra large diaphragm. With a response range of 15 to 35,000 Hz, the new Koss HV/X will drive you into ecstasy and our competitors nuts.

## HEARING IS BELIEVING.

Slip into the new Koss HV/X or HV/XLC with volume/balance controls at your audio dealer soon. You'll like the best of both worlds: the open, airy, up-front sound of hear-thru stereophones and the deep, rich bass performance of closed-type stereophones.

*For more information on the HV/X and our full line of stereophones write to*



**ELECTRO-VOICE  
AUSTRALIA PTY. LTD.**

© 1980 Koss Corp.

**KOSS® stereophones/loudspeakers**  
**hearing is believing™**

ELECTRO-VOICE AUSTRALIA PTY. LTD. 174 Taren Point Road, Taren Point, NSW, 2229. Phone (02) 525-8588.



# WIN A TOP LINE MARUNI MICROPHONE AND PAIR OF HEADPHONES \$3000 in prizes !



## 20 sets to win

### HV 3000 MARUNI HEADPHONE

Frequency Response:	8 Hz - 28 kHz
Mylar Diaphragm:	16 micron thin
Rare Earth Samarium Magnet	
Sensitivity:	98 dB
Total Harmonic Distortion:	0.17% (90 dB)
Matching Impedance:	8-750 Ohm
High Velocity Open Air System	
Maximum Input:	300 mW
Weight w/out cord:	170
R. Retail Price:	\$69.00

### MARUNI DYNAMIC MICROPHONE DM901

Frequency Response:	80 Hz - 16 kHz
Polar Pattern:	Unidirectional
Sensitivity:	-77 dB
Impedance:	Low-Z, 600 Ohm
Built-In Noise & Pop Filter	
XLR Connector — 15 ft lead — Phono Plug	
Grey Hammertone Finish	
R. Retail Price:	\$61.20



**WE'RE LOOKING TO GIVE AWAY** a top line Maruni microphone and pair of headphones to each of twenty knowledgeable/studious/crafty/cunning/lucky winners in this great contest. Each prize is worth around \$150 (rrp) a set. All you have to do is answer these seven questions. If you don't know or can't find the answer, have a guess, you could well be correct!

You may enter as many times as you wish but you must use a separate entry form for each entry and include the month and page number cut from the bottom right hand portion of this page. You must include your name and address and sign each entry form where indicated.

Please read the contest rules carefully, especially if sending in multiple entries.

**This contest is jointly sponsored by ETI and Maruni Corporation — who have generously donated the prizes.**

## RULES

This contest is open to all persons normally resident in Australia with the exception of members of the staff of Maruni Corporation, Modern Magazines (Holdings) Ltd, K.G.Murray Ltd, Australian Consolidated Press, Wilkes Pty Ltd and/or associated companies.

**Entries should be addressed to ETI/Maruni Contest, Electronics Today Int., 15 Boundary St, Rushcutters Bay, NSW 2011.**

Closing date for the contest is 31 December 1980. Entries received within seven days of that date will be accepted if postmarked prior to and including 31 December 1980.

The contest will be judged by the Managing Editor and Editor of ETI whose decisions will be final. No correspondence can be entered into regarding their decisions.

In the event of one or more tied results the finalists' entries will be thoroughly mixed and then drawn by the Managing Editor.

Winners will be advised by registered letter the same day the results are declared. The names of the winners, together with the answers will be published in the next possible issue of ETI.

Contestants must enter their names and address where indicated on each entry form. Photostats or clearly written copies will be accepted but if sending copies you must cut out and include with each entry the month and page number from the bottom of the page of the contest. In other words you can send in multiple entries but you will need extra copies of the magazine so that you send an original page number with each entry.

This contest is invalid in States where local laws prohibit entries.

Entrants must sign the declaration, accompanying this contest, that they have read the above rules and agree to abide by their conditions.

(1) The superhet receiver pioneered a boom in AM broadcasting in the 1930s, as the technique made available stable, cheap, sensitive receivers for mass production. During that era the techniques of FM transmission for broadcasting and communications were developed. Who was the man associated with both developments ?

(2) What was his title ?

(3) The following quote, about an early stereo sound demonstration, has been taken from an Australian publication. What year did that demonstration take place ?

"At the Plaza Theatre, Sydney, on Sunday, April 10, a special demonstration arranged by Mr Ray Allsop, M.Inst. R.E.(Aust), F.S.M.P.E. (USA), and made possible by courtesy of Raycophone Ltd., was given as part of the proceedings of the World Radio Convention.

"Almost 2000 guests were present at the Plaza Theatre to hear for the first time in Australia electrical reproduction of an orchestra, possessing effects in the aural field similar to stereoscopy in optics.

"... Pick up was effected by binaural microphone technique, employing separate telephone transmission channels, and finally reproduced over separate amplifying and reproducing systems."

(4) Microphones may be divided into two basic groups: pressure- and velocity-operated types. Into which group does the Maruni DM901 fall ?

(5) In what units is the output voltage rating of a microphone quoted ?

(6) There are seven basic different types of headphones. List them.

(7) In fifty words or less, tell us why you would like to win a Maruni microphone and pair of headphones as offered in the prizes for this contest.

Name .....

Address .....

Postcode .....

I have read the contest rules and agree to abide by their conditions

Signed .....

Date .....



Facts from Fluke on low-cost DMM's

## Investigator at work: The shortcut to continuity checking.

At times like this, every minute matters. You could spend hours searching for a single short or open.

You could pack a continuity checker around with all your other gear. Or you could make your life a lot simpler and get the new 8024A Investigator from Fluke.

The Investigator is the only DMM on the market with nine functions including a built-in continuity/level detector. With 3½-digit resolution, 0.1% basic accuracy and a full line of accessories, it's the most versatile handheld DMM you can buy.

When you need a quick, trouble-free continuity tester, the 8024A provides an instant visual (♦) and audible signal whenever a good connection is found. You can make


rapid-fire circuit checks while keeping both eyes on the test points and count on the Investigator's "beep" to pinpoint opens or shorts.

For active circuit checking, the level detector's "up" arrow indicates voltages above a threshold level, the "down" arrow shows signals below that point. And a pulse stretcher captures and displays signals that other analog or digital meters would never see.

Other Investigator exclusives you'll appreciate are the peak hold

feature — a short-term memory that captures and holds transient signals until you can turn back to read the display — and the ability of the 8024A to deliver direct temperature readings via any K-type thermocouple. Plus conductance lets you measure leakage and high resistance to 10,000 Megohms. All this performance at a low price.

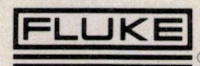For all the facts on the new 8024A Investigator, call or contact your Fluke stocking distributor, sales office or representative.



### **ELMEASCO** **Instruments Pty. Ltd.**

PO Box 30, Concord, NSW 2137  
13-15 McDonald St, Mortlake, NSW 2137  
Phone: (02) 736 2888. Telex: 25887

PO Box 107, Mt Waverley, Vic 3149  
21-23 Anthony Drive, Mt Waverley, Vic 3149  
Phone: (03) 233 4044. Telex: 36206

Adelaide: (08) 271 1839  
Brisbane: (07) 229 3161  
Perth: (09) 398 3362



# ALL TOGETHER !



## — the top projects from the past few years' issues of ETI !


Assembled in one great volume, here are more than 25 projects including: the Series 4000 stereo hi-fi amplifier system; the superb Series 4000 four-way speaker system; the monstrous 300 W amplifier module; Guitar Practice Amp; Fuzz/Sustain Unit; Electronic Tuning Fork; Aircraft Band Converter; Analogue Frequency Meter; Linear Scale Capacitance Meter; Electronic Ohmmeter; Ultrasonic Switch; Radio Remote Control Unit; Transistor Assisted Ignition; Theatrical Lighting Controller; Electromyogram; Disco Strobe . . . and many more.

On sale now at newsagents and selected specialist suppliers. If sold out (highly likely), you can obtain a copy from **Electronics Today International, Subscription Department, 3rd Floor, 15 Boundary St, Rushcutters Bay NSW 2011. Send \$3.95 plus 65 cents post and handling.**


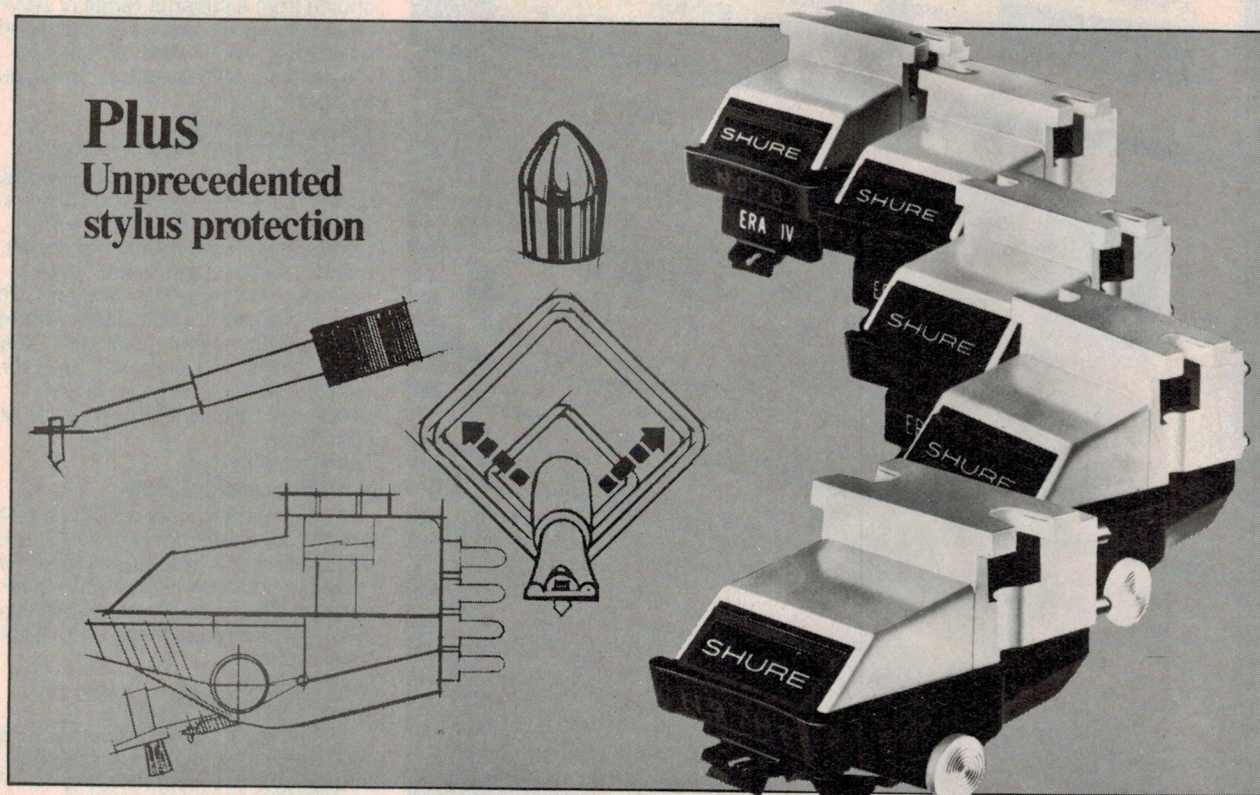
# fact: five new Shure Cartridges feature the technological breakthroughs of the V15 Type IV

**Plus  
Unprecedented  
stylus protection**



## the M97 Era IV Series phono cartridges

Model	Stylus Configuration	Tip Tracking Force	Applications
M97HE	Nude Hyperelliptical	$\frac{3}{4}$ to $1\frac{1}{2}$ grams	Highest fidelity where light tracking forces are essential.
M97ED	Nude Biradial (Elliptical)	$\frac{3}{4}$ to $1\frac{1}{2}$ grams	
M97GD	Nude Spherical	$\frac{3}{4}$ to $1\frac{1}{2}$ grams	
M97EJ	Biradial (Elliptical)	$1\frac{1}{2}$ to 3 grams	Where slightly heavier tracking forces are required.
M97B	Spherical	$1\frac{1}{2}$ to 3 grams	
78 rpm Stylus for all M97's	Biradial (Elliptical)	$1\frac{1}{2}$ to 3 grams	For 78 rpm records.

Shure has written a new chapter in the history of affordable hi-fi by making the space-age technological breakthroughs of the incomparable V15 Type IV available in a *complete line* of high-performance, moderately-priced cartridges: the M97 Era IV Series Phono Cartridges, available with five different interchangeable stylus configurations to fit every system and every budget.

The critically acclaimed V15 Type IV is the cartridge that astonished audiophiles with such vanguard features as the Dynamic Stabilizer—which simultaneously overcomes record-warp caused problems, provides electrostatic neutralization of the record surface, and effectively removes dust and lint from the record—and, the unique telescoped stylus assembly which results in lower effective stylus mass and dramatically improved trackability.

Each of these features... and more... has been incorporated in the five cartridges in the M97 Series—there is even an M97 cartridge that offers the low distortion Hyperelliptical stylus! What's more, every M97 cartridge features a unique lateral deflection assembly, called the SIDE-GUARD, which responds to side thrusts on the stylus by withdrawing the entire stylus shank and tip safely into the stylus housing before it can bend.

**NEW! M97 Series Era IV Phono Cartridges...**  
**Five new invitations to the new era in hi-fi.**



**AUDIO ENGINEERS P/L**  
342 Kent Street,  
SYDNEY 2000 N.S.W.


**AUDIO ENGINEERS (Vic.)**  
2A Hill Street,  
THORNBURY 3071 Vic.

**AUDIO ENGINEERS (Qld.)**  
51a Castlemaine Street,  
MILTON 4064 Qld.

**AE 151/FP**  
**ATHOL M. HILL P/L**  
33 Wittenoom Street,  
EAST PERTH 6000 W.A.


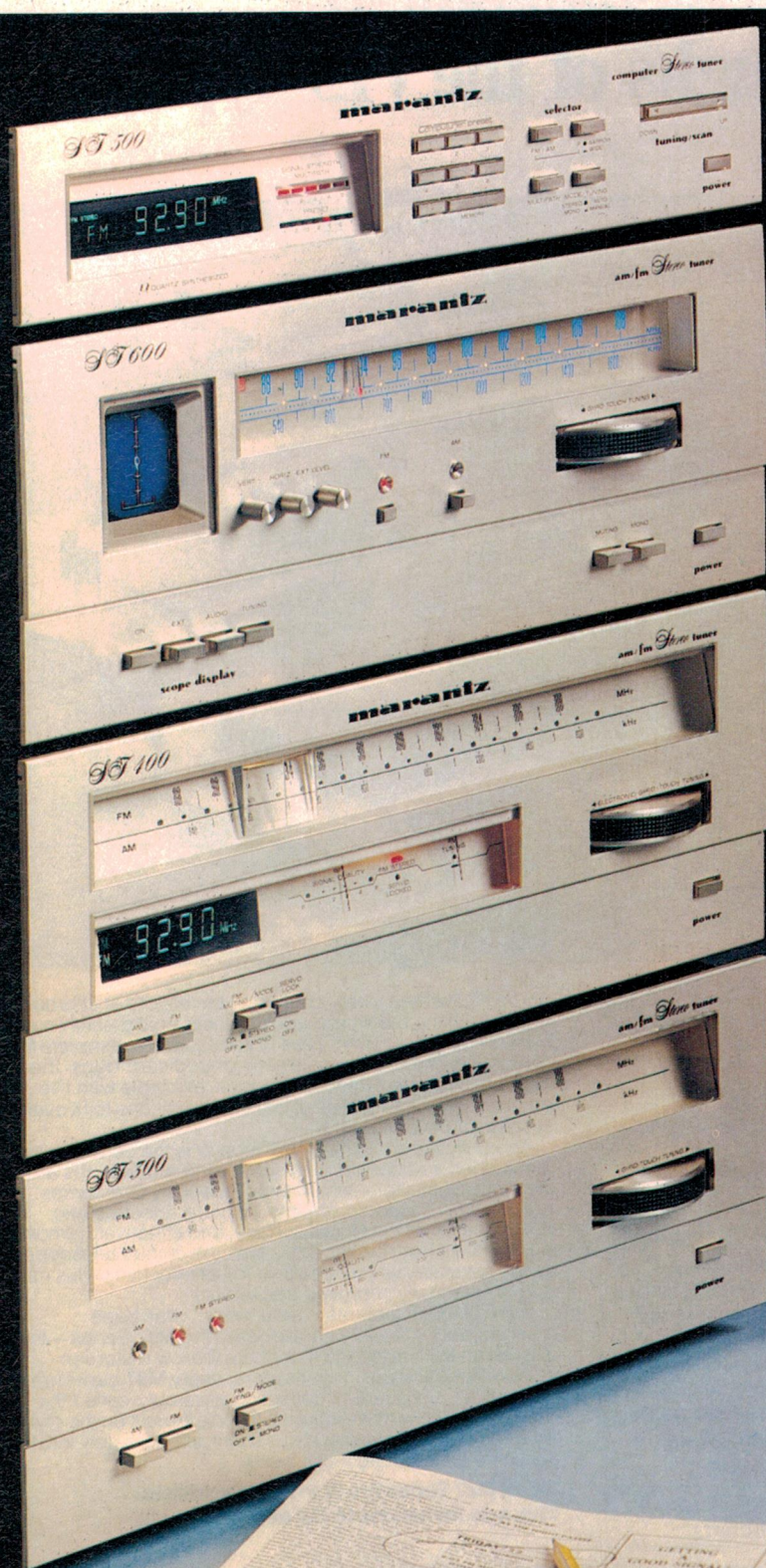
# RARE ADDITIONS FROM MARANTZ. SUPERIOR FM TUNERS.



**Rare:** very valuable.

**Additions:** the things added.

**Ma'rantz:** a range of ultra-high performance FM Tuners which blend state-of-the-art engineering with operational versatility.

The name Marantz guarantees your choice from a superior range of AM/FM Stereo Tuners, guarantees exceptional quality and, with the advent of more FM stations, Marantz guarantees your total listening pleasure.

## **MARANTZ ST500 AM/FM STEREO COMPUTUNER**

Sleek, slimline and microprocessor controlled — tune and recall stations with amazing speed and precision. The Computuner features state-of-the-art, quartz-locked, drift free frequency synthesised tuning with 7AM and 7FM memory presets. The LED signal strength display doubles as a multipath indicator and the Wide and Narrow IF Selector enables the switching of a tuning bandwidth best suited to reception area conditions.

## **MARANTZ ST600 AM/FM STEREO TUNER**

This model incorporates a built-in oscilloscope that affords the most precise means possible to determine optimum reception, even from weak or distant stations. The functions of the oscilloscope extend well beyond those of conventional tuner meters.

## **MARANTZ ST400 AM/FM STEREO TUNER**

A large, fuss-free Vacuum Fluorescent readout clearly displays the selected frequency and Electronic Gyro-Touch with Servo-Lock guarantees drift-free, razor-sharp tuning every time. Uncompromising quality through and through.

## **MARANTZ ST300 AM/FM STEREO TUNER**

Consistent with all quality Marantz tuners, the ST300 features MOSFET FM front end and Phase Lock Loop demodulator for superlative performance — low distortion, extremely linear operation and wide dynamic range. Illuminated dial cursor, LED function indicators and Gyro-Touch tuning make the ST300 an exceptionally sophisticated buy at a modest price.

Your Marantz stockist will be pleased to demonstrate the complete range of Marantz tuners. If you see your hi-fi as an investment and, if you demand critical performance standards as well as the best value for money, listen to the future.

Listen to Marantz.

**marantz**  
Now you're listening.

Distributed by: MARANTZ (AUST.) PTY. LTD.  
32 Cross Street, Brookvale, N.S.W. 2100  
Telephone: (02) 939 1900 Telex AA 24121  
Melbourne (03) 329 7655 Brisbane (07) 48 8882  
Adelaide (08) 223 2699 Perth (09) 328 3874